

# 电子电路基础

## 第七讲~正弦交流电路-part2

# 课程纲要

- 3.3 交流功率分析
  - 3.3.1 重要物理量：瞬时功率、平均功率、无功功率、有功功率、视在功率、复功率和功率因数等
  - 3.3.2 交流功率守恒
  - 3.3.3 功率因数的校正
  - 3.3.4 最大功率传递定理
- 3.4 三相交流电的基本概念
  - 3.4.1 平衡三相交流电的概念
  - 3.4.2 简单了解Y-Y、Y- $\Delta$ 、 $\Delta$ - $\Delta$ 和 $\Delta$ -Y四种连接方式
  - 3.4.3 了解线电流、相电流、线电压和相电压的定义

# AC Power Analysis

## Chapter 11

- 11.1 Instantaneous and Average Power 瞬时功率 & 平均功率
- 11.2 Maximum Average Power Transfer 最大平均功率传递
- 11.3 Effective or RMS Value 有效值 (均方值)
- 11.4 Apparent Power and Power Factor 视在功率 & 功率因数
- 11.5 Complex Power 复功率
- 11.6 Conservation of AC Power 交流功率守恒
- 11.7 Power Factor Correction 功率因数的校正
- 11.8 Power Measurement 功率测量

# 11.1 Instantaneous and Average Power 瞬时功率 & 平均功率

- 瞬时功率**：元件两端**瞬时电压**与流经元件**瞬时电流**的**乘积**。

The **instantaneous power** (in watts) is the power at any instant of time.

$$p(t) = v(t)i(t)$$

单位是 W

$$v(t) = V_m \cos(\omega t + \theta_v)$$


$$i(t) = I_m \cos(\omega t + \theta_i)$$

$$\Rightarrow p(t) = v(t)i(t) = V_m I_m \cos(\omega t + \theta_v) \cos(\omega t + \theta_i)$$

$$= \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) + \frac{1}{2} V_m I_m \cos(2\omega t + \theta_v + \theta_i)$$


Constant power

Sinusoidal power at  $2\omega$

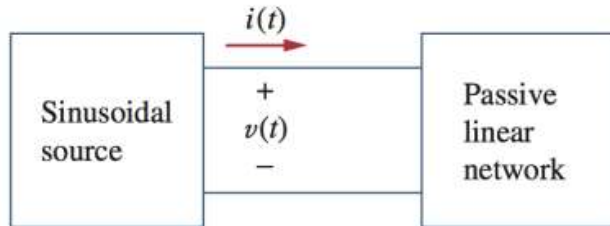

**Figure 11.1**

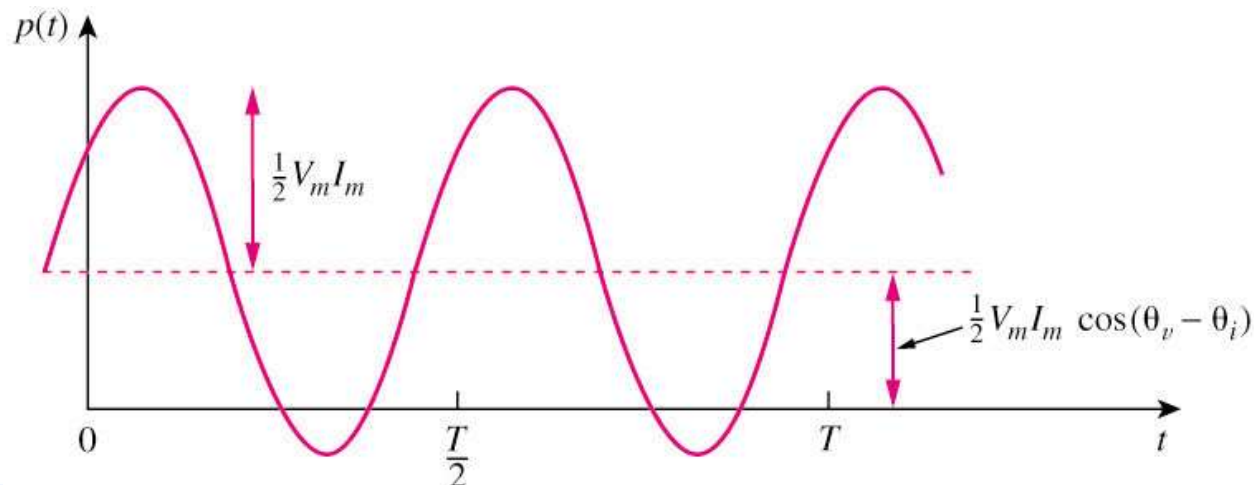Sinusoidal source and passive linear circuit.



$p(t) > 0$ : power is absorbed by the circuit;  $p(t) < 0$ : power is absorbed by the source.

# 11.1 Instantaneous and Average Power

单位是 W

Power


$$\begin{aligned}
 P &= \frac{1}{T} \int_0^T \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) dt \\
 &+ \frac{1}{T} \int_0^T \frac{1}{2} V_m I_m \cos(2\omega t + \theta_v + \theta_i) dt \\
 &= \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) \frac{1}{T} \int_0^T dt \\
 &+ \frac{1}{2} V_m I_m \frac{1}{T} \int_0^T \cos(2\omega t + \theta_v + \theta_i) dt
 \end{aligned}$$

- 平均功率：** 瞬时功率在一个周期内的平均值

The **average power**, in watts, is the average of the instantaneous power over one period.

瞬时功率由两部分构成：常数部分+正弦部分，其中常数部分就是平均功率。（因为正弦函数的平均值为0）
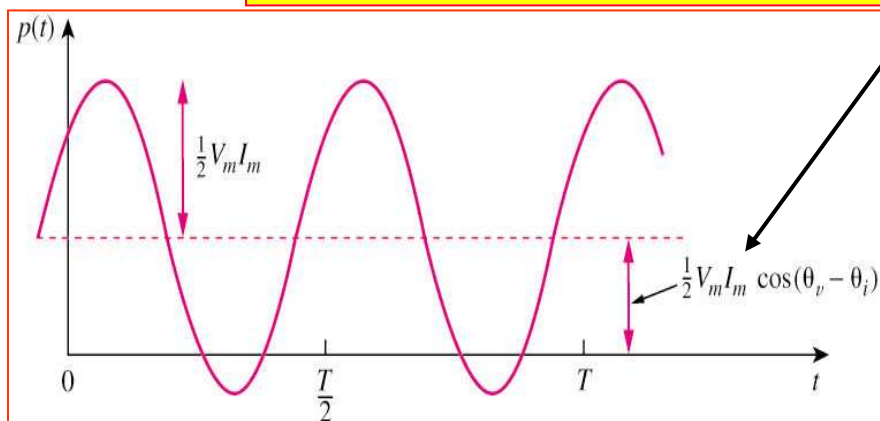
$$P = \frac{1}{T} \int_0^T p(t) dt = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)$$



A resistive load ( $R$ ) absorbs power at all times, while a reactive load ( $L$  or  $C$ ) absorbs zero average power.

1.  $P$  is not **time dependent**.
2. When  $\theta_v = \theta_i$ , it is a **purely resistive** load case.
3. When  $\theta_v - \theta_i = \pm 90^\circ$ , it is a **purely reactive** load case.
4.  $P = 0$  means that the circuit absorbs **no average power**.

# 平均功率的相量求法

- 瞬时功率，是时变的，必须知道  $v(t)$  和  $i(t)$ ;
- 平均功率，是常数，可以从  $v(t)$  和  $i(t)$  求出，也可以从相量  $\mathbf{V}$  和  $\mathbf{I}$  求出;

$$\mathbf{V} = V_m \angle \theta_v \text{ and } \mathbf{I} = I_m \angle \theta_i \quad \xrightarrow{\text{?}} \quad P = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)$$

$$\begin{aligned} \frac{1}{2} \mathbf{V} \mathbf{I}^* &= \frac{1}{2} V_m I_m \angle \theta_v - \theta_i \\ &= \frac{1}{2} V_m I_m [\cos(\theta_v - \theta_i) + j \sin(\theta_v - \theta_i)] \end{aligned}$$

1. 直接法，根据  $V_m$ ,  $I_m$ ,  $\theta_v$ ,  $\theta_i$  直接写出。但对应什么数学运算呢？

$$P = \frac{1}{2} \text{Re}[\mathbf{V} \mathbf{I}^*] = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)$$


2. 数学运算法

## Example 11.1

Given that

$$v(t) = 120 \cos(377t + 45^\circ) \text{ V} \quad \text{and} \quad i(t) = 10 \cos(377t - 10^\circ) \text{ A}$$

find the instantaneous power and the average power absorbed by the passive linear network of Fig. 11.1.

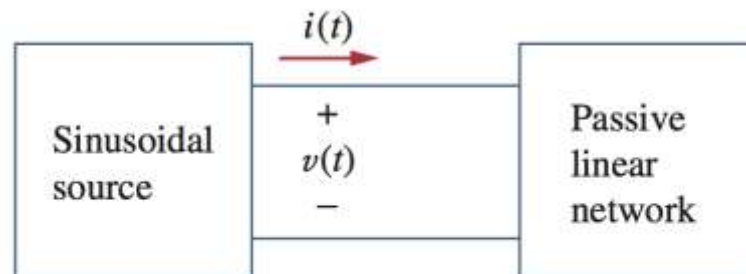

**Figure 11.1**

Sinusoidal source and passive linear circuit.

平均功率可以根据公式直接写出

$$P = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)$$



## Example 11.2

Calculate the average power absorbed by an impedance  $\mathbf{Z} = 30 - j70 \, \Omega$  when a voltage  $\mathbf{V} = 120 \angle 0^\circ$  is applied across it.


小心功率不是线性的！！！！





### Example 11.3

For the circuit shown in Fig. 11.3, find the average power supplied by the source and the average power absorbed by the resistor.

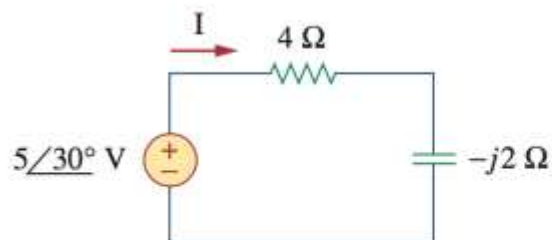


**Figure 11.3**

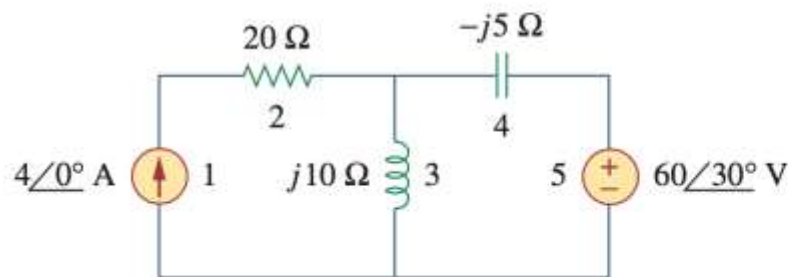
For Example 11.3.

## Example 11.4

Determine the average power generated by each source and the average power absorbed by each passive element in the circuit of Fig. 11.5(a).



(a)

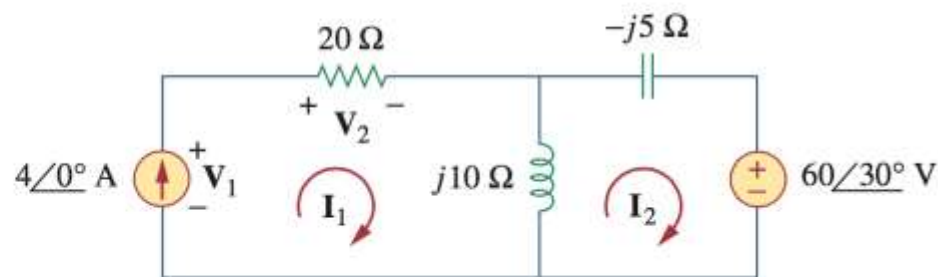

(b)

$$(j10 - j5)\mathbf{I}_2 - j10\mathbf{I}_1 + 60\angle 30^\circ = 0, \quad \mathbf{I}_1 = 4 \text{ A} \Rightarrow \mathbf{I}_2 = 10.58\angle 79.1^\circ \text{ A}$$

$$P_5 = \frac{1}{2}(60)(10.58) \cos(30^\circ - 79.1^\circ) = 207.8 \text{ W}$$

$$\begin{aligned} \mathbf{V}_1 &= 20\mathbf{I}_1 + j10(\mathbf{I}_1 - \mathbf{I}_2) = 80 + j10(4 - 2 - j10.39) \\ &= 183.9 + j20 = 184.984\angle 6.21^\circ \text{ V} \end{aligned}$$

$$P_1 = -\frac{1}{2}(184.984)(4) \cos(6.21^\circ - 0) = -367.8 \text{ W}$$

$$P_2 = \frac{1}{2}(80)(4) = 160 \text{ W}$$

For the capacitor, the current through it is  $\mathbf{I}_2 = 10.58\angle 79.1^\circ$  and the voltage across it is  $-j5\mathbf{I}_2 = (5\angle -90^\circ)(10.58\angle 79.1^\circ) = 52.9\angle 79.1^\circ - 90^\circ$ . The average power absorbed by the capacitor is

$$P_4 = \frac{1}{2}(52.9)(10.58) \cos(-90^\circ) = 0$$

For the inductor, the current through it is  $\mathbf{I}_1 - \mathbf{I}_2 = 2 - j10.39 = 10.58\angle -79.1^\circ$ . The voltage across it is  $j10(\mathbf{I}_1 - \mathbf{I}_2) = 10.58\angle -79.1^\circ + 90^\circ$ . Hence, the average power absorbed by the inductor is

$$P_3 = \frac{1}{2}(105.8)(10.58) \cos 90^\circ = 0$$

$$P_1 + P_2 + P_3 + P_4 + P_5 = -367.8 + 160 + 0 + 0 + 207.8 = 0$$

# 最大平均功率传递

$$\mathbf{Z}_{Th} = R_{Th} + jX_{Th}$$

$$\mathbf{Z}_L = R_L + jX_L$$



$$\mathbf{I} = \frac{\mathbf{V}_{Th}}{\mathbf{Z}_{Th} + \mathbf{Z}_L} = \frac{\mathbf{V}_{Th}}{(R_{Th} + jX_{Th}) + (R_L + jX_L)}$$

$$P = \frac{1}{2} |\mathbf{I}|^2 R_L = \frac{|\mathbf{V}_{Th}|^2 R_L / 2}{(R_{Th} + R_L)^2 + (X_{Th} + X_L)^2}$$


$$\frac{\partial P}{\partial X_L} = - \frac{|\mathbf{V}_{Th}|^2 R_L (X_{Th} + X_L)}{[(R_{Th} + R_L)^2 + (X_{Th} + X_L)^2]^2}$$

$$\frac{\partial P}{\partial R_L} = \frac{|\mathbf{V}_{Th}|^2 [(R_{Th} + R_L)^2 + (X_{Th} + X_L)^2 - 2R_L(R_{Th} + R_L)]}{2[(R_{Th} + R_L)^2 + (X_{Th} + X_L)^2]^2}$$


共轭匹配

$$P = \frac{1}{2} V_m I_m = \frac{1}{2} I_m^2 R = \frac{1}{2} |\mathbf{I}|^2 R$$

电阻上消耗的功率见上式；  
电抗元件上消耗的功率为零

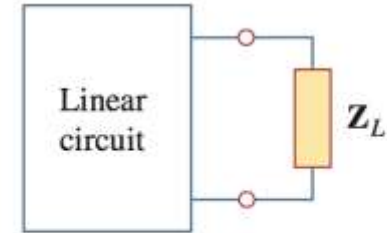

(a)

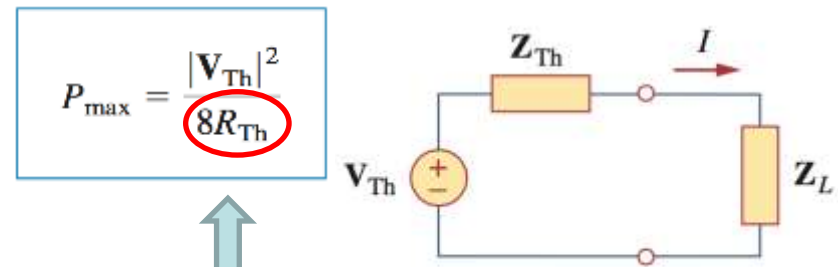

$$P_{max} = \frac{|\mathbf{V}_{Th}|^2}{8R_{Th}}$$


$$\mathbf{Z}_L = R_L + jX_L = R_{Th} - jX_{Th} = \mathbf{Z}_{Th}^*$$

$$X_L = -X_{Th}$$

$$R_L = \sqrt{R_{Th}^2 + (X_{Th} + X_L)^2}$$

For **maximum average power transfer**, the load impedance  $\mathbf{Z}_L$  must be equal to the complex conjugate of the Thevenin impedance  $\mathbf{Z}_{Th}$ .

## Example 11.5

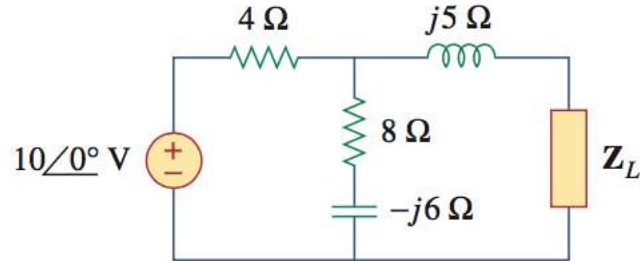

**Figure 11.8**  
For Example 11.5.

Determine the load impedance  $Z_L$  that maximizes the average power drawn from the circuit of Fig. 11.8. What is the maximum average power?

将左边电路用戴维南定理等效

In the circuit in Fig. 11.11, find the value of  $R_L$  that will absorb the maximum average power. Calculate that power.

### Solution:

We first find the Thevenin equivalent at the terminals of  $R_L$ .

$$\mathbf{Z}_{Th} = (40 - j30) \parallel j20 = \frac{j20(40 - j30)}{j20 + 40 - j30} = 9.412 + j22.35 \Omega$$

By voltage division,

$$\mathbf{V}_{Th} = \frac{j20}{j20 + 40 - j30} (150 \angle 30^\circ) = 72.76 \angle 134^\circ \text{ V}$$

The value of  $R_L$  that will absorb the maximum average power is

$$R_L = |\mathbf{Z}_{Th}| = \sqrt{9.412^2 + 22.35^2} = 24.25 \Omega$$


The current through the load is

$$\mathbf{I} = \frac{\mathbf{V}_{Th}}{\mathbf{Z}_{Th} + R_L} = \frac{72.76 \angle 134^\circ}{33.66 + j22.35} = 1.8 \angle 100.42^\circ \text{ A}$$

The maximum average power absorbed by  $R_L$  is

$$P_{max} = \frac{1}{2} |\mathbf{I}|^2 R_L = \frac{1}{2} (1.8)^2 (24.25) = 39.29 \text{ W}$$

### Example 11.6

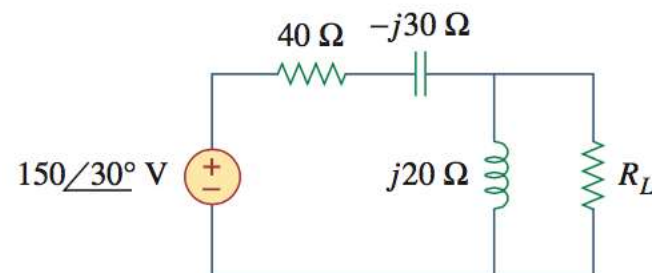

**Figure 11.11**

For Example 11.6.

将左边电路用戴维南定理等效  
负载为纯电阻情况

注意不是  $R_L = R_{Th}$

$$R_L = \sqrt{R_{Th}^2 + (X_{Th} + X_L)^2}$$

若负载指定为纯电阻，则  
共轭匹配不适用！匹配阻  
值为戴维南阻抗的幅度



# What is root mean square (rms)

- In **statistics** and its applications, the root mean square (abbreviated RMS or rms) is defined as the **square root of the mean square** (the arithmetic mean of the squares of a set of numbers)


$$x_{\text{rms}} = \sqrt{\frac{1}{n} (x_1^2 + x_2^2 + \cdots + x_n^2)}.$$

- For **alternating electric current**, RMS is equal to the value of the direct current that would produce the same average power dissipation in a resistive load.

$$f_{\text{rms}} = \sqrt{\frac{1}{T_2 - T_1} \int_{T_1}^{T_2} [f(t)]^2 dt}.$$


- In estimation theory of **machine learning**, the root mean square error of an estimator is a measure of the imperfection of the fit of the estimator to the data
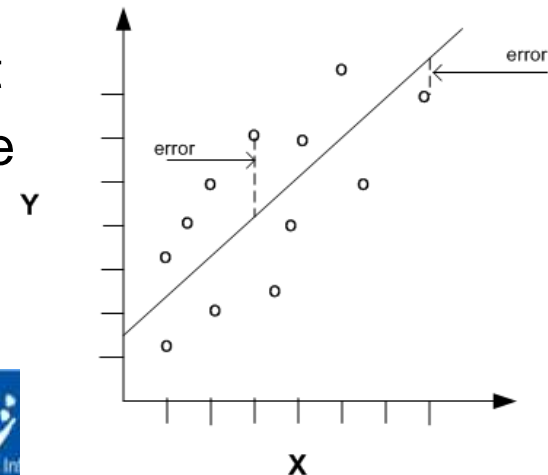
$$RMSE = \sqrt{\frac{\sum_{i=1}^N (\text{Predicted}_i - \text{Actual}_i)^2}{N}}$$


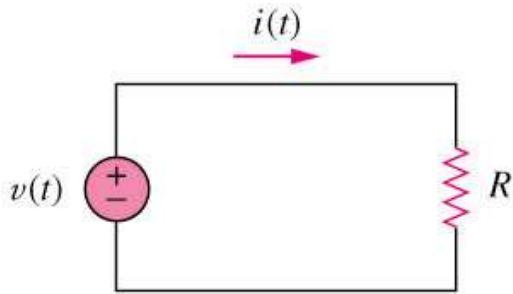
# 11.3 Effective or RMS Value 有效值

The effective of a periodic current is the dc current that delivers the same average power to a resistor as the periodic current.




(a)

The total power dissipated by R is given by:

$$P = \frac{1}{T} \int_0^T i^2 R dt = \frac{R}{T} \int_0^T i^2 dt = I_{rms}^2 R$$

Hence,  $I_{eff}$  is equal to:
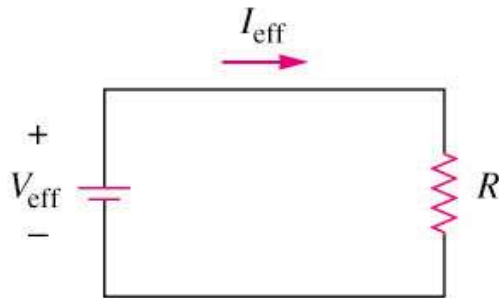
$$I_{eff} = \sqrt{\frac{1}{T} \int_0^T i^2 dt} = I_{rms}$$



(b)


$$X_{rms} = \sqrt{\frac{1}{T} \int_0^T x^2 dt}$$

The **effective value** of a periodic signal is its root mean square (rms) value.

The rms value is a constant, which depending on the shape of the function.



# 11.3 Effective or RMS Value

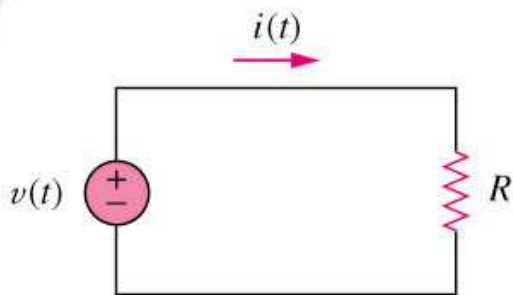

(a)

The rms value of a sinusoid  $i(t) = I_m \cos(\omega t)$  is given by:

$$I_{\text{rms}} = \frac{I_m}{\sqrt{2}}$$

$$V_{\text{rms}} = \frac{V_m}{\sqrt{2}}$$

$$I_{\text{rms}} = \sqrt{\frac{1}{T} \int_0^T I_m^2 \cos^2 \omega t \, dt} = \sqrt{\frac{I_m^2}{T} \int_0^T \frac{1}{2} (1 + \cos 2\omega t) \, dt} = \frac{I_m}{\sqrt{2}}$$

仅对正弦信号而言！

The average power can be written in terms of the rms values: 振幅（峰值）

$$P = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) = \frac{V_m}{\sqrt{2}} \frac{I_m}{\sqrt{2}} \cos(\theta_v - \theta_i)$$


回顾平均功率的表达式  $= V_{\text{rms}} I_{\text{rms}} \cos(\theta_v - \theta_i)$

有效值

消耗在电阻上的平均功率:  $P = I_{\text{rms}}^2 R = \frac{V_{\text{rms}}^2}{R}$

在电力行业，习惯于使用rms值，比如家用电 220V 指的是电压幅度的有效值（而非幅值）为 220V，采用有效值后，功率的计算公式就如直流时一样了

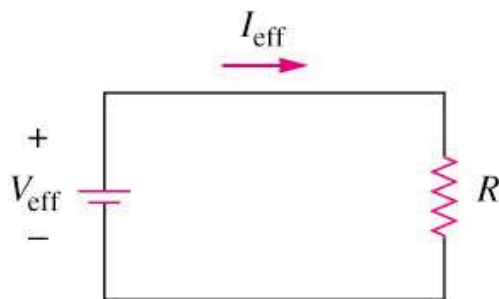Note: If you express amplitude of a phasor source(s) in rms, then all the answer as a result of this phasor source(s) must also be in rms value.



(b)

Determine the rms value of the current waveform in Fig. 11.14. If the current is passed through a  $2\text{-}\Omega$  resistor, find the average power absorbed by the resistor.

### Solution:

The period of the waveform is  $T = 4$ . Over a period, we can write the current waveform as

$$i(t) = \begin{cases} 5t, & 0 < t < 2 \\ -10, & 2 < t < 4 \end{cases}$$


The rms value is

$$\begin{aligned} I_{\text{rms}} &= \sqrt{\frac{1}{T} \int_0^T i^2 dt} = \sqrt{\frac{1}{4} \left[ \int_0^2 (5t)^2 dt + \int_2^4 (-10)^2 dt \right]} \\ &= \sqrt{\frac{1}{4} \left[ 25 \frac{t^3}{3} \Big|_0^2 + 100t \Big|_2^4 \right]} = \sqrt{\frac{1}{4} \left( \frac{200}{3} + 200 \right)} = 8.165 \text{ A} \end{aligned}$$

The power absorbed by a  $2\text{-}\Omega$  resistor is

$$P = I_{\text{rms}}^2 R = (8.165)^2 (2) = 133.3 \text{ W}$$

## Example 11.7

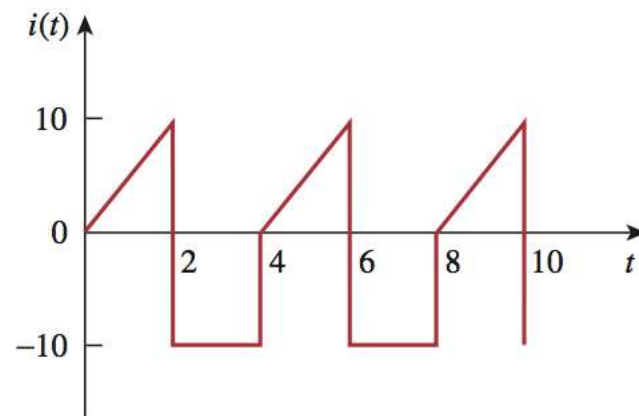


**Figure 11.14**

For Example 11.7.

周期信号。有效值：计算一个周期内的均方根



## Example 11.8

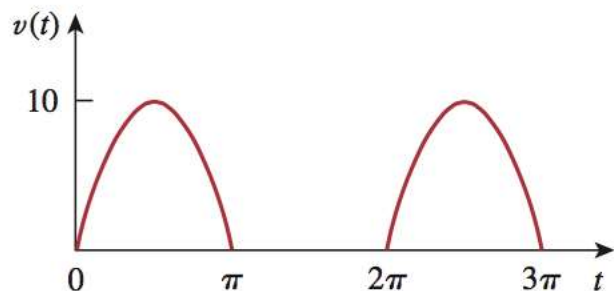

**Figure 11.16**

For Example 11.8.

周期信号。有效值：计算一个周期内的均方根

The waveform shown in Fig. 11.16 is a half-wave rectified sine wave. Find the rms value and the amount of average power dissipated in a  $10\text{-}\Omega$  resistor.

### Solution:

The period of the voltage waveform is  $T = 2\pi$ , and

$$v(t) = \begin{cases} 10 \sin t, & 0 < t < \pi \\ 0, & \pi < t < 2\pi \end{cases}$$

The rms value is obtained as

$$V_{\text{rms}}^2 = \frac{1}{T} \int_0^T v^2(t) dt = \frac{1}{2\pi} \left[ \int_0^\pi (10 \sin t)^2 dt + \int_\pi^{2\pi} 0^2 dt \right]$$

But  $\sin^2 t = \frac{1}{2}(1 - \cos 2t)$ . Hence,

$$\begin{aligned} V_{\text{rms}}^2 &= \frac{1}{2\pi} \int_0^\pi \frac{100}{2} (1 - \cos 2t) dt = \frac{50}{2\pi} \left( t - \frac{\sin 2t}{2} \right) \Big|_0^\pi \\ &= \frac{50}{2\pi} \left( \pi - \frac{1}{2} \sin 2\pi - 0 \right) = 25, \quad V_{\text{rms}} = 5 \text{ V} \end{aligned}$$

The average power absorbed is

$$P = \frac{V_{\text{rms}}^2}{R} = \frac{5^2}{10} = 2.5 \text{ W}$$

# 11.4 Apparent Power and Power Factor 视在功率 & 功率因数

- Apparent Power (视在功率)  $S$ , is the product of the **rms** values of voltage and current.
- It is measured in volt-amperes or VA to distinguish it from the average or real power that is measured in watts.

单位是VA

$$P = V_{\text{rms}} I_{\text{rms}} \cos(\theta_v - \theta_i) = S \cos(\theta_v - \theta_i)$$

平均功率 = 视在功率 x 功率因数

$$S = V_{\text{rms}} I_{\text{rms}}$$

Apparent Power,  $S$

Power Factor,  $\text{pf}$

视在功率不是真实功率，所以单位不用W，而用VA

定义 对于正弦信号

$$\text{pf} = \frac{P}{S} = \cos(\theta_v - \theta_i)$$

- Power factor (功率因数) is the cosine of the phase difference between the voltage and current. It is also the cosine of the angle of the load impedance.

功率因数是电压电流相位差（也即负载相位）的cos

$$\mathbf{Z} = \frac{\mathbf{V}}{\mathbf{I}} = \frac{V_{\text{rms}}}{I_{\text{rms}}} \angle \theta_v - \theta_i$$

# 11.4 Apparent Power and Power Factor

Purely resistive load (R)	$\theta_v - \theta_i = 0, \text{ pf} = 1$	$P/S = 1$ , all power are consumed
Purely reactive load (L or C)	$\theta_v - \theta_i = \pm 90^\circ, \text{ pf} = 0$	$P = 0$ , no real power consumption
Resistive and reactive load (R and L/C)	$\theta_v - \theta_i > 0$ 感性 $\theta_v - \theta_i < 0$ 容性	<ul style="list-style-type: none"> <li>• <u>pf Lagging</u> - inductive load, 电流 lags 电压</li> <li>• <u>pf Leading</u> - capacitive load, 电流 leads 电压</li> </ul>

leading means current leads voltage ~ capacitive load;



## Example 11.9

平均功率 = 视在功率 × 功率因数

$$S = V_{\text{rms}} I_{\text{rms}}$$

$$\text{pf} = \frac{P}{S} = \cos(\theta_v - \theta_i)$$

A series-connected load draws a current  $i(t) = 4 \cos(100\pi t + 10^\circ)$  A when the applied voltage is  $v(t) = 120 \cos(100\pi t - 20^\circ)$  V. Find the apparent power and the power factor of the load. Determine the element values that form the series-connected load.

### Solution:

The apparent power is

$$S = V_{\text{rms}} I_{\text{rms}} = \frac{120}{\sqrt{2}} \frac{4}{\sqrt{2}} = 240 \text{ VA}$$

The power factor is

$$\text{pf} = \cos(\theta_v - \theta_i) = \cos(-20^\circ - 10^\circ) = 0.866 \quad (\text{leading})$$

The pf is leading because the current leads the voltage. The pf may also be obtained from the load impedance.

$$\mathbf{Z} = \frac{\mathbf{V}}{\mathbf{I}} = \frac{120 \angle -20^\circ}{4 \angle 10^\circ} = 30 \angle -30^\circ = 25.98 - j15 \, \Omega$$

$$\text{pf} = \cos(-30^\circ) = 0.866 \quad (\text{leading})$$


The load impedance  $\mathbf{Z}$  can be modeled by a 25.98- $\Omega$  resistor in series with a capacitor with

$$X_C = -15 = -\frac{1}{\omega C}$$

or

$$C = \frac{1}{15\omega} = \frac{1}{15 \times 100\pi} = 212.2 \, \mu\text{F}$$

## Example 11.10

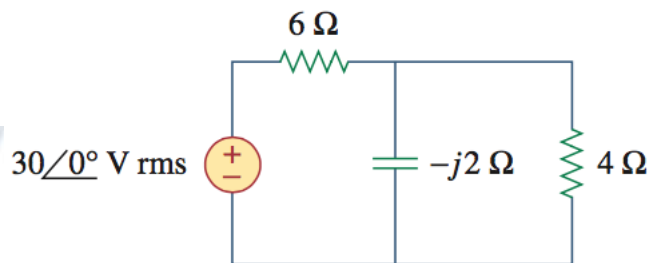

**Figure 11.18**

For Example 11.10.

功率因数 = 负载相位的cos  
平均功率 = 视在功率 × 功率因数

计算技巧!!! 掌握!

Determine the power factor of the entire circuit of Fig. 11.18 as seen by the source. Calculate the average power delivered by the source.

### Solution:

The total impedance is

$$\mathbf{Z} = 6 + 4 \parallel (-j2) = 6 + \frac{-j2 \times 4}{4 - j2} = 6.8 - j1.6 = 7 \angle -13.24^\circ \Omega$$

The power factor is

$$\text{pf} = \cos(-13.24) = 0.9734 \quad (\text{leading})$$

since the impedance is capacitive. The rms value of the current is

$$\mathbf{I}_{\text{rms}} = \frac{\mathbf{V}_{\text{rms}}}{\mathbf{Z}} = \frac{30 \angle 0^\circ}{7 \angle -13.24^\circ} = 4.286 \angle 13.24^\circ \text{ A}$$

The average power supplied by the source is

$$P = V_{\text{rms}} I_{\text{rms}} \text{pf} = (30)(4.286)0.9734 = 125 \text{ W}$$

or

$$P = I_{\text{rms}}^2 R = (4.286)^2 (6.8) = 125 \text{ W}$$


where  $R$  is the resistive part of  $\mathbf{Z}$ .


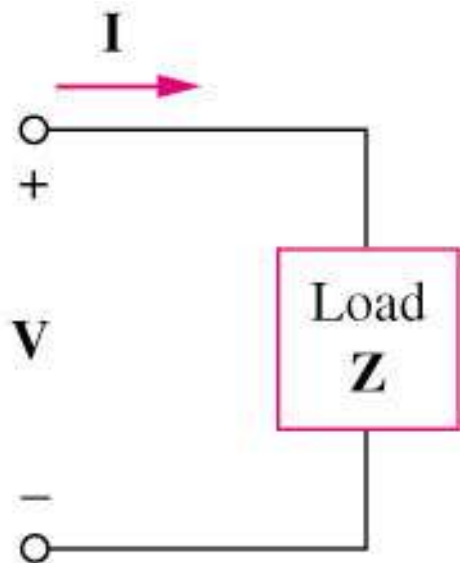
# 11.5 Complex Power 复功率

Complex power **S** is the product of the voltage and the complex **conjugate** of the current:

复功率 = 0.5 × 电压相量（振幅） × 电流相量（振幅）的共轭  
= 电压相量（有效值） × 电流相量（有效值）的共轭




$$\mathbf{V} = V_m \angle \theta_v$$

$$\mathbf{I} = I_m \angle \theta_i$$

$$\mathbf{S} = \frac{1}{2} \mathbf{V} \mathbf{I}^* = V_{\text{rms}} I_{\text{rms}} \angle \theta_v - \theta_i$$

# 11.5 Complex Power

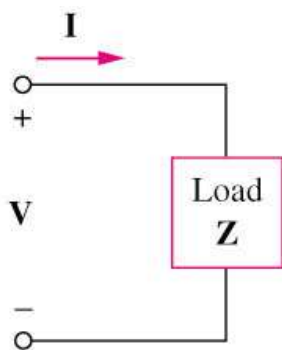

$$S = \frac{1}{2} V I^* = V_{\text{rms}} I_{\text{rms}} \angle \theta_v - \theta_i$$

$$S = I_{\text{rms}}^2 Z = \frac{V_{\text{rms}}^2}{Z^*} = V_{\text{rms}} I_{\text{rms}}^*$$

$$\Rightarrow S = V_{\text{rms}} I_{\text{rms}} \cos(\theta_v - \theta_i) + j V_{\text{rms}} I_{\text{rms}} \sin(\theta_v - \theta_i)$$

$$S = P + j Q$$


$P$ : is the average power in watts delivered to a load and it is the only useful power. 有功功率, 即平均功率, 单位 **W**

$Q$ : is the reactive power exchange between the source and the reactive part of the load. It is measured in VAR. 无功功率, 复功率的虚部, 单位 **VAR** (VA reactive)

- $Q = 0$  for **resistive loads** (unity pf).
- $Q < 0$  for **capacitive loads** (leading pf).
- $Q > 0$  for **inductive loads** (lagging pf).

$Q$  的正负与  $Z$  相同

# 11.5 Complex Power

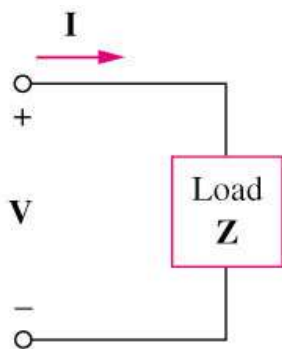

$$\Rightarrow S = \underbrace{V_{\text{rms}} I_{\text{rms}} \cos(\theta_v - \theta_i)}_P + j \underbrace{V_{\text{rms}} I_{\text{rms}} \sin(\theta_v - \theta_i)}_Q$$

$$\mathbf{S} = P + jQ$$

复功率是重要概念，包含了所有描述功率的量

$$\text{Complex Power} = \mathbf{S} = P + jQ = \mathbf{V}_{\text{rms}}(\mathbf{I}_{\text{rms}})^* \quad \text{VA}$$

$$= |\mathbf{V}_{\text{rms}}| |\mathbf{I}_{\text{rms}}| \angle \theta_v - \theta_i$$

$$\text{Apparent Power} = S = |\mathbf{S}| = |\mathbf{V}_{\text{rms}}| |\mathbf{I}_{\text{rms}}| = \sqrt{P^2 + Q^2} \quad (11.51)$$

$$\text{Real Power} = P = \text{Re}(\mathbf{S}) = S \cos(\theta_v - \theta_i)$$

$$\text{Reactive Power} = Q = \text{Im}(\mathbf{S}) = S \sin(\theta_v - \theta_i)$$

$$\text{Power Factor} = \frac{P}{S} = \cos(\theta_v - \theta_i)$$


1) 它的模：视在功率 **VA**

2) 它的相位：→ 功率因数 **无量纲**

3) 它的实部：平均功率（有功功率）**W**

4) 它的虚部：无功功率 **VAR**




# 11.5 Complex Power

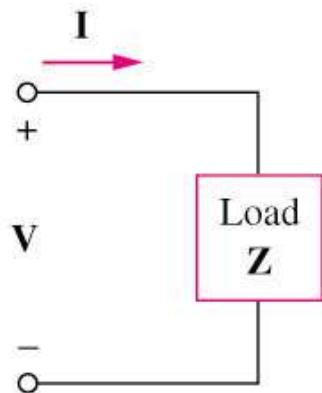

$$\Rightarrow S = \underbrace{V_{\text{rms}} I_{\text{rms}} \cos(\theta_v - \theta_i)}_P + j \underbrace{V_{\text{rms}} I_{\text{rms}} \sin(\theta_v - \theta_i)}_Q$$

$$\mathbf{S} = P + jQ$$

复功率在复数平面的表示

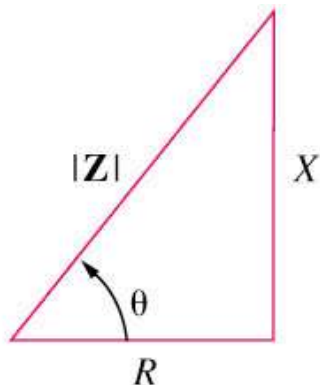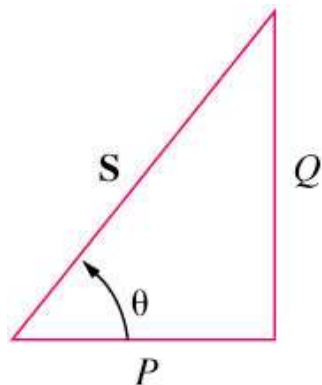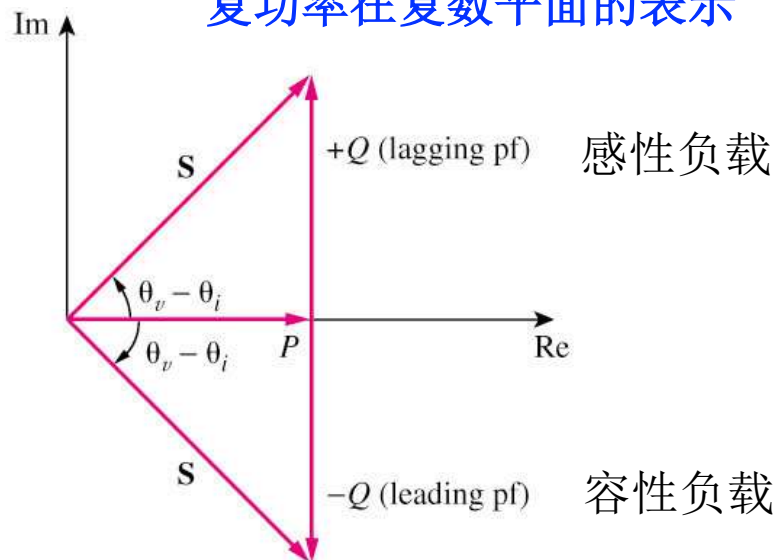

Power Triangle   Impedance Triangle

Power Factor

The voltage across a load is  $v(t) = 60 \cos(\omega t - 10^\circ)$  V and the current through the element in the direction of the voltage drop is  $i(t) = 1.5 \cos(\omega t + 50^\circ)$  A. Find: (a) the complex and apparent powers, (b) the real and reactive powers, and (c) the power factor and the load impedance.

**Solution:**

(a) For the rms values of the voltage and current, we write

$$\mathbf{V}_{\text{rms}} = \frac{60}{\sqrt{2}} \angle -10^\circ, \quad \mathbf{I}_{\text{rms}} = \frac{1.5}{\sqrt{2}} \angle +50^\circ$$

The complex power is

$$\mathbf{S} = \mathbf{V}_{\text{rms}} \mathbf{I}_{\text{rms}}^* = \left( \frac{60}{\sqrt{2}} \angle -10^\circ \right) \left( \frac{1.5}{\sqrt{2}} \angle -50^\circ \right) = 45 \angle -60^\circ \text{ VA}$$

The apparent power is

$$S = |\mathbf{S}| = 45 \text{ VA}$$

(b) We can express the complex power in rectangular form as

$$\mathbf{S} = 45 \angle -60^\circ = 45 [\cos(-60^\circ) + j \sin(-60^\circ)] = 22.5 - j38.97$$

Since  $\mathbf{S} = P + jQ$ , the real power is

$$P = 22.5 \text{ W}$$

while the reactive power is

$$Q = -38.97 \text{ VAR}$$

(c) The power factor is

$$\text{pf} = \cos(-60^\circ) = 0.5 \text{ (leading)}$$

It is leading, because the reactive power is negative. The load impedance is

$$\mathbf{Z} = \frac{\mathbf{V}}{\mathbf{I}} = \frac{60 \angle -10^\circ}{1.5 \angle +50^\circ} = 40 \angle -60^\circ \Omega$$

which is a capacitive impedance.

①写出电压、电流的相量形式（用有效值表示）

②写出复功率

$$\mathbf{S} = \mathbf{V}_{\text{rms}} (\mathbf{I}_{\text{rms}})^*$$

③依次写出其他功率量



## Example 11.12

- 单位 VA，说明是“视在功率”
- lagging → 电流 lags 电压 → 感性负载

①根据视在功率和功率因数，可以写出复功率，以及复功率的实部（平均功率）、虚部（无功功率）

②有了复功率，根据电压有效值，可以写出电流有效值

③根据电压电流求阻抗

A load  $\mathbf{Z}$  draws 12 kVA at a power factor of 0.856 lagging from a 120-V rms sinusoidal source. Calculate: (a) the average and reactive powers delivered to the load, (b) the peak current, and (c) the load impedance.

### Solution:

(a) Given that  $\text{pf} = \cos \theta = 0.856$ , we obtain the power angle as  $\theta = \cos^{-1} 0.856 = 31.13^\circ$ . If the apparent power is  $S = 12,000$  VA, then the average or real power is

$$P = S \cos \theta = 12,000 \times 0.856 = 10.272 \text{ kW}$$

while the reactive power is

$$Q = S \sin \theta = 12,000 \times 0.517 = 6.204 \text{ kVA}$$

(b) Since the pf is lagging, the complex power is

$$\mathbf{S} = P + jQ = 10.272 + j6.204 \text{ kVA}$$

From  $\mathbf{S} = \mathbf{V}_{\text{rms}} \mathbf{I}_{\text{rms}}^*$ , we obtain

$$\mathbf{I}_{\text{rms}}^* = \frac{\mathbf{S}}{\mathbf{V}_{\text{rms}}} = \frac{10,272 + j6,204}{120 \angle 0^\circ} = 85.6 + j51.7 \text{ A} = 100 \angle 31.13^\circ \text{ A}$$

Thus  $\mathbf{I}_{\text{rms}} = 100 \angle -31.13^\circ$  and the peak current is

$$I_m = \sqrt{2} I_{\text{rms}} = \sqrt{2}(100) = 141.4 \text{ A}$$


(c) The load impedance

$$\mathbf{Z} = \frac{\mathbf{V}_{\text{rms}}}{\mathbf{I}_{\text{rms}}} = \frac{120 \angle 0^\circ}{100 \angle -31.13^\circ} = 1.2 \angle 31.13^\circ \Omega$$


which is an inductive impedance.
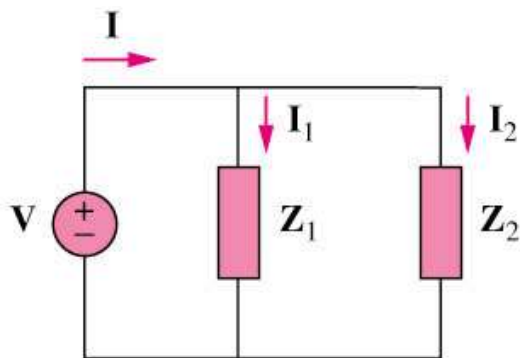
# 11.6 Conservation of AC Power 交流功率守恒

The **complex, real, and reactive powers** of the sources **equal** the respective **sums of** the complex, real, and reactive powers of the **individual loads**.



(a)

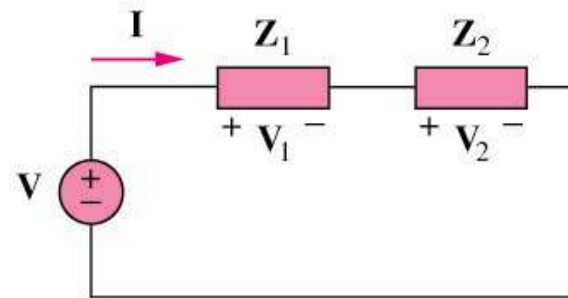

(b)

$$S = VI^* = V(I_1^* + I_2^*) = VI_1^* + VI_2^* = S_1 + S_2$$

$$S = VI^* = (V_1 + V_2)I^* = V_1I^* + V_2I^* = S_1 + S_2$$

$$S = S_1 + S_2 + \cdots + S_N$$


复数的加减是实部虚部的  
加减，不是幅度的加减

复功率、有功功率、无功功率满足相加性，视在功率不满足



## Example 11.13

Figure 11.24 shows a load being fed by a voltage source through a transmission line. The impedance of the line is represented by the  $(4 + j2) \Omega$  impedance and a return path. Find the real power and reactive power absorbed by: (a) the source, (b) the line, and (c) the load.   
supplied by

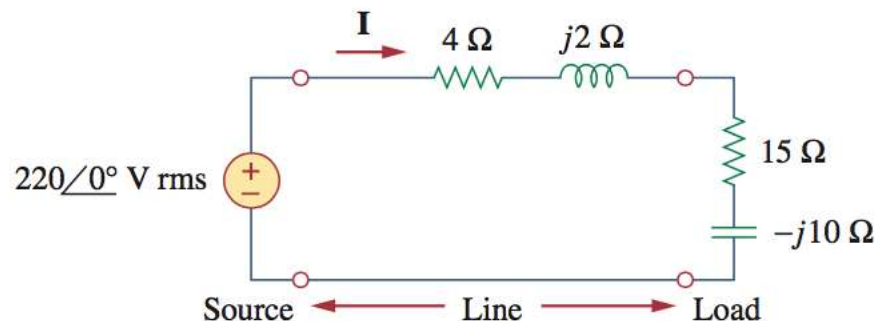

**Figure 11.24**

For Example 11.13.

$$\mathbf{Z} = (4 + j2) + (15 - j10) = 19 - j8 = 20.62 \angle -22.83^\circ \Omega \quad \mathbf{I} = \frac{\mathbf{V}_s}{\mathbf{Z}} = \frac{220 \angle 0^\circ}{20.62 \angle -22.83^\circ} = 10.67 \angle 22.83^\circ \text{ A rms}$$


$$\begin{aligned} \mathbf{S}_s &= \mathbf{V}_s \mathbf{I}^* = (220 \angle 0^\circ)(10.67 \angle -22.83^\circ) \\ &= 2347.4 \angle -22.83^\circ = (2163.5 - j910.8) \text{ VA} \end{aligned}$$

$$\begin{aligned} \mathbf{S}_{\text{line}} &= \mathbf{V}_{\text{line}} \mathbf{I}^* = (47.72 \angle 49.4^\circ)(10.67 \angle -22.83^\circ) \\ &= 509.2 \angle 26.57^\circ = 455.4 + j227.7 \text{ VA} \end{aligned}$$

$$\mathbf{S}_s = \mathbf{S}_{\text{line}} + \mathbf{S}_L$$

$$\begin{aligned} \mathbf{S}_L &= \mathbf{V}_L \mathbf{I}^* = (192.38 \angle -10.87^\circ)(10.67 \angle -22.83^\circ) \\ &= 2053 \angle -33.7^\circ = (1708 - j1139) \text{ VA} \end{aligned}$$

## Example 11.14

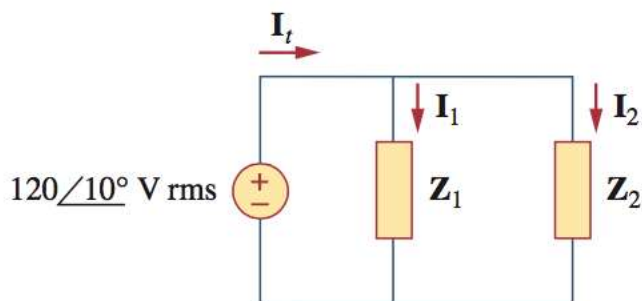

**Figure 11.26** 根据  $\mathbf{VI}$  写出复功率  
For Example 11.14.

In the circuit of Fig. 11.26,  $\mathbf{Z}_1 = 60\angle-30^\circ \Omega$  and  $\mathbf{Z}_2 = 40\angle45^\circ \Omega$ . Calculate the total: (a) apparent power, (b) real power, (c) reactive power, and (d) pf, supplied by the source and seen by the source.

### Solution:

The current through  $\mathbf{Z}_1$  is

$$\mathbf{I}_1 = \frac{\mathbf{V}}{\mathbf{Z}_1} = \frac{120\angle10^\circ}{60\angle-30^\circ} = 2\angle40^\circ \text{ A rms}$$

while the current through  $\mathbf{Z}_2$  is

$$\mathbf{I}_2 = \frac{\mathbf{V}}{\mathbf{Z}_2} = \frac{120\angle10^\circ}{40\angle45^\circ} = 3\angle-35^\circ \text{ A rms}$$

The complex powers absorbed by the impedances are

$$\mathbf{S}_1 = \frac{V_{\text{rms}}^2}{\mathbf{Z}_1^*} = \frac{(120)^2}{60\angle30^\circ} = 240\angle-30^\circ = 207.85 - j120 \text{ VA}$$

$$\mathbf{S}_2 = \frac{V_{\text{rms}}^2}{\mathbf{Z}_2^*} = \frac{(120)^2}{40\angle-45^\circ} = 360\angle45^\circ = 254.6 + j254.6 \text{ VA}$$

The total complex power is

$$\mathbf{S}_t = \mathbf{S}_1 + \mathbf{S}_2 = 462.4 + j134.6 \text{ VA}$$

(a) The total apparent power is

$$|\mathbf{S}_t| = \sqrt{462.4^2 + 134.6^2} = 481.6 \text{ VA.}$$

(b) The total real power is

$$P_t = \text{Re}(\mathbf{S}_t) = 462.4 \text{ W or } P_t = P_1 + P_2.$$

(c) The total reactive power is

$$Q_t = \text{Im}(\mathbf{S}_t) = 134.6 \text{ VAR or } Q_t = Q_1 + Q_2.$$

(d) The pf =  $P_t/|\mathbf{S}_t| = 462.4/481.6 = 0.96$  (lagging).

We may cross check the result by finding the complex power  $\mathbf{S}_s$  supplied by the source.

$$\begin{aligned} \mathbf{I}_t &= \mathbf{I}_1 + \mathbf{I}_2 = (1.532 + j1.286) + (2.457 - j1.721) \\ &= 4 - j0.435 = 4.024\angle-6.21^\circ \text{ A rms} \end{aligned}$$



$$\begin{aligned} \mathbf{S}_s &= \mathbf{V}\mathbf{I}_t^* = (120\angle10^\circ)(4.024\angle6.21^\circ) \\ &= 482.88\angle16.21^\circ = 463 + j135 \text{ VA} \end{aligned}$$

which is the same as before.

# 11.7 Power Factor Correction 功率因数校正

Power factor correction is the process of increasing the power factor without altering the voltage or current to the original load.



大部分家用电器都是感性负载  
→ low lagging pf

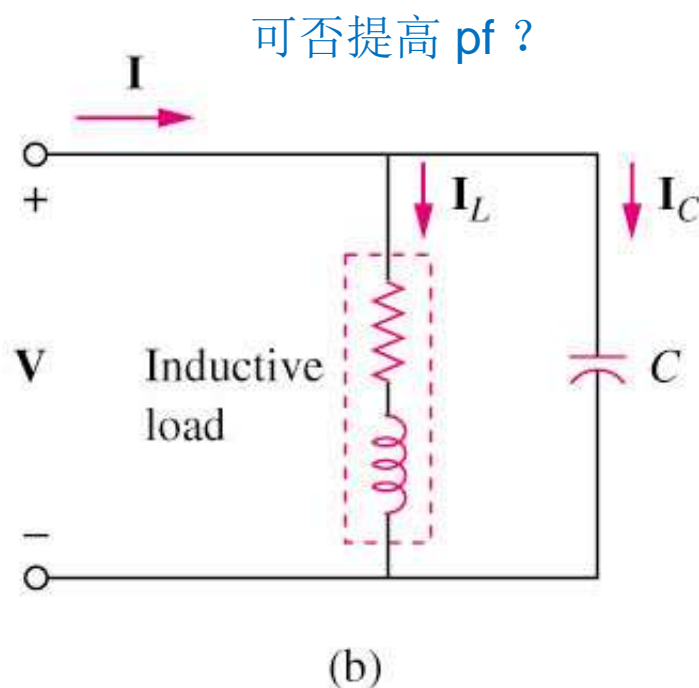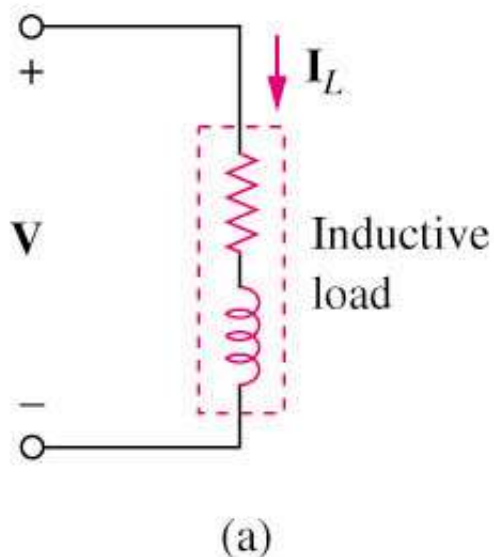


Power factor correction is necessary for economic reason.

国家电网是根据视在功率收费的

# 11.7 Power Factor Correction

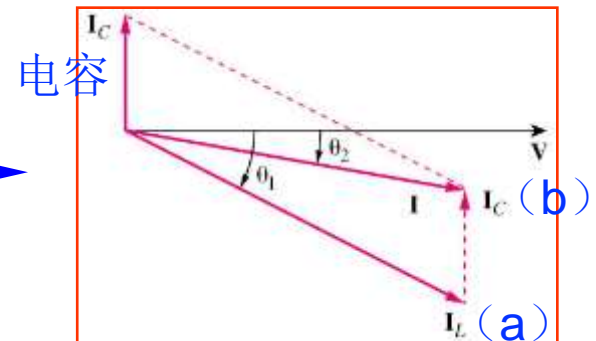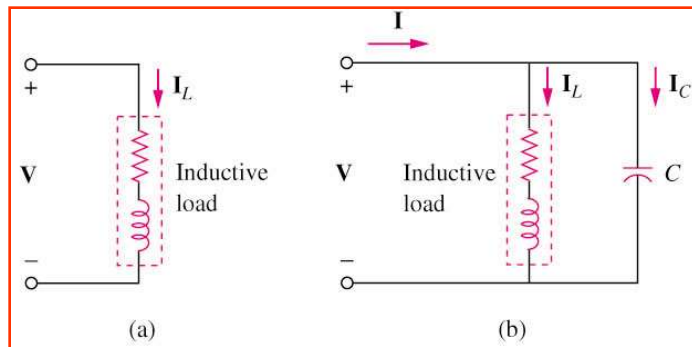

电阻不变，  
所以投影到  
横坐标的值  
不变

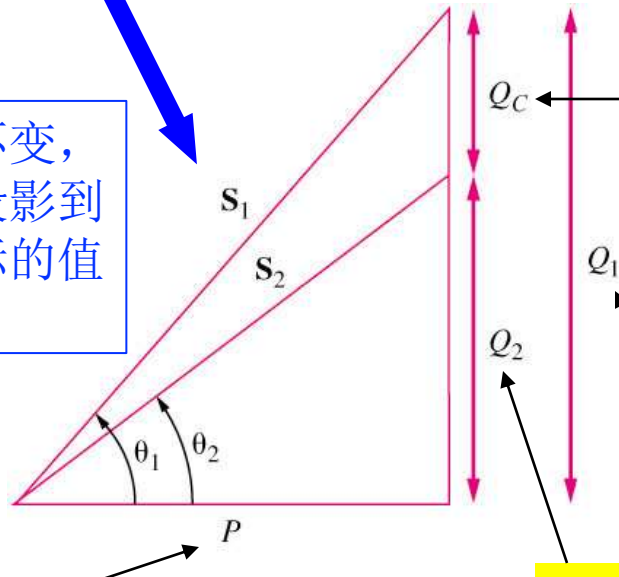

$$Q_c = Q_1 - Q_2$$

$$= P (\tan \theta_1 - \tan \theta_2)$$

$$Q_c = V_{rms}^2 / X_C = \omega C V_{rms}^2$$

$$S = I_{rms}^2 Z = \frac{V_{rms}^2}{Z^*}$$

$$Y_2 = Y_1 + j\omega C$$

$$S_2 = S_1 - V_{rms}^2 \cdot j\omega C$$

$$Q_1 = S_1 \sin \theta_1$$

$$= P \tan \theta_1$$

$$C = \frac{Q_c}{\omega V_{rms}^2} = \frac{P (\tan \theta_1 - \tan \theta_2)}{\omega V_{rms}^2}$$

$$P = S_1 \cos \theta_1$$

$$Q_2 = P \tan \theta_2$$





## Example 11.15

单位 kW，说明是平均功率

When connected to a 120-V (rms), 60-Hz power line, a load absorbs 4 kW at a lagging power factor of 0.8. Find the value of capacitance necessary to raise the pf to 0.95.

### Solution:

If the pf = 0.8, then

$$\cos \theta_1 = 0.8 \quad \Rightarrow \quad \theta_1 = 36.87^\circ$$

where  $\theta_1$  is the phase difference between voltage and current. We obtain the apparent power from the real power and the pf as


$$S_1 = \frac{P}{\cos \theta_1} = \frac{4000}{0.8} = 5000 \text{ VA}$$

The reactive power is

$$Q_1 = S_1 \sin \theta = 5000 \sin 36.87 = 3000 \text{ VAR}$$

When the pf is raised to 0.95,
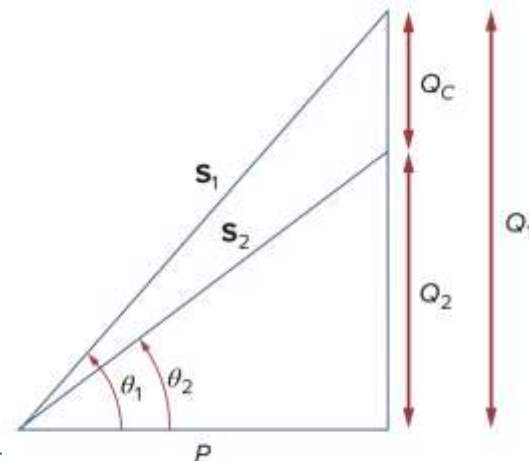
$$\cos \theta_2 = 0.95 \quad \Rightarrow \quad \theta_2 = 18.19^\circ$$



The real power  $P$  has not changed. But the apparent power has changed; its new value is

$$S_2 = \frac{P}{\cos \theta_2} = \frac{4000}{0.95} = 4210.5 \text{ VA}$$

The new reactive power is

$$Q_2 = S_2 \sin \theta_2 = 1314.4 \text{ VAR}$$

The difference between the new and old reactive powers is due to the parallel addition of the capacitor to the load. The reactive power due to the capacitor is

$$Q_C = Q_1 - Q_2 = 3000 - 1314.4 = 1685.6 \text{ VAR}$$


and

$$C = \frac{Q_C}{\omega V_{\text{rms}}^2} = \frac{1685.6}{2\pi \times 60 \times 120^2} = 310.5 \mu\text{F}$$

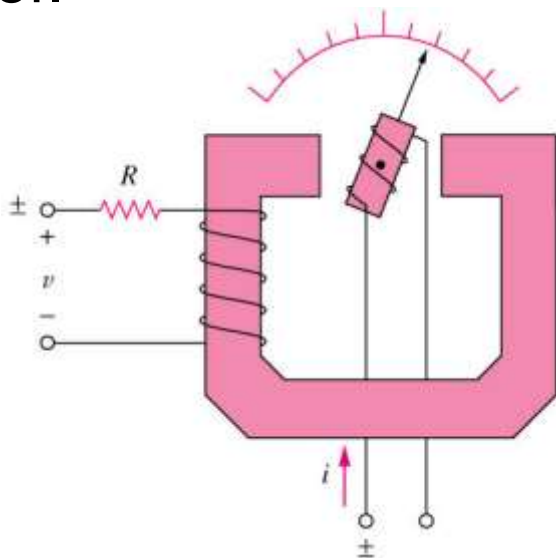
# 11.8 Power Measurement

测量得到的是平均功率（有功功率）

The wattmeter is the instrument for measuring the average power.



The basic structure

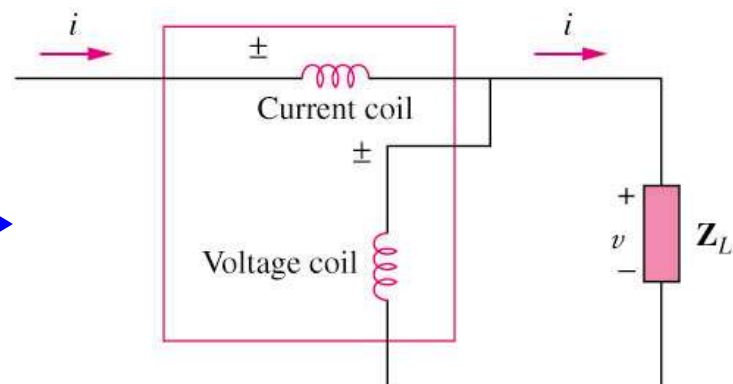

Equivalent Circuit with load

If  $v(t) = V_m \cos(\omega t + \theta_v)$  and  $i(t) = I_m \cos(\omega t + \theta_i)$

$$P = |V_{\text{rms}}| |I_{\text{rms}}| \cos(\theta_v - \theta_i) = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)$$

# Three-Phase Circuits


## Chapter 12 三相电路

- 12.1 What is a Three-Phase Circuit?
- 12.2 Balanced Three-Phase Voltages
- 12.3 Balanced Three-Phase Connection
- 12.4 Power in a Balanced System
- 12.5 Unbalanced Three-Phase Systems
- 12.6 Application – Residential Wiring


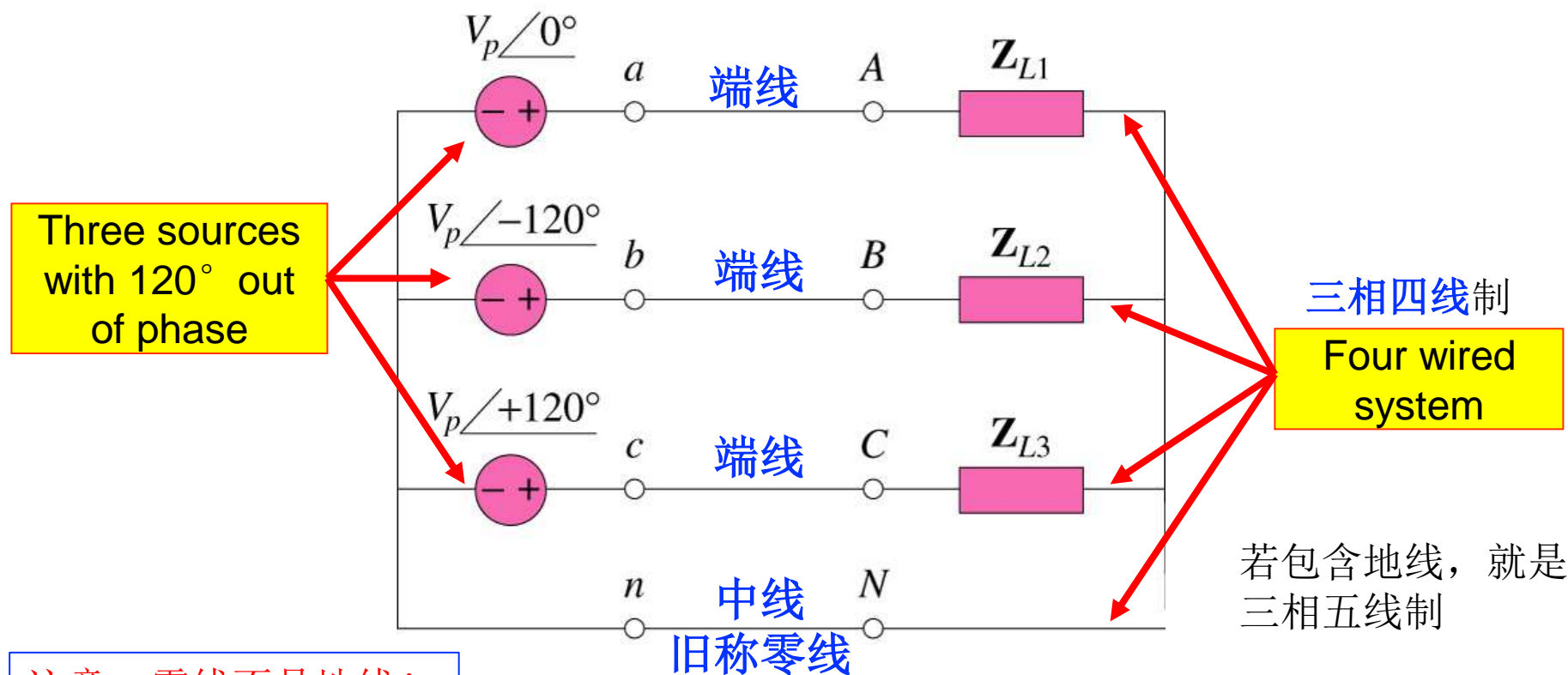
# 12.1 What is a Three-Phase Circuit?

- It is a system produced by a generator consisting of **three sources** having the same amplitude and frequency but **out of phase** with each other by  $120^\circ$ .




注意：零线不是地线！

# 12.1 What is a Three-Phase Circuit?


## Advantages:

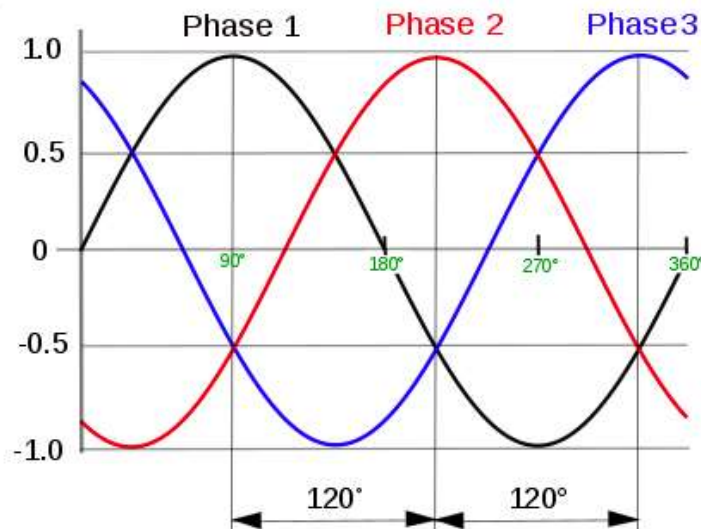1. Most of the electric power is generated and distributed in three-phase.
2. The instantaneous power in a three-phase system can be constant. 瞬时功率和为常数
3. The amount of power, the three-phase system is more economical than the single-phase. 发电机容易做
4. In fact, the amount of wire required for a three-phase system is less than that required for an equivalent single-phase system.




## 12.2 Balanced Three-Phase Voltages

- A three-phase generator consists of a rotating magnet (rotor) surrounded by a stationary winding (stator).

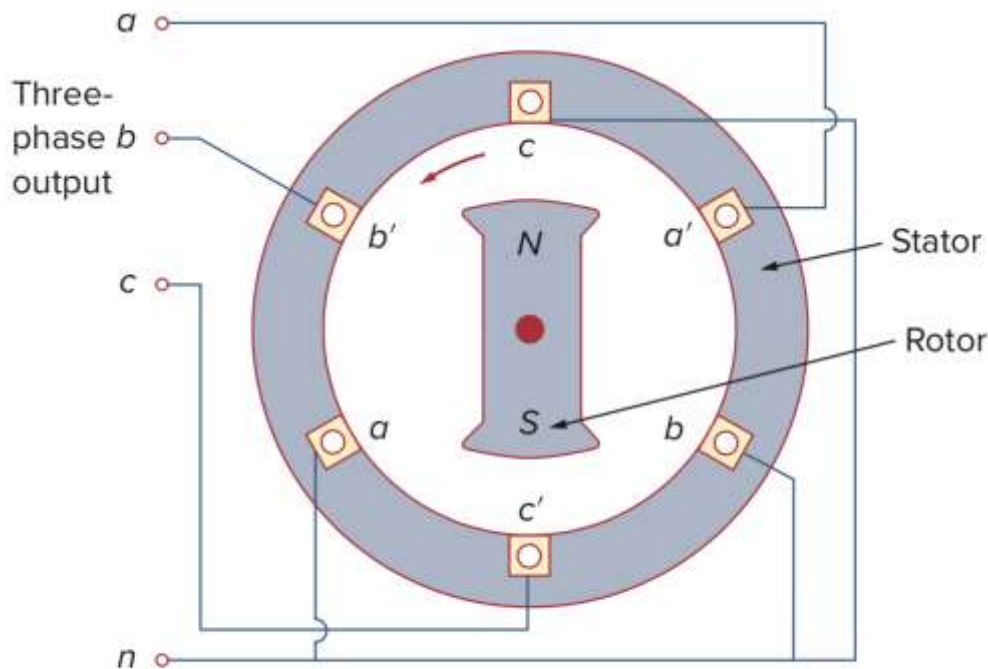



**Figure 12.4**  
A three-phase generator.

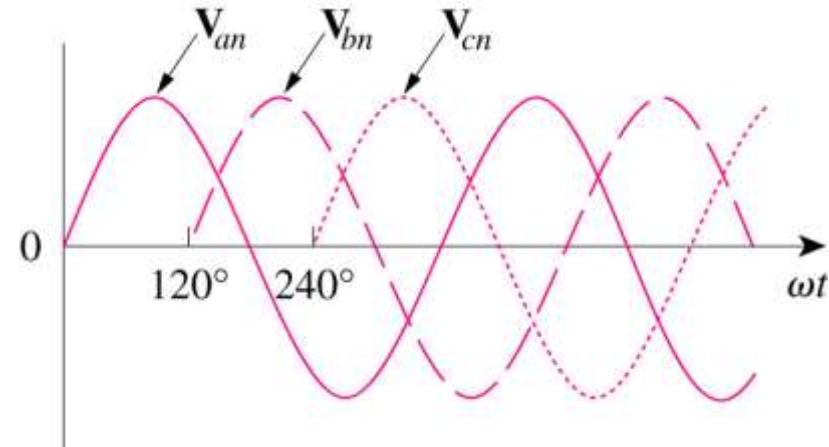

The generated voltages

# 12.2 Balanced Three-Phase Voltages

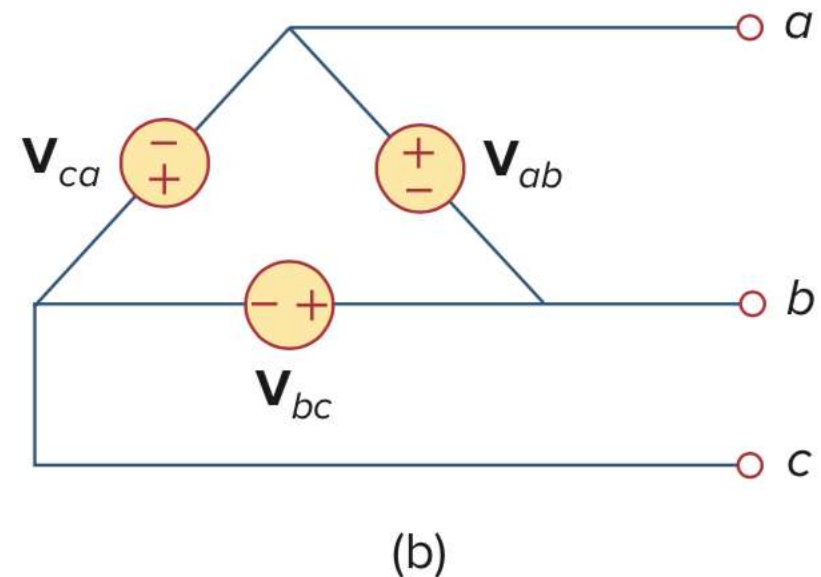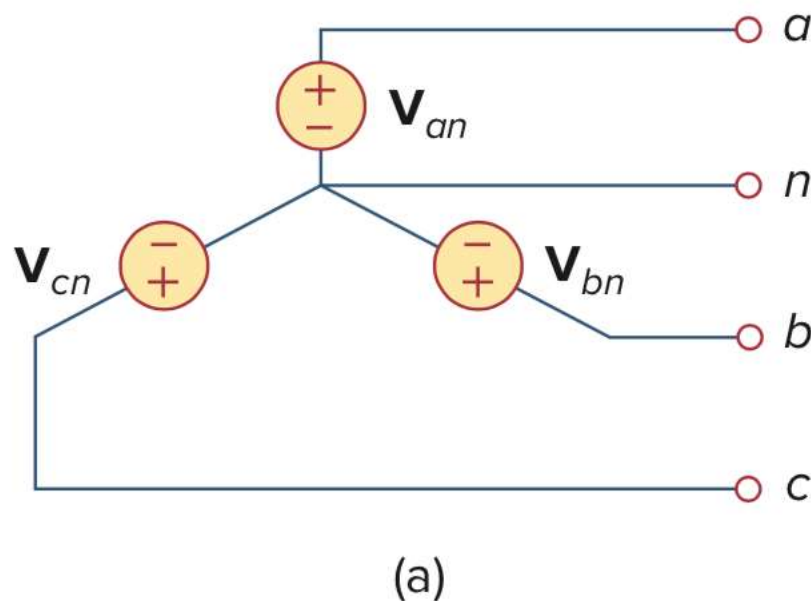- Two possible configurations:

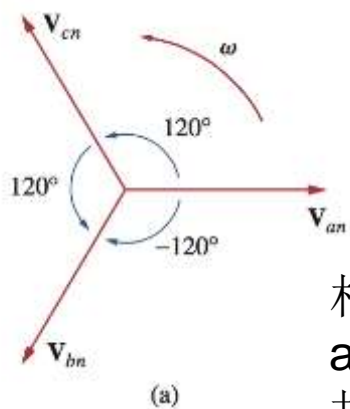


**Figure 12.6**

Three-phase voltage sources: (a) Y-connected source, (b)  $\Delta$ -connected source.


## 12.2 Balanced Three-Phase Voltages

- **Balanced phase voltages** （平衡相电压） are equal in magnitude and are out of phase with each other by  $120^\circ$  .
- The **phase sequence** （相序） is the time order in which the voltages pass through their respective maximum values.



$$\begin{aligned} V_{an} &= V_p \angle 0^\circ \\ V_{bn} &= V_p \angle -120^\circ \\ V_{cn} &= V_p \angle -240^\circ = V_p \angle +120^\circ \end{aligned}$$

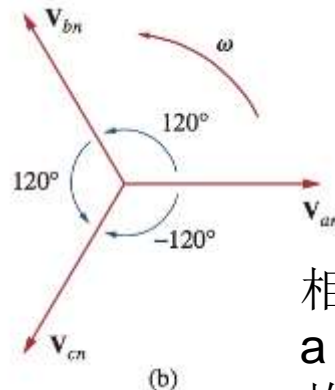相位关系：  
a leads b, b leads c  
故称为**abc序列**，或顺序  
【电力系统常用】




$$\begin{aligned} V_{an} &= V_p \angle 0^\circ \\ V_{cn} &= V_p \angle -120^\circ \\ V_{bn} &= V_p \angle -240^\circ = V_p \angle +120^\circ \end{aligned}$$

相位关系：  
a leads c, c leads b  
故称为**acb序列**，或逆序



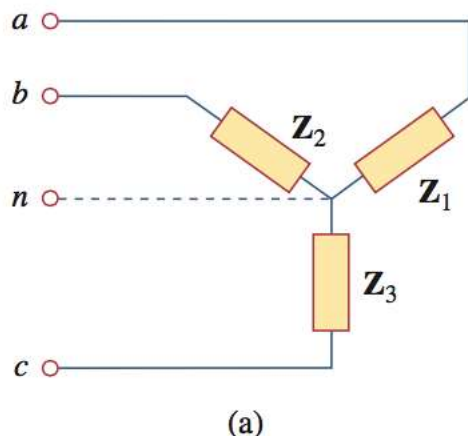• A **balanced load** (平衡负载) is one in which the phase impedances are equal in magnitude and in phase



For a *balanced* wye-connected load,


$$\mathbf{Z}_1 = \mathbf{Z}_2 = \mathbf{Z}_3 = \mathbf{Z}_Y$$

where  $\mathbf{Z}_Y$  is the load impedance per phase. For a *balanced* delta-connected load,

$$\mathbf{Z}_a = \mathbf{Z}_b = \mathbf{Z}_c = \mathbf{Z}_\Delta \quad (12.7)$$

where  $\mathbf{Z}_\Delta$  is the load impedance per phase in this case. We recall from Eq. (9.69) that

$$\mathbf{Z}_\Delta = 3\mathbf{Z}_Y \quad \text{or} \quad \mathbf{Z}_Y = \frac{1}{3}\mathbf{Z}_\Delta \quad (12.8)$$

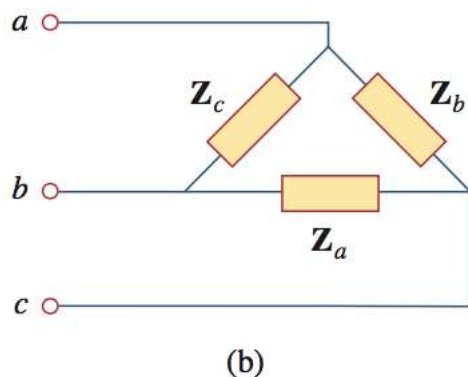

**Figure 12.8**

Two possible three-phase load configurations: (a) a Y-connected load, (b) a  $\Delta$ -connected load.



## Example 12.1

Determine the phase sequence of the set of voltages

$$v_{an} = 200 \cos(\omega t + 10^\circ)$$

$$v_{bn} = 200 \cos(\omega t - 230^\circ), \quad v_{cn} = 200 \cos(\omega t - 110^\circ)$$

### Solution:

The voltages can be expressed in phasor form as

$$\mathbf{V}_{an} = 200 \angle 10^\circ \text{ V}, \quad \mathbf{V}_{bn} = 200 \angle -230^\circ \text{ V}, \quad \mathbf{V}_{cn} = 200 \angle -110^\circ \text{ V}$$

We notice that  $\mathbf{V}_{an}$  leads  $\mathbf{V}_{cn}$  by  $120^\circ$  and  $\mathbf{V}_{cn}$  in turn leads  $\mathbf{V}_{bn}$  by  $120^\circ$ . Hence, we have an *acb* sequence.

## 12.3 Balanced Three-Phase Connection

- Four possible connections
  1. Y-Y connection (Y-connected source with a Y-connected load) 最容易理解
  2. Y- $\Delta$  connection (Y-connected source with a  $\Delta$ -connected load) 最常用
  3.  $\Delta$ - $\Delta$  connection
  4.  $\Delta$ -Y connection

电源端若是 $\Delta$ 连接，则不能接中线，所以一般电源端都是Y连接


# 三相电的电压电流概念

## • 线电压、线电流

- 流经**输电线**中的电流，称为线电流
- 各**输电线之间**的电压，称为线电压
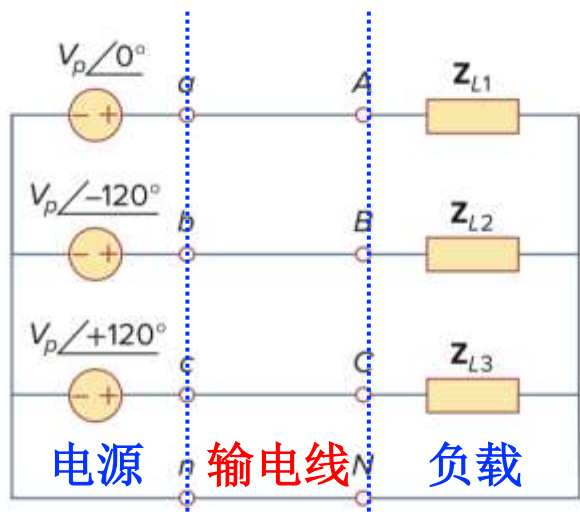
## • 相电压、相电流


- 三相电源或三相负载中，**每一相的电压**，称为相电压
- 三相电源或三相负载中，**每一相的电流**，称为相电流



实际三相电路中，三相电源是对称的，三条端线阻抗是相等的，但负载阻抗不一定是相等的。  
负载阻抗相等的情况，称为**平衡三相电**
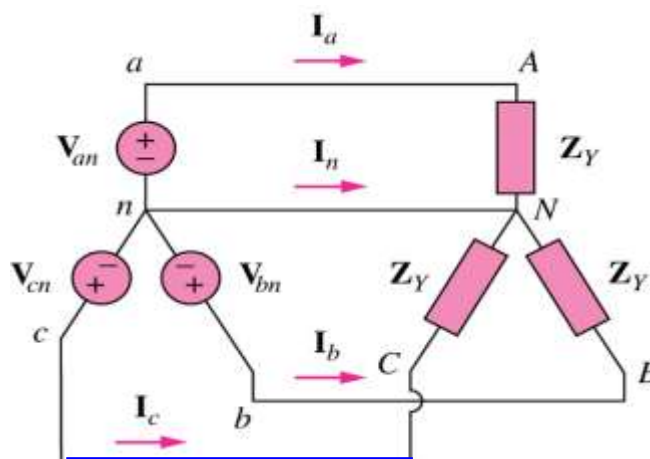
## 12.3 Balanced Three-Phase Connection

- A **balanced Y-Y** system is a three-phase system with a balanced Y-connected source and a balanced Y-connected load.



Phase voltage, **相电压**, 即电源或负载中每一相的电压, 相线 (火线, abc) 与中线 (零线, n) 之间的电压

$$V_{an} = V_p \angle 0^\circ$$


$$V_{bn} = V_p \angle -120^\circ, \quad V_{cn} = V_p \angle +120^\circ$$

Line-to-line voltage, **线电压**, 即输电线 abc 两两之间的电压 (ab, bc, ca)

$$\begin{aligned} V_{ab} &= V_{an} + V_{nb} = V_{an} - V_{bn} = V_p \angle 0^\circ - V_p \angle -120^\circ \\ &= V_p \left( 1 + \frac{1}{2} + j\frac{\sqrt{3}}{2} \right) = \sqrt{3} V_p \angle 30^\circ \end{aligned}$$

$$V_{bc} = V_{bn} - V_{cn} = \sqrt{3} V_p \angle -90^\circ$$
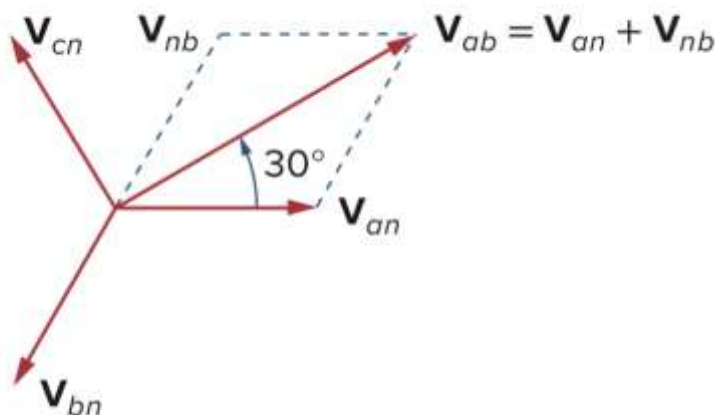
$$V_{ca} = V_{cn} - V_{an} = \sqrt{3} V_p \angle -210^\circ$$





$$V_L = \sqrt{3} V_p, \text{ where}$$

$$V_p = |V_{an}| = |V_{bn}| = |V_{cn}|$$

$$V_L = |V_{ab}| = |V_{bc}| = |V_{ca}|$$
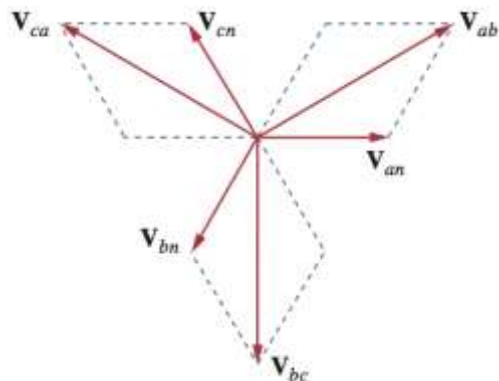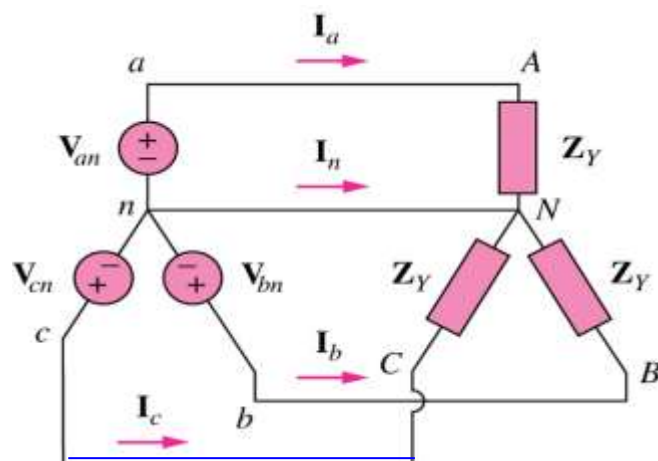
## 12.3 Balanced Three-Phase Connection

- A **balanced Y-Y** system is a three-phase system with a balanced Y-connected source and a balanced Y-connected load.



While the **line current** is the current in each line, the **phase current** is the current in each phase of the source or load. In the Y-Y system, the line current is the same as the phase current. We will use single subscripts

**线电流**: 流经输电线中的电流; **相电流**: 电源或负载中每一相的电流; 对于Y-Y连接, **线电流 = 相电流**


$$I_a = \frac{V_{an}}{Z_Y}, \quad I_b = \frac{V_{bn}}{Z_Y} = \frac{V_{an} \angle -120^\circ}{Z_Y} = I_a \angle -120^\circ$$

$$I_c = \frac{V_{cn}}{Z_Y} = \frac{V_{an} \angle -240^\circ}{Z_Y} = I_a \angle -240^\circ$$

中线几乎无电流, 线可以细一点, 省材料

$$I_a + I_b + I_c = 0$$


$$I_n = -(I_a + I_b + I_c) = 0$$

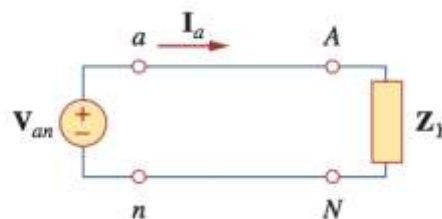

可以单独拿出一相作分析

$$I_a = \frac{V_{an}}{Z_Y}$$


**Figure 12.12**  
A single-phase equivalent circuit.

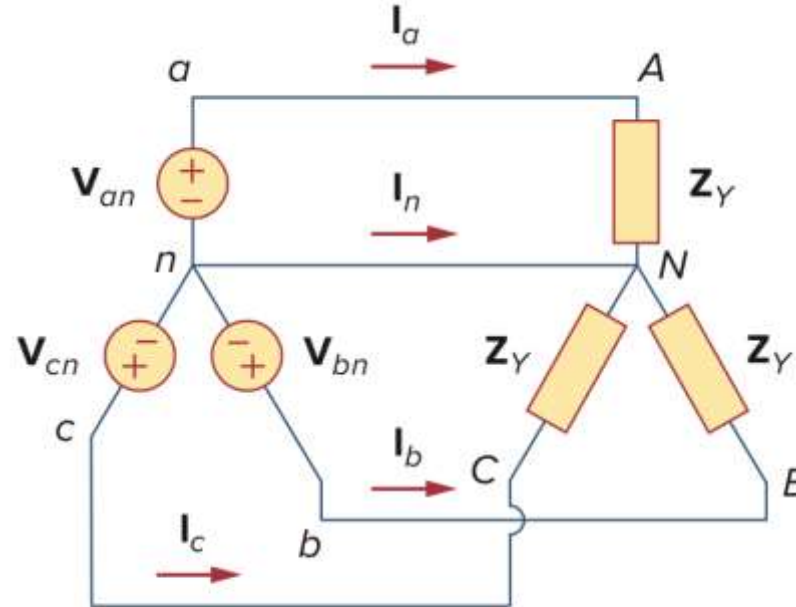

**Figure 12.10**  
Balanced Y-Y connection.

Connection	Phase voltages/currents	Line voltages/currents
Y-Y	$V_{an} = V_p \angle 0^\circ$	$V_{ab} = \sqrt{3} V_p \angle 30^\circ$
	$V_{bn} = V_p \angle -120^\circ$	$V_{bc} = V_{ab} \angle -120^\circ$
	$V_{cn} = V_p \angle +120^\circ$	$V_{ca} = V_{ab} \angle +120^\circ$
	Same as line currents	$I_a = V_{an} / Z_Y$
		$I_b = I_a \angle -120^\circ$
		$I_c = I_a \angle +120^\circ$



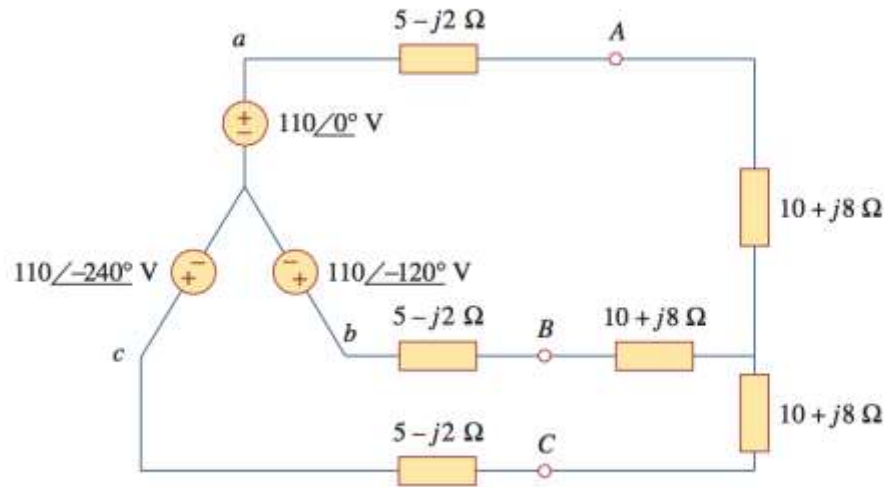


**Figure 12.13**

Three-wire Y-Y system; for Example 12.2.

Y-Y情况下，  
把中线添加回去，简化分析

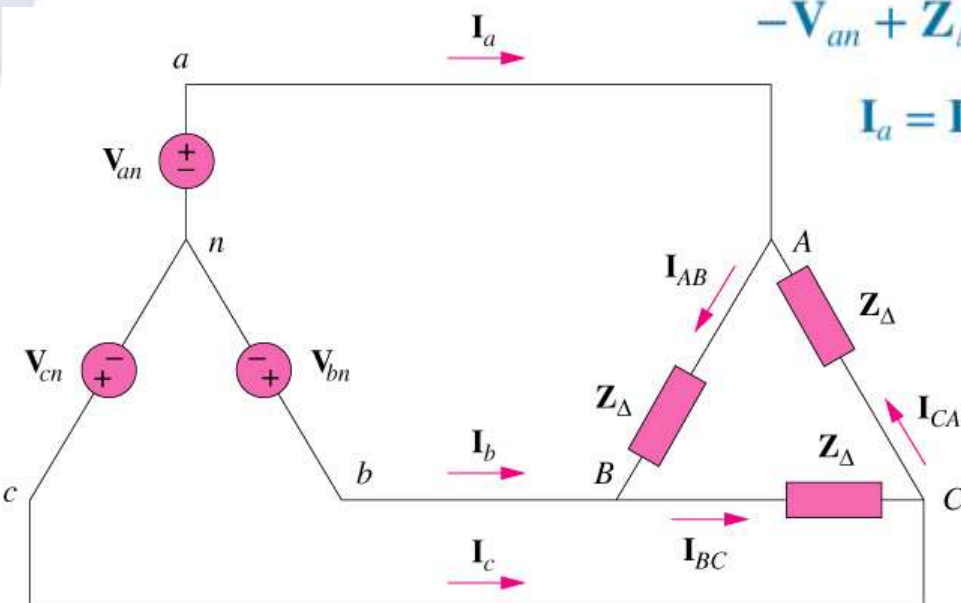
## 12.3 Balanced Three-Phase Connection

- A **balanced Y- $\Delta$**  system is a three-phase system with a balanced Y-connected source and a balanced  $\Delta$ -connected load.



$$-V_{an} + Z_{\Delta} I_{AB} + V_{bn} = 0 \quad I_{AB} = \frac{V_{an} - V_{bn}}{Z_{\Delta}} = \frac{V_{ab}}{Z_{\Delta}} = \frac{V_{AB}}{Z_{\Delta}}$$
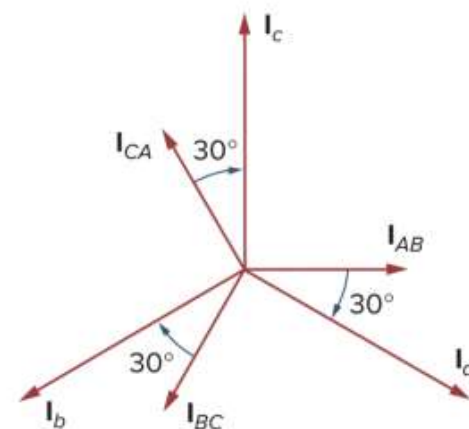
$$I_a = I_{AB} - I_{CA} = I_{AB}(1 - 1 \angle -240^\circ) \\ = I_{AB}(1 + 0.5 - j0.866) = I_{AB}\sqrt{3} \angle -30^\circ$$




- 相电压看源端  $V_{an} = V_p \angle 0^\circ$
- 相电流看负载端
- 线电压线电流无歧义

$$V_{ab} = \sqrt{3} V_p \angle 30^\circ = V_{AB}$$

$$I_L = \sqrt{3} I_p, \text{ where}$$

$$I_L = |I_a| = |I_b| = |I_c|$$

$$I_p = |I_{AB}| = |I_{BC}| = |I_{CA}|$$

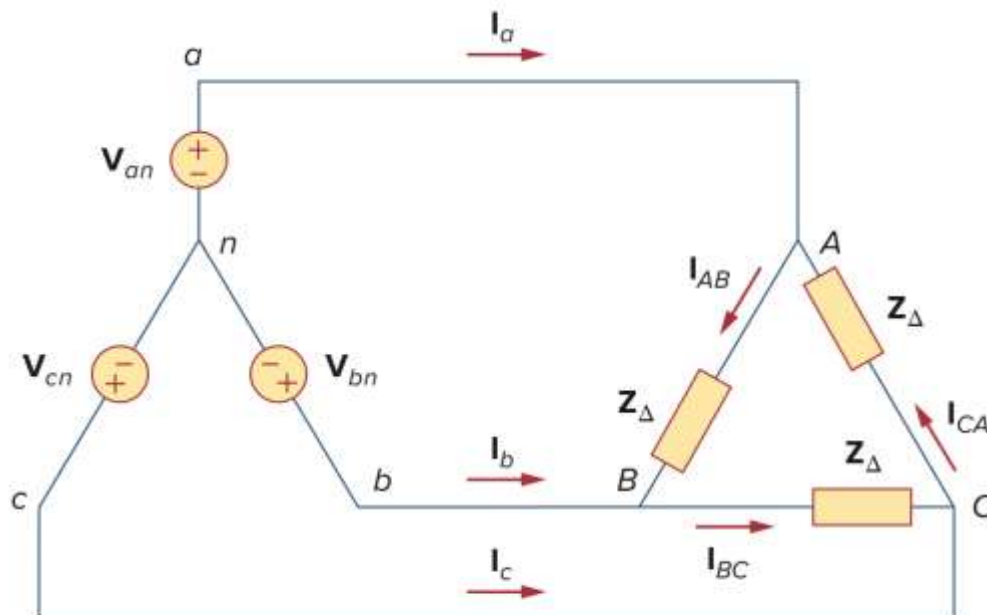


**Figure 12.14**  
Balanced Y-Δ connection.

Connection	Phase voltages/currents	Line voltages/currents
Y-Δ	$\begin{aligned} V_{an} &= V_p \angle 0^\circ \\ V_{bn} &= V_p \angle -120^\circ \\ V_{cn} &= V_p \angle +120^\circ \\ I_{AB} &= V_{AB} / Z_\Delta \\ I_{BC} &= V_{BC} / Z_\Delta \\ I_{CA} &= V_{CA} / Z_\Delta \end{aligned}$	$\begin{aligned} V_{ab} &= V_{AB} = \sqrt{3} V_p \angle 30^\circ \\ V_{bc} &= V_{BC} = V_{ab} \angle -120^\circ \\ V_{ca} &= V_{CA} = V_{ab} \angle +120^\circ \\ I_a &= I_{AB} \sqrt{3} \angle -30^\circ \\ I_b &= I_a \angle -120^\circ \\ I_c &= I_a \angle +120^\circ \end{aligned}$

## Example 12.3

A balanced  $abc$ -sequence Y-connected source with  $\mathbf{V}_{an} = 100\angle 10^\circ$  V is connected to a  $\Delta$ -connected balanced load  $(8 + j4) \Omega$  per phase. Calculate the phase and line currents.

把负载的 $\Delta$ 转换成Y后，用Y-Y的单相计算

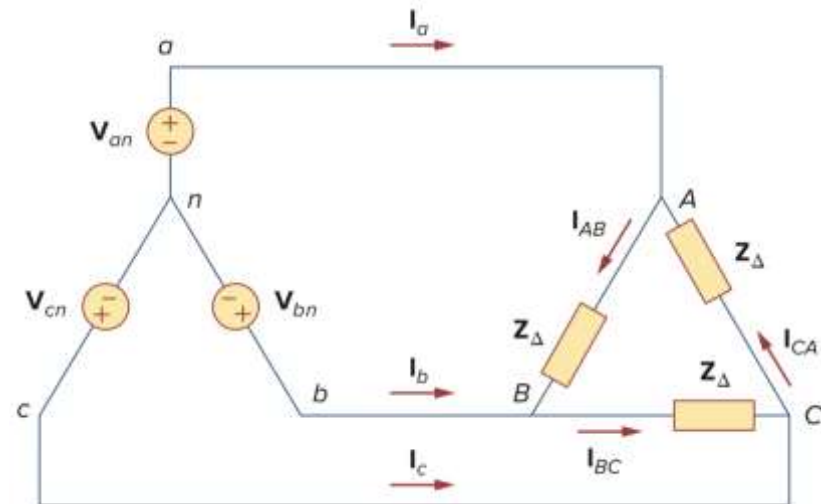


■ **METHOD 2** Alternatively, using single-phase analysis,


$$\mathbf{I}_a = \frac{\mathbf{V}_{an}}{\mathbf{Z}_{\Delta}/3} = \frac{100\angle 10^\circ}{2.981\angle 26.57^\circ} = 33.54\angle -16.57^\circ \text{ A}$$

as above. Other line currents are obtained using the  $abc$  phase sequence.

## 12.3 Balance Three-Phase Connection (6)

- A **balanced  $\Delta$ - $\Delta$**  system is a three-phase system with a balanced  $\Delta$ -connected source and a balanced  $\Delta$ -connected load.

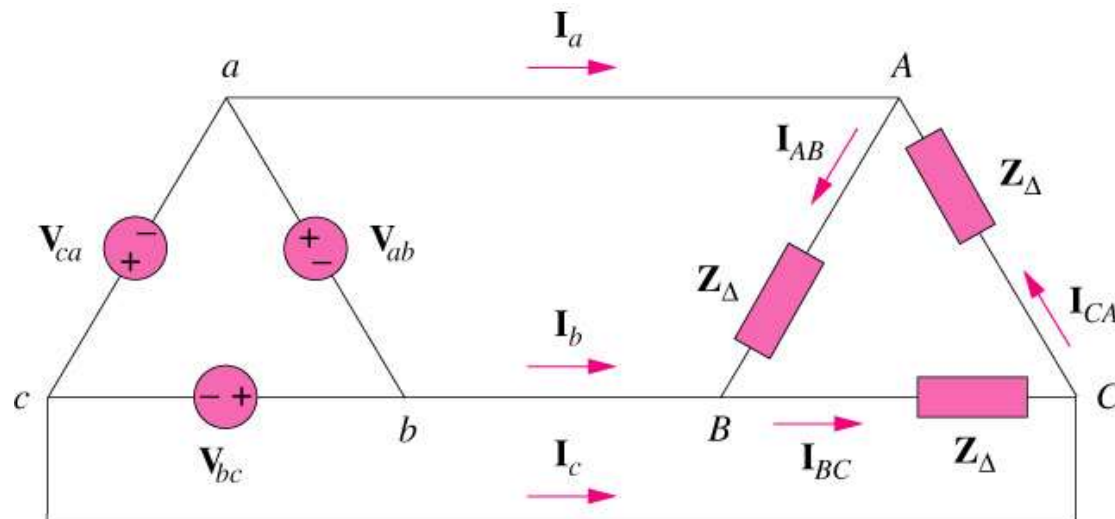

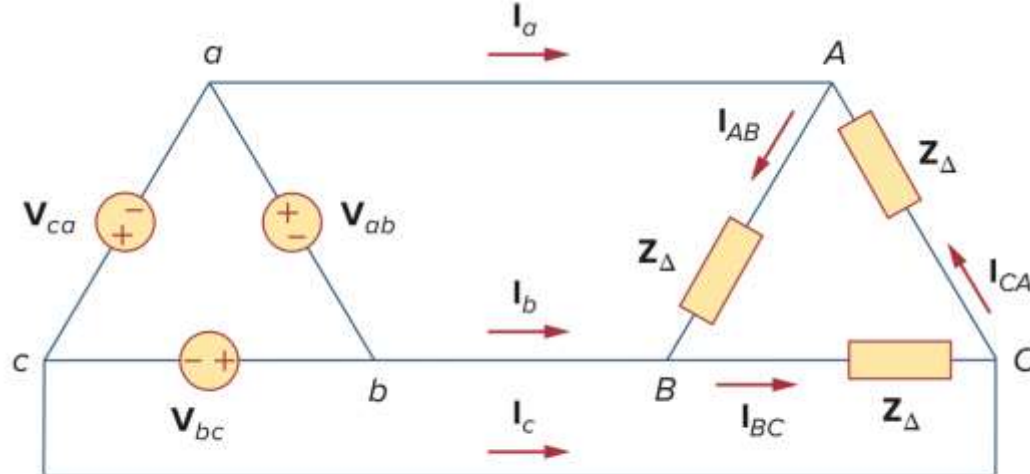


**Figure 12.17**  
A balanced  $\Delta$ - $\Delta$  connection.


Connection	Phase voltages/currents	Line voltages/currents
$\Delta$ - $\Delta$	$\mathbf{V}_{ab} = V_p \angle 0^\circ$ $\mathbf{V}_{bc} = V_p \angle -120^\circ$ $\mathbf{V}_{ca} = V_p \angle +120^\circ$ $\mathbf{I}_{AB} = \mathbf{V}_{ab} / \mathbf{Z}_\Delta$ $\mathbf{I}_{BC} = \mathbf{V}_{bc} / \mathbf{Z}_\Delta$ $\mathbf{I}_{CA} = \mathbf{V}_{ca} / \mathbf{Z}_\Delta$	<p>Same as phase voltages</p> $\mathbf{I}_a = \mathbf{I}_{AB} \sqrt{3} \angle -30^\circ$ $\mathbf{I}_b = \mathbf{I}_a \angle -120^\circ$ $\mathbf{I}_c = \mathbf{I}_a \angle +120^\circ$


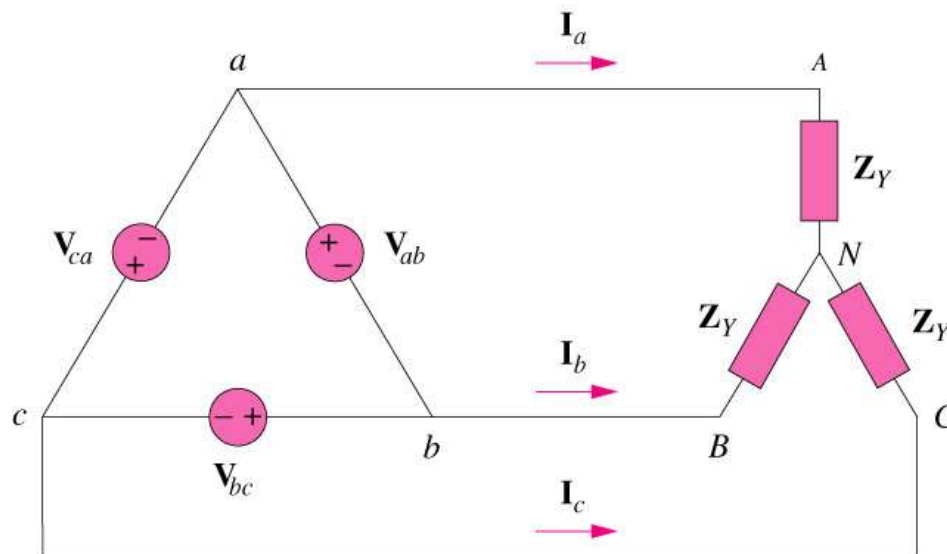
## 12.3 Balance Three-Phase Connection (8)

- A **balanced  $\Delta$ -Y** system is a three-phase system with a balanced  $\Delta$ -connected source and a balanced Y-connected load.



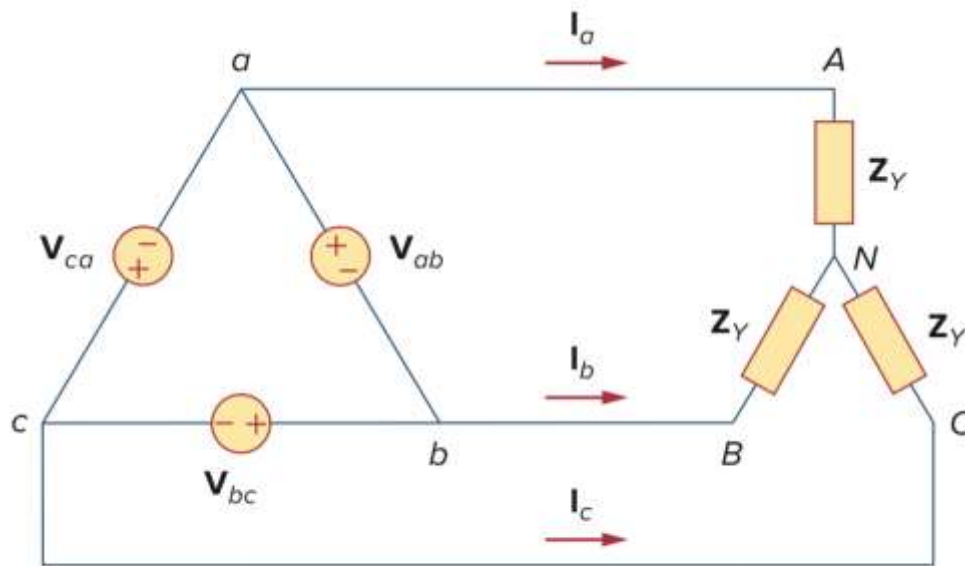

把负载的Y 转换成 $\Delta$ 再分析

**Figure 12.18**

A balanced  $\Delta$ -Y connection.

Connection	Phase voltages/currents	Line voltages/currents
$\Delta$ -Y	$\mathbf{V}_{ab} = V_p \angle 0^\circ$ $\mathbf{V}_{bc} = V_p \angle -120^\circ$ $\mathbf{V}_{ca} = V_p \angle +120^\circ$ <p>Same as line currents</p>	<p>Same as phase voltages</p> $\mathbf{I}_a = \frac{V_p \angle -30^\circ}{\sqrt{3} \mathbf{Z}_Y}$ $\mathbf{I}_b = \mathbf{I}_a \angle -120^\circ$ $\mathbf{I}_c = \mathbf{I}_a \angle +120^\circ$

TABLE 12.1

Summary of phase and line voltages/currents for balanced three-phase systems.<sup>1</sup>

Connection	Phase voltages/currents	Line voltages/currents
Y-Y	$\mathbf{V}_{an} = V_p \angle 0^\circ$ $\mathbf{V}_{bn} = V_p \angle -120^\circ$ $\mathbf{V}_{cn} = V_p \angle +120^\circ$ <p>Same as line currents</p>	$\mathbf{V}_{ab} = \sqrt{3}V_p \angle 30^\circ$ $\mathbf{V}_{bc} = \mathbf{V}_{ab} \angle -120^\circ$ $\mathbf{V}_{ca} = \mathbf{V}_{ab} \angle +120^\circ$ $\mathbf{I}_a = \mathbf{V}_{an} / \mathbf{Z}_Y$ $\mathbf{I}_b = \mathbf{I}_a \angle -120^\circ$ $\mathbf{I}_c = \mathbf{I}_a \angle +120^\circ$
Y- $\Delta$	$\mathbf{V}_{an} = V_p \angle 0^\circ$ $\mathbf{V}_{bn} = V_p \angle -120^\circ$ $\mathbf{V}_{cn} = V_p \angle +120^\circ$ $\mathbf{I}_{AB} = \mathbf{V}_{AB} / \mathbf{Z}_\Delta$ $\mathbf{I}_{BC} = \mathbf{V}_{BC} / \mathbf{Z}_\Delta$ $\mathbf{I}_{CA} = \mathbf{V}_{CA} / \mathbf{Z}_\Delta$	$\mathbf{V}_{ab} = \mathbf{V}_{AB} = \sqrt{3}V_p \angle 30^\circ$ $\mathbf{V}_{bc} = \mathbf{V}_{BC} = \mathbf{V}_{ab} \angle -120^\circ$ $\mathbf{V}_{ca} = \mathbf{V}_{CA} = \mathbf{V}_{ab} \angle +120^\circ$ $\mathbf{I}_a = \mathbf{I}_{AB} \sqrt{3} \angle -30^\circ$ $\mathbf{I}_b = \mathbf{I}_a \angle -120^\circ$ $\mathbf{I}_c = \mathbf{I}_a \angle +120^\circ$
$\Delta$ - $\Delta$	$\mathbf{V}_{ab} = V_p \angle 0^\circ$ $\mathbf{V}_{bc} = V_p \angle -120^\circ$ $\mathbf{V}_{ca} = V_p \angle +120^\circ$ $\mathbf{I}_{AB} = \mathbf{V}_{ab} / \mathbf{Z}_\Delta$ $\mathbf{I}_{BC} = \mathbf{V}_{bc} / \mathbf{Z}_\Delta$ $\mathbf{I}_{CA} = \mathbf{V}_{ca} / \mathbf{Z}_\Delta$	<p>Same as phase voltages</p> $\mathbf{I}_a = \mathbf{I}_{AB} \sqrt{3} \angle -30^\circ$ $\mathbf{I}_b = \mathbf{I}_a \angle -120^\circ$ $\mathbf{I}_c = \mathbf{I}_a \angle +120^\circ$
$\Delta$ -Y	$\mathbf{V}_{ab} = V_p \angle 0^\circ$ $\mathbf{V}_{bc} = V_p \angle -120^\circ$ $\mathbf{V}_{ca} = V_p \angle +120^\circ$ <p>Same as line currents</p>	<p>Same as phase voltages</p> $\mathbf{I}_a = \frac{V_p \angle -30^\circ}{\sqrt{3} \mathbf{Z}_Y}$ $\mathbf{I}_b = \mathbf{I}_a \angle -120^\circ$ $\mathbf{I}_c = \mathbf{I}_a \angle +120^\circ$

# 小结

- 瞬时功率

$$p(t) = v(t)i(t)$$

- 平均功率

$$P = \frac{1}{2} \text{Re}[\mathbf{VI}^*] = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)$$

- 最大功率传输（共轭匹配）

$$\mathbf{Z}_L = R_L + jX_L = R_{Th} - jX_{Th} = \mathbf{Z}_{Th}^*$$

$$P_{\max} = \frac{|\mathbf{V}_{Th}|^2}{8R_{Th}}$$

- 纯阻性负载情况

$$R_L = \sqrt{R_{Th}^2 + X_{Th}^2} = |\mathbf{Z}_{Th}|$$

# 小结

- 周期信号的有效值：信号的均方根，对于正弦信号  $V_{\text{rms}} = \frac{V_m}{\sqrt{2}}$

$$X_{\text{rms}} = \sqrt{\frac{1}{T} \int_0^T x^2 dt}$$

$$P = I_{\text{rms}}^2 R = \frac{V_{\text{rms}}^2}{R}$$

- 视在功率 & 功率因数

平均功率 = 视在功率 × 功率因数

$$S = V_{\text{rms}} I_{\text{rms}}$$

$$\text{pf} = \frac{P}{S} = \cos(\theta_v - \theta_i)$$

复功率

$$S = \frac{1}{2} \mathbf{V} \mathbf{I}^*$$

$$S = V_{\text{rms}} \mathbf{I}_{\text{rms}}^*$$

# 小结

$$\text{Complex Power} = \mathbf{S} = P + jQ = \mathbf{V}_{\text{rms}}(\mathbf{I}_{\text{rms}})^* \quad \text{VA}$$

$$= |\mathbf{V}_{\text{rms}}| |\mathbf{I}_{\text{rms}}| \angle \theta_v - \theta_i$$

$$\text{Apparent Power} = S = |\mathbf{S}| = |\mathbf{V}_{\text{rms}}| |\mathbf{I}_{\text{rms}}| = \sqrt{P^2 + Q^2} \quad (11.51)$$

$$\text{Real Power} = P = \text{Re}(\mathbf{S}) = S \cos(\theta_v - \theta_i)$$

$$\text{Reactive Power} = Q = \text{Im}(\mathbf{S}) = S \sin(\theta_v - \theta_i)$$

$$\text{Power Factor} = \frac{P}{S} = \cos(\theta_v - \theta_i)$$

1) 它的模：视在功率 **VA**

2) 它的相位：→ 功率因数 **无量纲**

3) 它的实部：平均功率（有功功率）**W**

4) 它的虚部：无功功率 **VAR**


- 从复功率导出所有功率量

$$\mathbf{S} = I_{\text{rms}}^2 \mathbf{Z} = \frac{V_{\text{rms}}^2}{\mathbf{Z}^*} = \mathbf{V}_{\text{rms}} \mathbf{I}_{\text{rms}}^*$$

- 复功率守恒

— 实部、虚部可相加，幅度不行

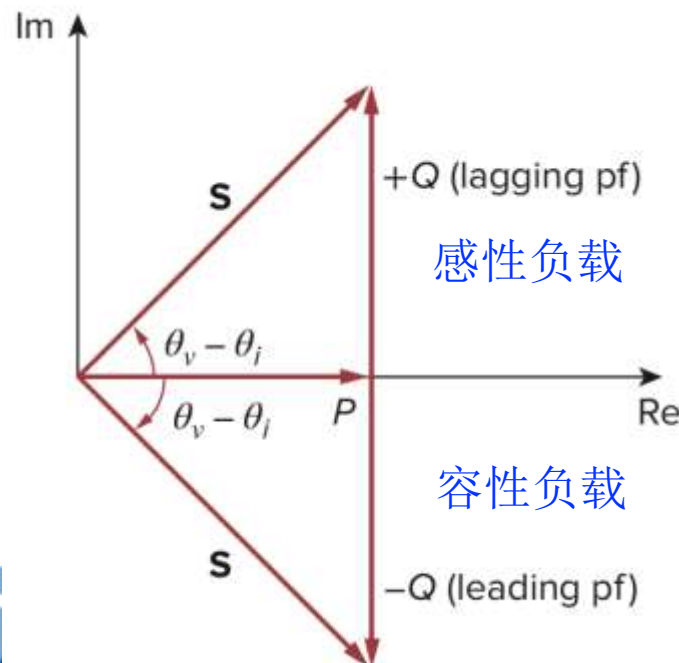
$$\mathbf{S} = \mathbf{S}_1 + \mathbf{S}_2 + \cdots + \mathbf{S}_N$$






# 小结

- 功率因数校准

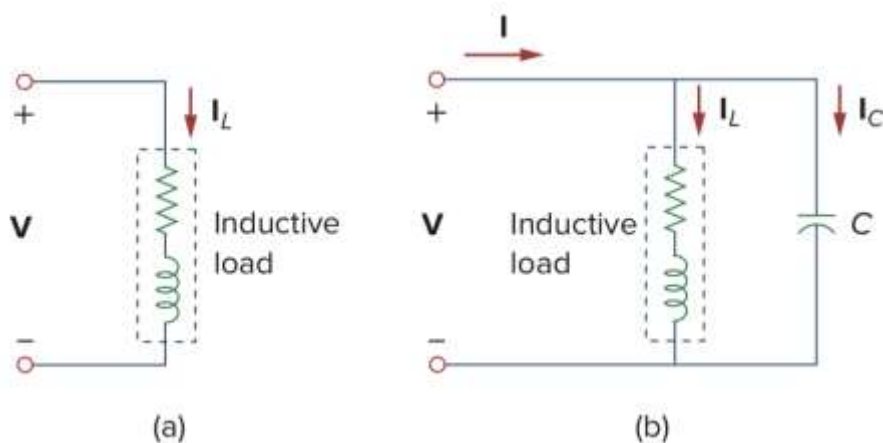

- 家用电器一般是感性负载
- 并联一个合适的C，可以增加功率因数

$$S = V_{rms}^2 \cdot Y_L^*$$

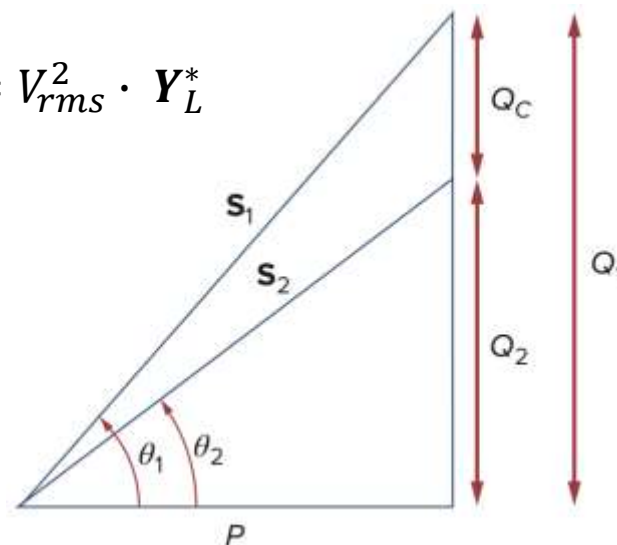

$$C = \frac{Q_C}{\omega V_{rms}^2} = \frac{P(\tan \theta_1 - \tan \theta_2)}{\omega V_{rms}^2}$$



# 小结

- 三相电传输
  - 三相四线制（ABC三端线 + 中线）
  - 三相五线制（ABC三端线 + 中线 + 地线）
- 电力系统常用abc顺序
  - 相位 a 领先 b 120度，b 领先 c 120度
- 线电流、线电压、相电流、相电压的概念
  - 输电线上的电流——线电流；输电线之间的电压——线电压
  - 电源或负载端，每一相的电压——相电压；每一相的电流——相电流。相电压看电源端；相电流看负载端。

# 小结

- 三相电的常用接法：电源端Y，负载端Y或 $\Delta$
- 三相电的分析技巧
  - 将负载端的Y或 $\Delta$ 进行转换，有时可简化分析；
  - 添加中线，有时可简化分析；
  - 电压电流相加减：矢量运算

Connection	Phase voltages/currents	Line voltages/currents
Y-Y	$V_{an} = V_p \angle 0^\circ$ $V_{bn} = V_p \angle -120^\circ$ $V_{cn} = V_p \angle +120^\circ$ Same as line currents	$V_{ab} = \sqrt{3} V_p \angle 30^\circ$ $V_{bc} = V_{ab} \angle -120^\circ$ $V_{ca} = V_{ab} \angle +120^\circ$ $I_a = V_{an} / Z_Y$ $I_b = I_a \angle -120^\circ$ $I_c = I_a \angle +120^\circ$
Y- $\Delta$	$V_{an} = V_p \angle 0^\circ$ $V_{bn} = V_p \angle -120^\circ$ $V_{cn} = V_p \angle +120^\circ$ $I_{AB} = V_{AB} / Z_\Delta$ $I_{BC} = V_{BC} / Z_\Delta$ $I_{CA} = V_{CA} / Z_\Delta$	$V_{ab} = V_{AB} = \sqrt{3} V_p \angle 30^\circ$ $V_{bc} = V_{BC} = V_{ab} \angle -120^\circ$ $V_{ca} = V_{CA} = V_{ab} \angle +120^\circ$ $I_a = I_{AB} \sqrt{3} \angle -30^\circ$ $I_b = I_a \angle -120^\circ$ $I_c = I_a \angle +120^\circ$

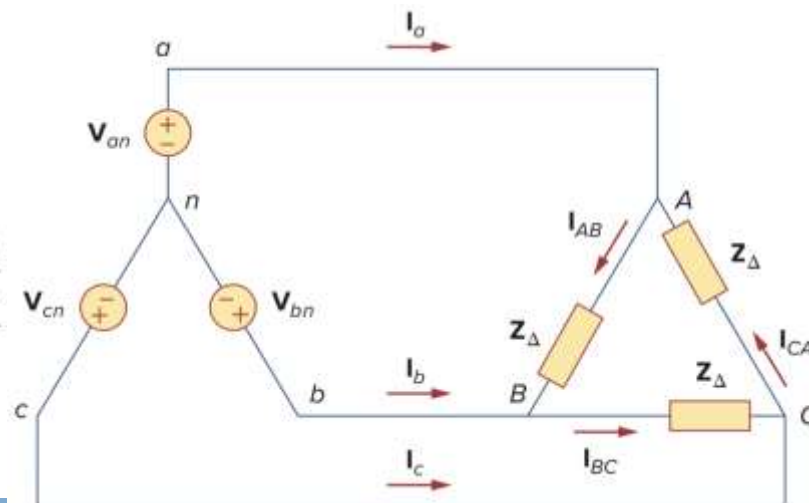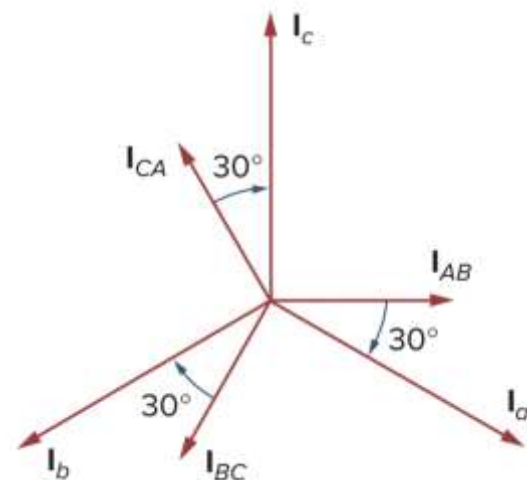



# 作业

## Practice Problem 11.1

Calculate the instantaneous power and average power absorbed by the passive linear network of Fig. 11.1 if


$$v(t) = 330 \cos(10t + 20^\circ) \text{ V} \quad \text{and} \quad i(t) = 33 \sin(10t + 60^\circ) \text{ A}$$

**Answer:**  $3.5 + 5.445 \cos(20t - 10^\circ) \text{ kW}$ ,  $3.5 \text{ kW}$ .

$$p(t) = v(t)i(t)$$

$$P = \frac{1}{T} \int_0^T p(t) dt$$


瞬时功率和平均功率的定义

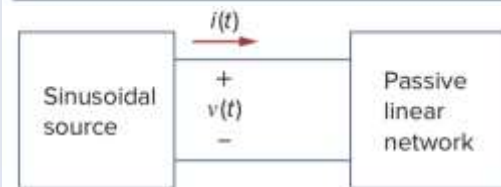

**Figure 11.1**

Sinusoidal source and passive linear circuit.

## Practice Problem 11.5

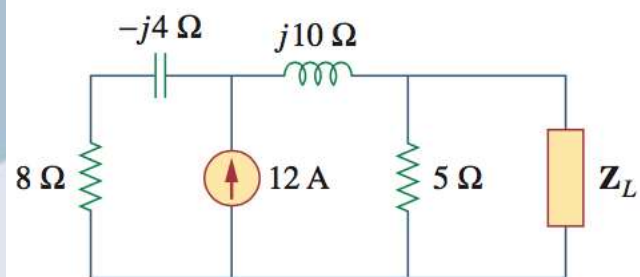

**Figure 11.10**

For Practice Prob. 11.5.

For the circuit shown in Fig. 11.10, find the load impedance  $\mathbf{Z}_L$  that absorbs the maximum average power. Calculate that maximum average power.

**Answer:**  $3.415 - j0.7317\ \Omega$ , 51.47 W.

共轭匹配



### Practice Problem 11.11

For a load,  $\mathbf{V}_{\text{rms}} = 110 \angle 85^\circ \text{ V}$ ,  $\mathbf{I}_{\text{rms}} = 3 \angle 15^\circ \text{ A}$ . Determine: (a) the complex and apparent powers, (b) the real and reactive powers, and (c) the power factor and the load impedance.

从复功率导出其他所有功率量

**Answer:** (a)  $330 \angle 70^\circ \text{ VA}$ ,  $330 \text{ VA}$  (b)  $112.87 \text{ W}$ ,  $310.1 \text{ VAR}$ , (c)  $0.342$  lagging,  $(12.541 + j34.46) \Omega$ .

Find the value of parallel capacitance needed to correct a load of 140 kVAR at 0.85 lagging pf to unity pf. Assume that the load is supplied by a 220-V (rms), 60-Hz line.

**Answer:** 7.673 mF.

功率因数校正

## Practice Problem 11.15

$$C = \frac{Q_C}{\omega V_{\text{rms}}^2} = \frac{P(\tan \theta_1 - \tan \theta_2)}{\omega V_{\text{rms}}^2}$$