

电子电路基础

第九讲 ~ 谐振电路和滤波器

谐振电路和滤波器

- **5.1 RLC串联谐振电路**
 - 5.1.1 RLC串联谐振电路的组成和参数特性（包括谐振条件、谐振时的电压、功率和能量、品质因数）
 - 5.1.2 RLC串联谐振电路的频率响应
- **5.2 RLC并联谐振电路**
 - 5.2.1 RLC并联谐振电路的组成和参数特性（包括谐振条件、谐振时的功率和能量、品质因数）
 - 5.2.2 RLC并联谐振电路的频率响应
- **5.3 基本滤波器**
 - 5.3.1 滤波器的分类及其频率响应（低通、高通、带通、带阻和全通）
 - 5.3.2 无源滤波器简介（低通、高通、带通和带阻）

Frequency Response

Chapter 14

- 14.1 Introduction
- 14.2 Transfer Function
- 14.3 Series Resonance
- 14.4 Parallel Resonance
- 14.5 Passive Filters

频率响应

什么是电路的频率响应？


The **frequency response** of a circuit is the variation in its behavior with change in signal frequency.

电路的**频率响应**：当正弦激励信号的**振幅保持不变**，而**频率变化**时，分析**电路特性**随频率变化的情况。尤其是分析**电路传递函数**的**幅度**（增益）和**相位**随频率变化的情况。

- 振幅 **vs** 频率：幅频特性
- 相位 **vs** 频率：相频特性

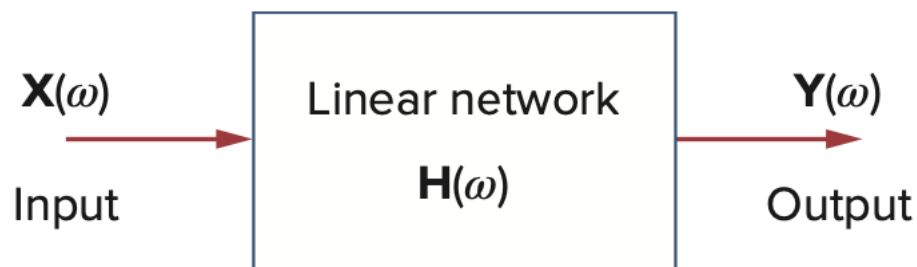14.2 Transfer Function 传递函数

The **transfer function** $\mathbf{H}(\omega)$ of a circuit is the frequency-dependent ratio of a phasor output $\mathbf{Y}(\omega)$ (an element voltage or current) to a phasor input $\mathbf{X}(\omega)$ (source voltage or current).



$$\mathbf{H}(\omega) = \frac{\mathbf{Y}(\omega)}{\mathbf{X}(\omega)}$$

Figure 14.1


A block diagram representation of a linear network.

14.2 Transfer Function (2)

- 四种可能的传递函数:

$$H(\omega) = \text{Voltage gain} = \frac{V_o(\omega)}{V_i(\omega)}$$
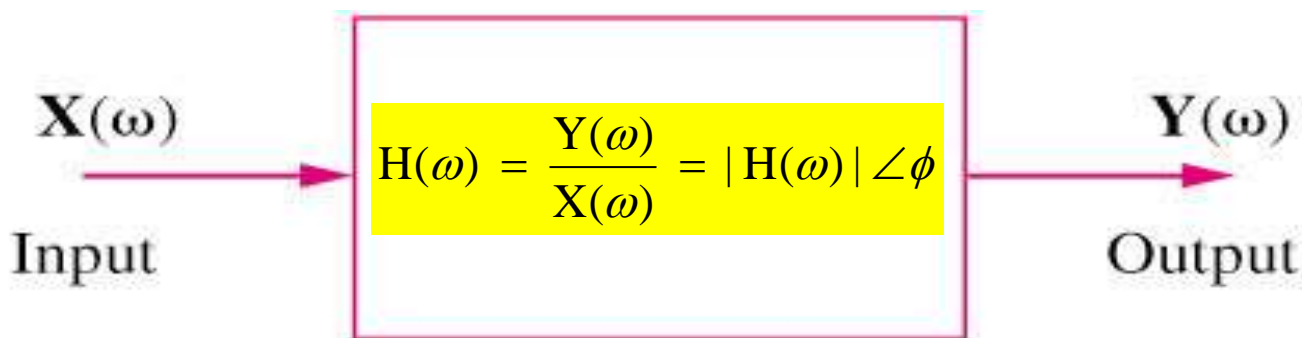
$$H(\omega) = \text{Transfer Impedance} = \frac{V_o(\omega)}{I_i(\omega)}$$



$$H(\omega) = \text{Current gain} = \frac{I_o(\omega)}{I_i(\omega)}$$

$$H(\omega) = \text{Transfer Admittance} = \frac{I_o(\omega)}{V_i(\omega)}$$

14.2 Transfer Function (3)

Example 14.1

For the RC circuit in Fig. 14.2(a), obtain the transfer function V_o/V_s and its frequency response. Let $v_s = V_m \cos \omega t$.

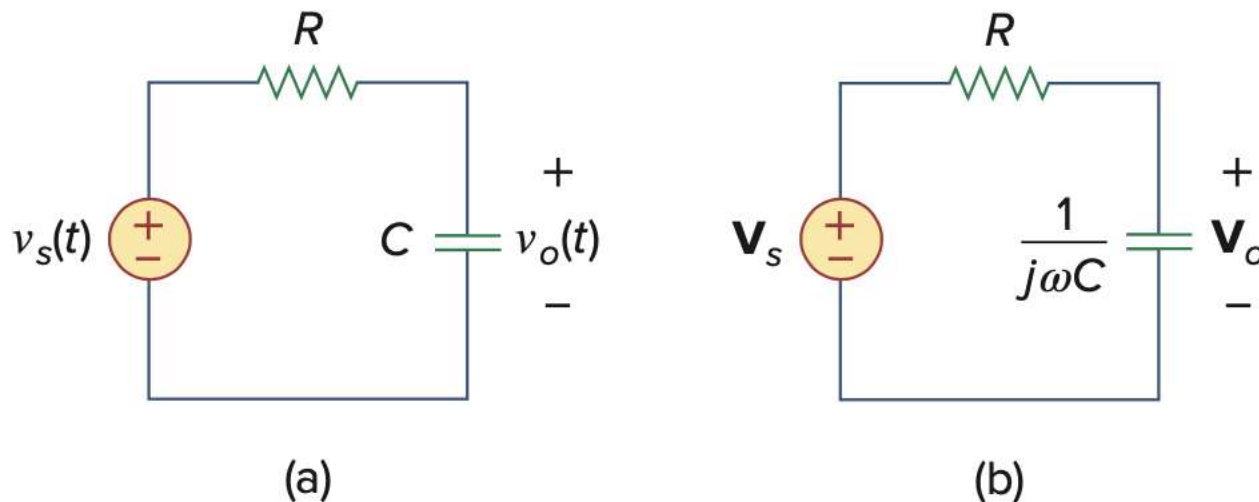


Figure 14.2

For Example 14.1: (a) time-domain RC circuit, (b) frequency-domain RC circuit.

14.2 Transfer Function (4)

Solution:

The transfer function is

$$H(\omega) = \frac{V_o}{V_s} = \frac{\frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} = \frac{1}{1 + j\omega RC} = \frac{1 - j\omega RC}{1 + (\omega RC)^2}$$




The **magnitude** is

$$|H(\omega)| = \frac{1}{\sqrt{1 + (\omega / \omega_o)^2}}$$

The **phase** is

$$\phi = -\tan^{-1} \frac{\omega}{\omega_o}$$

$$\omega_o = 1/RC$$

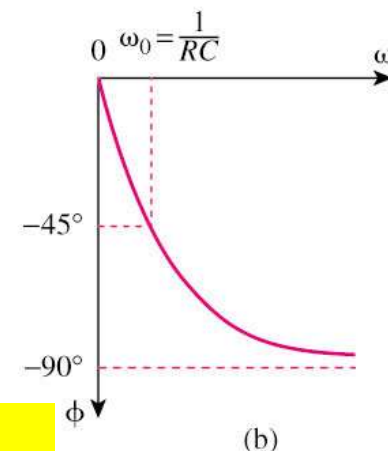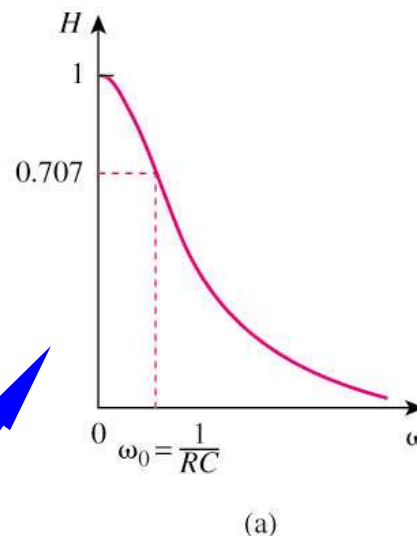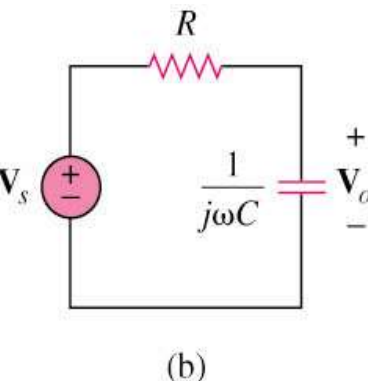


Low Pass Filter

14.2 Transfer Function (5)

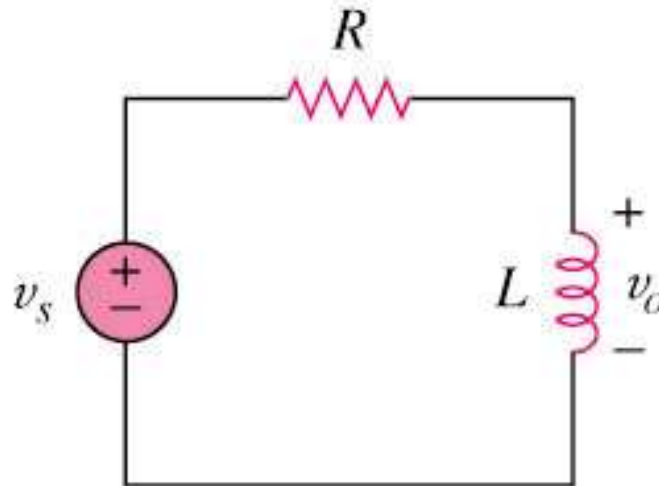Example 2


Obtain the transfer function $\mathbf{V}_o / \mathbf{V}_s$ of the RL circuit shown below, assuming $v_s = V_m \cos(\omega t)$. Sketch its frequency response.



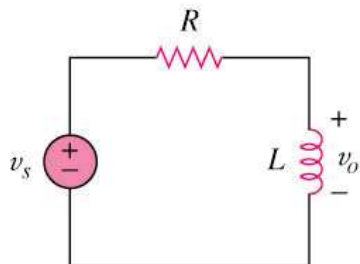14.2 Transfer Function (6)

Solution:

The transfer function is $H(\omega) = \frac{V_o}{V_s} = \frac{j\omega L}{R + j\omega L} = \frac{1}{1 + \frac{R}{j\omega L}} = \frac{1 + jR/(\omega L)}{1 + R^2/(\omega L)^2}$



The magnitude is


$$H(\omega) = \frac{1}{\sqrt{1 + (\frac{\omega_o}{\omega})^2}}$$

The phase is

$$\phi = \angle 90^\circ - \tan^{-1} \frac{\omega}{\omega_o}$$

$$\omega_o = R/L$$

High Pass Filter

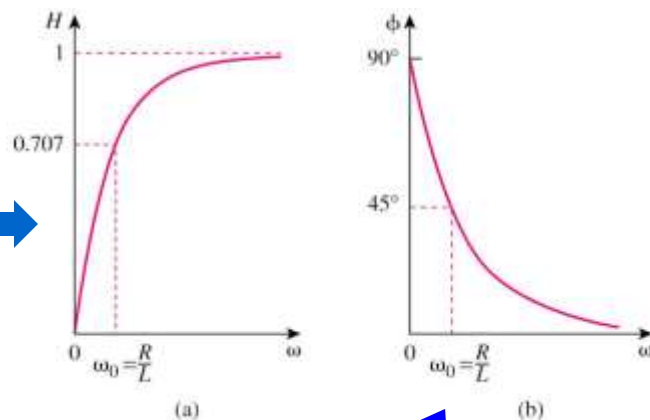

零极点分析

$$H(\omega) = \frac{N(\omega)}{D(\omega)}$$

分子为零 → 传递函数的零点

分母为零 → 传递函数的极点

A **zero**, as a *root* of the numerator polynomial, is a value that results in a zero value of the function. A **pole**, as a *root* of the denominator polynomial, is a value for which the function is infinite.

A zero may also be regarded as the value of $s = j\omega$ that makes $H(s)$ zero, and a pole as the value of $s = j\omega$ that makes $H(s)$ infinite.

零极点的分析也往往在S域进行

For the circuit in Fig. 14.6, calculate the gain $\mathbf{I}_o(\omega)/\mathbf{I}_i(\omega)$ and its poles and zeros.

Solution:

By current division,

$$\mathbf{I}_o(\omega) = \frac{4 + j2\omega}{4 + j2\omega + 1/j0.5\omega} \mathbf{I}_i(\omega)$$

or

$$\frac{\mathbf{I}_o(\omega)}{\mathbf{I}_i(\omega)} = \frac{j0.5\omega(4 + j2\omega)}{1 + j2\omega + (j\omega)^2} = \frac{s(s + 2)}{s^2 + 2s + 1}, \quad s = j\omega$$

The zeros are at

$$s(s + 2) = 0 \Rightarrow z_1 = 0, z_2 = -2$$

The poles are at

$$s^2 + 2s + 1 = (s + 1)^2 = 0$$

Thus, there is a repeated pole (or double pole) at $p = -1$.

Example 14.2

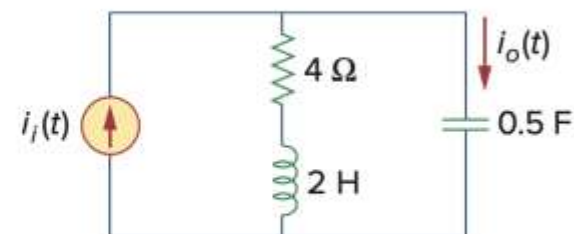


Figure 14.6

For Example 14.2.

dB

- 对数运算法则

1. $\log P_1 P_2 = \log P_1 + \log P_2$
2. $\log P_1 / P_2 = \log P_1 - \log P_2$
3. $\log P^n = n \log P$
4. $\log 1 = 0$

- 将两个**功率的比值**用对数表示 → 单位为**dB**

$$G_{\text{dB}} = 10 \log_{10} \frac{P_2}{P_1}$$

$$G_{\text{dB}} = 10 \log_{10} 2 \simeq 3 \text{ dB}$$

$$G_{\text{dB}} = 10 \log_{10} 0.5 \simeq -3 \text{ dB}$$

– 功率与电压平方关联，所以若表示**电压的比值**：

$$G_{\text{dB}} = 20 \log_{10} \frac{V_2}{V_1}$$


dB

Three things are important to note from Eqs. (14.5), (14.10), and (14.11):

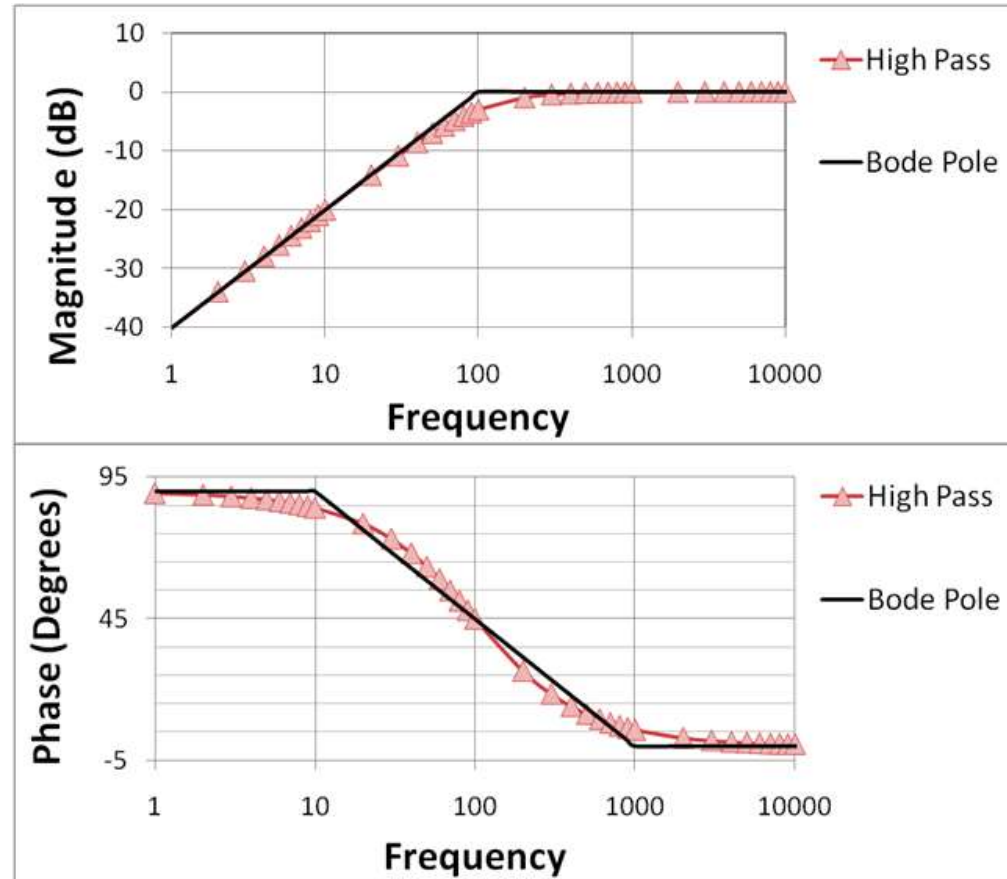1. That $10 \log_{10}$ is used for power, while $20 \log_{10}$ is used for voltage or current, because of the square relationship between them ($P = V^2/R = I^2R$).
2. That the dB value is a logarithmic measurement of the *ratio* of one variable to another of the *same type*. Therefore, it applies in expressing the transfer function H in Eqs. (14.2a) and (14.2b), which are dimensionless quantities, but not in expressing H in Eqs. (14.2c) and (14.2d).
3. It is important to note that we *only use* voltage and current *magnitudes* in Eqs. (14.10) and (14.11). Negative signs and angles will be handled independently as we will see in Section 14.4.

Bode Plots 波特图

- 电路的频率响应
 - 传递函数幅度 vs 频率
 - 传递函数相位 vs 频率
- 波特图
 - 描述频率响应的业界标准
 - 频率用对数坐标
 - 幅度用dB
 - 相位用角度



Bode plots are semilog plots of the magnitude (in decibels) and phase (in degrees) of a transfer function versus frequency.

波特图

- 传递函数：响应（电压或电流） \div 激励（电压或电流）

$$H_{\text{dB}} = 20 \log_{10} H$$

系数是20

Magnitude H	$20 \log_{10} H$ (dB)
0.001	-60
0.01	-40
0.1	-20
0.5	-6
$1/\sqrt{2}$	-3
1	0
$\sqrt{2}$	3
2	6
10	20
20	26
100	40
1000	60

常见的传递函数（如电压增益）
幅度所对应的dB值

波特图

- 分析电路，写出传递函数，转换为以下的**标准形式**

$$\mathbf{H}(\omega) = \frac{K(j\omega)^{\pm 1}(1 + j\omega/z_1)[1 + j2\zeta_1\omega/\omega_k + (j\omega/\omega_k)^2]\cdots}{(1 + j\omega/p_1)[1 + j2\zeta_2\omega/\omega_n + (j\omega/\omega_n)^2]\cdots} \quad (14.15)$$

$\mathbf{H}(\omega)$ may include up to **seven types** of different factors that can appear in various combinations in a transfer function. These are:


1. A gain K
2. A pole $(j\omega)^{-1}$ or zero $(j\omega)$ at the origin $\omega = 0$
3. A simple pole $1/(1 + j\omega/p_1)$ or zero $(1 + j\omega/z_1)$ $j\omega = -p_1$ or $-z_1$
4. A quadratic pole $1/[1 + j2\zeta_2\omega/\omega_n + (j\omega/\omega_n)^2]$ or zero $[1 + j2\zeta_1\omega/\omega_k + (j\omega/\omega_k)^2]$

幅度采用**dB**，增加了数学运算的方便性，在前计算机时代，大幅增加了工程计算便利性


- $\mathbf{H}(\omega)$ 的幅度（**dB**）：各项代数和（乘除在对数坐标下转化为加减）
- $\mathbf{H}(\omega)$ 的相位（**dB**）：各项代数和

波特图

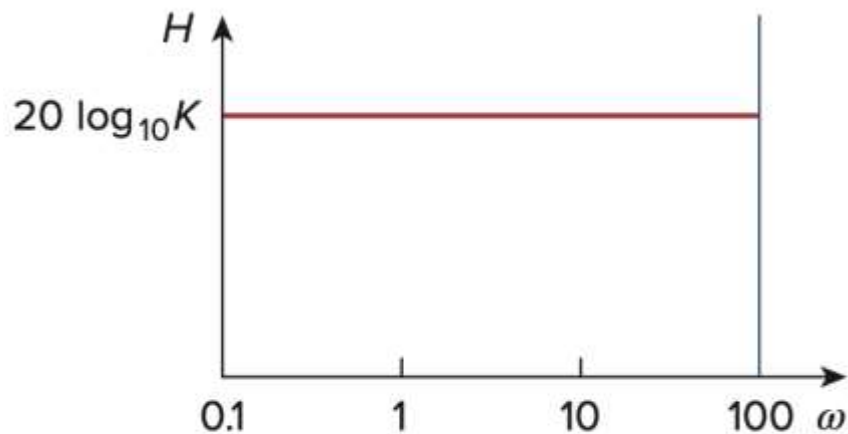- ①常数项 $\mathbf{H}(\omega) = \frac{K(j\omega)^{\pm 1}(1 + j\omega/z_1)[1 + j2\zeta_1\omega/\omega_k + (j\omega/\omega_k)^2]\cdots}{(1 + j\omega/p_1)[1 + j2\zeta_2\omega/\omega_n + (j\omega/\omega_n)^2]\cdots}$



(a)

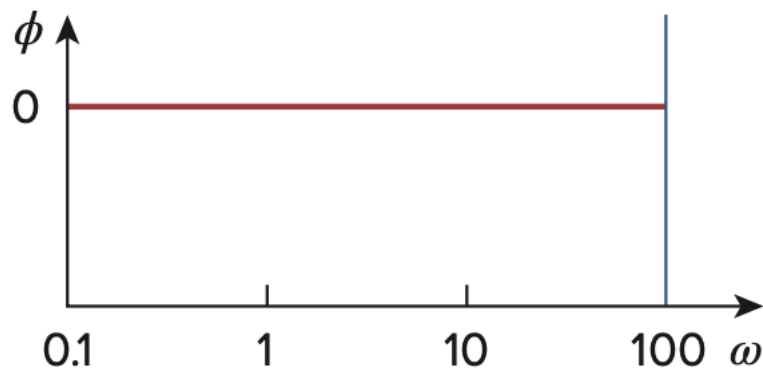

(b)

波特图


- ②③原点处的零极点 $H(\omega) = \frac{K(j\omega)^{\pm 1}(1 + j\omega/z_1)[1 + j2\zeta_1\omega/\omega_k + (j\omega/\omega_k)^2]\dots}{(1 + j\omega/p_1)[1 + j2\zeta_2\omega/\omega_n + (j\omega/\omega_n)^2]\dots}$

Pole/zero at the origin: For the zero ($j\omega$) at the origin, the magnitude is $20 \log_{10} \omega$ and the phase is 90° . These are plotted in Fig. 14.10, where we notice that the slope of the magnitude plot is 20 dB/decade , while the phase is constant with frequency. **Q1: 极点呢?**

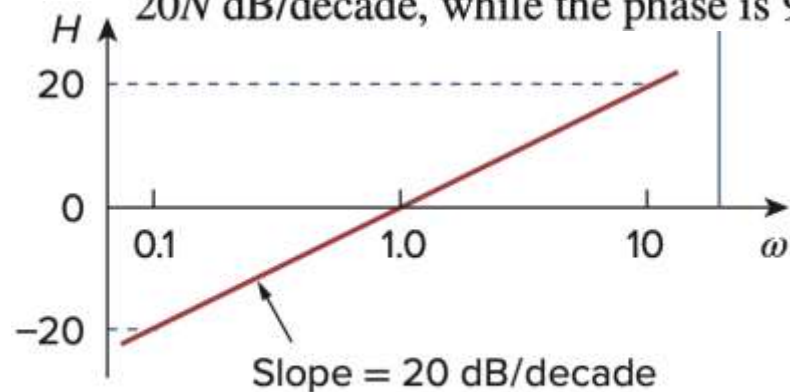
Q2: 原点处的N重零极点呢?

-20 dB/decade while the phase is -90°

for $(j\omega)^N$, where N is an integer, the magnitude plot will have a slope of $20N \text{ dB/decade}$, while the phase is $90N$ degrees.



(a)

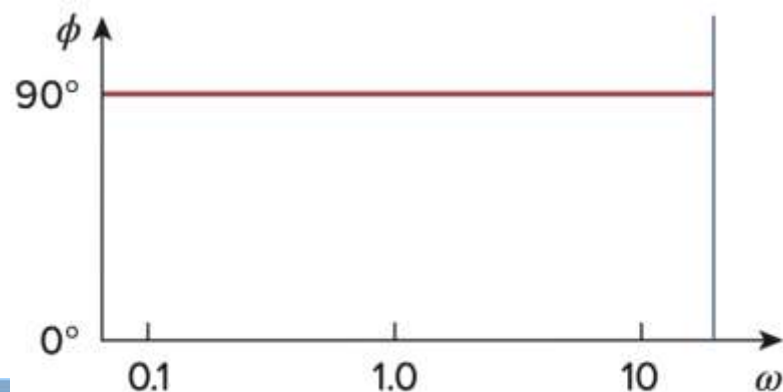

(b)

④⑤一阶零极点

$$H(\omega) = \frac{K(j\omega)^{\pm 1} (1 + j\omega/z_1) [1 + j2\zeta_1\omega/\omega_k + (j\omega/\omega_k)^2]^{20}}{(1 + j\omega/p_1) [1 + j2\zeta_2\omega/\omega_n + (j\omega/\omega_n)^2] \dots}$$

Simple pole/zero: For the simple zero $(1 + j\omega/z_1)$, the magnitude is $20 \log_{10} |1 + j\omega/z_1|$ and the phase is $\tan^{-1} \omega/z_1$. We notice that

$$H_{dB} = 20 \log_{10} \left| 1 + \frac{j\omega}{z_1} \right| \Rightarrow 20 \log_{10} 1 = 0 \quad (14.16)$$


as $\omega \rightarrow 0$

- * 勾勒出近似曲线（培养直觉）
- * 精确曲线用数学软件可以画出

$$H_{dB} = 20 \log_{10} \left| 1 + \frac{j\omega}{z_1} \right| \Rightarrow 20 \log_{10} \frac{\omega}{z_1} \quad (14.17)$$

as $\omega \rightarrow \infty$

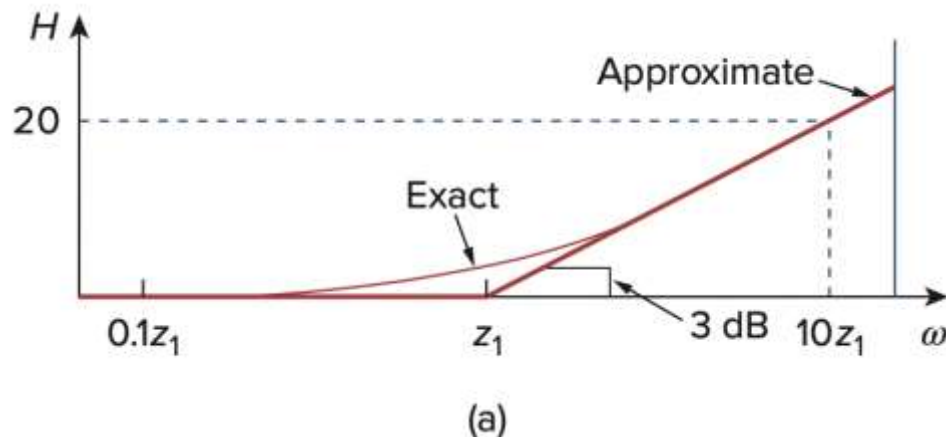showing that we can approximate the magnitude as **zero** (a straight line with zero slope) for small values of ω and by a straight line with slope 20 dB/decade for large values of ω . The frequency $\omega = z_1$ where the two asymptotic lines meet is called the **corner frequency** or **break frequency**.



一阶零极点项 $(1 + j\omega/z_1)$ $(1 + j\omega/p_1)$
对应着一个corner frequency,
有时也简单地把这个corner frequency
称为**零极点频率**

corner frequency 处有3 dB误差

• ④⑤一阶零极点

$$H(\omega) = \frac{K(j\omega)^{\pm 1} (1 + j\omega/z_1) [1 + j2\zeta_1\omega/\omega_k + (j\omega/\omega_k)^2]}{(1 + j\omega/p_1) [1 + j2\zeta_2\omega/\omega_n + (j\omega/\omega_n)^2] \dots}$$

The phase $\tan^{-1}(\omega/z_1)$ can be expressed as


$$\phi = \tan^{-1}\left(\frac{\omega}{z_1}\right) = \begin{cases} 0, & \omega = 0 \\ 45^\circ, & \omega = z_1 \\ 90^\circ, & \omega \rightarrow \infty \end{cases} \quad (14.18)$$

工程上差10倍即可略去

As a straight-line approximation, we let $\phi \simeq 0$ for $\omega \leq z_1/10$, $\phi \simeq 45^\circ$ for $\omega = z_1$, and $\phi \simeq 90^\circ$ for $\omega \geq 10z_1$. As shown in Fig. 14.11(b) along with the actual plot, the straight-line plot has a slope of 45° per decade.

Q: 一阶极点呢?

Fig. 14.11 except that the corner frequency is at $\omega = p_1$, the magnitude has a slope of -20 dB/decade, and the phase has a slope of -45° per decade.

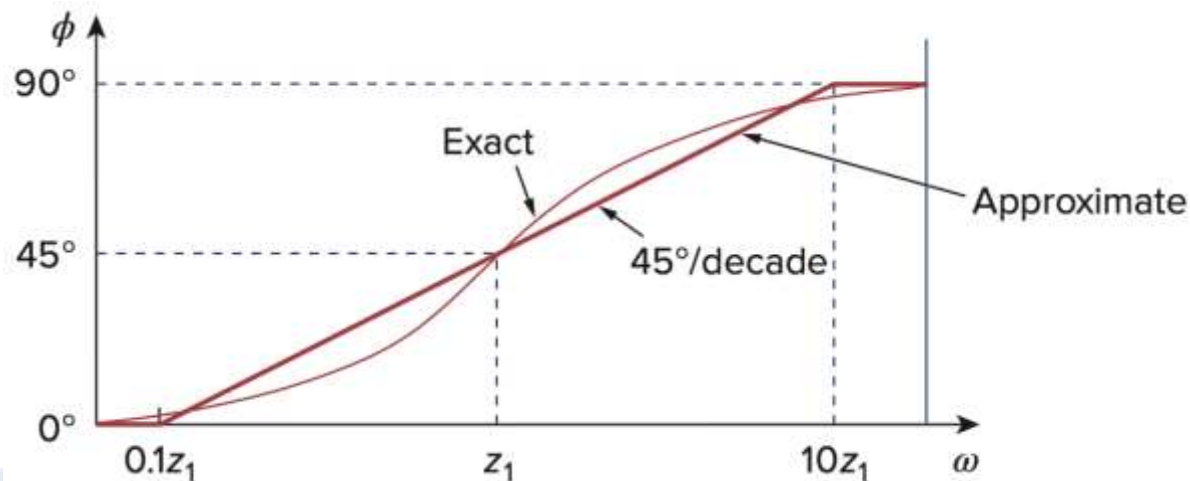

• ⑥⑦二阶零极点

$$\mathbf{H}(\omega) = \frac{K(j\omega)^{\pm 1}(1 + j\omega/z_1)[1 + j2\zeta_1\omega/\omega_k + (j\omega/\omega_k)^2]\dots}{(1 + j\omega/p_1)[1 + j2\zeta_2\omega/\omega_n + (j\omega/\omega_n)^2]\dots}$$

Quadratic pole/zero: The magnitude of the quadratic pole $1/[1 + j2\zeta_2\omega/\omega_n + (j\omega/\omega_n)^2]$ is $-20 \log_{10}|1 + j2\zeta_2\omega/\omega_n + (j\omega/\omega_n)^2|$ and the phase is $-\tan^{-1}(2\zeta_2\omega/\omega_n)/(1 - \omega^2/\omega_n^2)$. But

$$H_{dB} = -20 \log_{10} \left| 1 + \frac{j2\zeta_2\omega}{\omega_n} + \left(\frac{j\omega}{\omega_n} \right)^2 \right| \Rightarrow 0$$


as $\omega \rightarrow 0$

$$H_{dB} = -20 \log_{10} \left| 1 + \frac{j2\zeta_2\omega}{\omega_n} + \left(\frac{j\omega}{\omega_n} \right)^2 \right| \Rightarrow -40 \log_{10} \frac{\omega}{\omega_n}$$

as $\omega \rightarrow \infty$

Thus, the amplitude plot consists of two straight asymptotic lines: one with zero slope for $\omega < \omega_n$ and the other with slope -40 dB/decade for $\omega > \omega_n$, with ω_n as the corner frequency. Figure 14.12(a) shows

corner frequency 处有误差，误差值取决于一次项系数

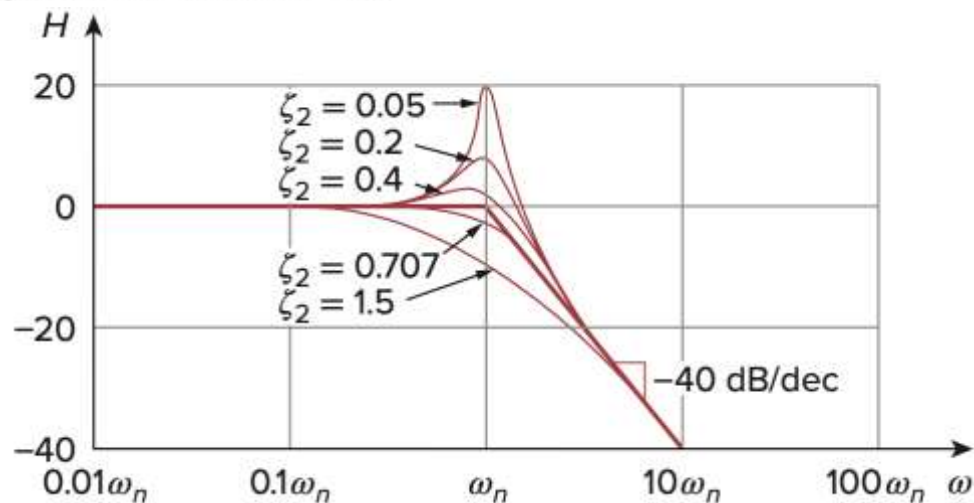

• ⑥⑦二阶零极点

$$\mathbf{H}(\omega) = \frac{K(j\omega)^{\pm 1}(1 + j\omega/z_1)[1 + j2\zeta_1\omega/\omega_k + (j\omega/\omega_k)^2]\cdots}{(1 + j\omega/p_1)[1 + j2\zeta_2\omega/\omega_n + (j\omega/\omega_n)^2]\cdots}$$

The phase can be expressed as


$$\phi = -\tan^{-1} \frac{2\zeta_2\omega/\omega_n}{1 - \omega^2/\omega_n^2} = \begin{cases} 0, & \omega = 0 \\ -90^\circ, & \omega = \omega_n \\ -180^\circ, & \omega \rightarrow \infty \end{cases} \quad (14.21)$$

The phase plot is a straight line with a slope of -90° per decade starting at $\omega_n/10$ and ending at $10\omega_n$, as shown in Fig. 14.12(b). We see again that

Q1: 二阶零点呢? 40 dB/decade while the phase plot has a slope of 90° per decade.

Q2: 双重零极点呢? the double pole $(1 + j\omega/\omega_n)^{-2}$ equals the quadratic pole $1/[1 + j2\zeta_2\omega/\omega_n + (j\omega/\omega_n)^2]$ when $\zeta_2 = 1$. Thus, the quadratic pole can be treated as a double pole as far as straight-line approximation is concerned.

二阶零极点的分析，可简单地用双重零极点的分析来近似


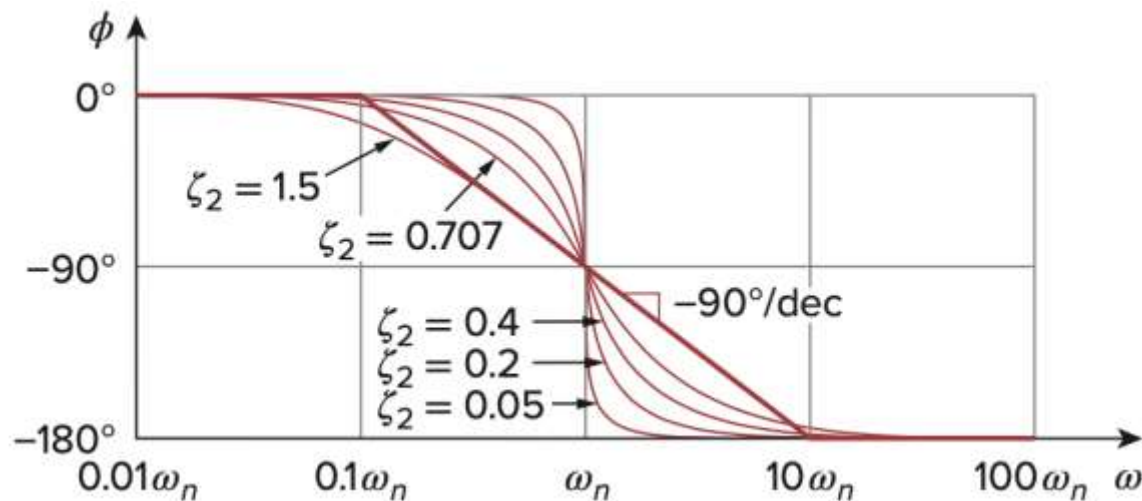


Summary of Bode straight-line magnitude and phase plots.



24

Factor	Magnitude	Phase
K	$20 \log_{10} K$ 	0°
$(j\omega)^N$	$20N \text{ dB/decade}$ 	$90N^\circ$
$\frac{1}{(j\omega)^N}$	$-20N \text{ dB/decade}$ 	$-90N^\circ$
$\left(1 + \frac{j\omega}{z}\right)^N$	$20N \text{ dB/decade}$ 	0° to $90N^\circ$
$\frac{1}{(1 + j\omega/p)^N}$	$-20N \text{ dB/decade}$ 	0° to $-90N^\circ$
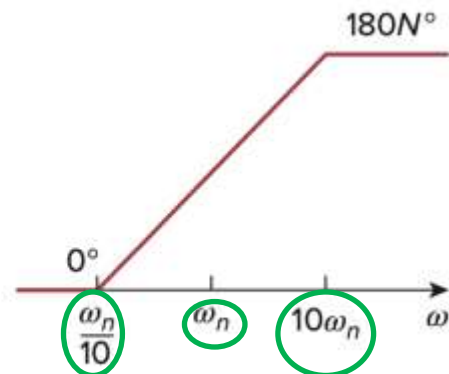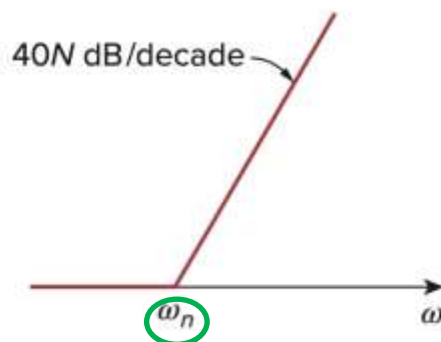
$$\left[1 + \frac{2j\omega\zeta}{\omega_n} + \left(\frac{j\omega}{\omega_n} \right)^2 \right]^N$$


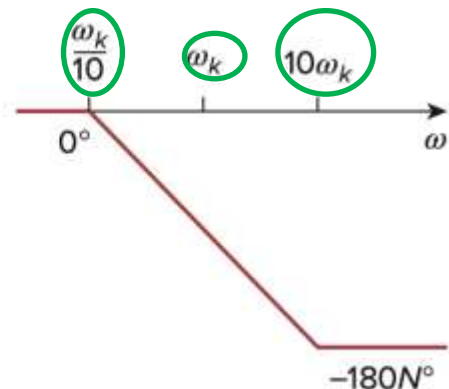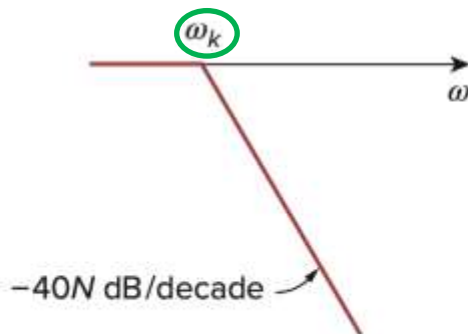
$$\frac{1}{[1 + 2j\omega\zeta/\omega_k + (j\omega/\omega_k)^2]^N}$$



• 构建波特图的方法

- 方法1: 按上述规则, 做各项的代数和
- 方法2: 先分析常数项和原点处的零极点, 然后, 随着频率的增加, **每碰到一个零点**, 幅度的斜率**增加20dB/十倍频**, 相位**增加90度** (从0.1到10倍频率); **每碰到一个极点**, 幅度的斜率**减小20dB/十倍频**, 相位**减小90度** (从0.1到10倍频率)

$$H(\omega) = \frac{200j\omega}{(j\omega + 2)(j\omega + 10)}$$

方法1:

①转换为标准形式:

$$H(\omega) = \frac{10j\omega}{(1 + j\omega/2)(1 + j\omega/10)}$$

先画常数或零点, 或全部各自画出

②分析常数项和零极点: 增益10; 原点处零点 $\omega=0$; 一阶极点 $\omega=2$, $\omega=10$



③画出各部分的波特图, 再做代数和

方法2:

①先分析常数项和原点处的零极点

②按低频到高频的顺序, 逐渐分析各个零极点的影响

* 若零极点之间频率间隔太近, 相位变化起止点会有重叠

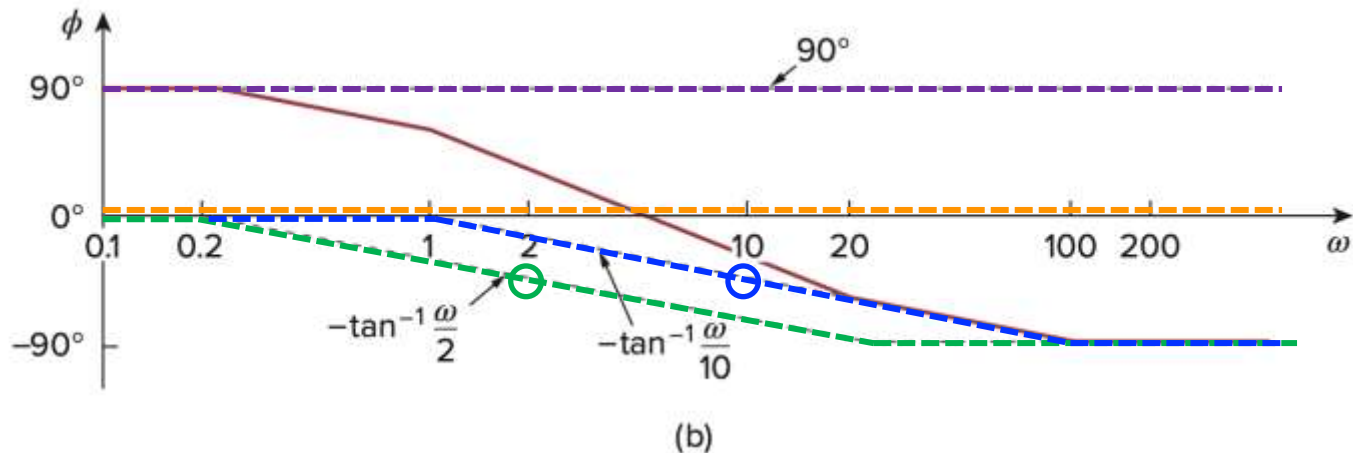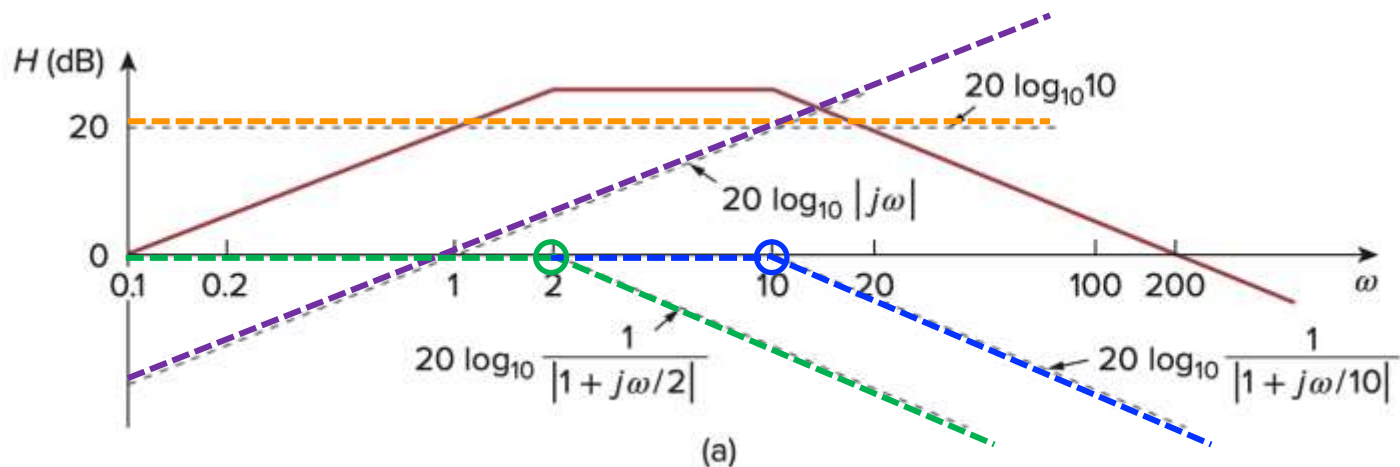

Example 14.6

Given the Bode plot in Fig. 14.19, obtain the transfer function $\mathbf{H}(\omega)$.

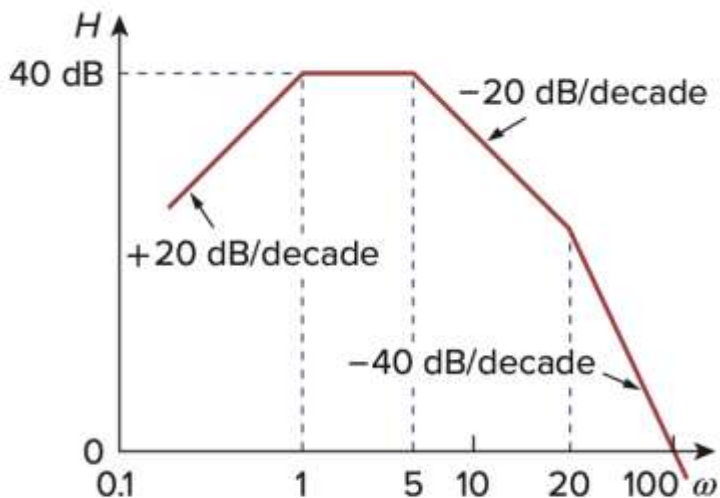


Figure 14.19
For Example 14.6.

① 低频的“20dB/十倍频”斜率是原点处的零点引起的，其与横轴的交点为 $\omega=1$ ，因此 $\omega=1$ 处实际的 40dB 幅度是常数项导致的

$$40 = 20 \log_{10} K \quad \Rightarrow \quad K = 10^2 = 100$$

② $\omega=1$ 处斜率下降“20dB/十倍频”，所以 $\omega=1$ 是一个极点

③ $\omega=5$ 处斜率再下降“20dB/十倍频”，所以 $\omega=5$ 也是一个极点



④ 同理， $\omega=20$ 也是一个极点



$$\mathbf{H}(\omega) = \frac{100 j\omega}{(1 + j\omega/1)(1 + j\omega/5)(1 + j\omega/20)}$$


谐振电路

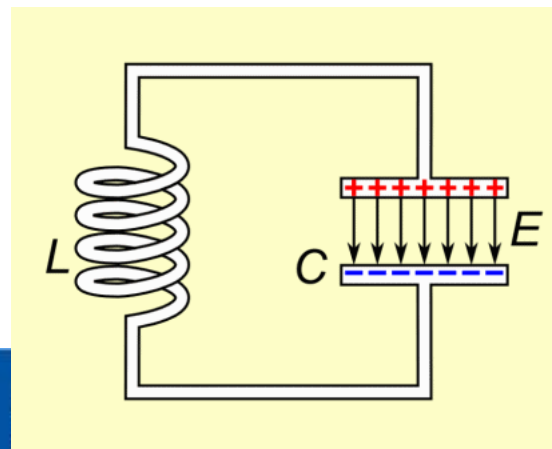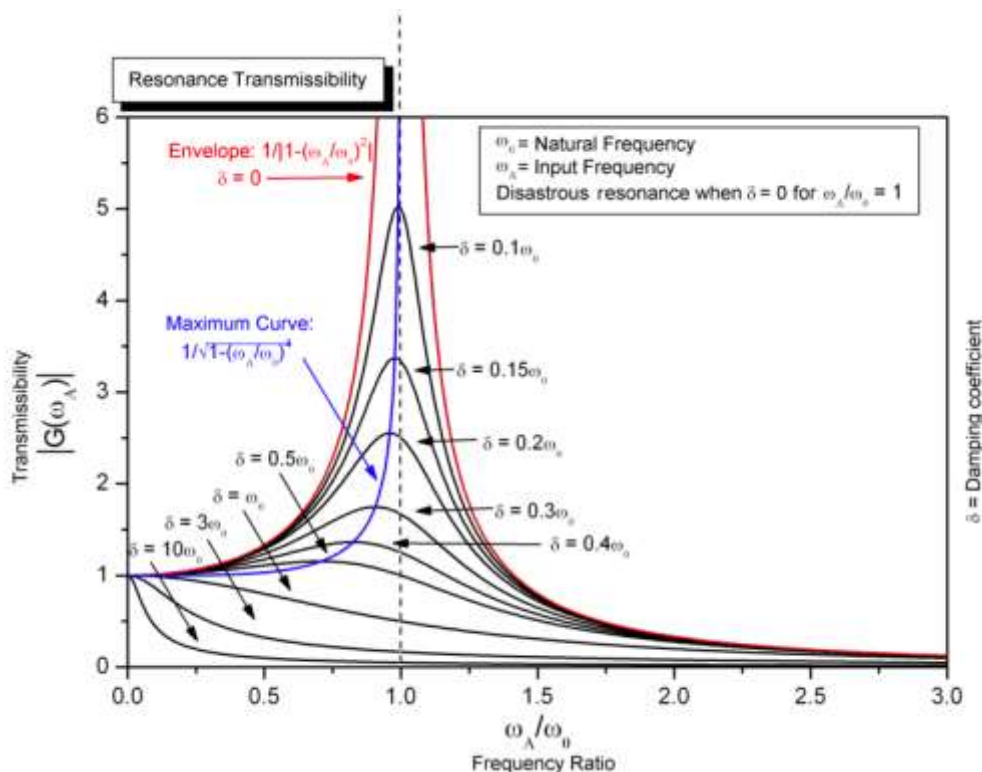- 谐振时频率响应曲线会出现一个**尖峰** (sharp peak)
- 电路（或系统）如果有一**对共轭极点**，则会产生谐振
- 若电路中**至少有一个L和一个C**，则会产生谐振
- 谐振是系统中**不同能量**之间的来回互换
- 谐振电路是**滤波器**的基础



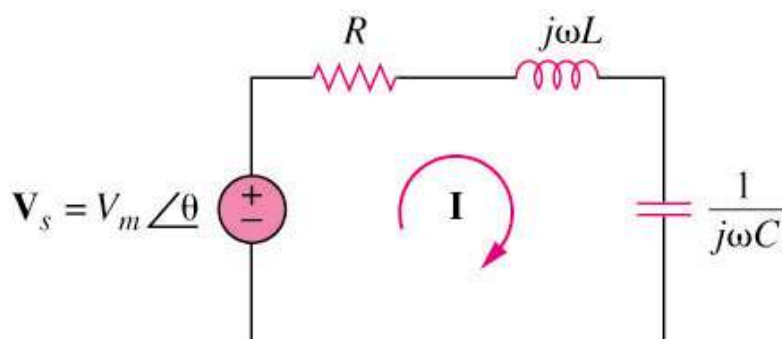14.3 Series Resonance 串联谐振

Resonance is a condition in an RLC circuit in which the capacitive and inductive reactances are equal in magnitude, thereby resulting in a purely resistive impedance.



$$Z = R + j\left(\omega L - \frac{1}{\omega C}\right)$$

谐振频率

Resonance frequency:


$$\omega_o = \frac{1}{\sqrt{LC}} \text{ rad/s} \quad \text{or}$$

$$f_o = \frac{1}{2\pi\sqrt{LC}} \text{ Hz}$$

谐振条件：虚部 = 0

14.3 Series Resonance (2)

串联谐振时的特性:

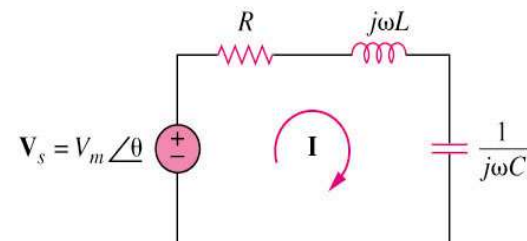

$$Z = R + j\left(\omega L - \frac{1}{\omega C}\right)$$

- The impedance is **purely resistive**, $Z = R$;
- The supply voltage V_s and the current I are **in phase**;
- The magnitude of the transfer function $H(\omega) = Z(\omega)$ is minimum; 串联谐振时，**阻抗幅度最小** \rightarrow **电流最大**
- The inductor voltage and capacitor voltage can be much more than the source voltage. 串联谐振时，**电容/电感上的电压幅度会大于所施加的电压源**

谐振电路里， Q 一般都大于10，也可达到几千甚至几万


$$|V_L| = \frac{V_m}{R} \omega_0 L = QV_m$$

$$|V_C| = \frac{V_m}{R} \frac{1}{\omega_0 C} = QV_m$$

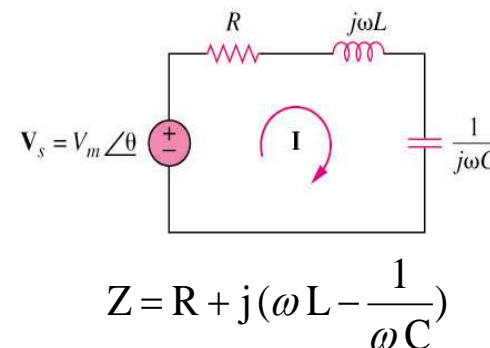
14.3 Series Resonance (3)

Bandwidth (带宽) B

The **frequency response** of the resonance circuit current is



$$I = |I| = \frac{V_m}{\sqrt{R^2 + (\omega L - 1/\omega C)^2}}$$

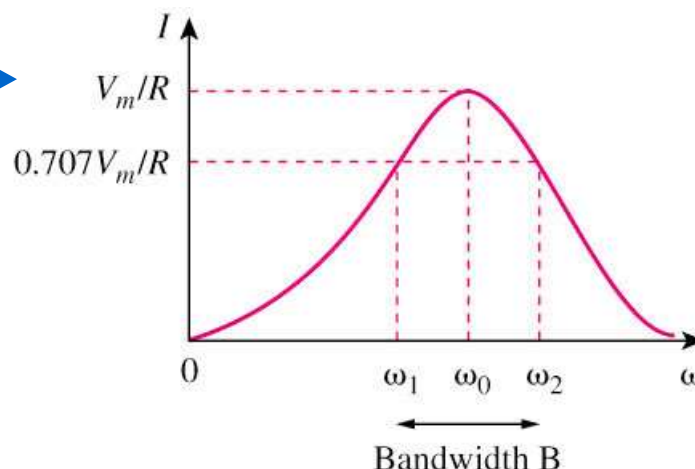

The average power absorbed by the RLC circuit is

$$P(\omega) = \frac{1}{2} I^2 R$$

The highest power dissipated occurs at resonance:

$$P(\omega_0) = \frac{1}{2} \frac{V_m^2}{R}$$

谐振时响应：电流特性
(施加信号为电压时)

14 3 Series Resonance (4)

Half-power frequencies ω_1 and ω_2 are frequencies at which the dissipated power is half the maximum value:

$$P(\omega_1) = P(\omega_2) = \frac{(V_m/\sqrt{2})^2}{2R} = \frac{V_m^2}{4R}$$

The half-power frequencies can be obtained by setting $\sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2} = \sqrt{2}R$

$$\omega_1 = -\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$


$$\omega_2 = \frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$

$$\omega_o = \sqrt{\omega_1 \omega_2}$$

带宽的定义：两个半功率频率点之间的频率差

Bandwidth B

$$B = \omega_2 - \omega_1$$

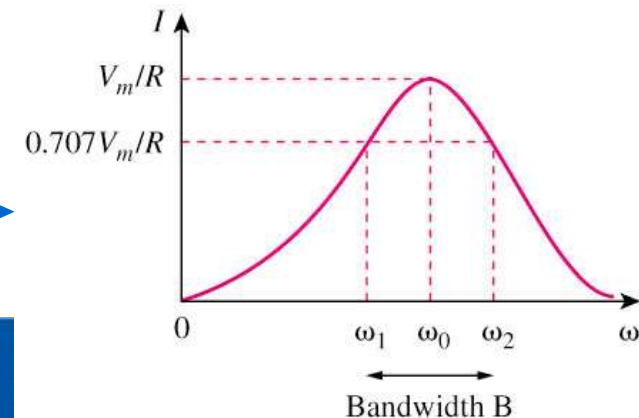

14.3 Series Resonance (5)

Quality factor,

品质因数

$$Q = 2\pi \frac{\text{Peak energy stored in the circuit}}{\text{Energy dissipated by the circuit in one period at resonance}} = 2\pi \frac{\frac{1}{2}LI^2}{\frac{1}{2}I^2R(1/f_0)} = \frac{2\pi f_0 L}{R}$$


R 越小, Q 越大

$$Q = \frac{\omega_0 L}{R} = \frac{1}{\omega_0 CR}$$

$$B = \frac{R}{L} = \frac{\omega_0}{Q}$$

R 越小, B 越小

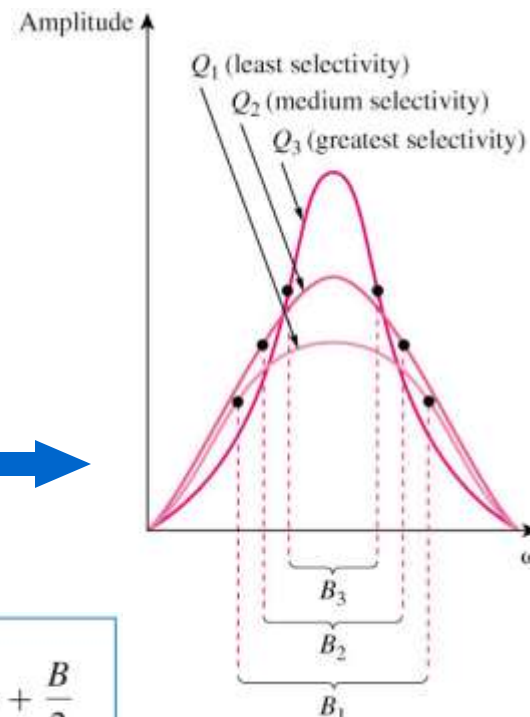- 曲线越窄 (带宽越小) $\rightarrow Q$ 值越大;
- Q 值的测量方法: 中心频率 \div 带宽



$$\omega_o = \sqrt{\omega_1 \omega_2}$$

If $Q > 10$

实际工程近似

$$\omega_1 \approx \omega_0 - \frac{B}{2}, \quad \omega_2 \approx \omega_0 + \frac{B}{2}$$

In the circuit of Fig. 14.24, $R = 2 \Omega$, $L = 1 \text{ mH}$, and $C = 0.4 \mu\text{F}$. (a) Find the resonant frequency and the half-power frequencies. (b) Calculate the quality factor and bandwidth. (c) Determine the amplitude of the current at ω_0 , ω_1 , and ω_2 .

Solution:

(a) The resonant frequency is

$$\textcircled{1} \quad \omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{10^{-3} \times 0.4 \times 10^{-6}}} = 50 \text{ krad/s}$$

$$\textcircled{2} \quad Q = \frac{\omega_0 L}{R} = \frac{50 \times 10^3 \times 10^{-3}}{2} = 25$$

From Q , we find

$$\textcircled{3} \quad B = \frac{\omega_0}{Q} = \frac{50 \times 10^3}{25} = 2 \text{ krad/s}$$

Since $Q > 10$, this is a high- Q circuit and we can obtain the half-power frequencies as

$$\textcircled{4} \quad \omega_1 = \omega_0 - \frac{B}{2} = 50 - 1 = 49 \text{ krad/s}$$

$$\textcircled{5} \quad \omega_2 = \omega_0 + \frac{B}{2} = 50 + 1 = 51 \text{ krad/s}$$

串联谐振电路的5个基本参数

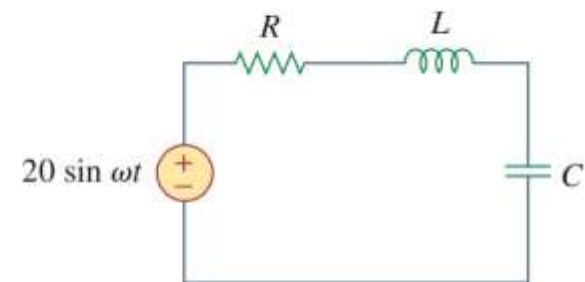


Figure 14.24
For Example 14.7.

思考：若不知RLC具体值，但可以测量出电流响应曲线（频率可直接读取），如何决定Q、B、R、L、C？

(c) At $\omega = \omega_0$,


$$I = \frac{V_m}{R} = \frac{20}{2} = 10 \text{ A}$$

At $\omega = \omega_1, \omega_2$,



$$I = \frac{V_m}{\sqrt{2}R} = \frac{10}{\sqrt{2}} = 7.071 \text{ A}$$

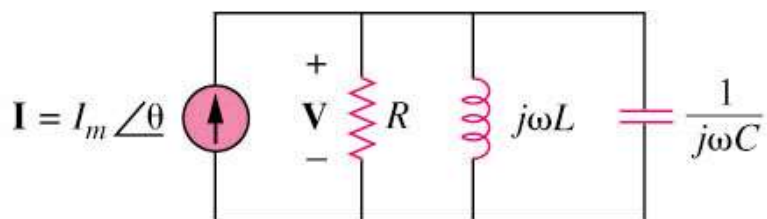14.4 Parallel Resonance 并联谐振

It occurs when imaginary part of Y is zero


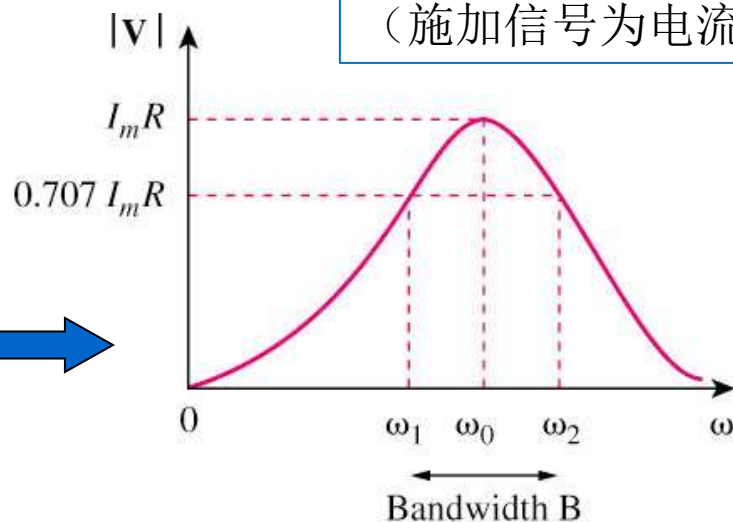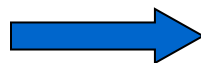
$$Y = \frac{1}{R} + j\left(\omega C - \frac{1}{\omega L}\right)$$



谐振时响应：电压特性
(施加信号为电流时)

Resonance frequency:

$$\omega_o = \frac{1}{\sqrt{LC}} \text{ rad/s} \quad \text{or} \quad f_o = \frac{1}{2\pi\sqrt{LC}} \text{ Hz}$$

$$|I_L| = \frac{I_m R}{\omega_0 L} = Q I_m$$

$$|I_C| = \omega_0 C I_m R = Q I_m$$

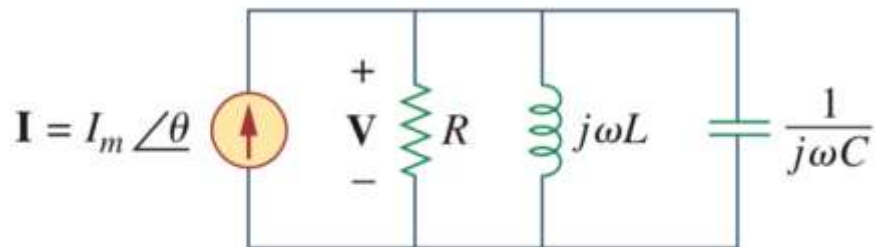


Figure 14.25


The parallel resonant circuit.

实际用不到

$$\omega_1 = -\frac{1}{2RC} + \sqrt{\left(\frac{1}{2RC}\right)^2 + \frac{1}{LC}}$$

$$\omega_2 = \frac{1}{2RC} + \sqrt{\left(\frac{1}{2RC}\right)^2 + \frac{1}{LC}}$$
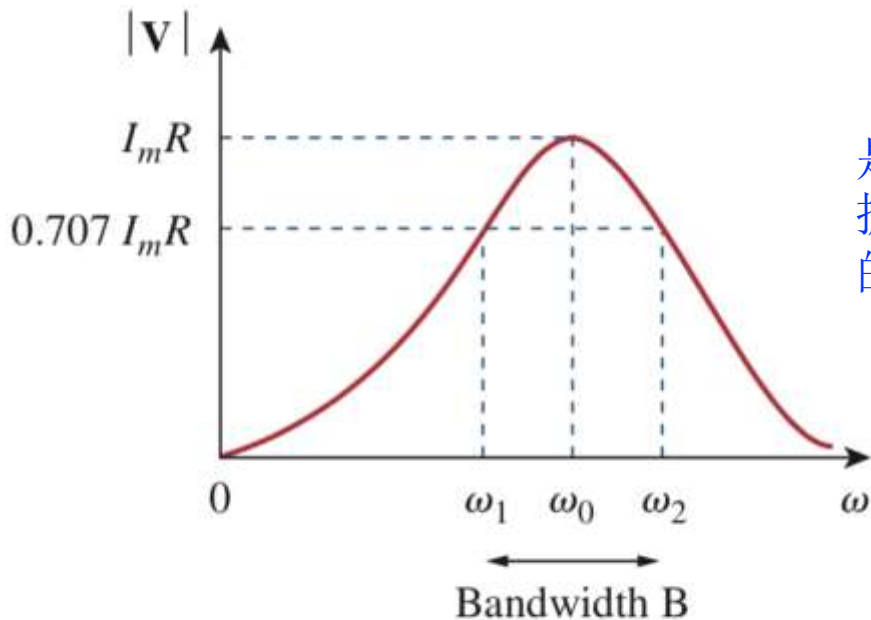
$$B = \omega_2 - \omega_1 = \frac{1}{RC}$$



是串联谐振Q公式的倒数

$$Q = \frac{\omega_0}{B} = \omega_0 RC = \frac{R}{\omega_0 L}$$

并联时R越大损耗越小

Again, for high- Q circuits ($Q \geq 10$)

实际工程近似用:

$$\omega_1 \approx \omega_0 - \frac{B}{2}, \quad \omega_2 \approx \omega_0 + \frac{B}{2}$$

Figure 14.26

The current amplitude versus frequency for the series resonant circuit of Fig. 14.25.

14.4 串并联比较

Summary of series and parallel resonance circuits:

<i>characteristic</i>	<i>Series circuit</i>	<i>Parallel circuit</i>
① ω_0	$\frac{1}{\sqrt{LC}}$	$\frac{1}{\sqrt{LC}}$
② Q	$\frac{\omega_0 L}{R}$ or $\frac{1}{\omega_0 RC}$	$\frac{R}{\omega_0 L}$ or $\omega_0 RC$
③ B	$\frac{\omega_0}{Q}$	$\frac{\omega_0}{Q}$
ω_1, ω_2	$\omega_0 \sqrt{1 + \left(\frac{1}{2Q}\right)^2} \pm \frac{\omega_0}{2Q}$	$\omega_0 \sqrt{1 + \left(\frac{1}{2Q}\right)^2} \pm \frac{\omega_0}{2Q}$
$Q \geq 10, \omega_1, \omega_2$ ④ ⑤	$\omega_0 \pm \frac{B}{2}$	$\omega_0 \pm \frac{B}{2}$

谐振电路的5个基本参数

Example 14.8

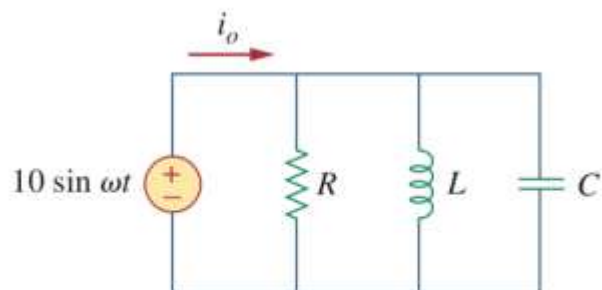


Figure 14.27
For Example 14.8.

In the parallel RLC circuit of Fig. 14.27, let $R = 8 \text{ k}\Omega$, $L = 0.2 \text{ mH}$, and $C = 8 \mu\text{F}$. (a) Calculate ω_0 , Q , and B . (b) Find ω_1 and ω_2 . (c) Determine the power dissipated at ω_0 , ω_1 , and ω_2 .

Solution:

(a)

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{0.2 \times 10^{-3} \times 8 \times 10^{-6}}} = \frac{10^5}{4} = 25 \text{ krad/s}$$

$$Q = \frac{R}{\omega_0 L} = \frac{8 \times 10^3}{25 \times 10^3 \times 0.2 \times 10^{-3}} = 1,600$$

$$B = \frac{\omega_0}{Q} = 15.625 \text{ rad/s}$$

$$\omega_1 = \omega_0 - \frac{B}{2} = 25,000 - 7.812 = 24,992 \text{ rad/s}$$

$$\omega_2 = \omega_0 + \frac{B}{2} = 25,000 + 7.812 = 25,008 \text{ rad/s}$$

(c) At $\omega = \omega_0$, $\mathbf{Y} = 1/R$ or $\mathbf{Z} = R = 8 \text{ k}\Omega$. Then

$$\mathbf{I}_o = \frac{\mathbf{V}}{\mathbf{Z}} = \frac{10 \angle -90^\circ}{8,000} = 1.25 \angle -90^\circ \text{ mA}$$

Since the entire current flows through R at resonance, the average power dissipated at $\omega = \omega_0$ is

At $\omega = \omega_1, \omega_2$,

$$P = \frac{1}{2} |\mathbf{I}_o|^2 R = \frac{1}{2} (1.25 \times 10^{-3})^2 (8 \times 10^3) = 6.25 \text{ mW}$$

$$P = \frac{V_m^2}{4R} = 3.125 \text{ mW}$$

Determine the resonant frequency of the circuit in Fig. 14.28.

Solution:

The input admittance is

$$\mathbf{Y} = j\omega 0.1 + \frac{1}{10} + \frac{1}{2 + j\omega 2} = 0.1 + j\omega 0.1 + \frac{2 - j\omega 2}{4 + 4\omega^2}$$

At resonance, $\text{Im}(\mathbf{Y}) = 0$ and

$$\omega_0 0.1 - \frac{2\omega_0}{4 + 4\omega_0^2} = 0 \quad \Rightarrow \quad \omega_0 = 2 \text{ rad/s}$$

Example 14.9

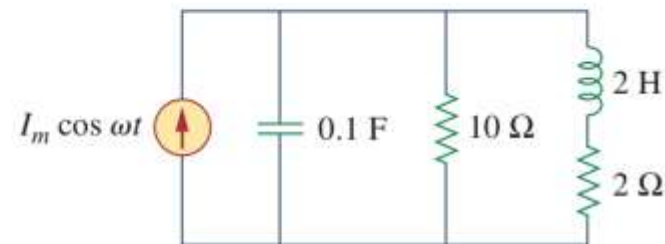


Figure 14.28
For Example 14.9.


当电路不是简单的RLC并联或
RLC串联时：
写出传递函数分析谐振频率

14.5 Passive Filters (1)


- **A filter** is a circuit that is designed to pass signals with desired frequencies and reject or attenuate others.
- **Passive filter** consists of only passive element R, L and C.
- There are four types of filters.

理想滤波器的传递函数


Low Pass
低通滤波器

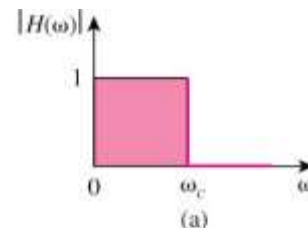


High Pass
高通滤波器

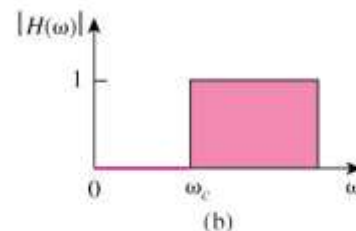


Band Pass
带通滤波器

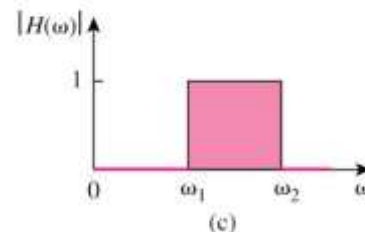

Band Stop
带阻滤波器

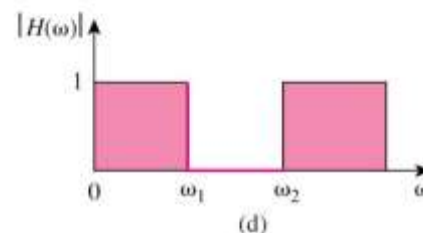

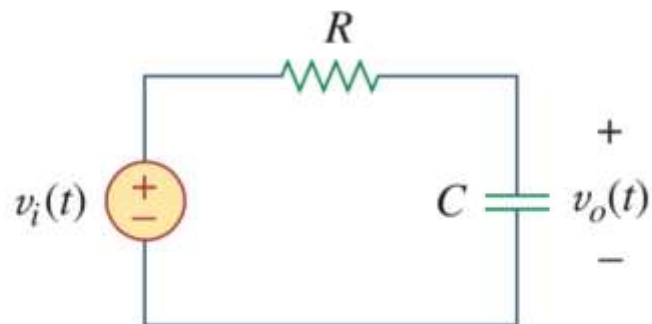


$$\mathbf{H}(\omega) = \frac{\mathbf{V}_o}{\mathbf{V}_i} = \frac{1/j\omega C}{R + 1/j\omega C} = \frac{1}{1 + j\omega RC}$$

Figure 14.31

A lowpass filter.

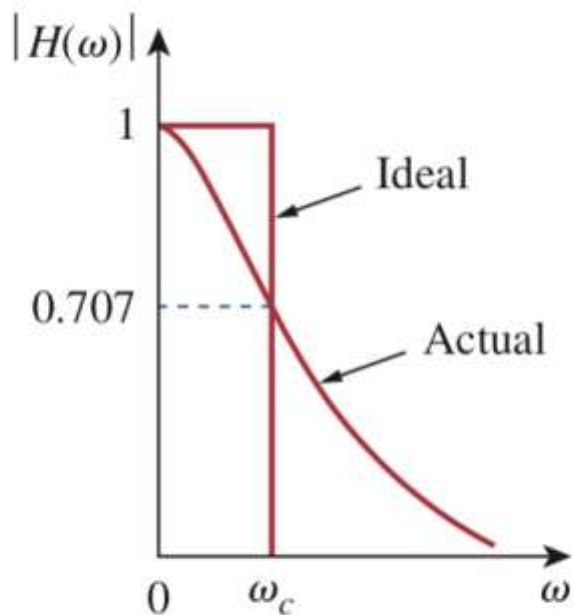A **lowpass filter** is designed to pass only frequencies from dc up to the cutoff frequency ω_c .



半功率处的频率称为“**截止频率**” (cutoff frequency)


$$H(\omega_c) = \frac{1}{\sqrt{1 + \omega_c^2 R^2 C^2}} = \frac{1}{\sqrt{2}}$$

$$\omega_c = \frac{1}{RC}$$

判断滤波特性的方法: **special cases**

Figure 14.32

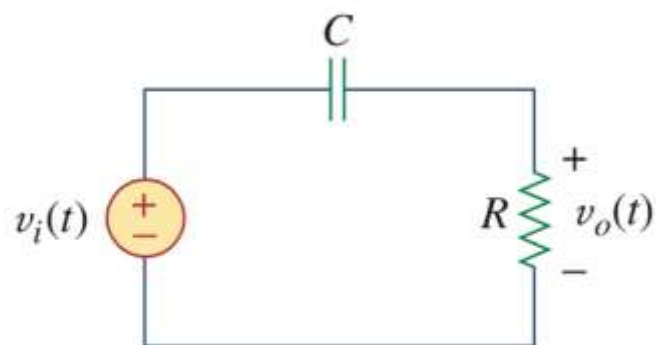
Ideal and actual frequency response of a lowpass filter.



$$\mathbf{H}(\omega) = \frac{\mathbf{V}_o}{\mathbf{V}_i} = \frac{R}{R + 1/j\omega C} = \frac{j\omega RC}{1 + j\omega RC}$$

Figure 14.33
A highpass filter.

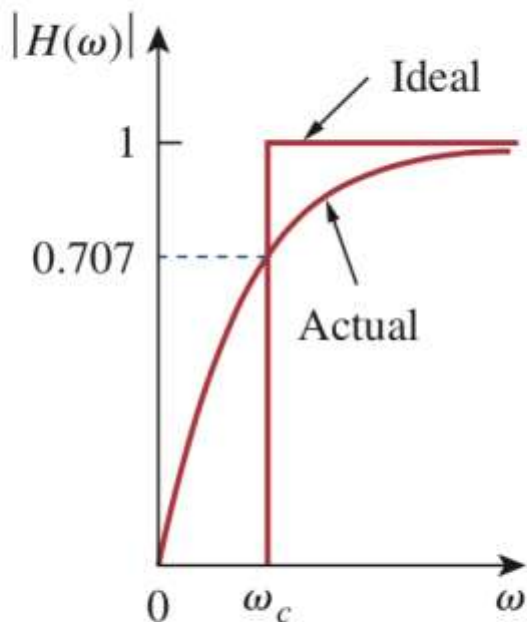
A **highpass filter** is designed to pass all frequencies above its cutoff frequency ω_c .



半功率处的频率称为“截止频率” (cutoff frequency)

$$\omega_c = \frac{1}{RC}$$

Figure 14.34
Ideal and actual frequency response of a highpass filter.

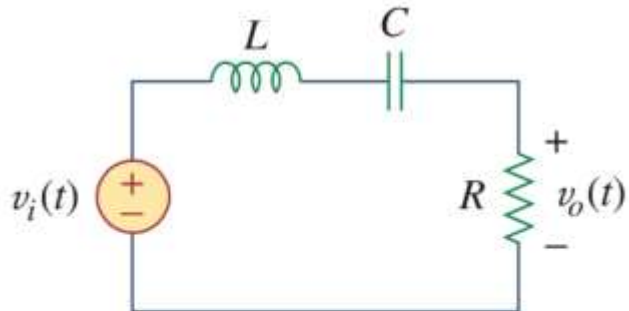


$$\mathbf{H}(\omega) = \frac{\mathbf{V}_o}{\mathbf{V}_i} = \frac{R}{R + j(\omega L - 1/\omega C)}$$

Figure 14.35

A bandpass filter.

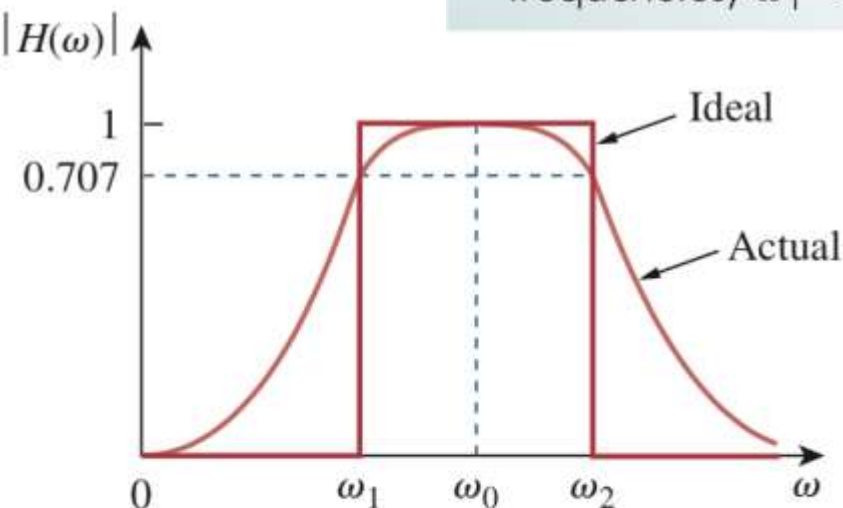
A **bandpass filter** is designed to pass all frequencies within a band of frequencies, $\omega_1 < \omega < \omega_2$.



$$\omega_0 = \frac{1}{\sqrt{LC}}$$

Figure 14.36

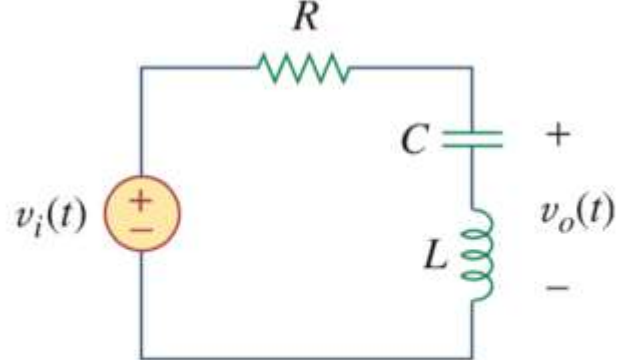Ideal and actual frequency response of a bandpass filter.




$$\mathbf{H}(\omega) = \frac{\mathbf{V}_o}{\mathbf{V}_i} = \frac{j(\omega L - 1/\omega C)}{R + j(\omega L - 1/\omega C)}$$

Figure 14.37

A bandstop filter.

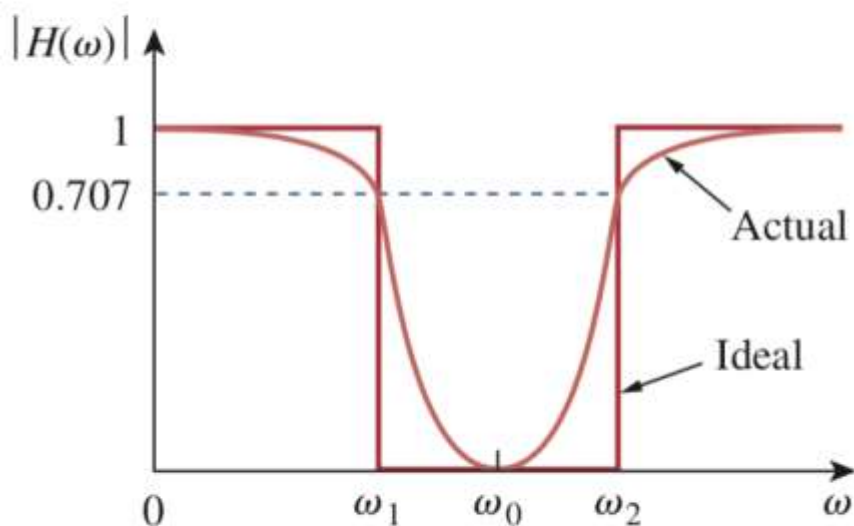A **bandstop filter** is designed to stop or eliminate all frequencies within a band of frequencies, $\omega_1 < \omega < \omega_2$.



$$\omega_0 = \frac{1}{\sqrt{LC}}$$

Figure 14.38

Ideal and actual frequency response of a bandstop filter.

Example 14.10

Determine what type of filter is shown in Fig. 14.39. Calculate the corner or cutoff frequency. Take $R = 2 \text{ k}\Omega$, $L = 2 \text{ H}$, and $C = 2 \text{ }\mu\text{F}$.

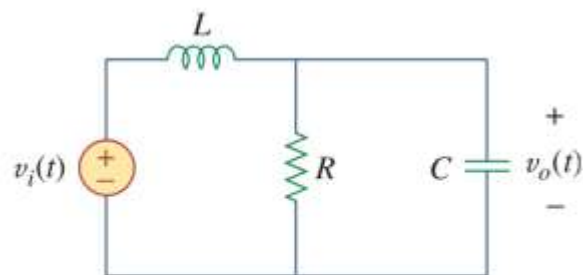


Figure 14.39

For Example 14.10.

$$\mathbf{H}(s) = \frac{\mathbf{V}_o}{\mathbf{V}_i} = \frac{R \parallel 1/sC}{sL + R \parallel 1/sC}, \quad s = j\omega$$

$$\mathbf{H}(\omega) = \frac{R}{-\omega^2 RLC + j\omega L + R}$$

Since $\mathbf{H}(0) = 1$ and $\mathbf{H}(\infty) = 0$,



猜测低通滤波器

传递函数的幅度: $H = \frac{R}{\sqrt{(R - \omega^2 RLC)^2 + \omega^2 L^2}}$






$$H^2 = \frac{1}{2} = \frac{R^2}{(R - \omega_c^2 RLC)^2 + \omega_c^2 L^2}$$




Solving the quadratic equation in ω_c^2 , we get $\omega_c^2 = 0.5509$ and -0.1134 .
Since ω_c is real,

$$\omega_c = 0.742 \text{ krad/s} = 742 \text{ rad/s}$$

$$H(\omega) = \frac{R}{-\omega^2 RLC + j\omega L + R}$$

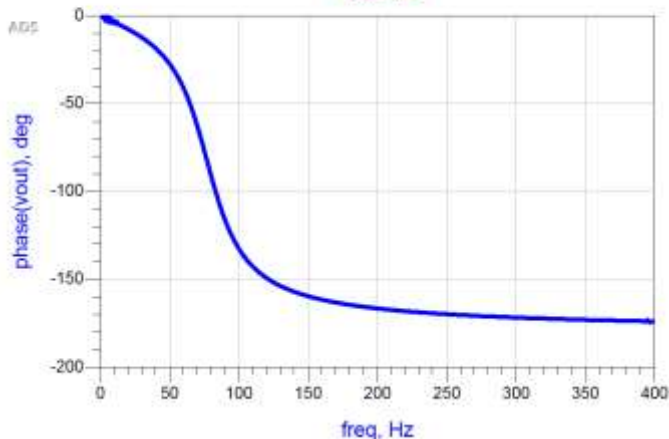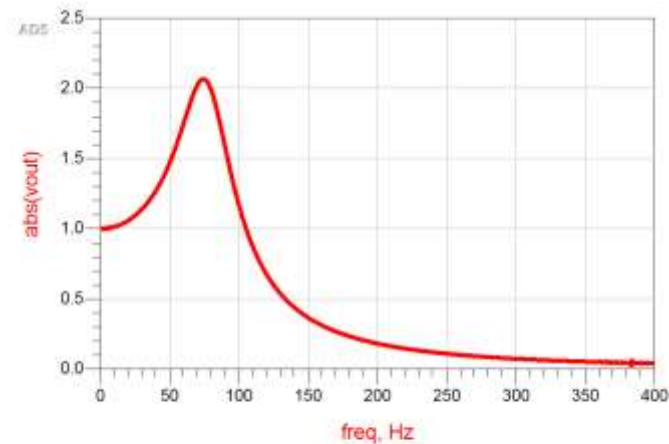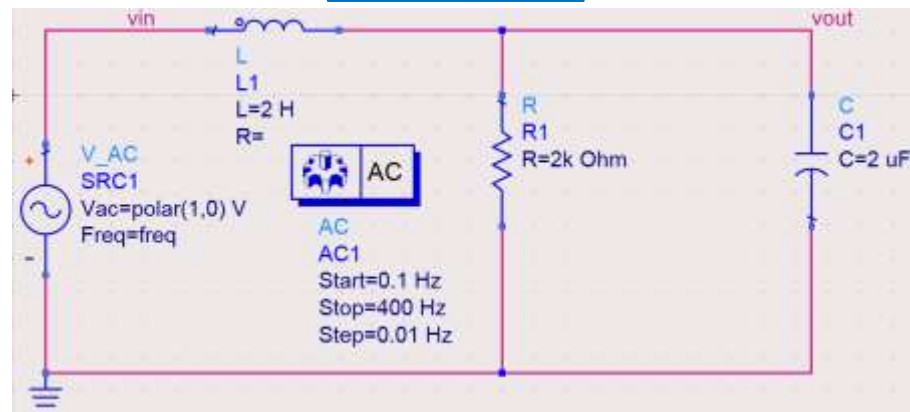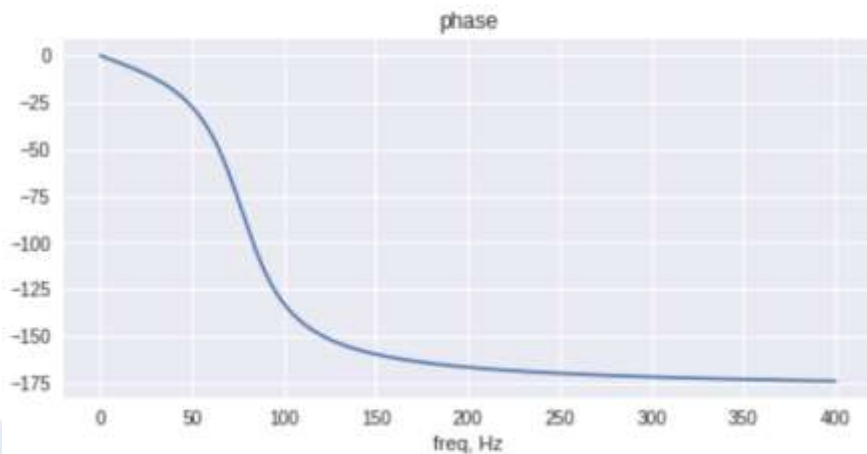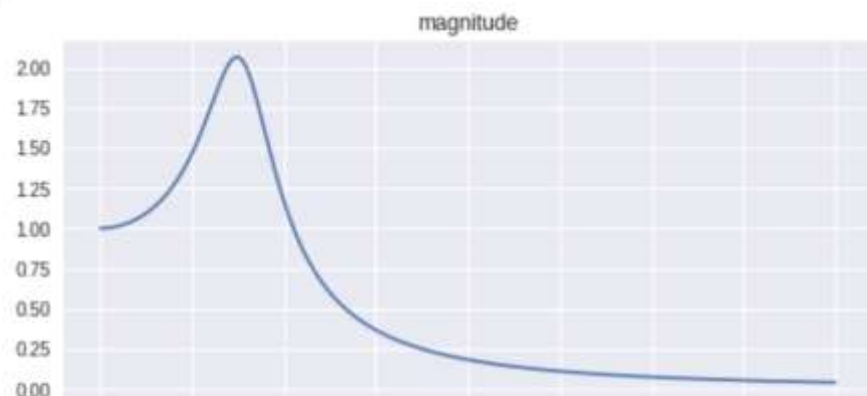

Example 14.11

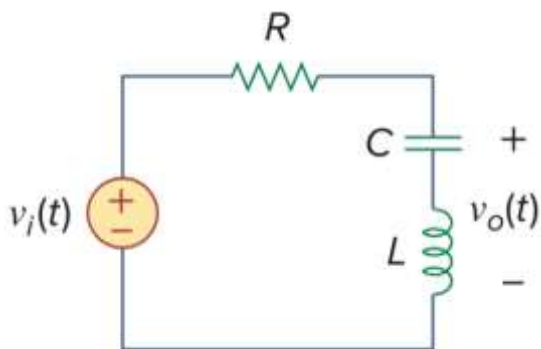

If the band-stop filter in Fig. 14.37 is to reject a 200-Hz sinusoid while passing other frequencies, calculate the values of L and C . Take $R = 150 \, \Omega$ and the bandwidth as 100 Hz.

Solution:

We use the formulas for a series resonant circuit in Section 14.5.

$$B = 2\pi(100) = 200\pi \text{ rad/s}$$

But

$$B = \frac{R}{L} \Rightarrow L = \frac{R}{B} = \frac{150}{200\pi} = 0.2387 \text{ H}$$

Rejection of the 200-Hz sinusoid means that f_0 is 200 Hz, so that ω_0 in Fig. 14.38 is

$$\omega_0 = 2\pi f_0 = 2\pi(200) = 400\pi$$


Given that $\omega_0 = 1/\sqrt{LC}$,

$$C = \frac{1}{\omega_0^2 L} = \frac{1}{(400\pi)^2 (0.2387)} = 2.653 \, \mu\text{F}$$

$$B = \frac{\omega_0}{Q} \Rightarrow Q = 2$$


$$Q = \frac{\omega_0 L}{R} \Rightarrow L = 300\pi/400$$

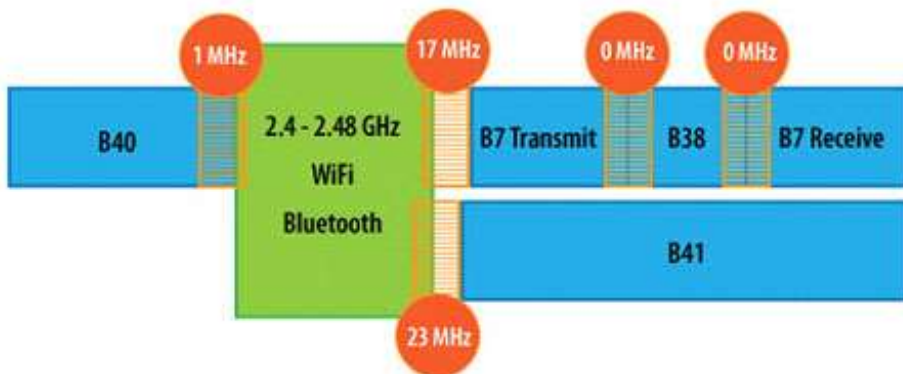2.3-2.7 GHz Ecosystem Coexistence Requirements




Minimal guard bands require FBAR Filter performance to solve difficult coexistence problems

FBAR Filter Advantages

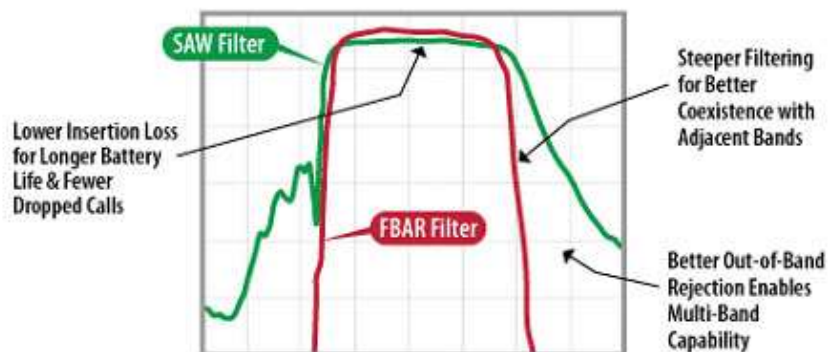

滤波器的在移动终端中的应用


Figure 11. Typical LTE RF Subsystem

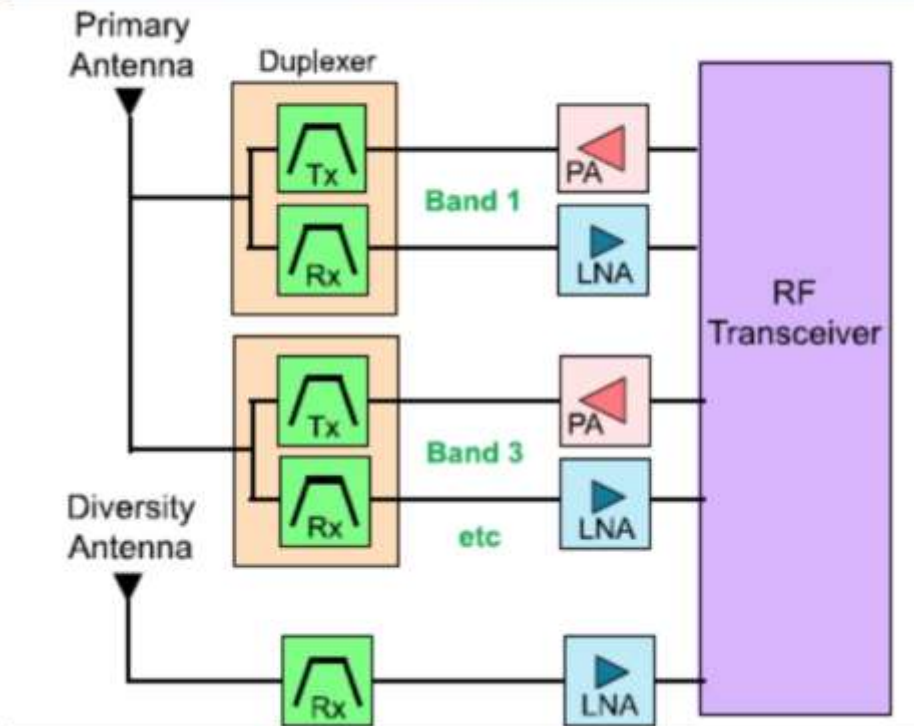


Sources: Company Reports and Joseph Gunnar

频谱资源越来越紧张 → 高性能滤波器需求

时分复用系统

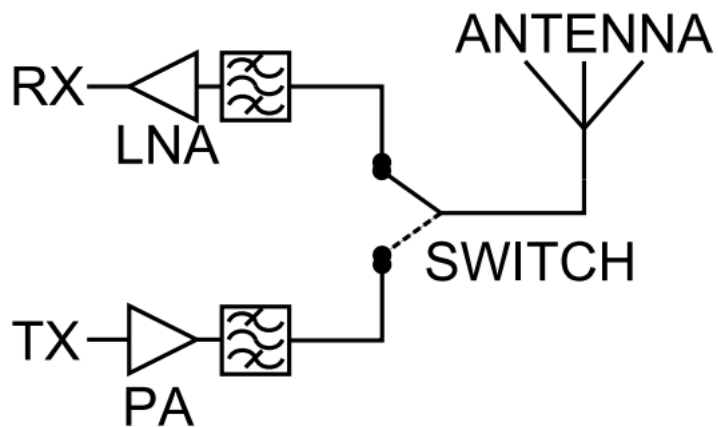

频分复用系统

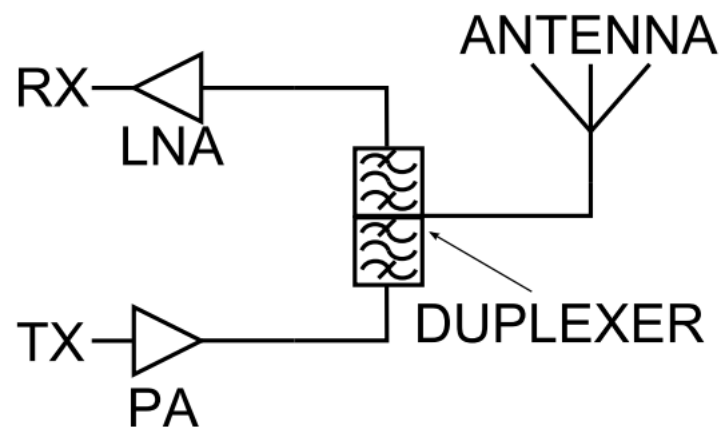

滤波器的主要参数

- 1) 中心频率 (Center Frequency) f_0 。
- 2) 3dB 带宽 (Band-Width) BW_{3dB} 。也称通频带。
- 3) 带内波动 (Ripple)。应尽量小, 以减少频率失真。
- 4) 选择性 (Selectivity)。也称带外衰减, 描述滤波器对频带外信号的衰减程度, 带外衰减越大, 选择性越好。
- 5) 插入损耗 (Insertion Loss)。插入损耗定义为通频带内滤波器的输入功率和输出功率之比:




$$IL = \frac{P_{in}}{P_{out}} \quad (1.1)$$

一般用 dB 表示, 无源滤波器都有一定的损耗, 损耗越小越好。

- 6) 零点 (Zeros) 和极点 (Poles)。即滤波器传输系数表达式的零点和极点, 在零点处, 传输系数为 0, 在极点处, 传输系数最大。
- 7) 滚降 (Roll-Off): 滤波器传输系数从滤波器通频带边缘到邻近零点的下滑程度, 要求越陡越好。
- 8) 品质因数 Q 。 Q 值定义为储能和损耗之比, 其值也可以用中心频率 f_0 和带宽 BW_{3dB} 之比来定量表示:

$$Q = \frac{f_0}{BW_{3dB}} \quad (1.2)$$

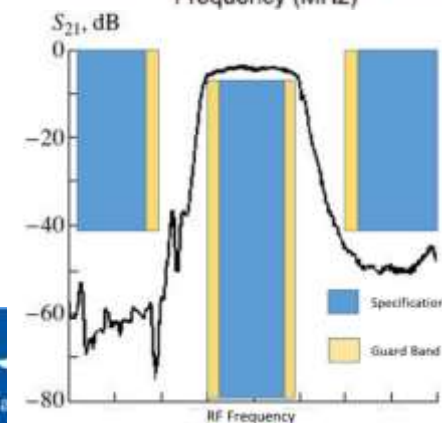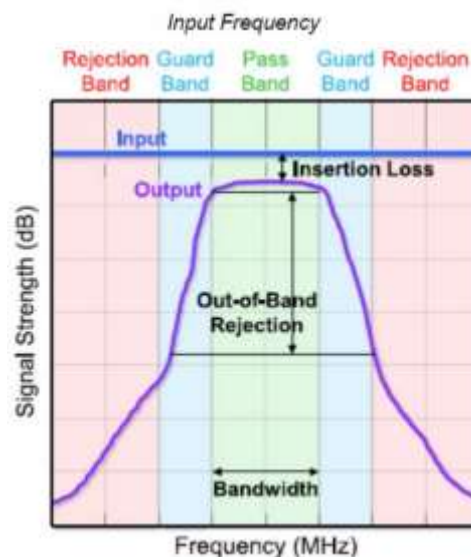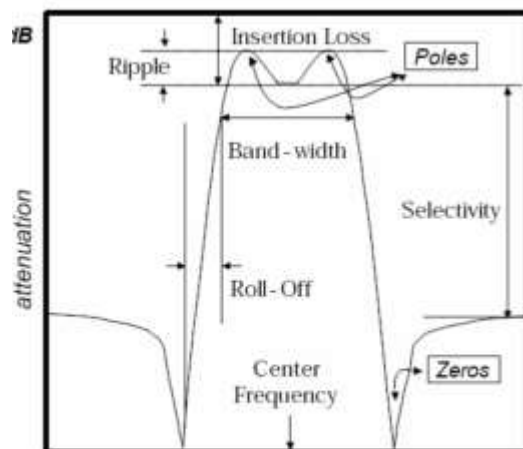- 9) 输入输出阻抗。滤波器的性能指标都是在其输入输出端均匹配时测得的, 在应用时, 必须知道其输入输出阻抗, 并很好的匹配, 才能使滤波器发挥其最佳性能。
- 10) 相频特性。滤波器传输系数相位随频率变化的曲线, 要求其接近线性。







移动终端滤波器方案


➤ 目前滤波器解决方案：介质滤波器、声表面波（SAW）、FBAR

	介质滤波器 	SAW 	FBAR 
工作频率	1MHz-10GHz	30MHz-2GHz	500MHz-10GHz
插入损耗	1-2 dB	2.5-4 dB	1-1.5 dB
带外抑制	<40 dB	<45 dB	<50 dB
温度系数	-10 ~ +10 ppm/°C	-35 ~ -95 ppm/°C	-25 ~ -30 ppm/°C
Q	300-700	200-400	700-1000
功率容量	>>1W	<1W	>1W
尺寸	5-10mm ²	2-8mm ²	0.1*0.1mm ²
制备工艺	成熟	成熟	工艺要求高
可集成性	不能	不能	可以


SAW原理

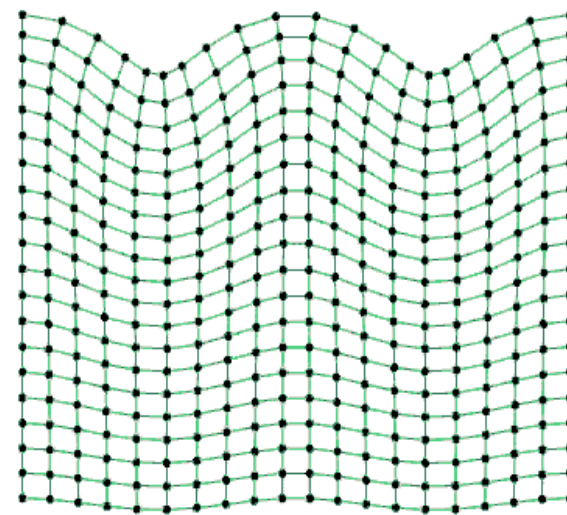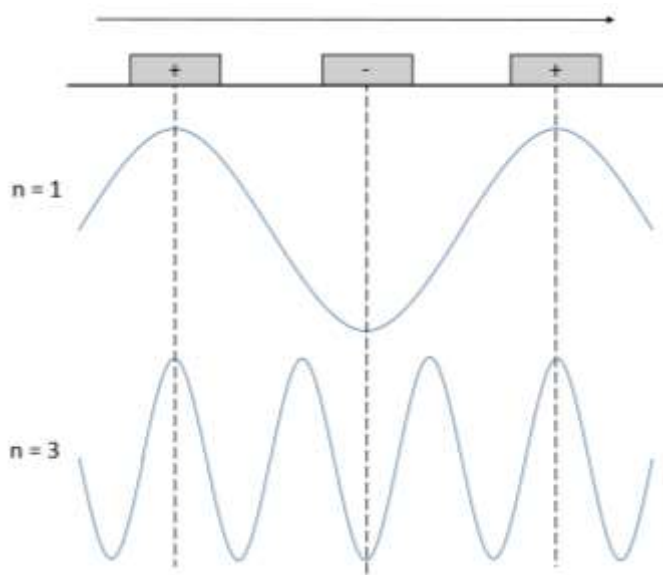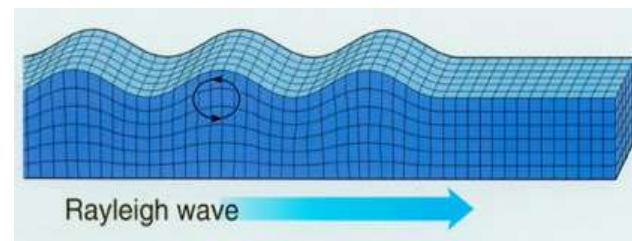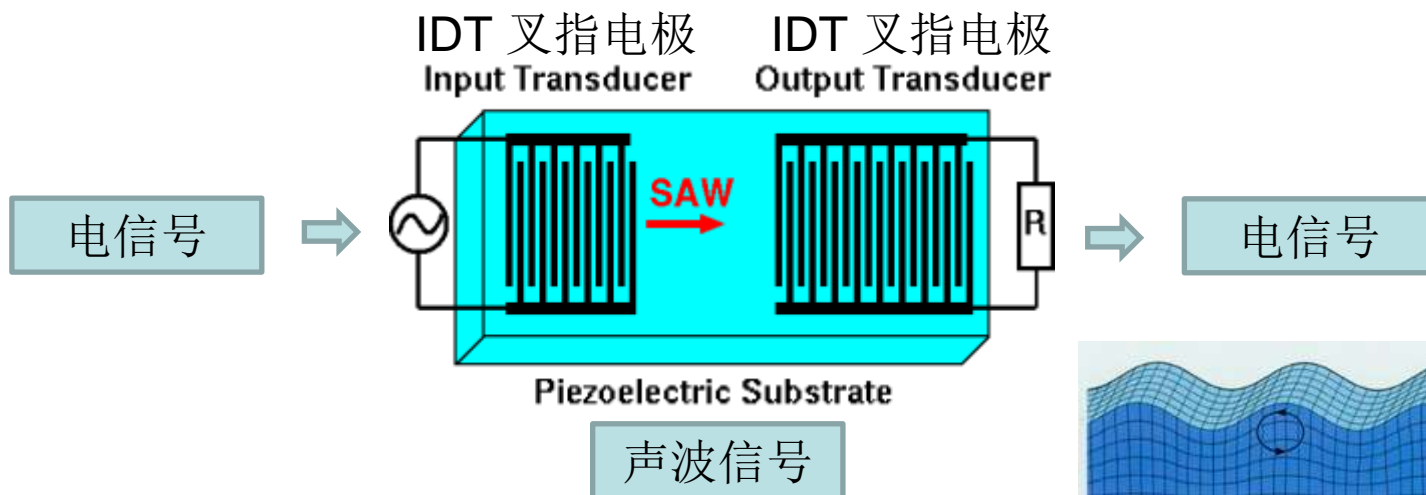

FBAR原理

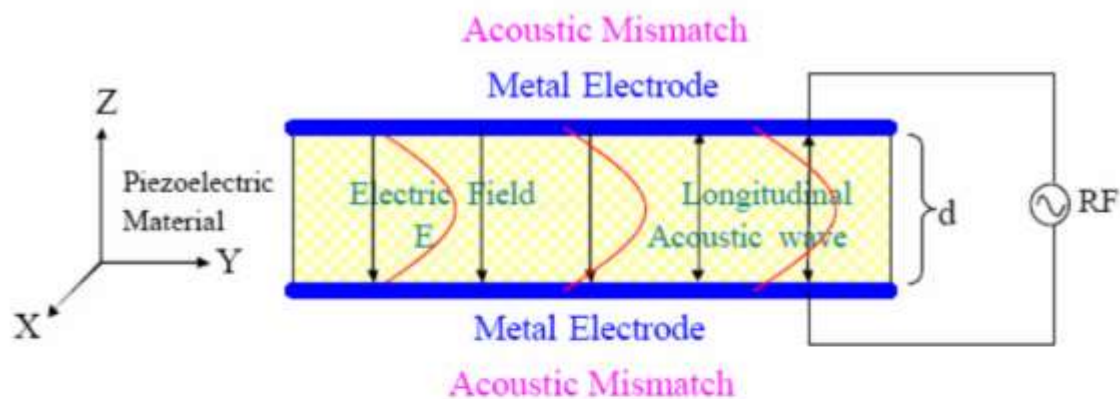



(a)

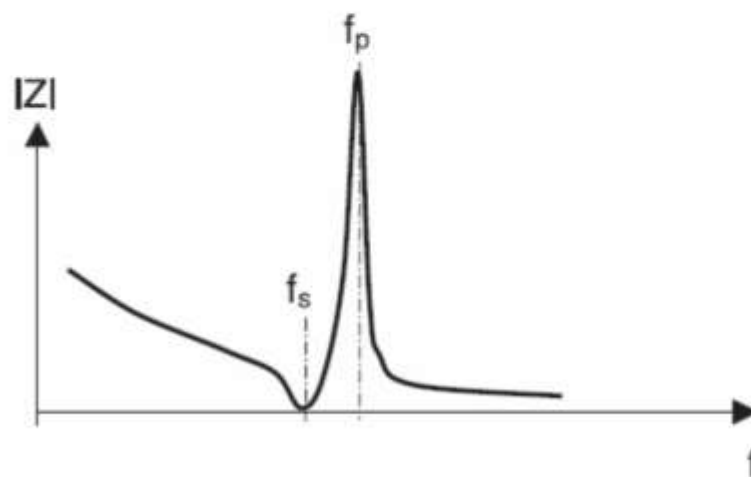

(b)

图 1.7 FBAR 工作原理: (a)声波激励; (b)电学阻抗特性[23]

SAW / FBAR 谐振器的等效电路

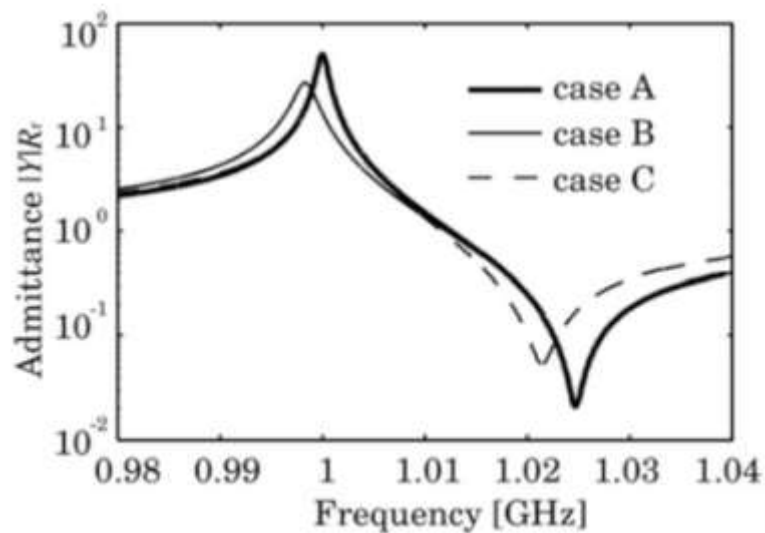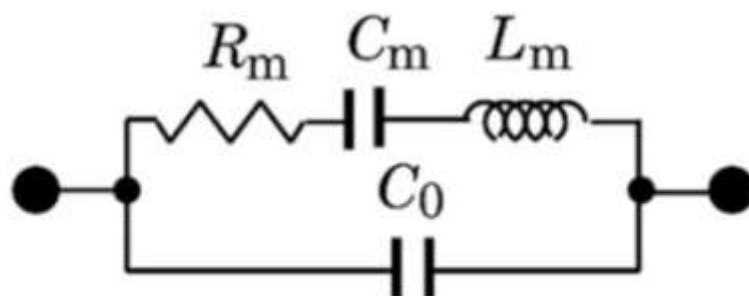

FBAR滤波器设计方法

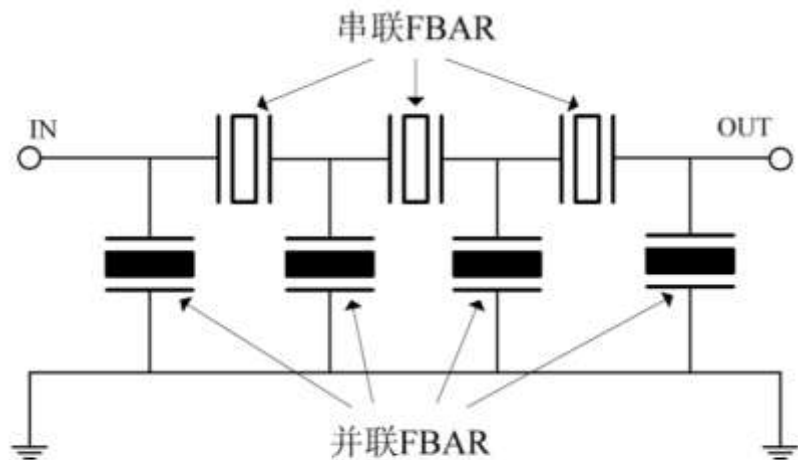


图 6.1 阶梯型 FBAR 滤波器拓扑结构


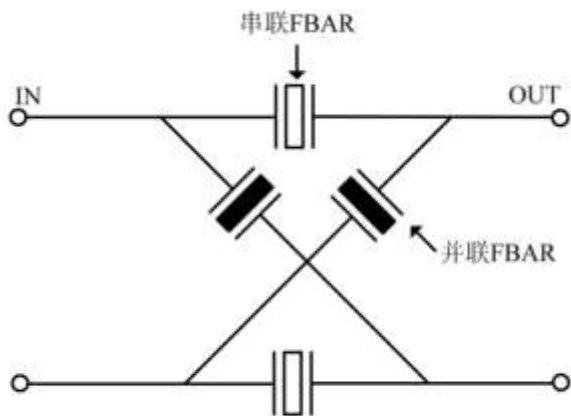


图 6.4 网格型 FBAR 滤波器拓扑结构


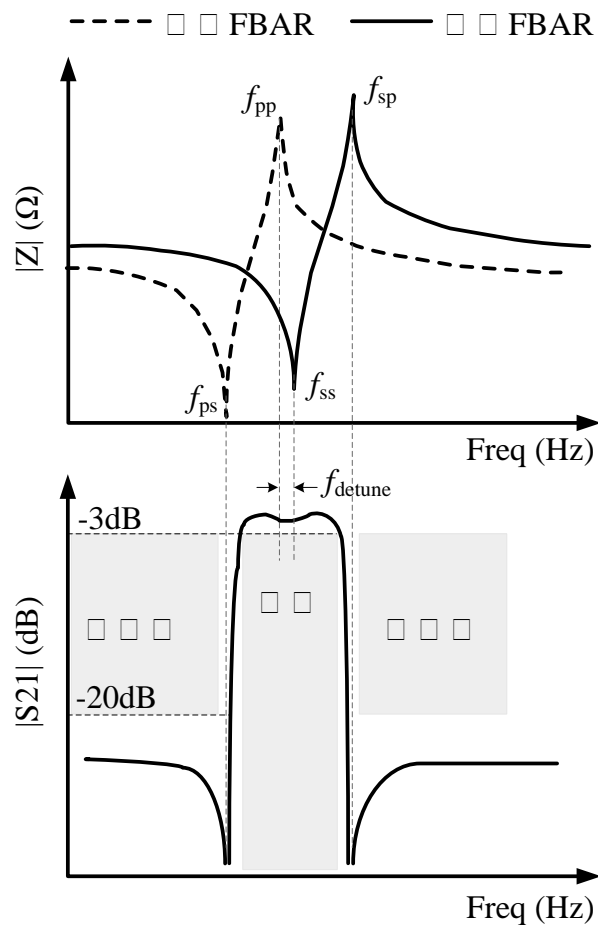


FBAR主要产品及剖析

第一款产业化的FBAR产品:



Avago的针对US PCS1900的第一代FBAR双工器HPMD-7904

✦ 样品整体情况

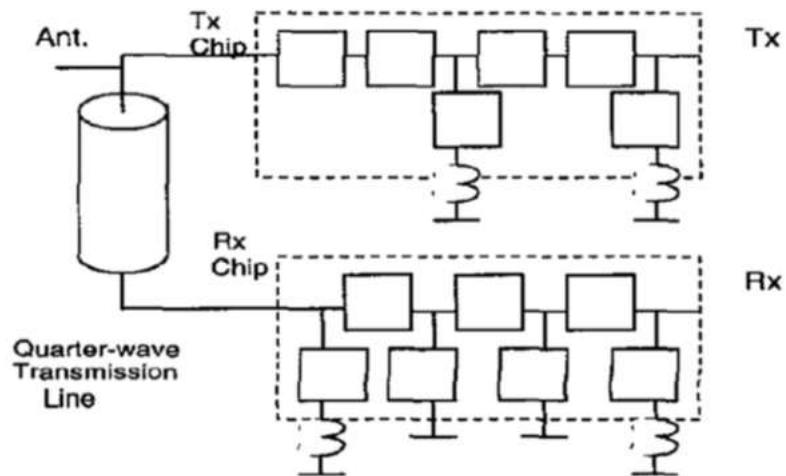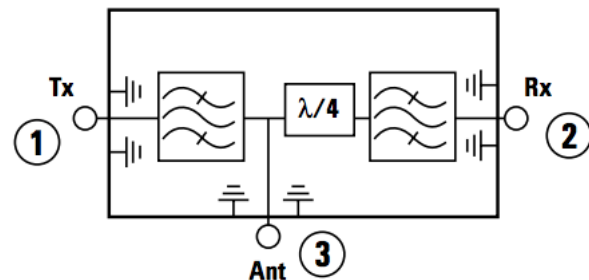

FBAR主要产品及剖析




TX部分结构

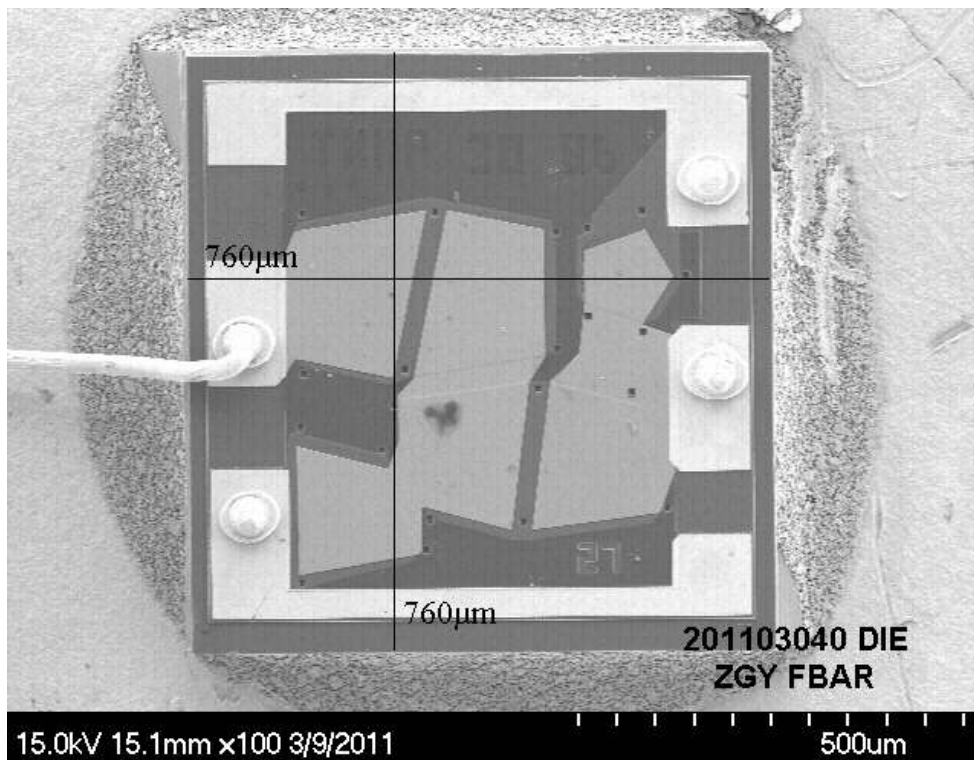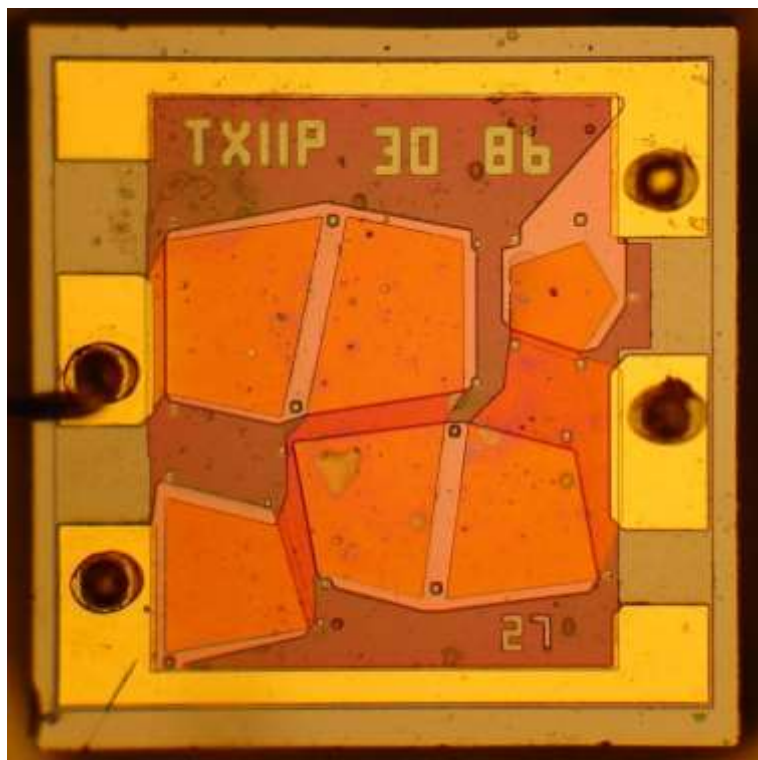


芯片大小为760um*760um

FBAR主要产品及剖析

剖面分析结果

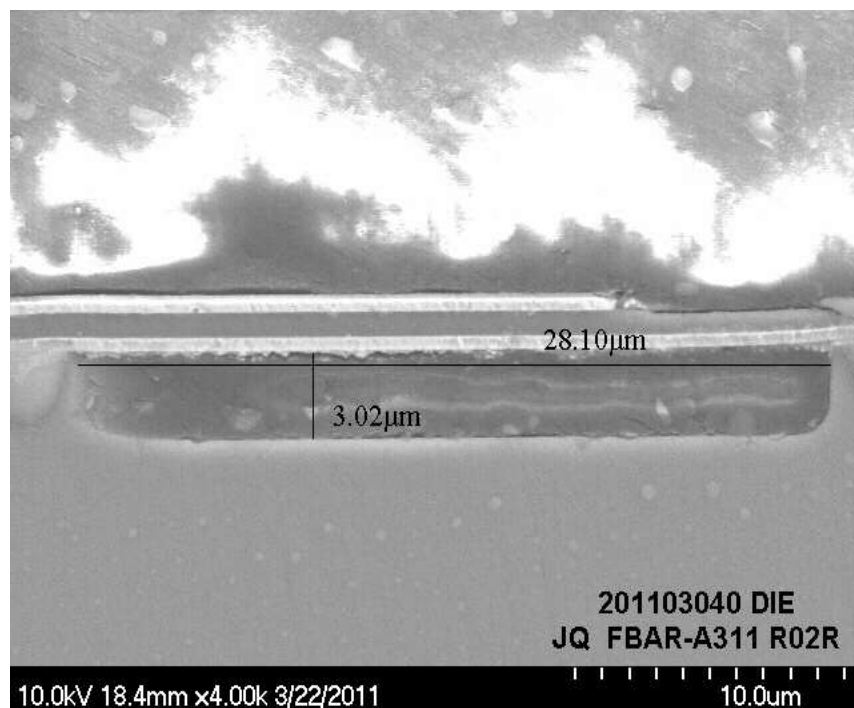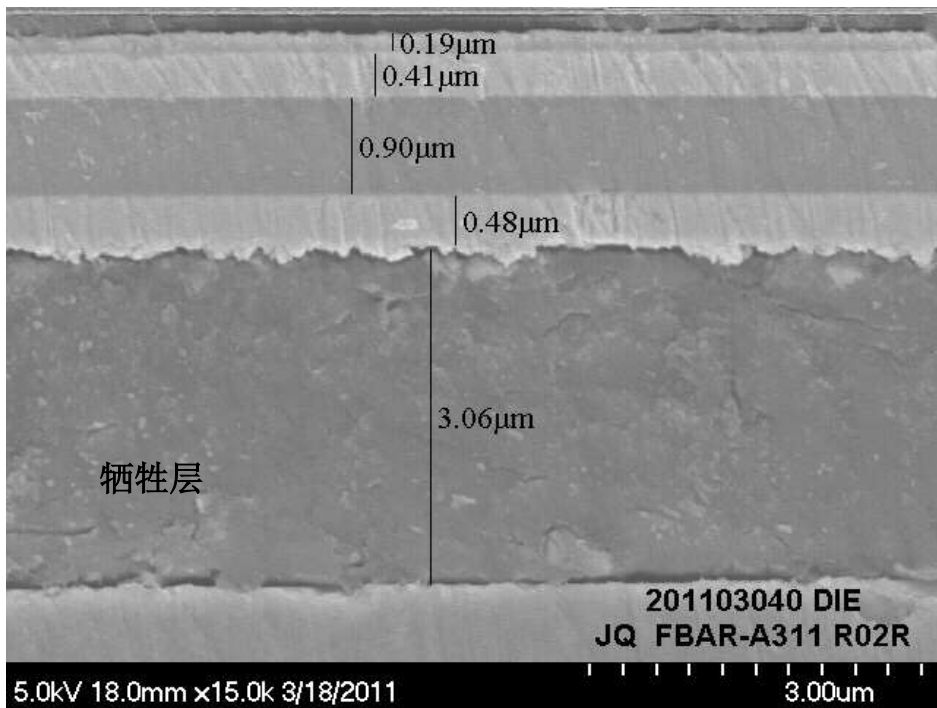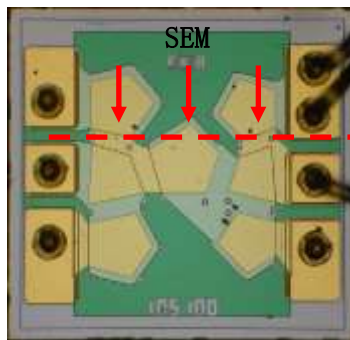

SEM显示牺牲层上存在四层结构，牺牲层厚度为3 μ m。

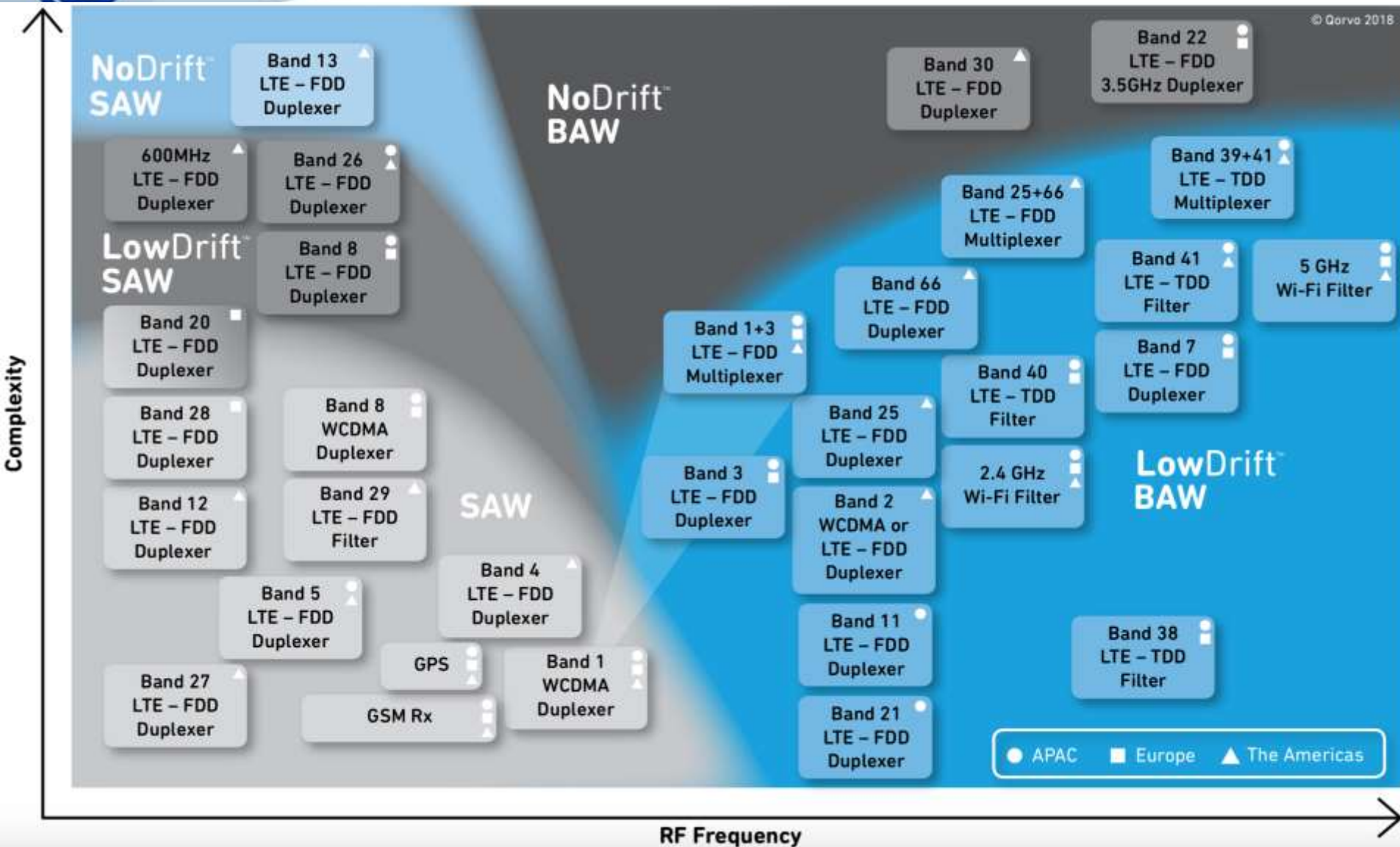

小结

- 频率响应

- dB的概念

$$G_{dB} = 10 \log_{10} \frac{P_2}{P_1}$$

$$G_{dB} = 20 \log_{10} \frac{V_2}{V_1}$$

- 会根据波特图写出传递函数；也会根据传递函数画出波特图
- 谐振电路的五个基本参数，注意串并联的Q值公式互为倒数

串联

① $\omega_0 = \frac{1}{\sqrt{LC}}$

② $Q = \frac{\omega_0 L}{R}$

③ $B = \frac{\omega_0}{Q}$

④ $\omega_1 = \omega_0 - \frac{B}{2}$

⑤ $\omega_2 = \omega_0 + \frac{B}{2}$

- 滤波器的类型，以及 special case 判断滤波器类型的方法



作业

Obtain the transfer function $H(\omega)$ corresponding to the Bode plot in Fig. 14.20.

Answer: $H(\omega) = \frac{2,000,000(s + 5)}{(s + 10)(s + 100)^2}$.

用双重极点表示

Practice Problem 14.6

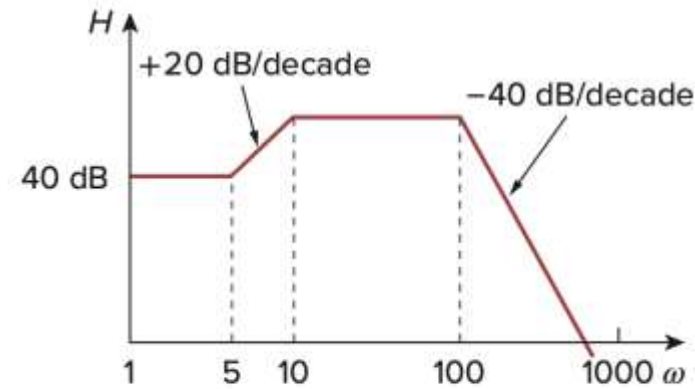


Figure 14.20
For Practice Prob. 14.6.

Draw the Bode plots for the transfer function

$$\mathbf{H}(\omega) = \frac{5(j\omega + 2)}{j\omega(j\omega + 10)}$$

Answer: See Fig. 14.14.


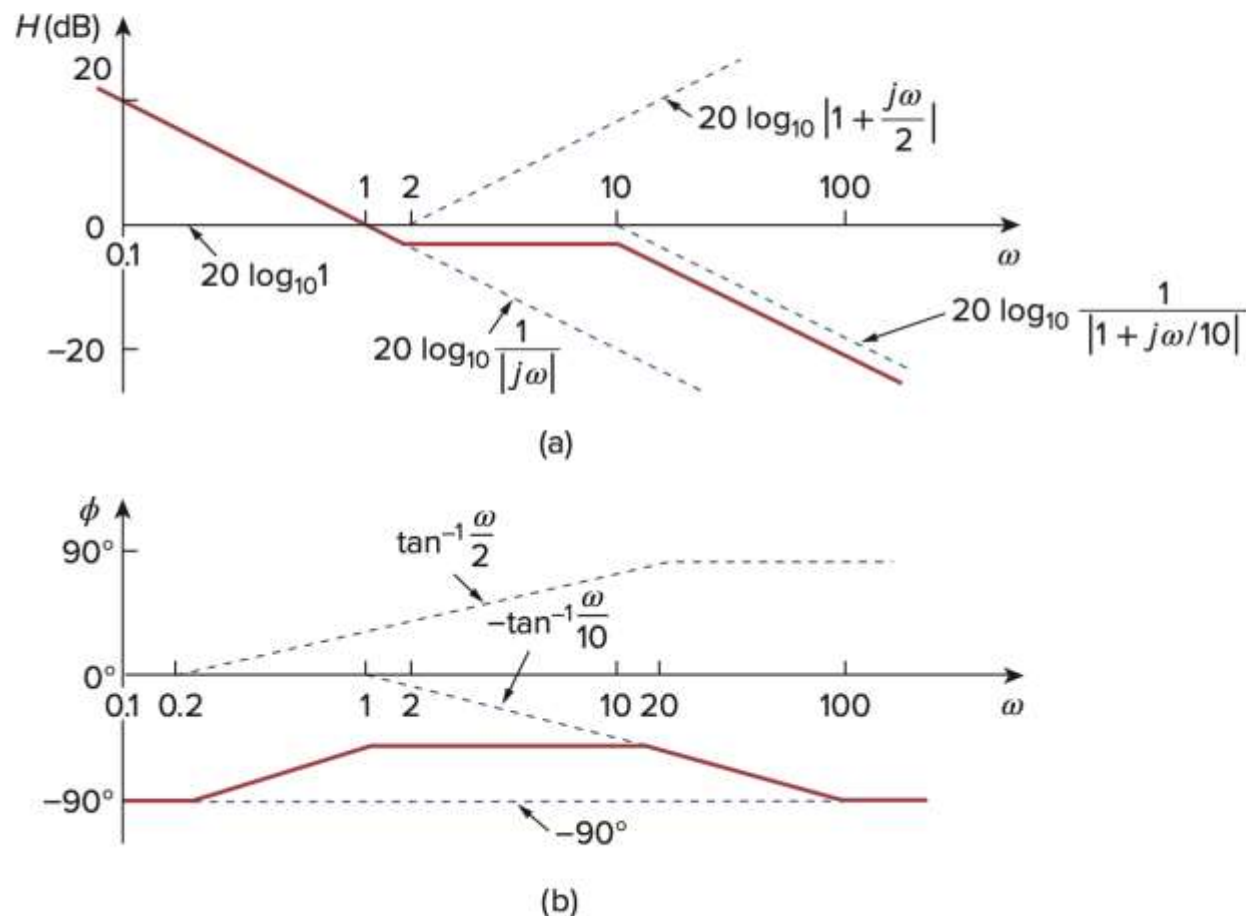


Figure 14.14

For Practice Prob. 14.3: (a) magnitude plot, (b) phase plot.

Practice Problem 14.7

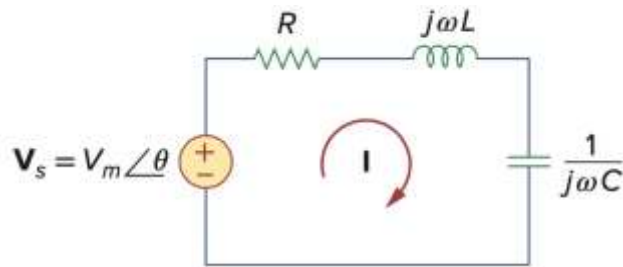

A series-connected circuit has $R = 4 \, \Omega$ and $L = 25 \, \text{mH}$. (a) Calculate the value of C that will produce a quality factor of 50. (b) Find ω_1 , ω_2 , and B . (c) Determine the average power dissipated at $\omega = \omega_0$, ω_1 , ω_2 . Take $V_m = 100 \, \text{V}$.


串联谐振

Answer: (a) $0.625 \, \mu\text{F}$, (b) $7920 \, \text{rad/s}$, $8080 \, \text{rad/s}$, $160 \, \text{rad/s}$, (c) $1.25 \, \text{kW}$, $0.625 \, \text{kW}$, $0.625 \, \text{kW}$.

Practice Problem 14.8

A parallel resonant circuit has $R = 100 \text{ k}\Omega$, $L = 50 \text{ mH}$, and $C = 2 \text{ nF}$. Calculate ω_0 , ω_1 , ω_2 , Q , and B .

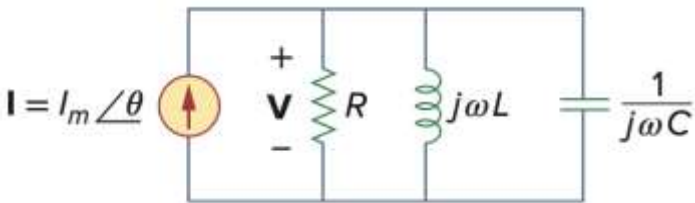Answer: 100 krad/s, 97.5 krad/s, 102.5 krad/s, 20, 5 krad/s.



并联谐振

Calculate the resonant frequency of the circuit in Fig. 14.29.

Answer: 173.21 rad/s.

Practice Problem 14.9

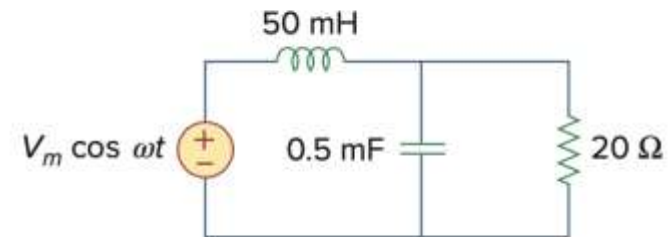


Figure 14.29
For Practice Prob. 14.9

非简单串并联情况计算谐振频率

Practice Problem 14.11

Design a band-pass filter of the form in Fig. 14.35 with a lower cutoff frequency of 20.1 kHz and an upper cutoff frequency of 20.3 kHz. Take $R = 30 \text{ k}\Omega$. Calculate L , C , and Q .

Answer: 23.87 H, 2.6 pF, 101.

帶通濾波器

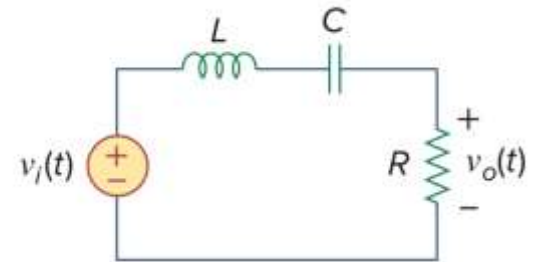


Figure 14.35
A band-pass filter.