

电子电路基础

第八讲~磁耦合电路

课程纲要

- 6.1 磁耦合基本概念
 - 6.1.1 互感的概念及其计算
 - 6.1.2 具有互感的电感的伏安特性
 - 6.1.3 具有互感的电感元件的串并联
- 6.2 互感耦合电路分析
 - （运用电路定理，分析计算包含互感线圈的电路的参数）
- 6.3 变压器
 - 6.3.1 变压器的原理和结构
 - 6.3.2 包含变压器的电路的分析计算（只考虑理想变压器）

Magnetically Coupled Circuit Chapter 13

13.1 What is a transformer?

13.2 Mutual Inductance

13.3 Energy in a Coupled Circuit

13.4 Linear Transformers

13.5 Ideal Transformers



13.6 Applications

13.1 What is a transformer 变压器?

- It is an electrical device designed on the basis of the concept of magnetic coupling 基于磁耦合原理的电气元件
- It uses magnetically coupled coils to transfer energy from one circuit to another 利用磁耦合线圈在电路间传输能量
- It is the key circuit elements for stepping up or stepping down **ac** voltages or currents, impedance matching, isolation, etc. 主要应用: 交流电压电流的升高或降低、阻抗匹配、隔离

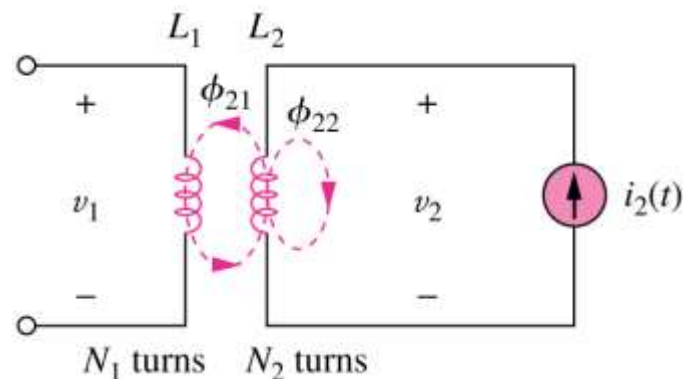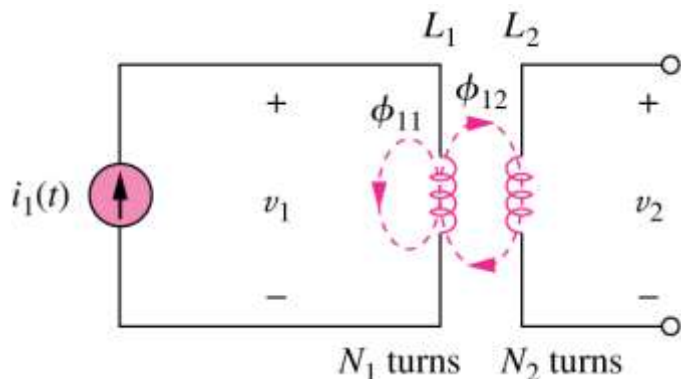13.2 Mutual Inductance 互感

- It is the ability of one inductor to induce a voltage across a neighboring inductor, measured in henrys (H). 互感: 电感对临近电感产生感应电压降的能力; 自感: 相应的, 电感自身的电感量就称为自感;



只有变化的
电流才能产
生互感电压

$$v_2 = M_{21} \frac{di_1}{dt}$$

注意M的下标顺序

$$M_{12} = M_{21} = M$$

$$v_1 = M_{12} \frac{di_2}{dt}$$

The open-circuit mutual
voltage across coil 2


线圈1上的电流变化, 在线
圈2上所产生的开路电压

The open-circuit mutual
voltage across coil 1

线圈2上的电流变化, 在线
圈1上所产生的开路电压

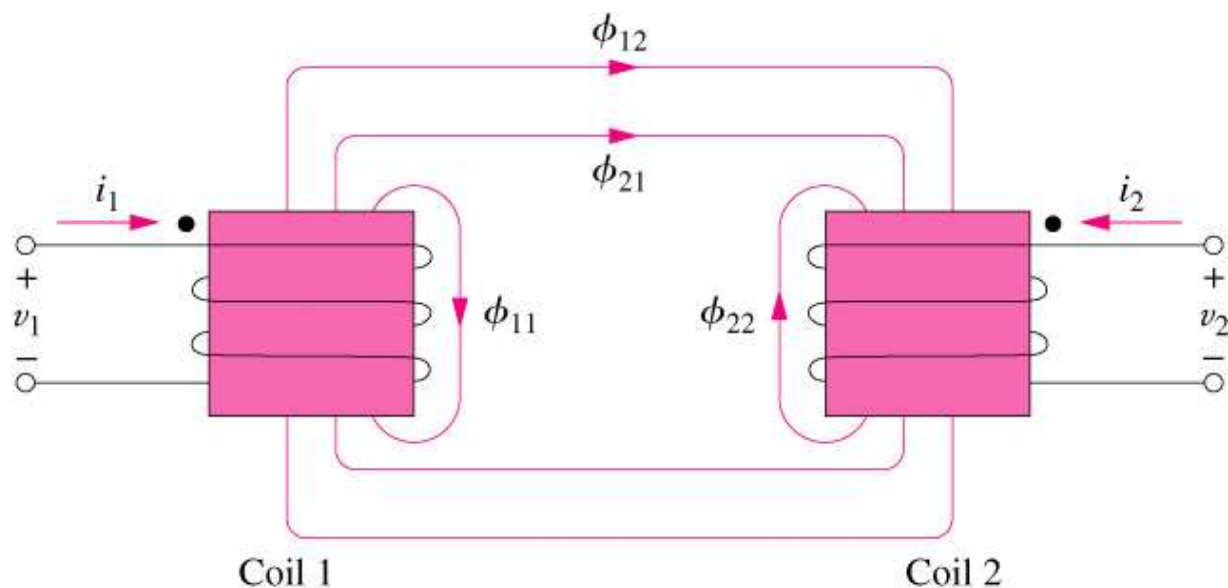
13.2 Mutual Inductance

- If a current enters the dotted terminal of one coil, the reference polarity of the mutual voltage in the second coil is positive at the dotted terminal of the second coil.
- 同名端（一对同标记端）：如果电流从某一线圈的标记端流入，那么其在另一线圈所产生的感应电压，正极在相应的标记端；




为何需要同名端：因为线圈可以顺时针绕，也可以逆时针绕


Illustration of the **dot convention**.

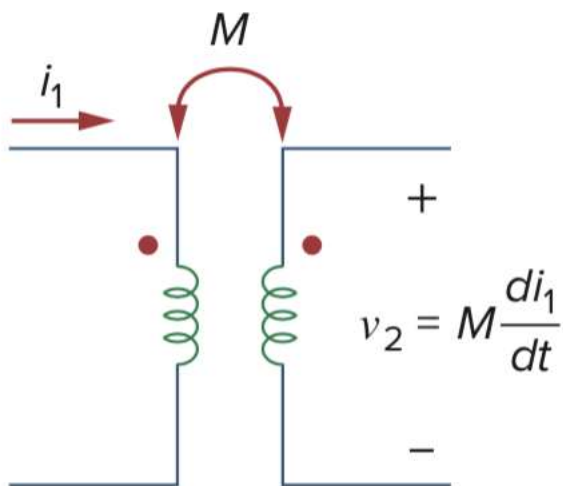


(a)

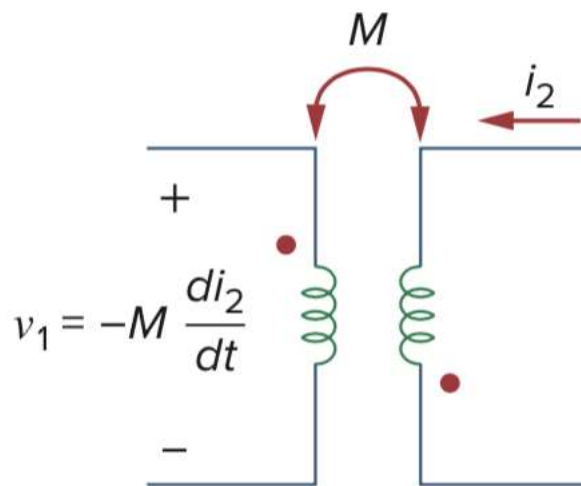

(c)

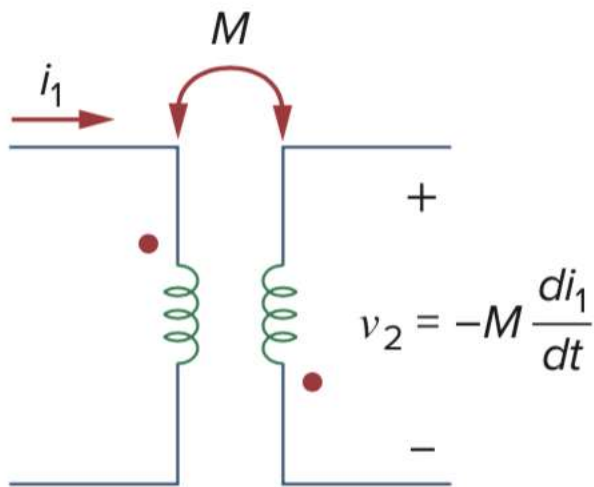

(b)

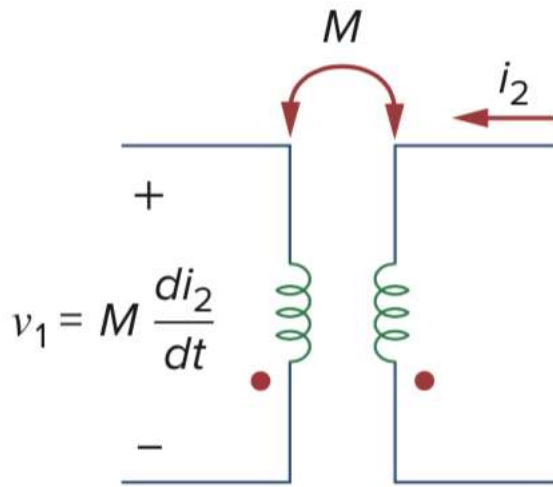


(d)


注意：未标红点的一对端点，也可以看作是一对同名端

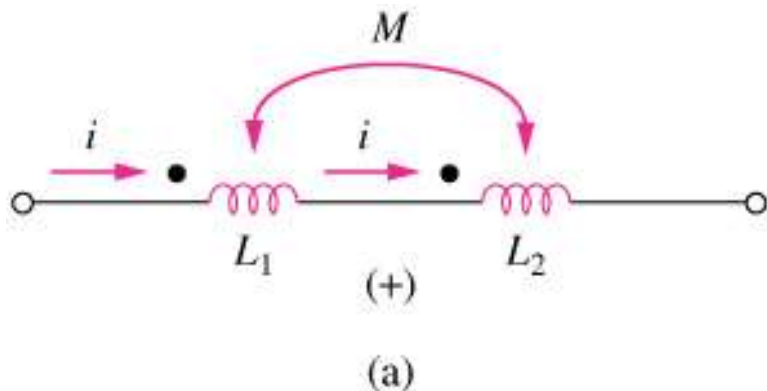13.2 Mutual Inductance

Dot convention for coils in series; the sign indicates the polarity of the mutual voltage; (a) series-aiding connection, (b) series-opposing connection.


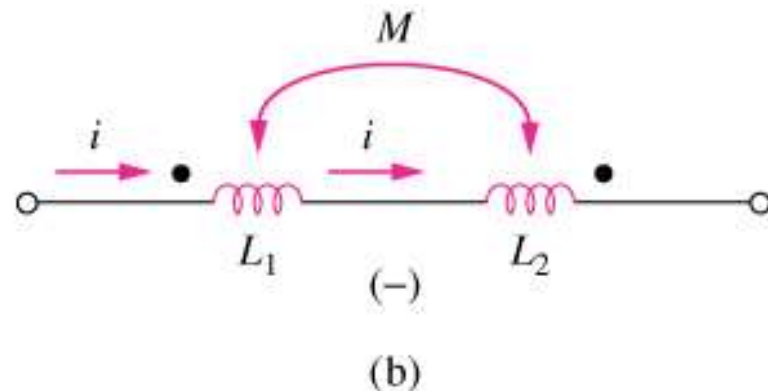
$$L = L_1 + L_2 + 2M \quad (\text{Series-aiding connection})$$




$$L = L_1 + L_2 - 2M \quad (\text{Series-opposing connection})$$


同向串联: 电流都从标记端流入，
感应电压与自身电压相加 → **电感加强**

反向串联: 电流从某一标记端流入，
从另一标记端流出，感应电压与自
身电压相减 → **电感减弱**

13.2 Mutual Inductance

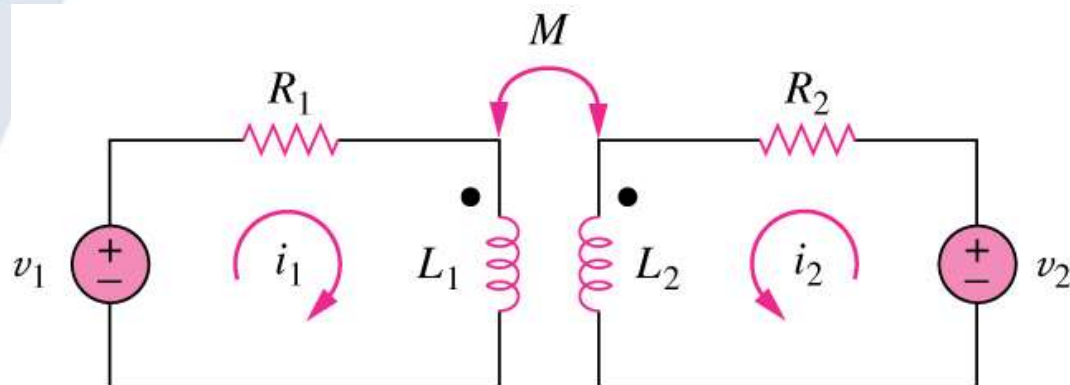

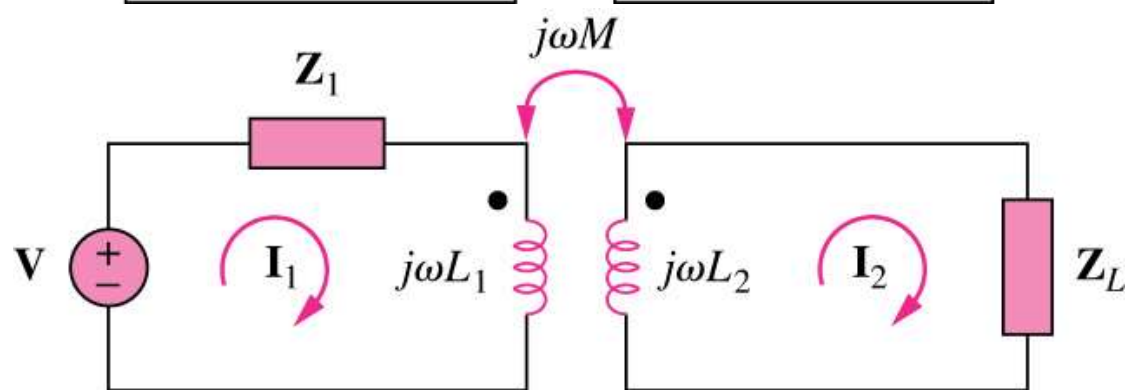Time-domain analysis of a circuit containing coupled coils.



Frequency-domain analysis of a circuit containing coupled coils

等效电路:

电流从标记端**流入**→ 在另一侧相应的标记端**同向串联**感应电压源（标红点是一对同名端，未标红点的也是一对同名端）

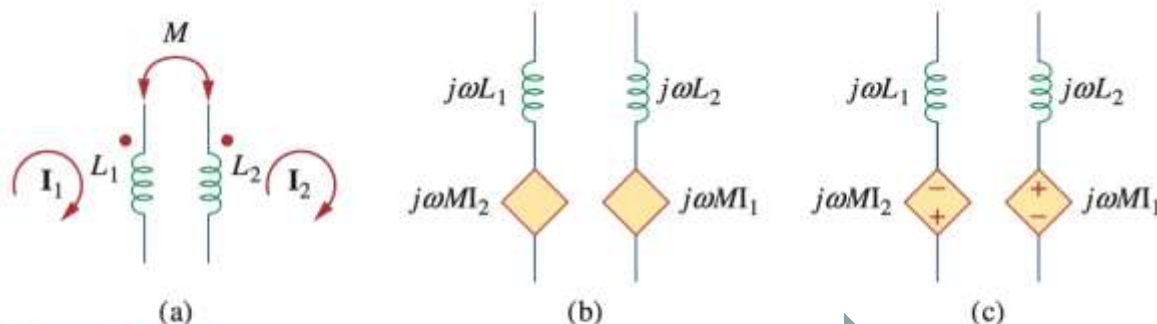




Figure 13.8

Model that makes analysis of mutually coupled easier to solve.

去耦

Calculate the phasor currents \mathbf{I}_1 and \mathbf{I}_2 in the circuit of Fig. 13.9.

Example 13.1

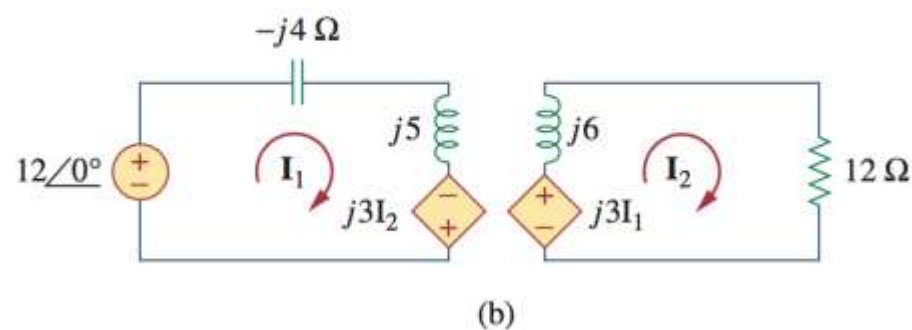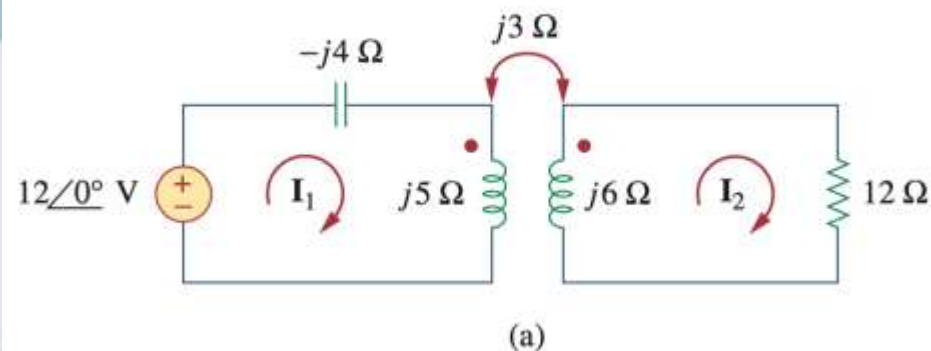

For loop 1, KVL gives

$$-12 + (-j4 + j5)\mathbf{I}_1 - j3\mathbf{I}_2 = 0$$

For loop 2, KVL gives

$$-j3\mathbf{I}_1 + (12 + j6)\mathbf{I}_2 = 0$$

注意: \mathbf{I}_1 和 \mathbf{I}_2 不是相邻网孔



$$\mathbf{I}_2 = \frac{12}{4 - j} = 2.91 \angle 14.04^\circ \text{ A}$$

$$\begin{aligned} \mathbf{I}_1 &= (2 - j4)\mathbf{I}_2 = (4.472 \angle -63.43^\circ)(2.91 \angle 14.04^\circ) \\ &= 13.01 \angle -49.39^\circ \text{ A} \end{aligned}$$

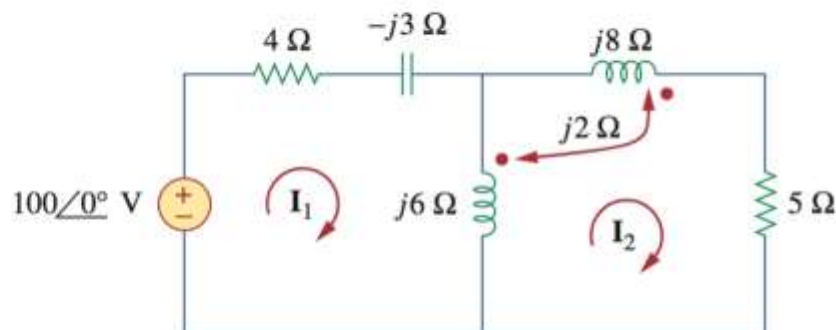
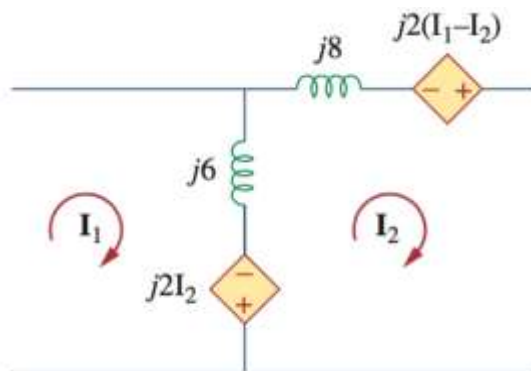


Figure 13.11
For Example 13.2.


先分析流过两个电感的电流分别是多少

$$-100 + \mathbf{I}_1(4 - j3 + j6) - j6\mathbf{I}_2 - j2\mathbf{I}_2 = 0$$

$$0 = -2j\mathbf{I}_1 - j6\mathbf{I}_1 + (j6 + j8 + j2 \times 2 + 5)\mathbf{I}_2$$

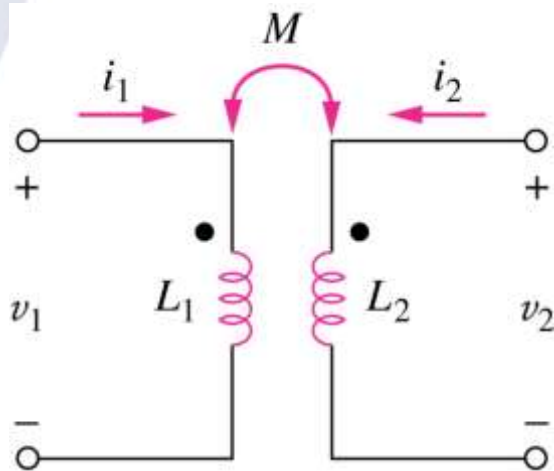13.3 Energy in a Coupled Circuit

- The coupling coefficient, k , is a measure of the magnetic coupling between two coils; $0 \leq k \leq 1$. 磁耦合的程度，用耦合系数 k 表示



$$k = \frac{M}{\sqrt{L_1 L_2}}$$

$$M = k \sqrt{L_1 L_2}$$

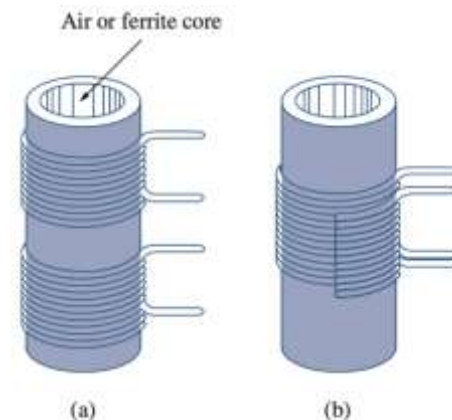


Figure 13.15
Windings: (a) loosely coupled, (b) tightly coupled; cutaway view demonstrates both windings.

- The instantaneous energy stored in the circuit is given by 互感线圈的总储能（瞬时值）

$$w = \frac{1}{2} L_1 i_1^2 + \frac{1}{2} L_2 i_2^2 \pm M i_1 i_2$$

电流都从同名端流入（或流出），则为“+”；一进一出则为“-”；

Example 13.3

Consider the circuit in Fig. 13.16. Determine the coupling coefficient. Calculate the energy stored in the coupled inductors at time $t = 1$ s if $v = 60 \cos(4t + 30^\circ)$ V.

13


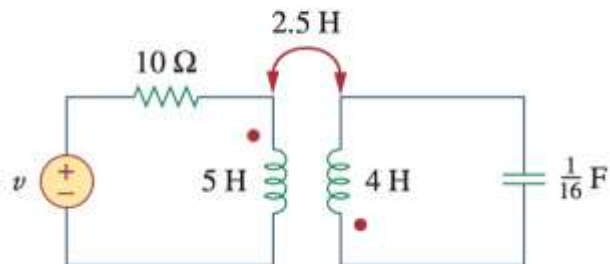


Figure 13.16

Solution:

The coupling coefficient is
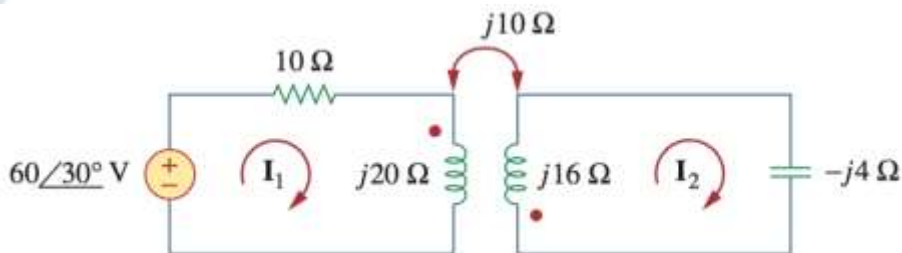
$$k = \frac{M}{\sqrt{L_1 L_2}} = \frac{2.5}{\sqrt{20}} = 0.56$$



$$60 \cos(4t + 30^\circ) \Rightarrow 60 \angle 30^\circ, \quad \omega = 4 \text{ rad/s}$$

$$5 \text{ H} \Rightarrow j\omega L_1 = j20 \Omega$$

$$2.5 \text{ H} \Rightarrow j\omega M = j10 \Omega$$

$$4 \text{ H} \Rightarrow j\omega L_2 = j16 \Omega$$

$$\frac{1}{16} \text{ F} \Rightarrow \frac{1}{j\omega C} = -j4 \Omega$$

For mesh 1,

$$(10 + j20)\mathbf{I}_1 + j10\mathbf{I}_2 = 60 \angle 30^\circ$$

$$w = \frac{1}{2}L_1 i_1^2 + \frac{1}{2}L_2 i_2^2 + M i_1 i_2$$

$$= \frac{1}{2}(5)(-3.389)^2 + \frac{1}{2}(4)(2.824)^2 + 2.5(-3.389)(2.824) = 20.73 \text{ J}$$

For mesh 2,


$$j10\mathbf{I}_1 + (j16 - j4)\mathbf{I}_2 = 0$$

$$\mathbf{I}_2 = 3.254 \angle 160.6^\circ \text{ A}$$

$$\mathbf{I}_1 = -1.2\mathbf{I}_2 = 3.905 \angle -19.4^\circ \text{ A}$$

$$i_1 = 3.905 \cos(4t - 19.4^\circ)$$


$$i_2 = 3.254 \cos(4t + 160.6^\circ)$$

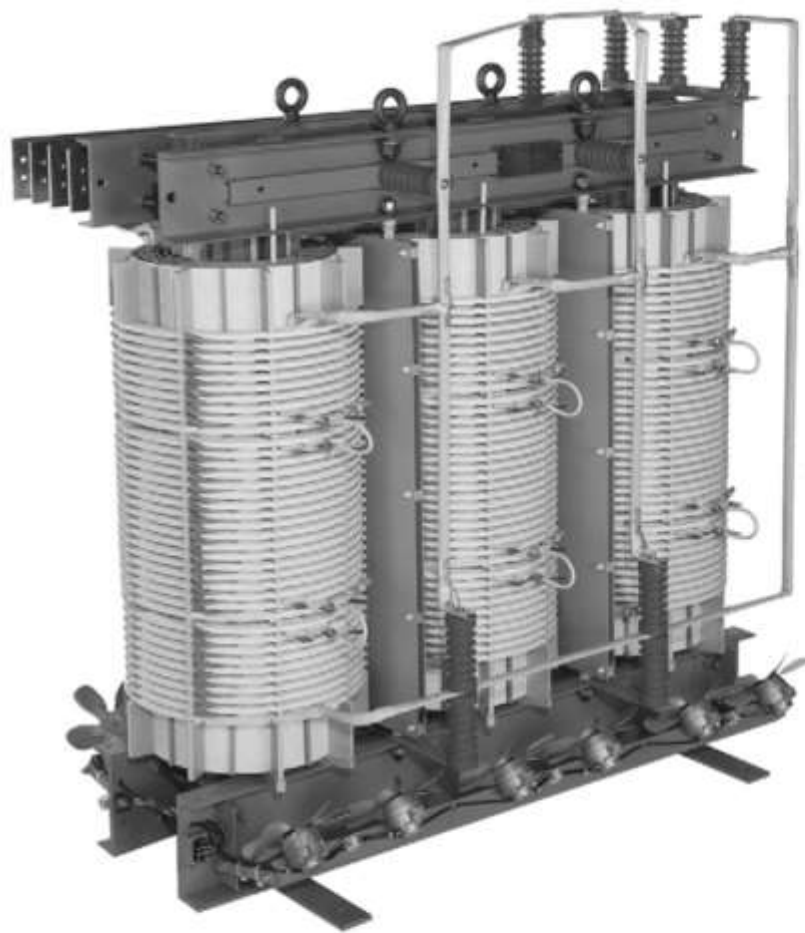

(a)

**Figure 13.20**


Different types of transformers: (a) copper wound dry power transformer
 Courtesy of: (a) Electric Service Co., (b) Jensen Transformers.

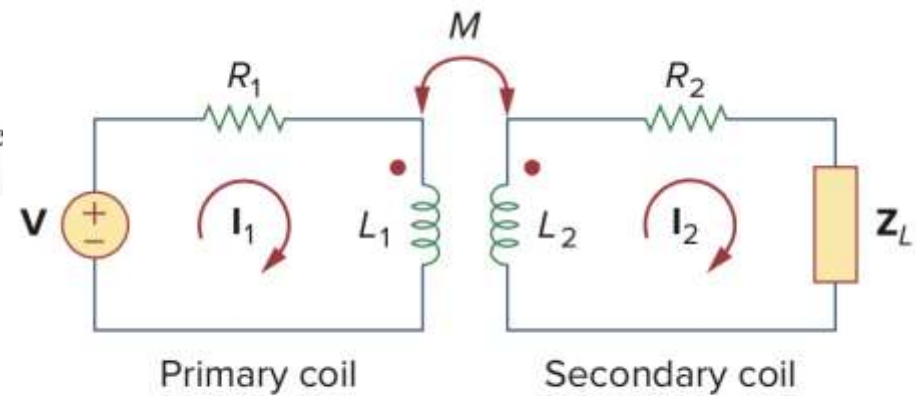**Figure 13.19**

A linear transformer.

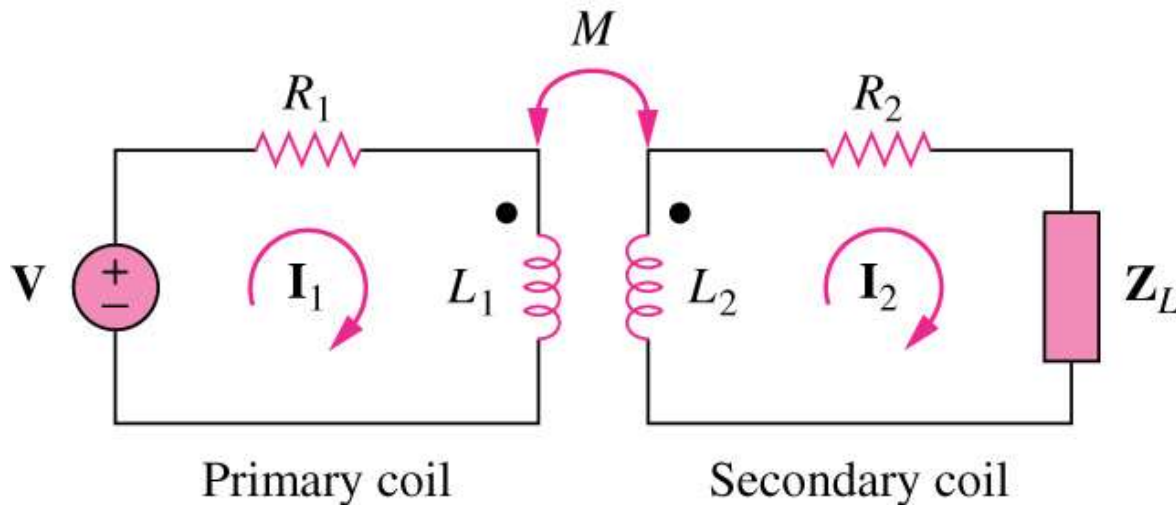13.4 Linear Transformer 线性变压器

- It is generally a four-terminal device comprising two (or more) magnetically coupled coils



线性变压器：线圈绕在“磁线性材料”上，该材料的磁导率为常数，如空气、塑料、电工胶木等

$$\begin{aligned} V &= (R_1 + j\omega L_1)I_1 - j\omega M I_2 \\ 0 &= -j\omega M I_1 + (R_2 + j\omega L_2 + Z_L)I_2 \end{aligned}$$


同名端标记不影响结果, $M^2 = (-M)^2$
相当于将 Z_L 折算到输入端的阻抗

$$\Rightarrow Z_{in} = \frac{V}{I_1} = R_1 + j\omega L_1 + Z_R, Z_R = \frac{\omega^2 M^2}{R_2 + j\omega L_2 + Z_L} \text{ is reflected impedance}$$



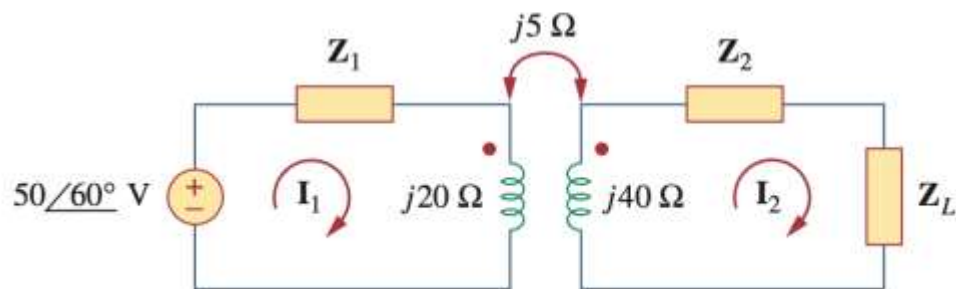Example 13.4

In the circuit of Fig. 13.24, calculate the input impedance and current \mathbf{I}_1 . Take $\mathbf{Z}_1 = 60 - j100 \Omega$, $\mathbf{Z}_2 = 30 + j40 \Omega$, and $\mathbf{Z}_L = 80 + j60 \Omega$.



$$\begin{aligned}\mathbf{Z}_{\text{in}} &= \mathbf{Z}_1 + j20 + \frac{(5)^2}{j40 + \mathbf{Z}_2 + \mathbf{Z}_L} \\ &= 60 - j100 + j20 + \frac{25}{110 + j140} \\ &= 60 - j80 + 0.14 \angle -51.84^\circ \\ &= 60.09 - j80.11 = 100.14 \angle -53.1^\circ \Omega\end{aligned}$$

线性变压器的去耦合等效法

耦合线性变压器电路
→ 非耦合电感电路

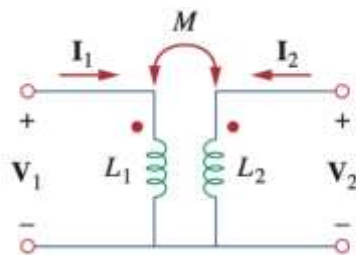


Figure 13.21

Determining the equivalent circuit of a linear transformer.

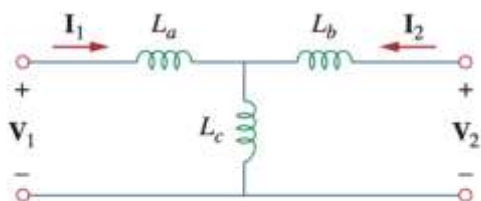


Figure 13.22

An equivalent T circuit.

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} j\omega(L_a + L_c) & j\omega L_c \\ j\omega L_c & j\omega(L_b + L_c) \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$$L_a = L_1 - M, \quad L_b = L_2 - M, \quad L_c = M$$

注意同名端标记，若不在同一侧，则 $M \rightarrow -M$

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} j\omega L_1 & j\omega M \\ j\omega M & j\omega L_2 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} \frac{L_2}{j\omega(L_1 L_2 - M^2)} & \frac{-M}{j\omega(L_1 L_2 - M^2)} \\ \frac{-M}{j\omega(L_1 L_2 - M^2)} & \frac{L_1}{j\omega(L_1 L_2 - M^2)} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

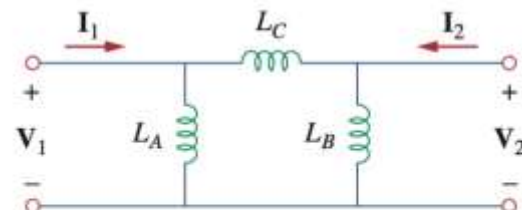


Figure 13.23

An equivalent Π circuit.

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} \frac{1}{j\omega L_A} + \frac{1}{j\omega L_C} & \frac{-1}{j\omega L_C} \\ \frac{-1}{j\omega L_C} & \frac{1}{j\omega L_B} + \frac{1}{j\omega L_C} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

$$L_A = \frac{L_1 L_2 - M^2}{L_2 - M}, \quad L_B = \frac{L_1 L_2 - M^2}{L_1 - M}$$

$$L_C = \frac{L_1 L_2 - M^2}{M}$$

Determine the T-equivalent circuit of the linear transformer in Fig. 13.26(a).

Example 13.5

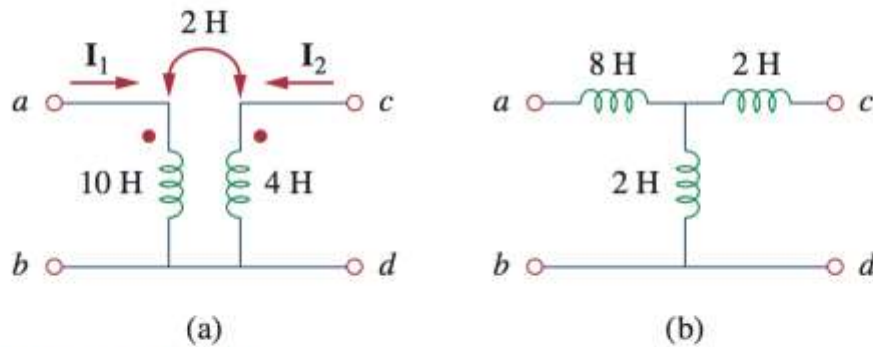


Figure 13.26

For Example 13.5: (a) a linear transformer, (b) its T-equivalent circuit.

Example 13.6

Solve for \mathbf{I}_1 , \mathbf{I}_2 , and \mathbf{V}_o in Fig. 13.27 (the same circuit as for Practice Prob. 13.1) using the T-equivalent circuit for the linear transformer.

同名端标记不在同一侧, $M \rightarrow -M$

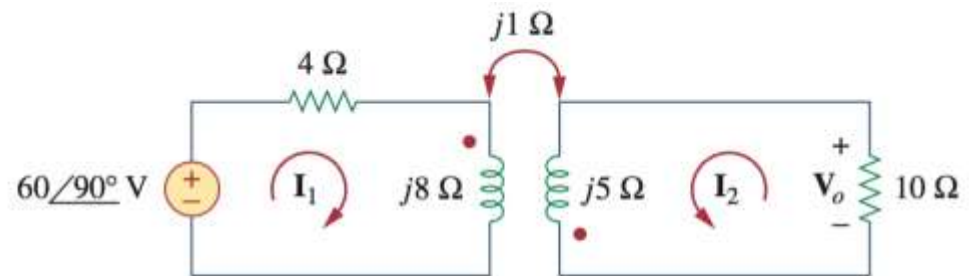
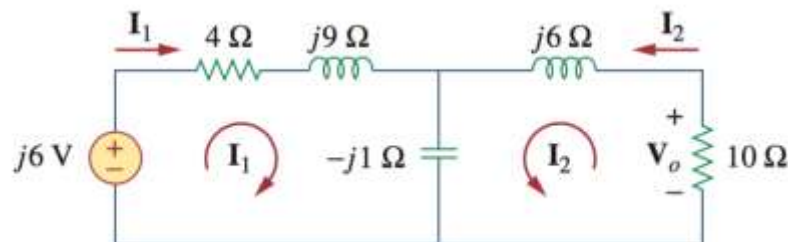
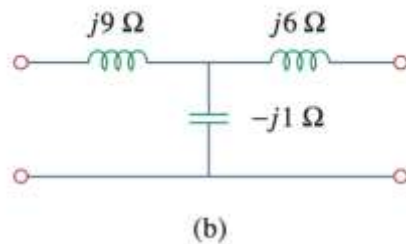
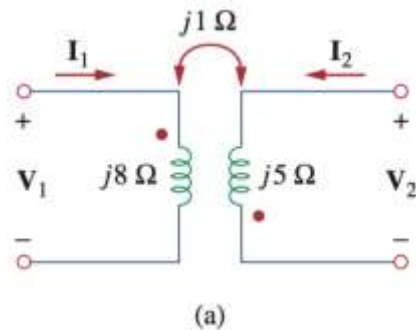


Figure 13.27

For Example 13.6.

$$j6 = \mathbf{I}_1(4 + j9 - j1) + \mathbf{I}_2(-j1)$$

$$0 = \mathbf{I}_1(-j1) + \mathbf{I}_2(10 + j6 - j1)$$


$$\mathbf{I}_2 = \frac{j6}{100} = j0.06 = 0.06\angle 90^\circ \text{ A}$$

$$\mathbf{I}_1 = (5 - j10)j0.06 = 0.6 + j0.3 \text{ A}$$

$$\mathbf{V}_o = -10\mathbf{I}_2 = -j0.6 = 0.6\angle -90^\circ \text{ V}$$

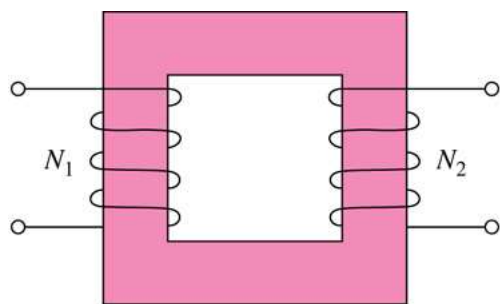
13.5 Ideal Transformer理想变压器

- An ideal transformer is a unity-coupled, lossless transformer in which the primary and secondary coils have infinite self-inductances.
- 理想变压器：耦合系数 $k = 1$ 、无耗、自感 L 无穷大；




初级回路 (a) 次级回路

||表示磁芯
 N 为线圈匝数

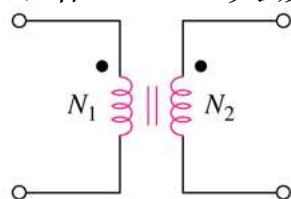

(b)

(a) Ideal Transformer
(b) Circuit symbol

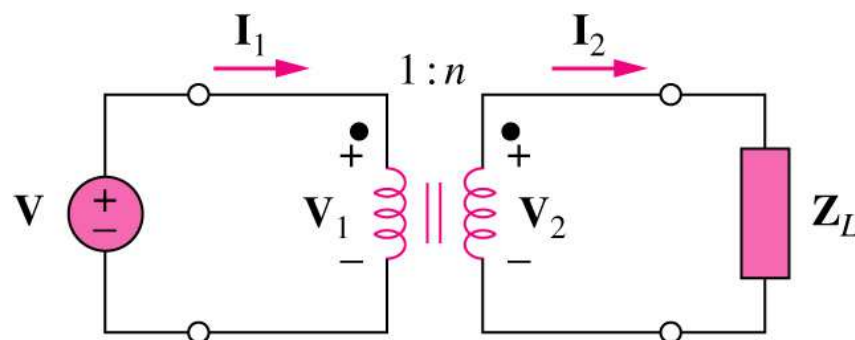

$$\frac{V_2}{V_1} = \frac{N_2}{N_1} = n$$


(13.52)

理想变压器的“电压电流约束关系”

$$\frac{I_2}{I_1} = \frac{N_1}{N_2} = \frac{1}{n}$$

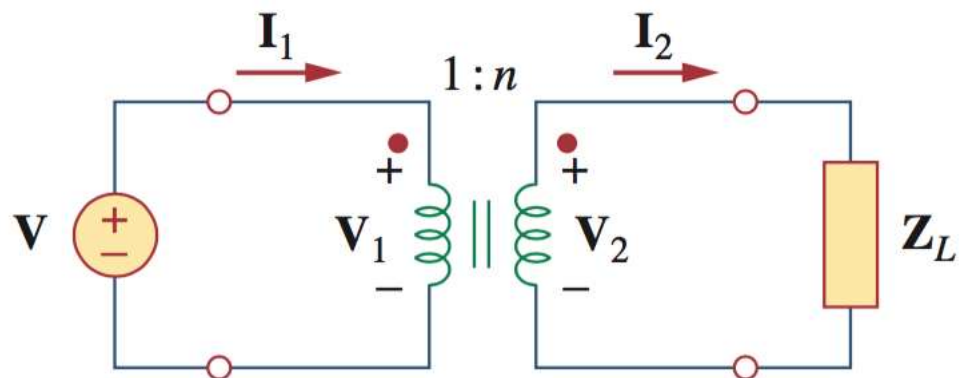(13.55)

$V_2 > V_1 \rightarrow$ **step-up transformer** 升压
 $V_2 < V_1 \rightarrow$ **step-down transformer** 降压




理想变压器记住此图示


电压“+”在同名端（比值为正）

电流从同名端一进一出（比值为正）

与此相反：比值为负

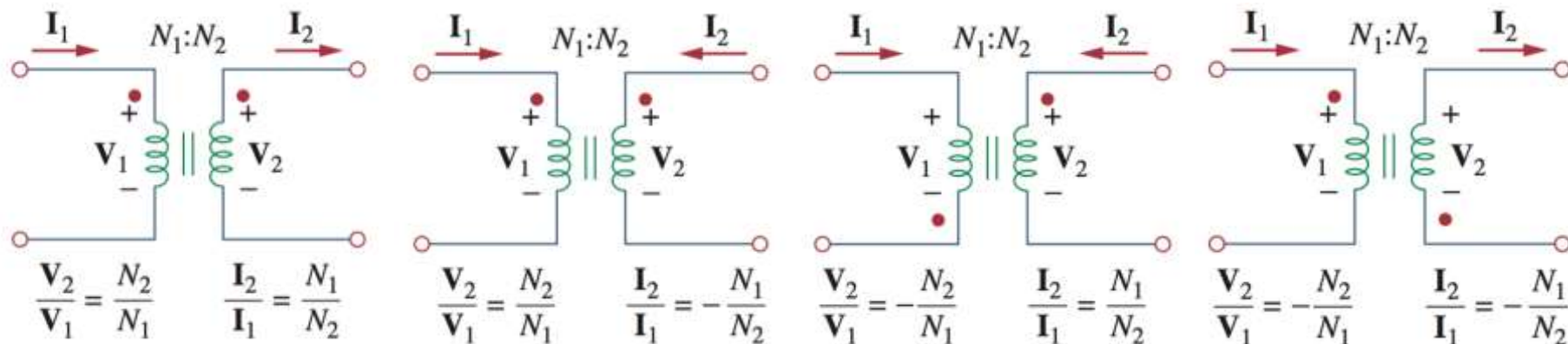1. If V_1 and V_2 are *both* positive or both negative at the dotted terminals, use $+n$ in Eq. (13.52). Otherwise, use $-n$.
2. If I_1 and I_2 *both* enter into or both leave the dotted terminals, use $-n$ in Eq. (13.55). Otherwise, use $+n$.



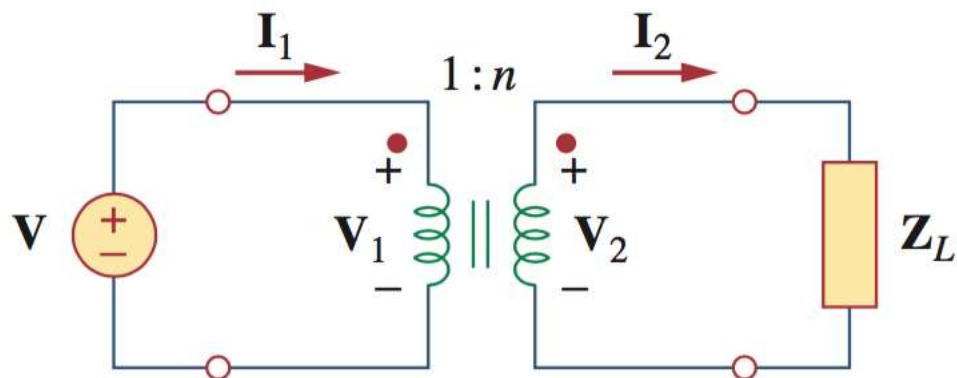

The complex power in the primary winding is

$$S_1 = \mathbf{V}_1 \mathbf{I}_1^* = \frac{\mathbf{V}_2}{n} (n \mathbf{I}_2)^* = \mathbf{V}_2 \mathbf{I}_2^* = S_2$$


$$\mathbf{Z}_{\text{in}} = \frac{\mathbf{V}_1}{\mathbf{I}_1} = \frac{1}{n^2} \frac{\mathbf{V}_2}{\mathbf{I}_2}$$



$$\mathbf{Z}_{\text{in}} = \frac{\mathbf{Z}_L}{n^2}$$

可实现阻抗变换

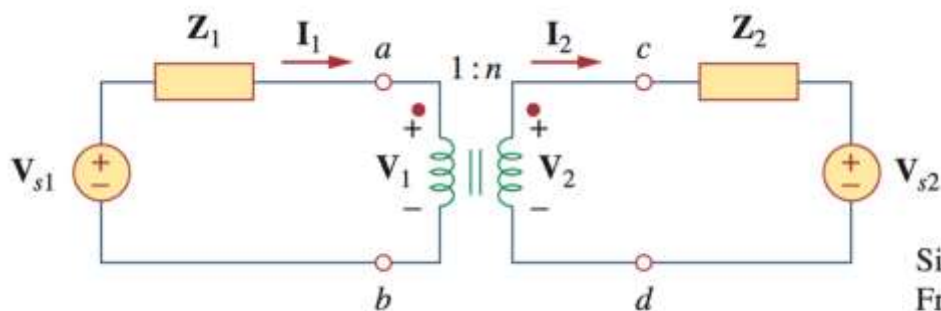- 若理想变压器的初级回路和次级回路没有额外的连接，那么，次级回路可以折算到初级回路；初级回路也可以折算到次级回路




Since terminals a - b are open, $I_1 = 0 = I_2$ so that $V_2 = V_{s2}$. Hence, From Eq. (13.56),

$$V_{Th} = V_1 = \frac{V_2}{n} = \frac{V_{s2}}{n} \quad (13.61)$$


To get Z_{Th} , we remove the voltage source in the secondary winding and insert a unit source at terminals a - b , as in Fig. 13.34(b). From Eqs. (13.56) and (13.57), $I_1 = nI_2$ and $V_1 = V_2/n$, so that


$$Z_{Th} = \frac{V_1}{I_1} = \frac{V_2/n}{nI_2} = \frac{Z_2}{n^2}, \quad V_2 = Z_2 I_2 \quad (13.62)$$

对ab右侧电路
做戴维南等效

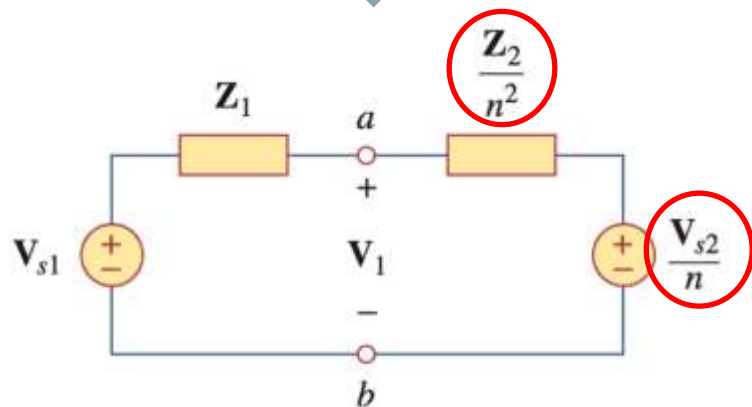


电压按比例折算；
阻抗按比例平方折算

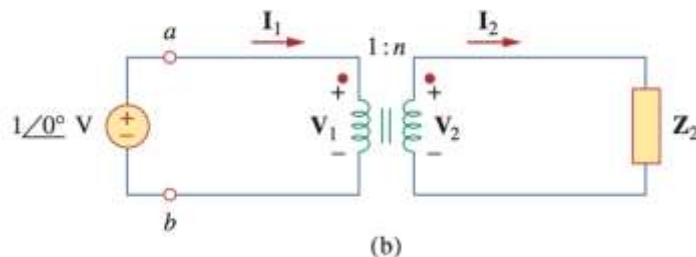

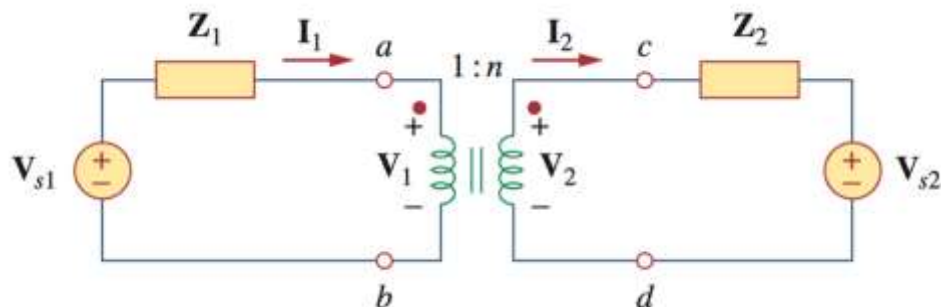

对ab左侧电路
做戴维南等效

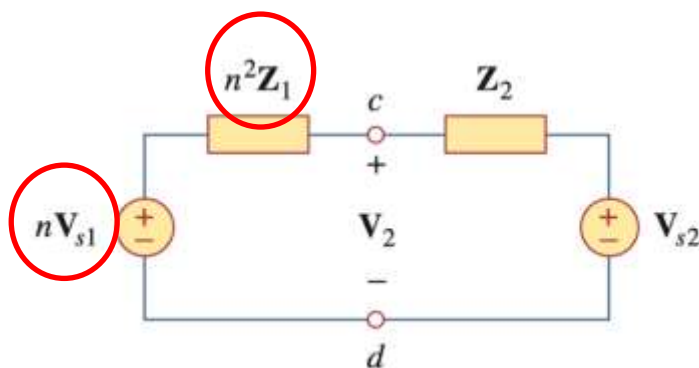

电压按比例折算；
阻抗按比例平方折算



Example 13.7

- 电压标称：初级/次级
- kVA \rightarrow 视在功率

An ideal transformer is rated at 2400/120 V, 9.6 kVA, and has 50 turns on the secondary side. Calculate: (a) the turns ratio, (b) the number of turns on the primary side, and (c) the current ratings for the primary and secondary windings.

Solution:

(a) This is a step-down transformer, since $V_1 = 2,400 \text{ V} > V_2 = 120 \text{ V}$.

$$n = \frac{V_2}{V_1} = \frac{120}{2,400} = 0.05$$

(b)

$$n = \frac{N_2}{N_1} \Rightarrow 0.05 = \frac{50}{N_1}$$

or

$$N_1 = \frac{50}{0.05} = 1,000 \text{ turns}$$


(c) $S = V_1 I_1 = V_2 I_2 = 9.6 \text{ kVA}$. Hence,

$$I_1 = \frac{9,600}{V_1} = \frac{9,600}{2,400} = 4 \text{ A}$$

$$I_2 = \frac{9,600}{V_2} = \frac{9,600}{120} = 80 \text{ A} \quad \text{or} \quad I_2 = \frac{I_1}{n} = \frac{4}{0.05} = 80 \text{ A}$$

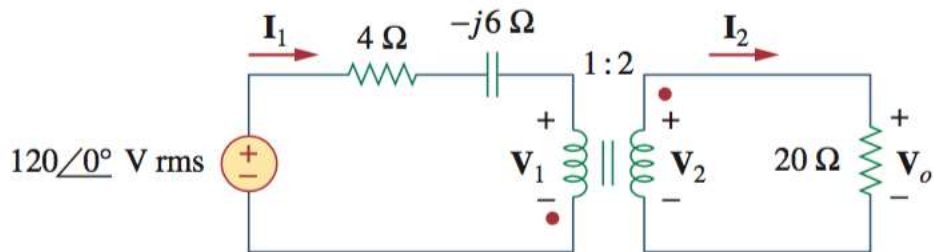Example 13.8

For the ideal transformer circuit of Fig. 13.37, find: (a) the source current \mathbf{I}_1 , (b) the output voltage \mathbf{V}_o , and (c) the complex power supplied by the source.



(a) The 20- Ω impedance can be reflected to the primary side and we get

$$\mathbf{Z}_R = \frac{20}{n^2} = \frac{20}{4} = 5 \Omega$$

将次级折算到初级

Thus,

$$\mathbf{Z}_{\text{in}} = 4 - j6 + \mathbf{Z}_R = 9 - j6 = 10.82 \angle -33.69^\circ \Omega$$

$$\mathbf{I}_1 = \frac{120 \angle 0^\circ}{\mathbf{Z}_{\text{in}}} = \frac{120 \angle 0^\circ}{10.82 \angle -33.69^\circ} = 11.09 \angle 33.69^\circ \text{ A}$$

(b) Since both \mathbf{I}_1 and \mathbf{I}_2 leave the dotted terminals,

$$\mathbf{I}_2 = -\frac{1}{n} \mathbf{I}_1 = -5.545 \angle 33.69^\circ \text{ A}$$


$$\mathbf{V}_o = 20 \mathbf{I}_2 = 110.9 \angle 213.69^\circ \text{ V}$$

(c) The complex power supplied is

$$\mathbf{S} = \mathbf{V}_s \mathbf{I}_1^* = (120 \angle 0^\circ)(11.09 \angle -33.69^\circ) = 1,330.8 \angle -33.69^\circ \text{ VA}$$

Calculate the power supplied to the $10\text{-}\Omega$ resistor in the ideal transformer circuit of Fig. 13.39.

Example 13.9

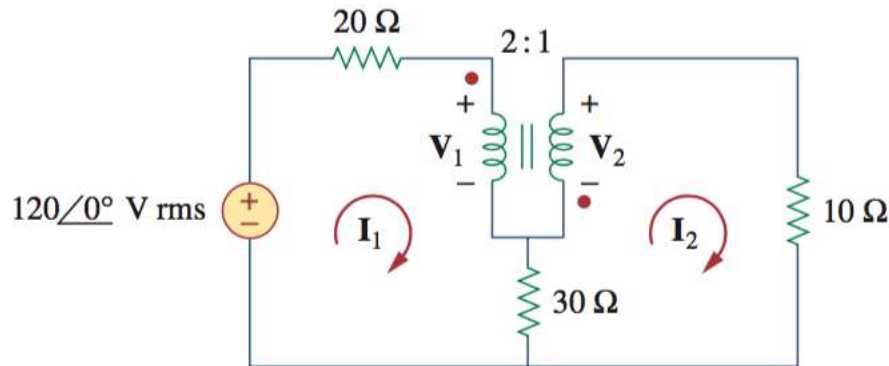

利用理想变压器的“电压电流约束关系”

$$-120 + (20 + 30)\mathbf{I}_1 - 30\mathbf{I}_2 + \mathbf{V}_1 = 0$$

$$-\mathbf{V}_2 + (10 + 30)\mathbf{I}_2 - 30\mathbf{I}_1 = 0$$

$$\mathbf{V}_2 = -\frac{1}{2}\mathbf{V}_1$$

$$\mathbf{I}_2 = -2\mathbf{I}_1$$




$$\mathbf{I}_2 = -\frac{120}{165} = -0.7272 \text{ A}$$

$$P = (-0.7272)^2(10) = 5.3 \text{ W}$$

Ideal Autotransformer 自耦变压器



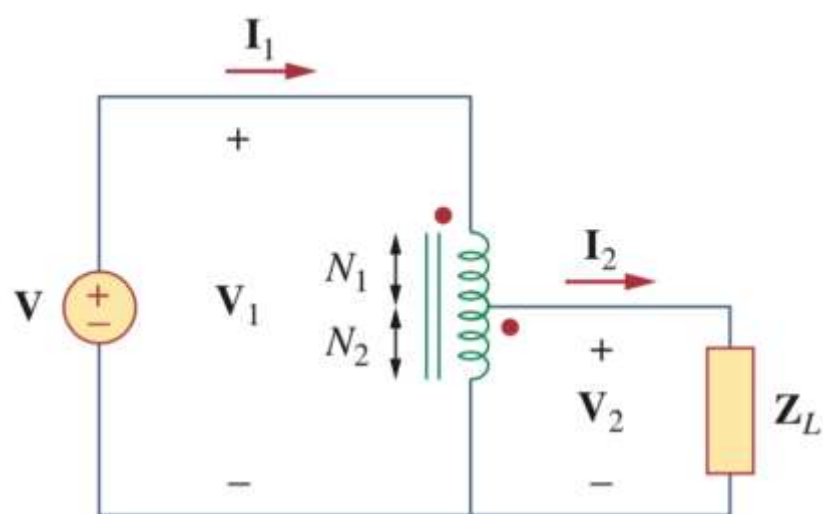
An **autotransformer** is a transformer in which both the primary and the secondary are in a single winding.



(a)

$$\frac{V_1}{V_2} = \frac{N_1 + N_2}{N_2} = 1 + \frac{N_1}{N_2}$$
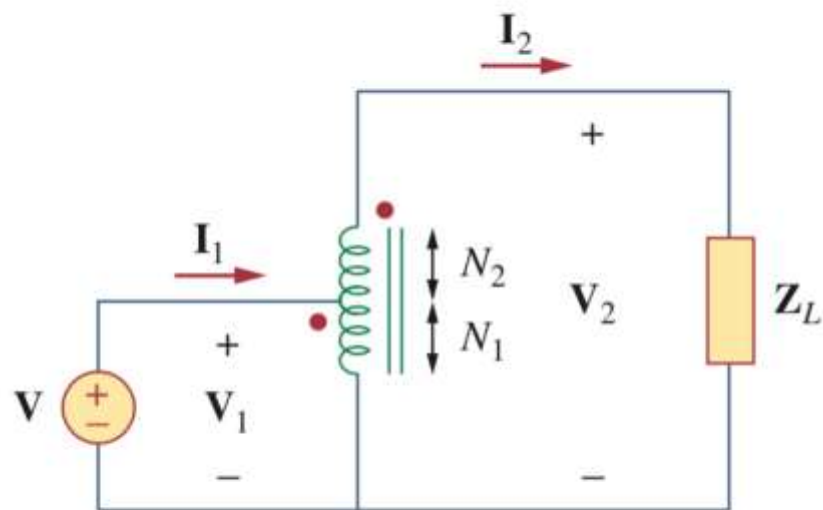
$$\frac{I_1}{I_2} = \frac{N_2}{N_1 + N_2}$$



(b)

Figure 13.42

(a) Step-down autotransformer, (b) step-up autotransformer.



Example 13.11

Refer to the autotransformer circuit in Fig. 13.44. Calculate: (a) \mathbf{I}_1 , \mathbf{I}_2 , and \mathbf{I}_o if $\mathbf{Z}_L = 8 + j6 \Omega$, and (b) the complex power supplied to the load.

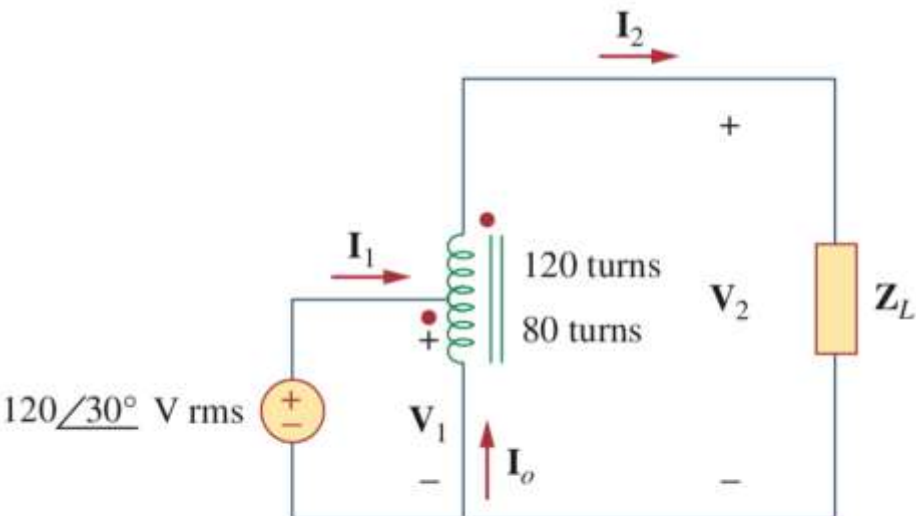


Figure 13.44
For Example 13.11.

$$\frac{\mathbf{V}_1}{\mathbf{V}_2} = \frac{N_1}{N_1 + N_2} = \frac{80}{200}$$

$$\mathbf{V}_2 = \frac{200}{80} \mathbf{V}_1 = \frac{200}{80} (120 \angle 30^\circ) = 300 \angle 30^\circ \text{ V}$$

$$\mathbf{I}_2 = \frac{\mathbf{V}_2}{\mathbf{Z}_L} = \frac{300 \angle 30^\circ}{8 + j6} = \frac{300 \angle 30^\circ}{10 \angle 36.87^\circ} = 30 \angle -6.87^\circ \text{ A}$$

$$\frac{\mathbf{I}_1}{\mathbf{I}_2} = \frac{N_1 + N_2}{N_1} = \frac{200}{80}$$


$$\mathbf{I}_1 = \frac{200}{80} \mathbf{I}_2 = \frac{200}{80} (30 \angle -6.87^\circ) = 75 \angle -6.87^\circ \text{ A}$$

$$\mathbf{I}_o = \mathbf{I}_2 - \mathbf{I}_1 = 30 \angle -6.87^\circ - 75 \angle -6.87^\circ = 45 \angle 173.13^\circ \text{ A}$$

$$\mathbf{S}_2 = \mathbf{V}_2 \mathbf{I}_2^* = |\mathbf{I}_2|^2 \mathbf{Z}_L = (30)^2 (10 \angle 36.87^\circ) = 9 \angle 36.87^\circ \text{ kVA}$$

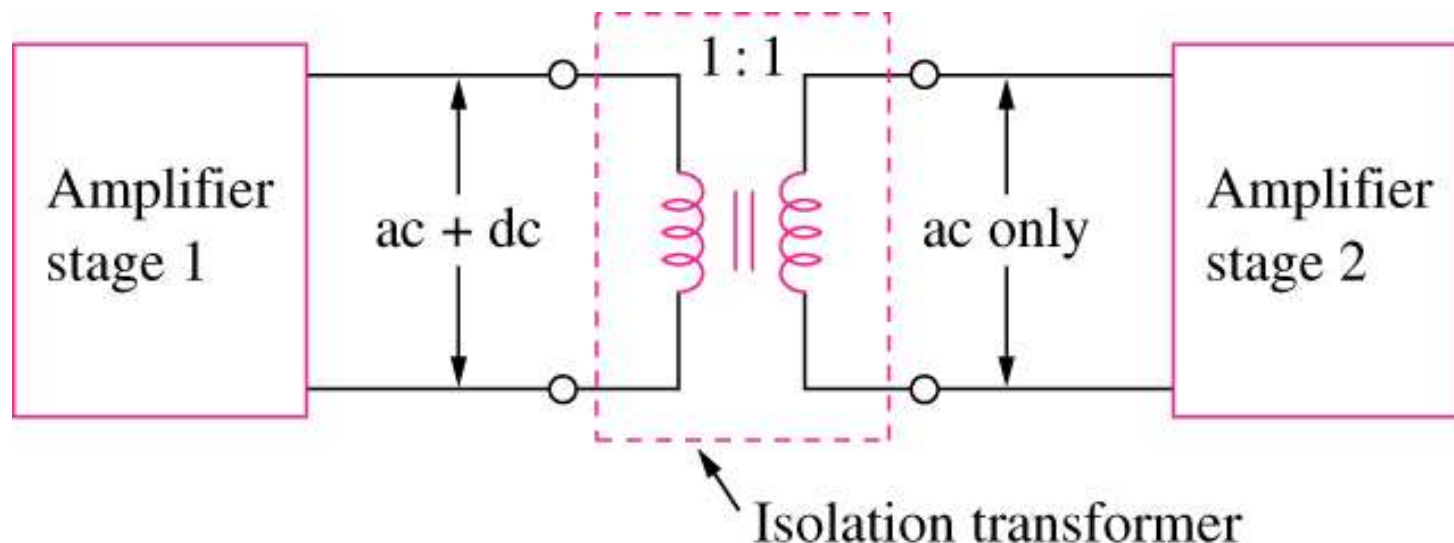13.6 Applications



- Transformer as an Isolation Device to isolate dc between two amplifier stages. 应用之一：隔离直流



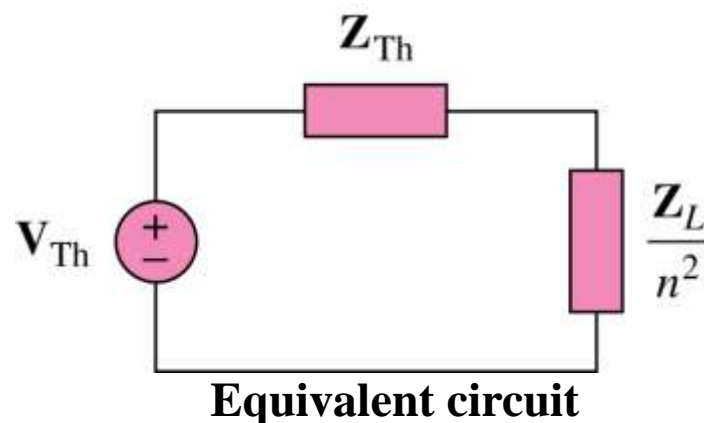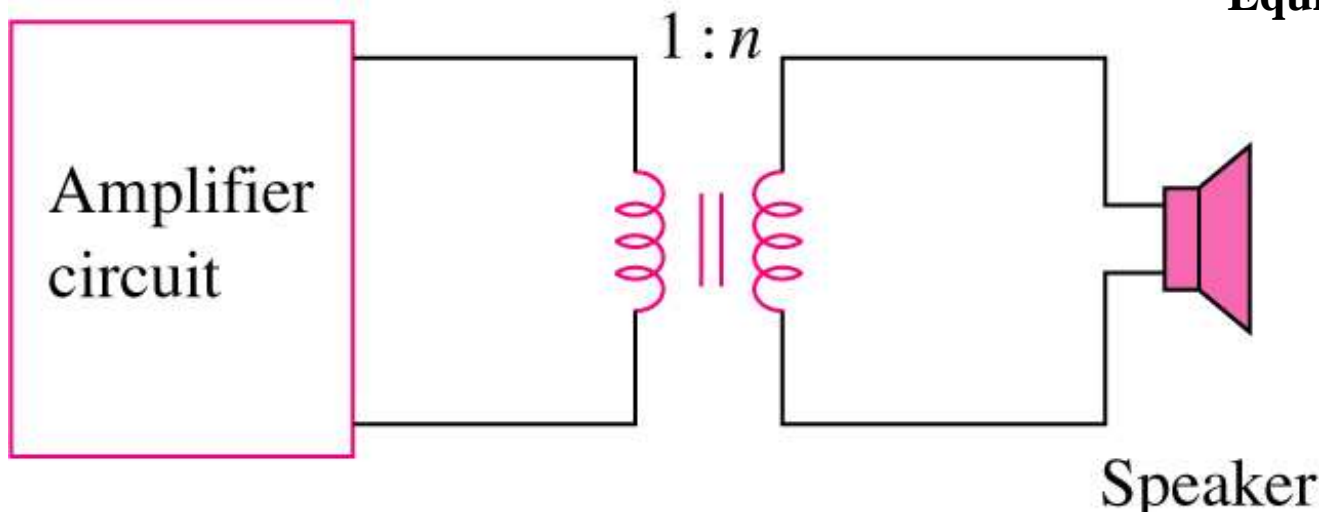13.6 Applications


- Transformer as a Matching Device
应用之二：阻抗匹配

Using an ideal transformer to match the speaker to the amplifier



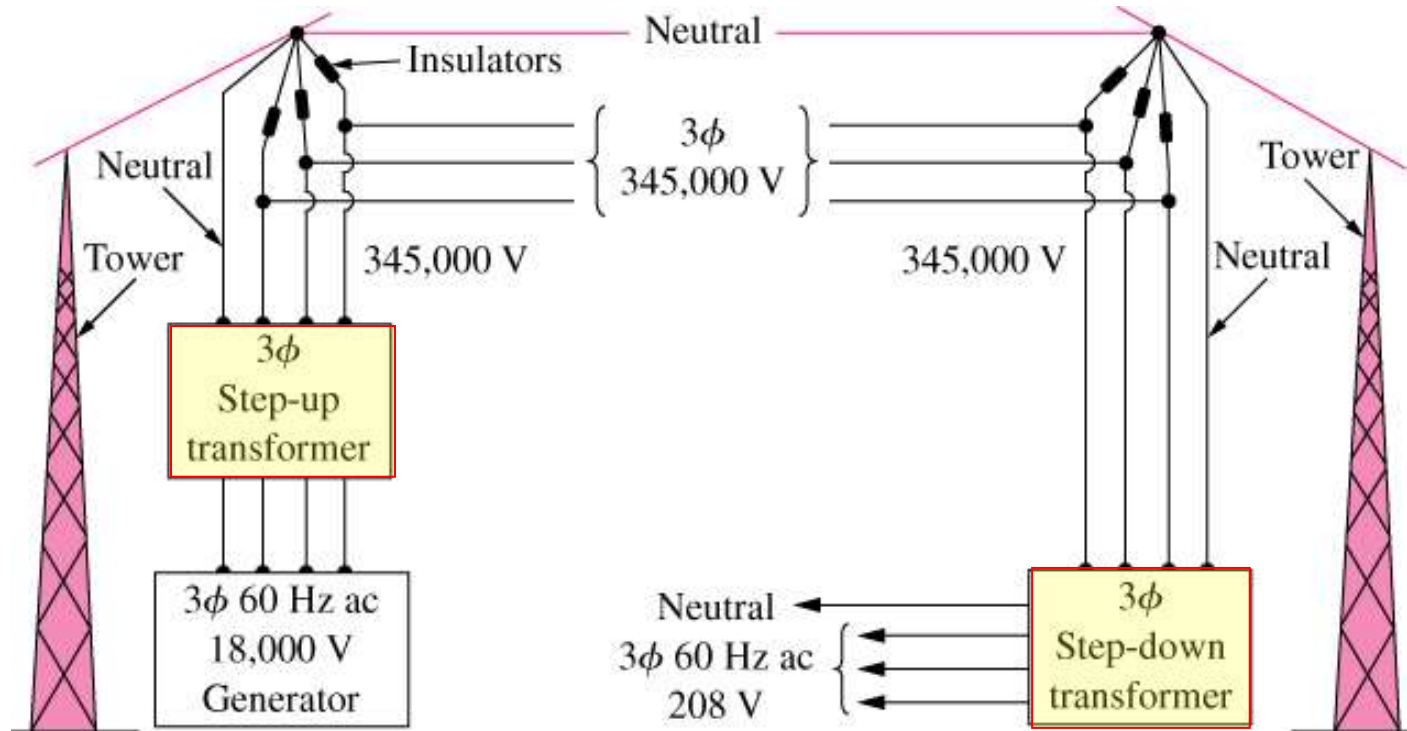13.6 Applications

- A typical power distribution system应用之三：供电系统



小结

- 耦合线圈 → 产生互感


$$v_2 = M_{21} \frac{di_1}{dt}$$

$$v_1 = M_{12} \frac{di_2}{dt}$$

$$M_{12} = M_{21} = M$$

$$\mathbf{V}_2 = j\omega M \mathbf{I}_1$$
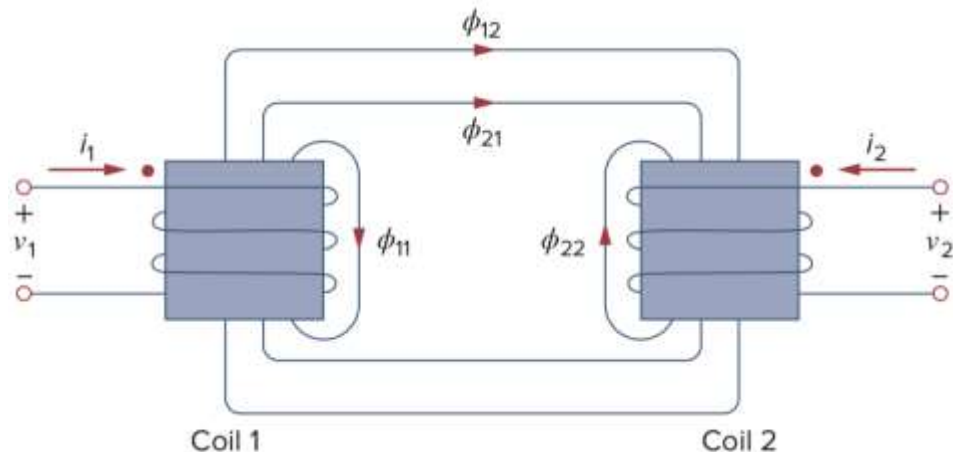
$$\mathbf{V}_1 = j\omega M \mathbf{I}_2$$




- 同名端（一对标记端）


- 标红点的是一对，不标红点的也是一对
- 电流从一个线圈的标记端流入，在另一线圈产生的感应电压的正极在相应的标记端

小结

- 互感线圈的串联: (a) 同向串联; (b) 反向串联

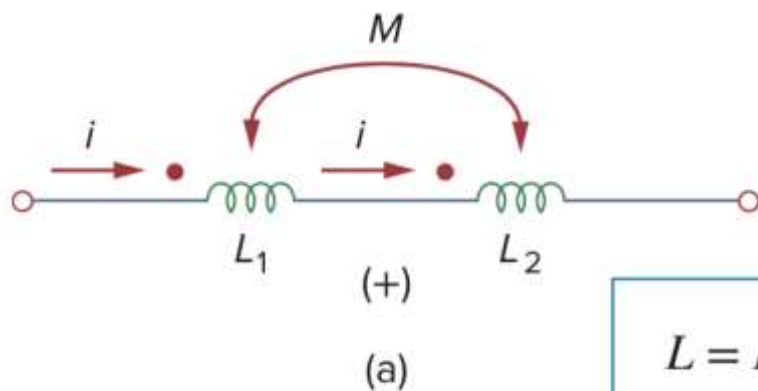
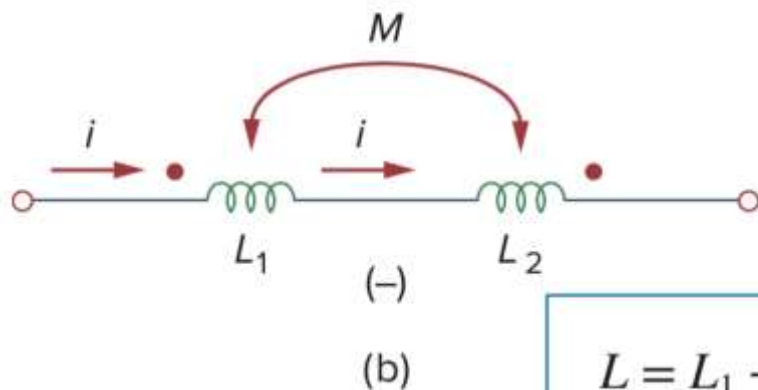
$$L = L_1 + L_2 + 2M \quad (\text{Series-aiding connection})$$



$$L = L_1 + L_2 - 2M \quad (\text{Series-opposing connection})$$

小结

- 含互感线圈的电路分析
 - 电流从标记端流入 \rightarrow 在另一线圈的标记端同向串联感应电压源

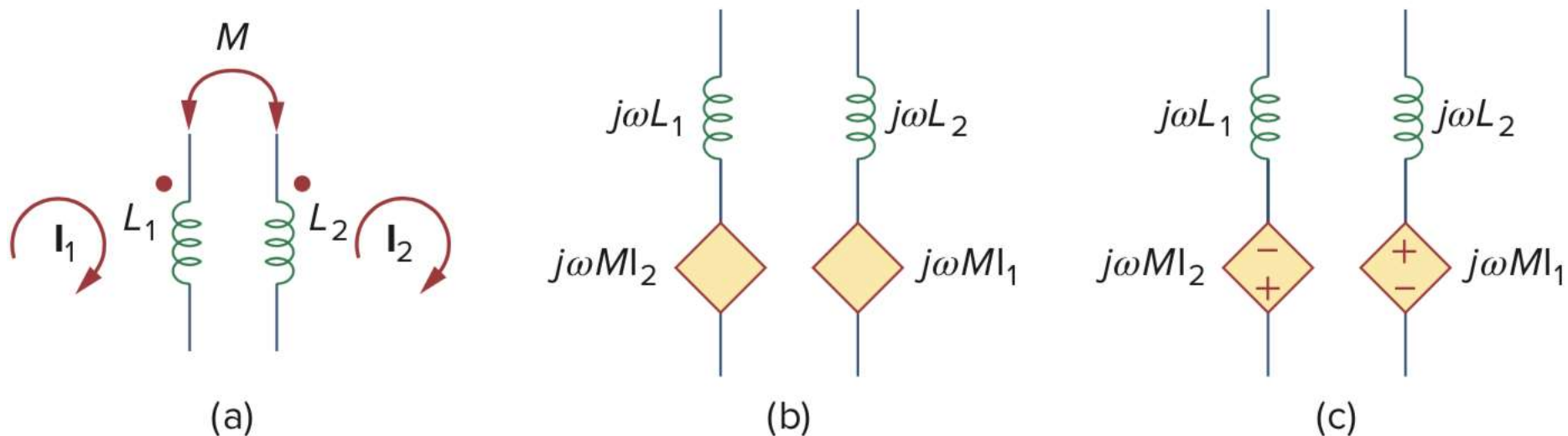


Figure 13.8

Model that makes analysis of mutually coupled easier to solve.

小结

- 磁耦合系数 $k = \frac{M}{\sqrt{L_1 L_2}} \quad 0 \leq k \leq 1$


- 磁耦合线圈的能量

$$w = \frac{1}{2} L_1 i_1^2 + \frac{1}{2} L_2 i_2^2 \pm M i_1 i_2$$



电流都从同名端流入，
则为“+”；一进一出
则为“-”；

- 线性变压器的次级线圈总阻抗折算到主线圈后的增加阻抗
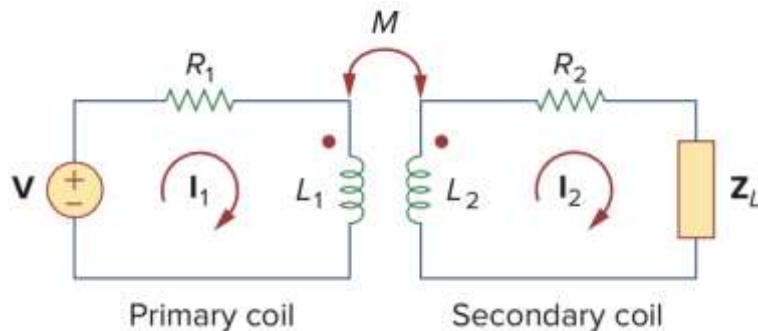
$$Z_R = \frac{\omega^2 M^2}{R_2 + j\omega L_2 + Z_L}$$




- 转换为非耦合电路

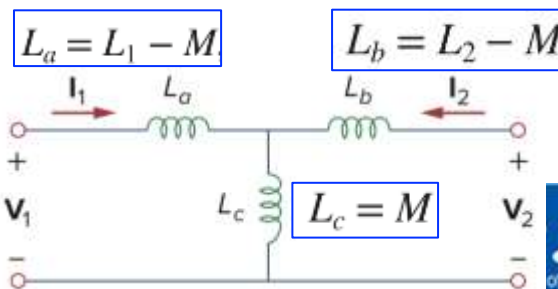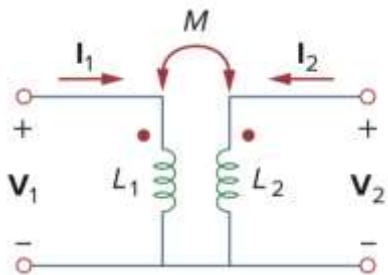

同名端在不同侧，
则 $M \rightarrow -M$

小结

- 理想变压器的“电压电流约束关系”

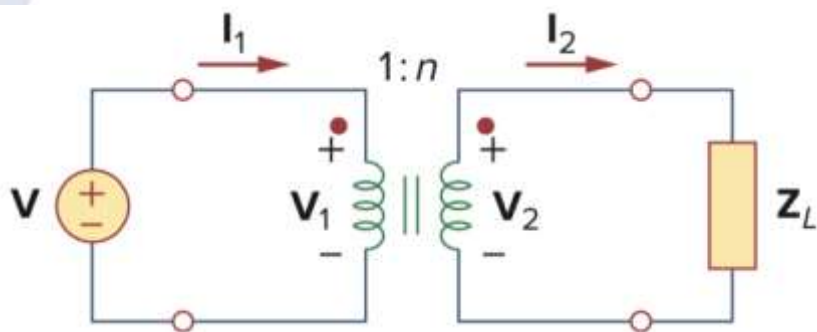

$$\frac{V_2}{V_1} = \frac{N_2}{N_1} = n$$

$$\frac{I_2}{I_1} = \frac{N_1}{N_2} = \frac{1}{n}$$

- 如何区分是磁耦合电路，还是理想变压器电路？
 - 看标注的是互感，还是线圈匝数的比例



作业

Determine the phasor currents \mathbf{I}_1 and \mathbf{I}_2 in the circuit of Fig. 13.13.

Practice Problem 13.2

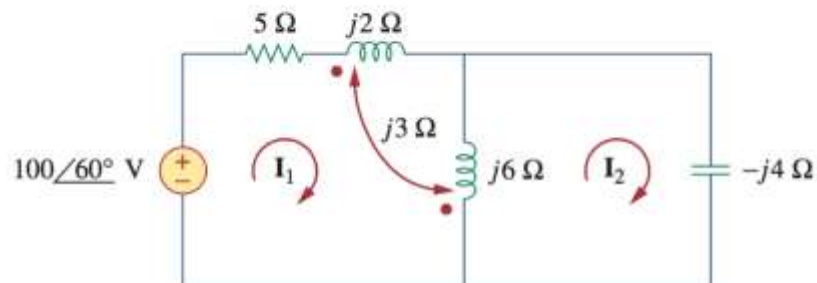


Figure 13.13

For Practice Prob. 13.2.

互感的概念~稍复杂情况
Focus on 流过线圈的电流

Answer: $\mathbf{I}_1 = 17.889\angle 86.57^\circ \text{ A}$, $\mathbf{I}_2 = 26.83\angle 86.57^\circ \text{ A}$.

For the circuit in Fig. 13.18, determine the coupling coefficient and the energy stored in the coupled inductors at $t = 1.5$ s.

Practice Problem 13.3

磁耦合系数和储能

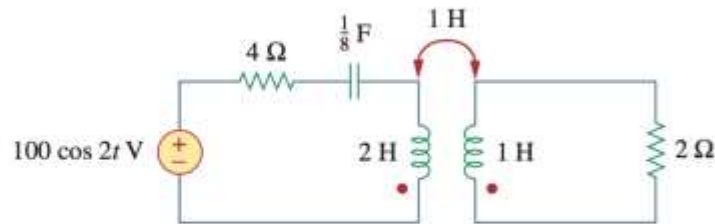


Figure 13.18

For Practice Prob. 13.3.

$$k = \frac{M}{\sqrt{L_1 L_2}}$$

$$w = \frac{1}{2}L_1 i_1^2 + \frac{1}{2}L_2 i_2^2 \pm M i_1 i_2$$

Answer: 0.7071, 246.2 J.

Find the input impedance of the circuit in Fig. 13.25 and the current from the voltage source.

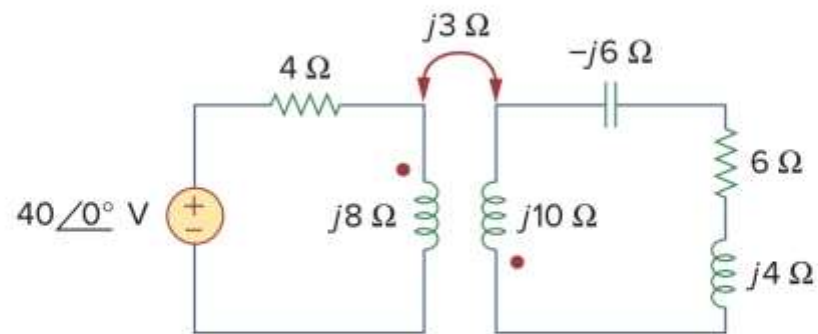


Figure 13.25

For Practice Prob. 13.4.

阻抗折算

$$\mathbf{Z}_R = \frac{\omega^2 M^2}{R_2 + j\omega L_2 + \mathbf{Z}_L}$$


Answer: $8.58 \angle 58.05^\circ \Omega$, $4.662 \angle -58.05^\circ \text{ A}$.

Practice Problem 13.6

Solve the problem in Example 13.1 (see Fig. 13.9) using the T-equivalent model for the magnetically coupled coils.

Answer: $13\angle-49.4^\circ$ A, $2.91\angle14.04^\circ$ A.

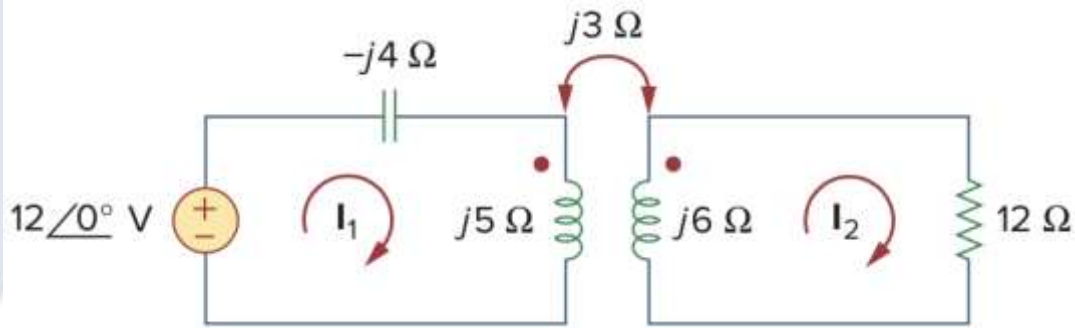Calculate the phasor currents \mathbf{I}_1 and \mathbf{I}_2 in the circuit



去耦合等效法

Practice Problem 13.8

In the ideal transformer circuit of Fig. 13.38, find V_o and the complex power supplied by the source.

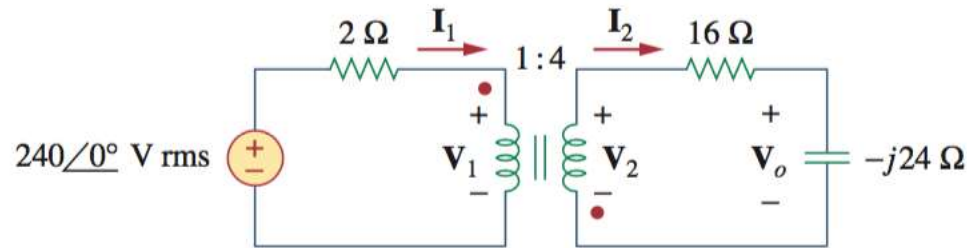


Figure 13.38

For Practice Prob. 13.8.

理想变压器的折算法简化

Answer: $429.4\angle 116.57^\circ$ V, $17.174\angle -26.57^\circ$ kVA.

Practice Problem 13.9

Find V_o in the circuit of Fig. 13.40.

折算法简化不能应用时，
采用传统电路分析法

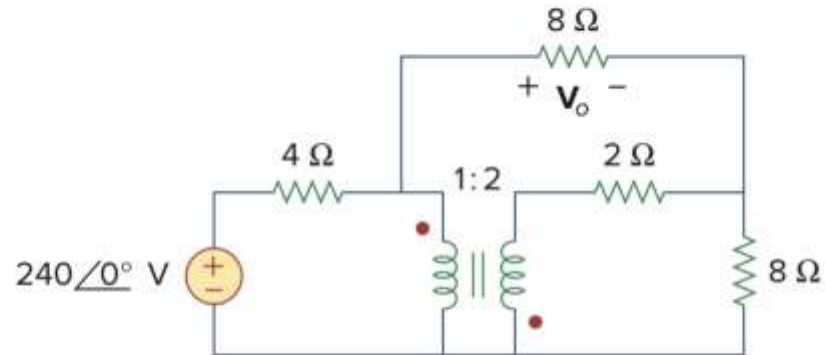


Figure 13.40

For Practice Prob. 13.9.

Answer: 96 V.