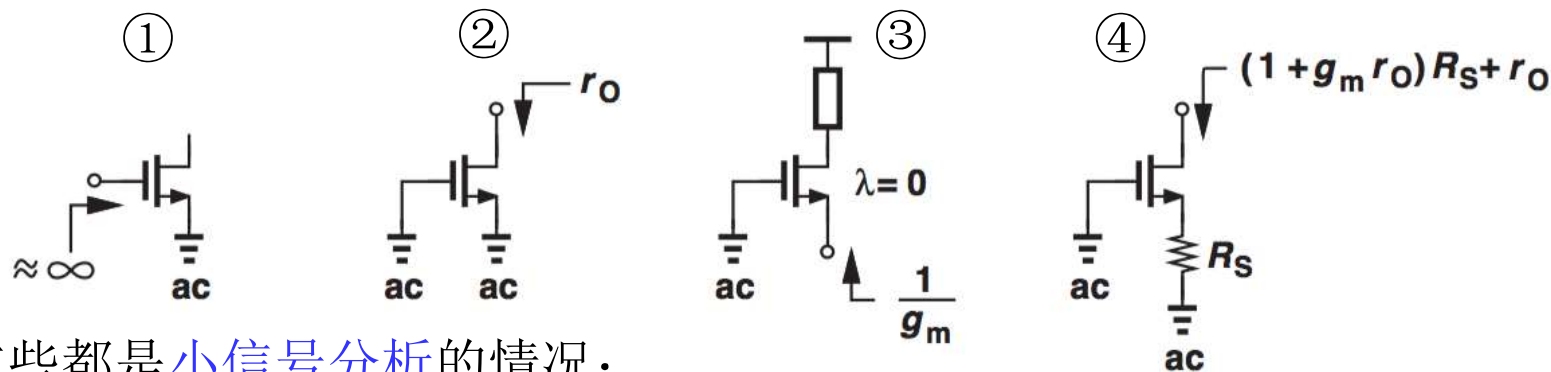


Lecture 18 – 晶体管放大器-part3

Chapter 7 from **Microelectronic
Circuits** Text by Sedra and Smith
Oxford Publishing



培养电路直觉的 Building Blocks




1. 这些都是小信号分析的情况；
2. 要逐渐习惯于从电路中某一点，向左、向右，或向上、向下看的阻抗
3. 计算输出阻抗时，输入信号 v_i 置零，所以图中的ac地，有可能是真正的ac地，也有可能是 v_i 输入端
4. ① 从G端向MOS管看的阻抗始终为 ∞ ；【因为有 SiO_2 绝缘, $i_G=0$ 】
5. ② G和S都接地时，从D端向MOS管看的阻抗为 r_o ；【因为信号都是从G或S端输入的（改变 v_{GS} ），所以从D端向MOS管看阻抗时，均为计算电路的输出阻抗；计算输出阻抗时输入信号 v_i 要置零；所以②既适用于CS（S接地， v_i 接G），也适用于CG（G接地， v_i 接S）】
6. ③ G端接地，从S端向MOS管看的阻抗为 $1/g_m$ 【与D端所接的负载无关；CG的输入阻抗，或CD， v_i 接G时，从S看向MOS管的输出阻抗】
7. ④ Source degeneration结构的主要作用：大幅提高输出阻抗 \rightarrow 更接近于理想电流源，提高的增量为S端串接的电阻 R_S 放大 $(1+g_m r_o)$ 倍；也可以看成CG结构（考虑信号源内阻时）的输出阻抗值

培养电路直觉的 Building Blocks

 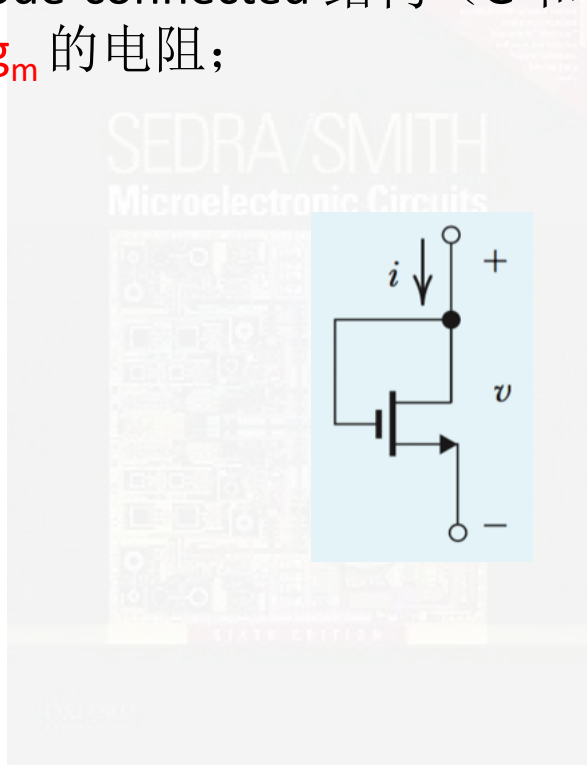1. Diode-connected 结构（G 和 D 直接相连），小信号分析时等效为阻值 $1/g_m$ 的电阻；



培养电路直觉的 Building Blocks

 CS

1. 输出阻抗: **D 端到 ac 地的总电阻** (向下看为 r_o 到地, 向上看为 R_D 到地)
2. 增益: **$-g_m \times$ (D 端到 ac 地的总电阻)**
3. 输入阻抗: ∞


$$A_v = -g_m (R_D \parallel r_o)$$

$$R_{in} = \infty$$


$$R_{out} = \underline{R_D \parallel r_o}$$

培养电路直觉的 Building Blocks

CS

 

CS Deg

 

$$A_v = -g_m (R_D \parallel r_o)$$

$$R_{in} = \infty$$

$$R_{out} = R_D \parallel r_o$$

$$A_v = -\frac{R_D}{\frac{1}{g_m} + R_S}$$

$$R_{in} = \infty$$

$$R_{out} = [(1 + g_m r_o) R_S + r_o] \parallel R_D$$

1. 输出阻抗：D 端到 ac 地的总电阻
(向下看为 source degeneration 结构，到 ac 地的电阻为 $r_o + (1 + g_m r_o) R_S$ ，向上看为 R_D 到地)

2. 增益：

$$A_v = -\frac{\text{D端到ac地的总电阻}}{\frac{1}{g_m} + R_S}$$

$$= -\frac{\text{res tied from "D" to ac GND}}{\frac{1}{g_m} + \text{res tied from "S" to ac GND}}$$

3. 输入阻抗： ∞

培养电路直觉的 Building Blocks

1. 输出阻抗：D 端到 ac 地的总电阻
 - ① 考虑信号源内阻 R_S 【向下看与 source degeneration 结构一致，到 ac 地的电阻为 $r_o + (1 + g_m r_o) R_S$ 】
 - ② 不考虑信号源内阻 R_S 【向下看到 ac 地的电阻为 r_o 】
 - ③ 向上看均为 R_D 到地）

2. 增益：

- ① 考虑信号源内阻 R_S


$$A_v = \frac{D \text{ 端到 ac 地的总电阻}}{\frac{1}{g_m} + R_S}$$

- ② 不考虑信号源内阻 R_S ，即从 x 点到 V_{out} 的电压增益

$$g_m \times (D \text{ 端到 ac 地的总电阻})$$

3. 输入阻抗： $1/g_m$

CG

 

$$A_v = \frac{R_D}{\frac{1}{g_m} + R_S}$$


$$R_{in} = \frac{1}{g_m}$$

$$R_{out} = [(1 + g_m r_o) R_S + r_o] \parallel R_D$$

培养电路直觉的 Building Blocks


1. 输出阻抗, 向上看为 $1/g_m \parallel r_o$, 向下看为 R_L
2. 输入阻抗, 无穷大
3. 增益, 可看成是s端的分压, V_{in} 和s之间是电阻 $1/g_m$, s和地之间是电阻 $R_L \parallel r_o$.

CD

 


$$A_v = \frac{r_o \parallel R_L}{\frac{1}{g_m} + r_o \parallel R_L}$$
$$R_{in} = \infty$$
$$R_{out} = \frac{1}{g_m} \parallel r_o \parallel R_L$$


CS

 


CS Deg

 

CG

 

CD

 

$$A_v = -g_m (R_D \parallel r_o)$$

$$R_{in} = \infty$$

$$R_{out} = R_D \parallel r_o$$

$$A_v = -\frac{R_D}{\frac{1}{g_m} + R_S}$$

$$R_{in} = \infty$$

$$R_{out} = [(1 + g_m r_o) R_S + r_o] \parallel R_D$$

$$A_v = \frac{R_D}{\frac{1}{g_m} + R_S}$$

$$R_{in} = \frac{1}{g_m}$$

$$R_{out} = [(1 + g_m r_o) R_S + r_o] \parallel R_D$$

$$A_v = \frac{r_o \parallel R_L}{\frac{1}{g_m} + r_o \parallel R_L}$$

$$R_{in} = \infty$$

$$R_{out} = \frac{1}{g_m} \parallel r_o \parallel R_L$$


提供增益
一级或多级

牺牲增益，获得更
大的输出电阻


输入电阻可适配
更好的高频特性

Voltage Buffer
可驱动小电阻

综合实例 (I)

 

(a)


 


(b)

$$A_v = -g_{m1} \left(\frac{1}{g_{m3}} \parallel r_{O1} \parallel r_{O2} \parallel r_{O3} \right)$$



$$R_{out} = \frac{1}{g_{m3}} \parallel r_{O1} \parallel r_{O2} \parallel r_{O3}$$

综合实例 (II)

  

$$A_v = - \frac{r_{O2}}{\frac{1}{g_{m1}} + \frac{1}{g_{m3}} \parallel r_{O3}}$$

综合实例 III

  


$$A_{v_CS} = -g_{m1} \left[(1 + g_{m2} r_{O2}) R_S + r_{O2} \right] \parallel r_{O1}$$


$$A_{v_CG} = \frac{r_{O1}}{\frac{1}{g_{m2}} + R_S}$$

- 同样的电路拓扑结构，若输入接在不同的地方，结果是完全不一样的

综合实例 (IV)

 

 
$$A_v = \frac{R_D}{\frac{1}{g_{m1}} + \frac{1}{g_{m2}}}$$



- 方法1: 左边用戴维南定理替代;
- 方法2: 级联计算






综合实例 (V)

 

$$\frac{v_{out2}}{v_{in}} = - \frac{\frac{1}{g_{m3}} \parallel r_{O3} \parallel r_{O4}}{\frac{1}{g_{m2}} \parallel r_{O2} + \frac{1}{g_{m1}}}$$

$$\frac{v_{out1}}{v_{in}} = \frac{\frac{1}{g_{m2}} \parallel r_{O2}}{\frac{1}{g_{m2}} \parallel r_{O2} + \frac{1}{g_{m1}}}$$


培养电路直觉的 Building Blocks

     


1. 计算输出阻抗时，输入信号 v_i 置零，所以图中的 **ac地**，有可能是真正的 **ac地**，也有可能是 v_i 输入端
2. 从B端看进去，E的电阻折算到B需乘以 $(1+\beta)$ ；从E端看进去，B的电阻折算到E需除以 $(1+\beta)$
3. ① r_{π} 或者 $r_e(1+\beta)$ ② r_o
4. ③B的ac可以是真正的ac地（CB输入电阻），也可以是 v_i （CC输出电阻）
5. ④当B接有电阻 R_B 时， R_B 除以 $(1+\beta)$ 折算到E
6. ⑤从B看输入电阻， R_E 乘以 $(1+\beta)$ 折算到B
7. ⑥信号可以从B输入（发射极退化），也可以从E输入（CB, R_E 可视为信号源内阻）；用混合 π 模型考虑，E到地的电阻是 R_E 和 r_{π} 并联
8. Emitter degeneration 结构的主要作用：大幅提高输出阻抗 \rightarrow 更接近于理想电流源，提高的增量为E端串接的电阻 $R_E || r_{\pi}$ 放大 $(1+g_m r_o)$ 倍

三极管放大电路总结


CE Stage

 

CB Stage

 


Follower

 

- 三种组态具有不同的特性→各有各的用途；
- CE和CB具有较大的电压增益，而射极跟随具有单位电压增益；
- CE是最常见的放大器结构；
- CB的输入阻抗具有 $1/g_m$ 特性，适合于设计成50欧姆输入阻抗，因此在射频电路中有广泛应用；
- 射极跟随因具有较大输入阻抗、较小输出阻抗、单位电压增益等特性，往往作为Buffer使用；



在理解的基础上熟记 (CE)

 

$$A_v = -g_m (R_C \parallel r_o)$$

$$R_{out} = R_C \parallel r_o$$

$$R_{in} = r_\pi$$

  

$$A_v = -\frac{R_C}{\frac{1}{g_m} + R_E}$$

$$R_{in} = r_\pi + (\beta + 1)R_E$$

$$R_{out} = R_C$$



$i_c \approx i_e$

E折算到B


$$R_{out} = r_o + (g_m r_o + 1)(R_E \parallel r_\pi)$$

B折算到E
  
$$A_v \approx \frac{-R_C}{\frac{1}{g_m} + R_E + \frac{R_B}{\beta + 1}}$$




在理解的基础上熟记 (CB)

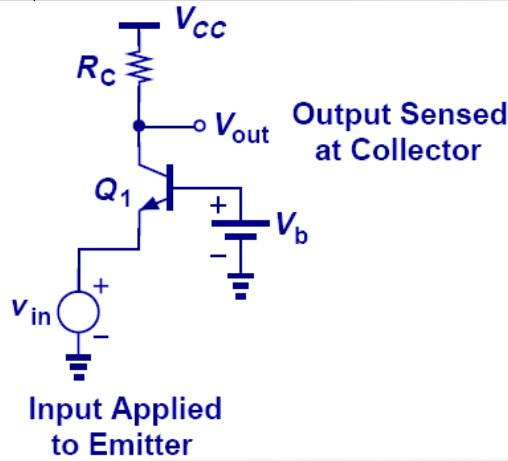

$$A_v = g_m (r_o \parallel R_C)$$



$$R_{in} = \frac{1}{g_m}$$

$$R_{out} = r_o \parallel R_C$$

 


$i_c \approx i_e$ B折算到E

  
$$A_v \approx \frac{R_C}{R_E + \frac{R_B}{\beta + 1} + \frac{1}{g_m}}$$



B折算到E

 

在理解的基础上熟记 (射极跟随)

 

$$A_v = \frac{R_E \parallel r_o}{R_E \parallel r_o + \frac{R_S}{\beta + 1} + \frac{1}{g_m}}$$



B折算到E

$$R_{in} = r_{\pi} + (\beta + 1)(R_E \parallel r_o) + R_S$$




E折算到B

$$R_{out} = \left(\frac{R_S}{\beta + 1} + \frac{1}{g_m} \right) \parallel R_E \parallel r_o$$

从E看进去，B要折算到E，再和 r_o 、 R_E 并联

 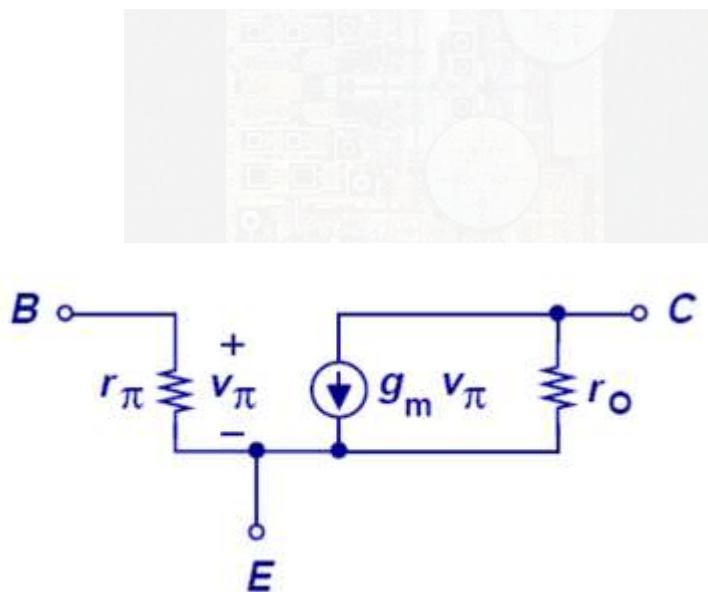



综合实例 I

   

$$\frac{v_{out}}{v_{in}} = - \frac{R_2 \parallel R_C}{\frac{R_1 \parallel R_S}{\beta + 1} + \frac{1}{g_m} + R_E} \cdot \frac{R_1}{R_1 + R_S}$$

通过X点级联, Q_1 的输入电阻很大, 与 R_1 并联时, 可以忽略

综合实例 II

 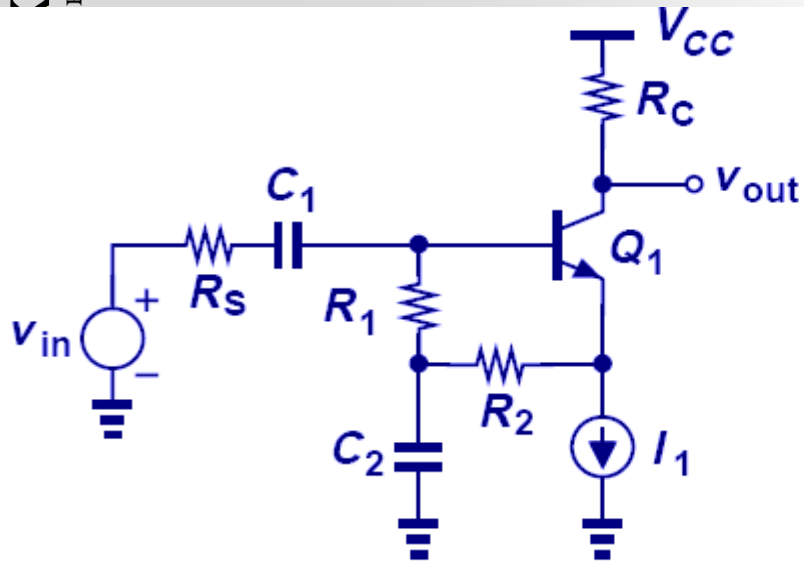

$$\frac{v_{out}}{v_{in}} = - \frac{R_C}{\frac{R_S \parallel R_1}{\beta + 1} + \frac{1}{g_m} + R_2} \cdot \frac{R_1}{R_1 + R_S}$$

**Example
5.50**

Assuming $V_A = \infty$, compute the voltage gain and input impedance of the circuit shown in Fig. 5.99(a).

 


Figure 5.99 (a) Example of CE stage, (b) simplified circuit.

Solution The circuit resembles a CE stage (why?) degenerated by the impedance seen at the emitter of Q_2 , R_{eq} . Recall from Fig. 5.75 that

$$R_{eq} = \frac{R_1}{\beta + 1} + \frac{1}{g_{m2}}. \quad (5.347)$$

The simplified model in Fig. 5.99(b) thus yields

$$A_v = \frac{-R_C}{\frac{1}{g_{m1}} + R_{eq}} \quad (5.348)$$



$$= \frac{-R_C}{\frac{1}{g_{m1}} + \frac{R_1}{\beta + 1} + \frac{1}{g_{m2}}}. \quad (5.349)$$

The input impedance is also obtained from Fig. 5.75:

$$R_{in} = r_{\pi 1} + (\beta + 1)R_{eq} \quad (5.350)$$



$$= r_{\pi 1} + R_1 + r_{\pi 2}. \quad (5.351)$$

综合实例IV

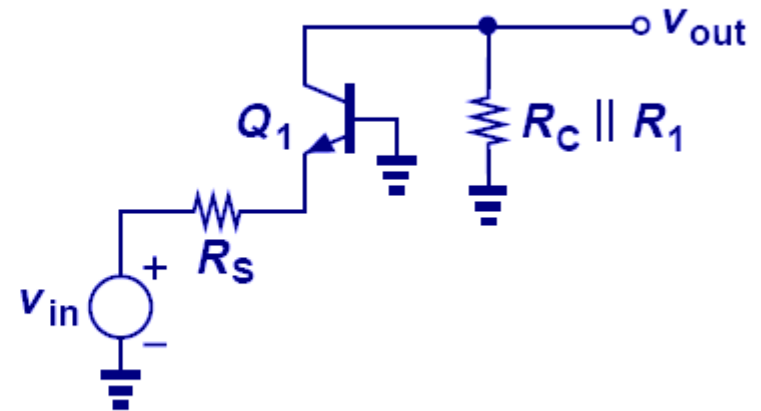 


$$A_v = \frac{R_C \parallel R_1}{R_S + \frac{1}{g_m}}$$

综合实例V

 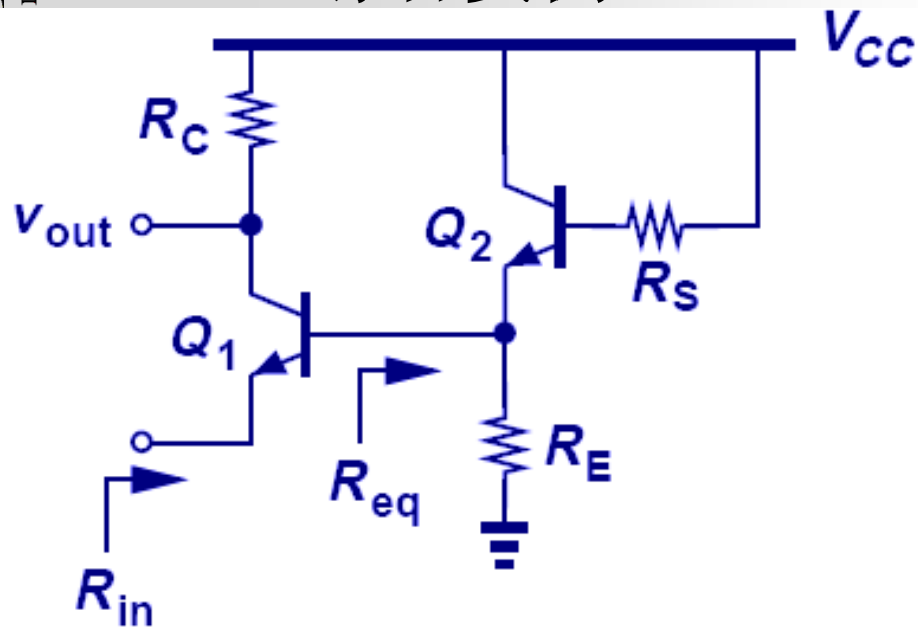


$$R_{in} = \frac{1}{\beta + 1} \left[\left(\frac{R_S}{\beta + 1} + \frac{1}{g_{m2}} \right) \parallel R_E \right] + \frac{1}{g_{m1}}$$


综合实例 VI

 

(a)

 

(b)

 


(c)

$$\frac{v_{out}}{v_{in}} = \frac{R_E \parallel R_2 \parallel r_o}{R_E \parallel R_2 \parallel r_o + \frac{1}{g_m} + \frac{R_S \parallel R_1}{\beta + 1}} \cdot \frac{R_1}{R_1 + R_S}$$

$$R_{out} = \left(\frac{R_S \parallel R_1}{\beta + 1} + \frac{1}{g_m} \right) \parallel R_E \parallel R_2 \parallel r_o$$

综合实例VII

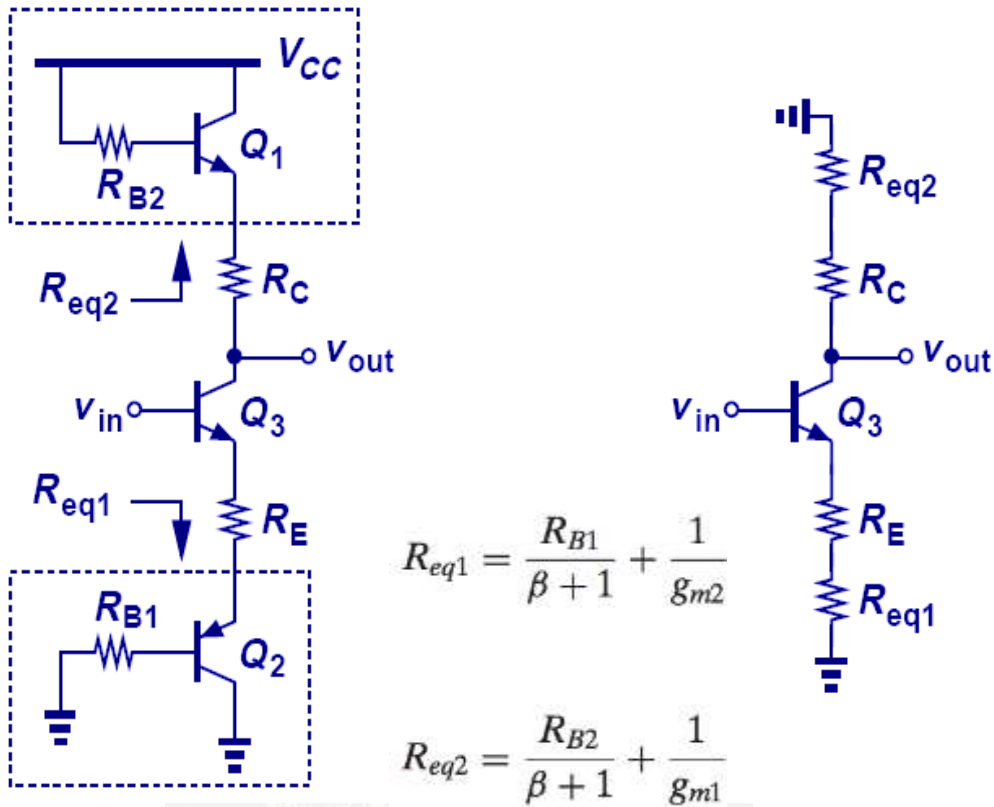

$$R_{in} = r_{\pi 3} + (\beta + 1) \left(R_E + \frac{R_{B1}}{\beta + 1} + \frac{1}{g_{m2}} \right)$$

$$R_{out} = R_C + \frac{R_{B2}}{\beta + 1} + \frac{1}{g_{m3}}$$

$$A_v = - \frac{R_C + \frac{R_{B2}}{\beta + 1} + \frac{1}{g_{m1}}}{\frac{R_{B1}}{\beta + 1} + \frac{1}{g_{m2}} + \frac{1}{g_{m3}} + R_E}$$

偏置电路方案1，直接固定 V_{GS}

Biasing by Fixing V_{GS}


 


Figure 7.47 (a) Biasing the MOSFET with a constant V_{GS} generated from V_{DD} using a voltage divider (R_{G1}, R_{G2}); (b) the use of fixed bias (constant V_{GS}) can result in a large variability in the value of I_D . Devices 1 and 2 represent extremes among units of the same type.


偏置电路方案2，引入源极退化电阻，负反馈提高稳定性

 

$$V_G = V_{GS} + R_S I_D$$


可有效降低工艺、温度变化的影响(I_D 变化较小)

单电源供电

 


(c)

双电源供电

 



(d)

 

(e)

Figure 7.48 Biasing using a fixed voltage at the gate, V_G , and a resistance in the source lead, R_S : (a) basic arrangement; (b) reduced variability in I_D ; (c) practical implementation using a single supply; (d) coupling of a signal source to the gate using a capacitor C_{C1} ; (e) practical implementation using two supplies.

It is required to design the circuit of Fig. 7.48(c) to establish a dc drain current $I_D = 0.5 \text{ mA}$. The MOSFET is specified to have $V_t = 1 \text{ V}$ and $k'_n W/L = 1 \text{ mA/V}^2$. For simplicity, neglect the channel-length modulation effect (i.e., assume $\lambda = 0$). Use a power-supply $V_{DD} = 15 \text{ V}$. Calculate the percentage change in the value of I_D obtained when the MOSFET is replaced with another unit having the same $k'_n W/L$ but $V_t = 1.5 \text{ V}$.
 一般直流分析时不考虑沟道调制效应

  

①为了使输出有最大可能的摆幅，一般设置 V_D 为 V_{DD} 的2/3， V_S 为 V_{DD} 的1/3

$$R_D = \frac{V_{DD} - V_D}{I_D} = \frac{15 - 10}{0.5} = 10 \text{ k}\Omega$$

$$R_S = \frac{V_S}{I_D} = \frac{5}{0.5} = 10 \text{ k}\Omega$$

②

$$I_D = \frac{1}{2} k'_n (W/L) V_{OV}^2 \Rightarrow V_{GS} = 2 \text{ V}$$



$$\Rightarrow V_G = V_S + V_{GS} = 5 + 2 = 7 \text{ V}$$



may select $R_{G1} = 8 \text{ M}\Omega$ and $R_{G2} = 7 \text{ M}\Omega$.

It is required to design the circuit of Fig. 7.48(c) to establish a dc drain current $I_D = 0.5 \text{ mA}$. The MOSFET is specified to have $V_t = 1 \text{ V}$ and $k'_n W/L = 1 \text{ mA/V}^2$. For simplicity, neglect the channel-length modulation effect (i.e., assume $\lambda = 0$). Use a power-supply $V_{DD} = 15 \text{ V}$. Calculate the percentage change in the value of I_D obtained when the MOSFET is replaced with another unit having the same $k'_n W/L$ but $V_t = 1.5 \text{ V}$.

一般直流分析时不考虑沟道调制效应

  

如果 $V_t = 1.5 \text{ V}$

$$I_D = \frac{1}{2} \times 1 \times (V_{GS} - 1.5)^2$$

$$V_G = V_{GS} + I_D R_S$$

$$7 = V_{GS} + 10 I_D$$




$$I_D = 0.455 \text{ mA}$$

$$\Delta I_D = 0.455 - 0.5 = -0.045 \text{ mA}$$

$$\frac{-0.045}{0.5} \times 100 = -9\% \text{ change.}$$


偏置电路方案3，自偏置：G和D连接一个较大电阻

 

- M1 始终处于饱和区；
- R_G 上面没有电压降

$$I_D R_D + V_{GS} + R_S I_D = V_{DD}$$
 
$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} [V_{DD} - (R_S + R_D) I_D - V_{TH}]^2$$



$$(R_S + R_D)^2 I_D^2 - 2 \left[(V_{DD} - V_{TH})(R_S + R_D) + \frac{1}{\mu_n C_{ox} \frac{W}{L}} \right] I_D + (V_{DD} - V_{TH})^2 = 0.$$

(7.31)

**Example
7.3**

Calculate the drain current of M_1 in Fig. 7.3 if $\mu_n C_{ox} = 100 \mu\text{A}/\text{V}^2$, $V_{TH} = 0.5 \text{ V}$, and $\lambda = 0$. What value of R_D is necessary to reduce I_D by a factor of two?

 


Figure 7.3 Example of self-biased MOS stage.

Solution Equation (7.31) gives

$$I_D = 556 \mu\text{A}. \quad (7.32)$$

To reduce I_D to $278 \mu\text{A}$, we solve Eq. (7.31) for R_D :

$$R_D = 2.867 \text{ k}\Omega. \quad (7.33)$$

偏置电路方案4，恒流源确定 I_D ：集成电路中常用的偏置方案³²


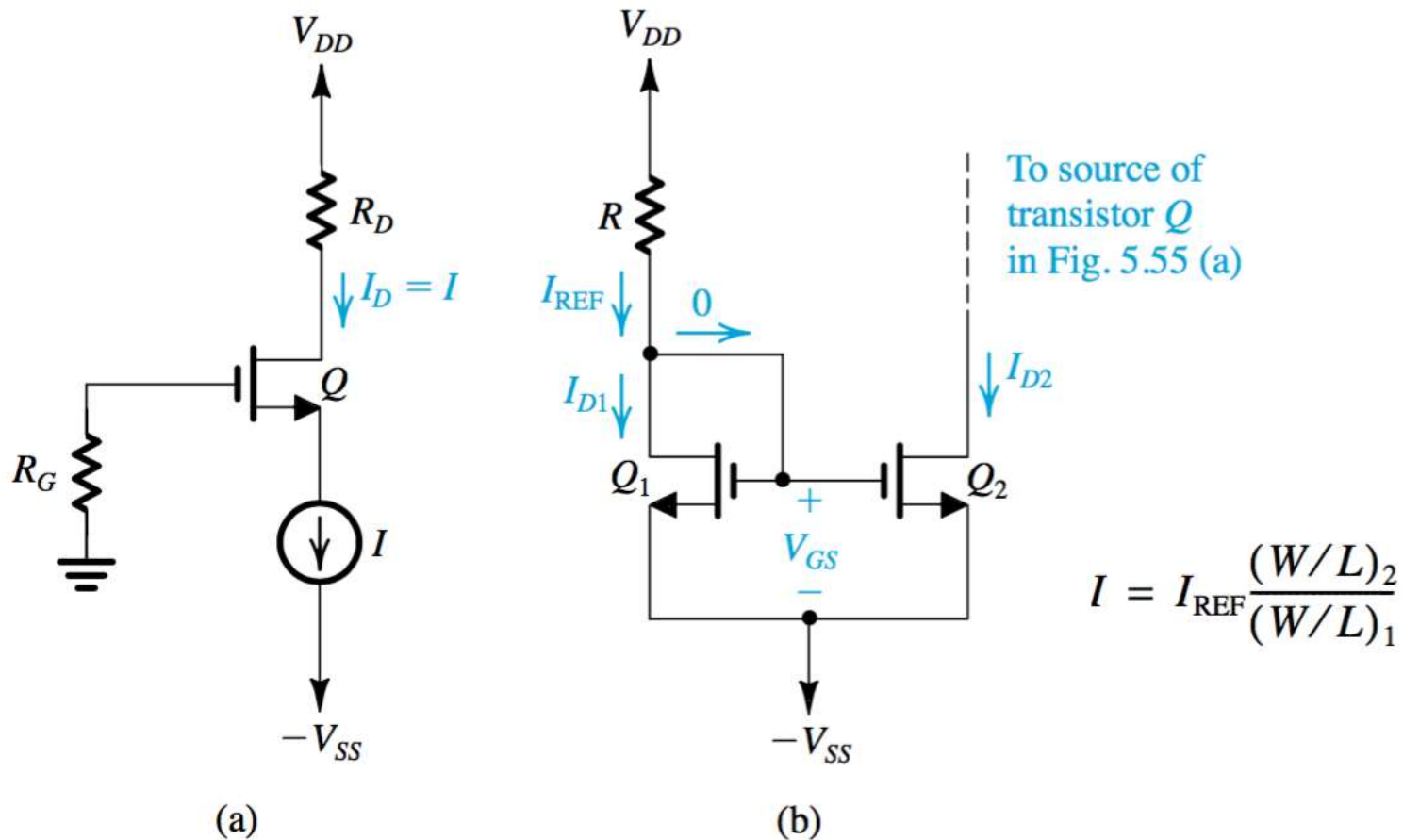
 
 
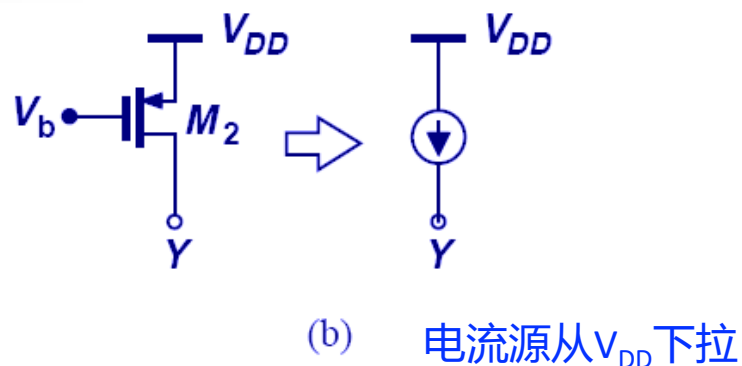


Figure 5.55 (a) Biasing the MOSFET using a constant-current source I . (b) Implementation of the constant-current source I using a current mirror.

电流源

 

- 工作在饱和区时，MOSFET 可以当做一个电流源；
- 思考：为何（c）和（d）不能当做电流源？ V_{GS} 不固定

偏置电路方案1，直接固定 V_{BE} 或 I_B

I_C 受工艺、温度偏差的影响较大，**不是好的偏置方案**

 


Figure 7.51 Two obvious schemes for biasing the BJT: (a) by fixing V_{BE} ; (b) by fixing I_B . Both result in wide variations in I_C and hence in V_{CE} and therefore are considered to be “bad.” Neither scheme is recommended.

偏置电路方案2，引入射极退化电阻，负反馈提高稳定性


① I_C (I_E) 由 I_B 和 β 决定，为了减小 β 的影响：

$$V_{BB} \gg V_{BE}$$


$$R_E \gg \frac{R_B}{\beta + 1}$$

② 为了使输出有较大的摆幅， V_{BB} 一般设置为 V_{CC} 的 $1/3$ ， V_C 一般设置为 V_{CC} 的 $2/3$

 ③ I_B 对 V_B 的影响要尽可能小 $\rightarrow R_1 R_2$ 上的电流要比 I_B 大得多，一般选 I_E to $0.1 I_E$



(a)

 


(b)

$$I_E = \frac{V_{BB} - V_{BE}}{R_E + R_B / (\beta + 1)}$$

Figure 7.52 Classical biasing for BJTs using a single power supply: (a) circuit; (b) circuit with the voltage divider supplying the base replaced with its Thévenin equivalent.

 We wish to design the bias network of the amplifier in Fig. 7.52 to establish a current $I_E = 1 \text{ mA}$ using a power supply $V_{CC} = +12 \text{ V}$. The transistor is specified to have a nominal β value of 100.



(a)

①根据三分之一设计规则

$$V_B = +4 \text{ V}$$

$$V_E = 4 - V_{BE} \simeq 3.3 \text{ V}$$



$$R_E = \frac{V_E}{I_E} = \frac{3.3}{1} = 3.3 \text{ k}\Omega$$

②根据 $R_1 R_2$ 电流设计规则

$$0.1 I_E = 0.1 \times 1 = 0.1 \text{ mA}$$

$$R_1 + R_2 = \frac{12}{0.1} = 120 \text{ k}\Omega$$

$$\frac{R_2}{R_1 + R_2} V_{CC} = 4 \text{ V}$$


$$R_2 = 40 \text{ k}\Omega \text{ and } R_1 = 80 \text{ k}\Omega$$

③重新计算 I_E , 发现与设计值相比偏小了, 可以通过减小 R_E 回到设计值

$$I_E = \frac{4 - 0.7}{3.3(\text{ k}\Omega) + \frac{(80 \parallel 40)(\text{ k}\Omega)}{101}} = 0.93 \text{ mA}$$

原因是 R_{BB} 折算到E极后与 R_E 相比并非明显可忽略

 We wish to design the bias network of the amplifier in Fig. 7.52 to establish a current $I_E = 1 \text{ mA}$ using a power supply $V_{CC} = +12 \text{ V}$. The transistor is specified to have a nominal β value of 100.



(a)

④也可以重新选择 $R_1 R_2$ 设计规则, 选择流过它们的电流为 I_E , 此时

$$R_1 + R_2 = \frac{12}{1} = 12 \text{ k}\Omega$$

$$\frac{R_2}{R_1 + R_2} V_{CC} = 4 \text{ V}$$

$$R_1 = 8 \text{ k}\Omega \text{ and } R_2 = 4 \text{ k}\Omega$$

$$I_E = \frac{4 - 0.7}{3.3 + 0.027} = 0.99 \simeq 1 \text{ mA}$$

⑤计算 R_C


Finally, the value of R_C can be determined from

$$R_C = \frac{12 - V_C}{I_C}$$

Substituting $I_C = \alpha I_E = 0.99 \times 1 = 0.99 \text{ mA} \simeq 1 \text{ mA}$ results, for both designs, in

$$R_C = \frac{12 - 8}{1} = 4 \text{ k}\Omega$$

双电源供电情况

 

$$I_E = \frac{V_{EE} - V_{BE}}{R_E + R_B/(\beta + 1)}$$

Figure 7.53 Biasing the BJT using two power supplies. Resistor R_B is needed only if the signal is to be capacitively coupled to the base. Otherwise, the base can be connected directly to ground, or to a grounded signal source, resulting in almost total β -independence of the bias current.

偏置电路方案3，自偏置：B和C连接一个较大电阻

$$\begin{aligned} V_{CC} &= I_E R_C + I_B R_B + V_{BE} \\ &= I_E R_C + \frac{I_E}{\beta + 1} R_B + V_{BE} \end{aligned}$$



$$I_E = \frac{V_{CC} - V_{BE}}{R_C + R_B/(\beta + 1)}$$

为了降低对 β 的敏感度，选择

$$R_B/(\beta + 1) \ll R_C$$


 
 


Figure 7.54 (a) A common-emitter transistor amplifier biased by a feedback resistor R_B . (b) Analysis of the circuit in (a).


偏置电路方案4，恒流源确定 I_C ：集成电路中常用的偏置方案 40

 

- 也可通过在E极接一恒流源来偏置，此时 V_{BE} , $I_B R_B$ 都有偏置恒流源决定，与供电电压 V_{CC} 无关.

完整PCB级电路分析 (偏置电路 + 小信号放大电路)


错误的输入连接

 

自偏置结构


- 因为麦克风的阻抗很小, 使得 Q_1 的B极经由一小电阻到地, 导致B极电压很小, 从而不能正确偏置 Q_1

使用耦合电容

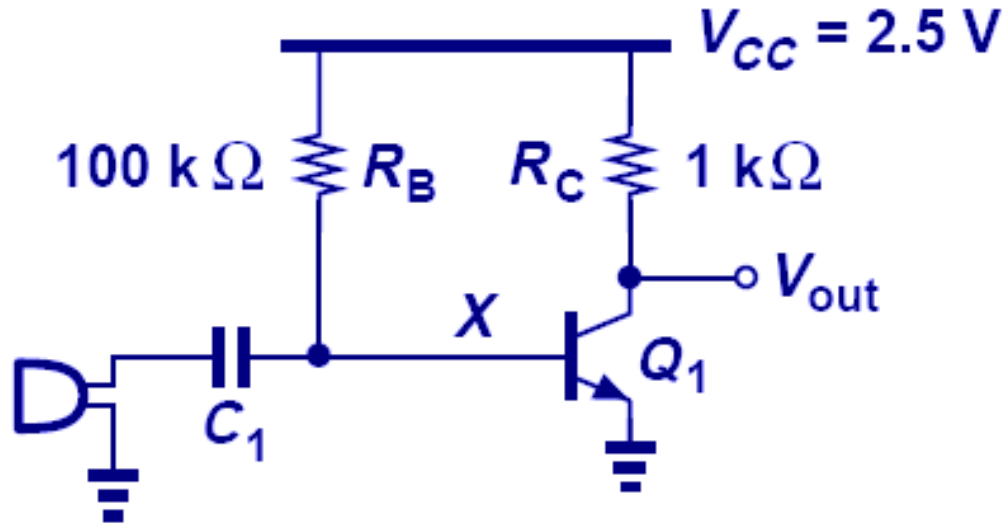



- DC: 电容将偏置网络与麦克风相隔离;
- AC (交流小信号): 电容相当于短路, 麦克风直接与放大电路相连;

错误的输出连接

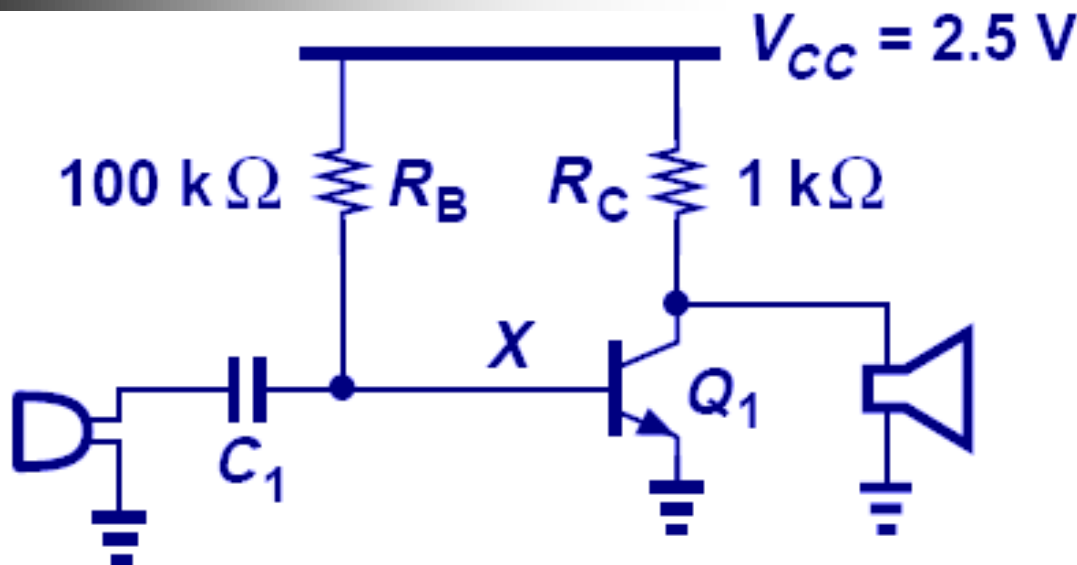

- 因为喇叭由螺线管（电感）构成，所以当其直接接到 Q_1 的C端时，将使C端短路，从而使三极管工作在深饱和区；


改进?

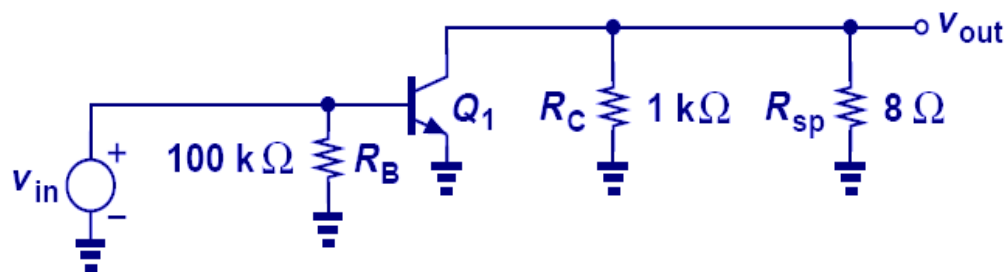 

怎么解决? 我们需要一个输入阻抗较大、输出阻抗较低的Buffer


- 依旧没有增益: 因为喇叭的输入阻抗很小, 导致整体的电压增益很小;

错误的偏置网络

 



- E到GND没有直流通路

改进?

 

- 仍有问题。小信号分析时，输入信号被短路到GND；

合适的偏置网络

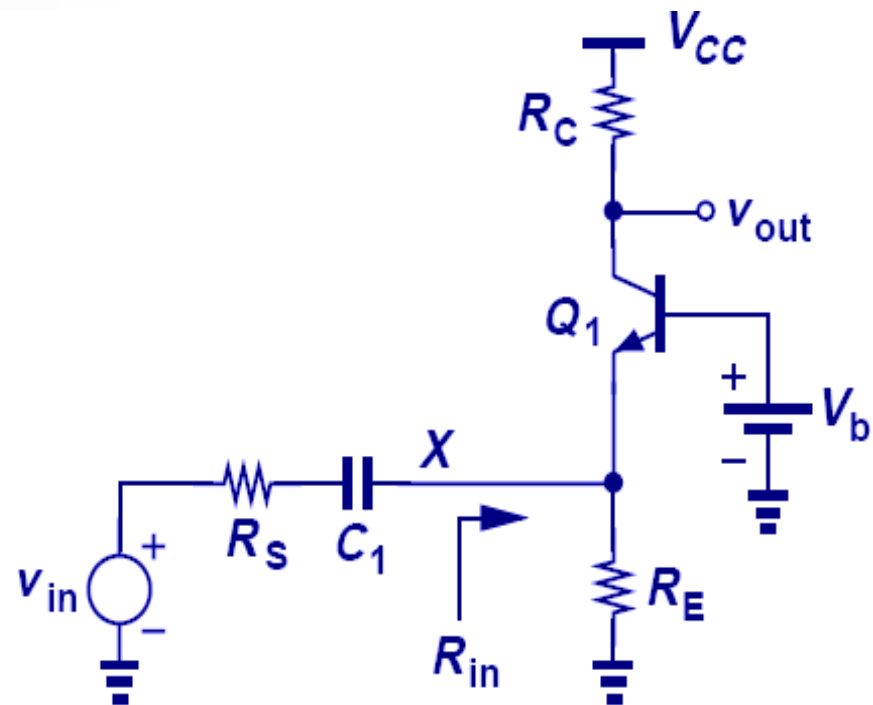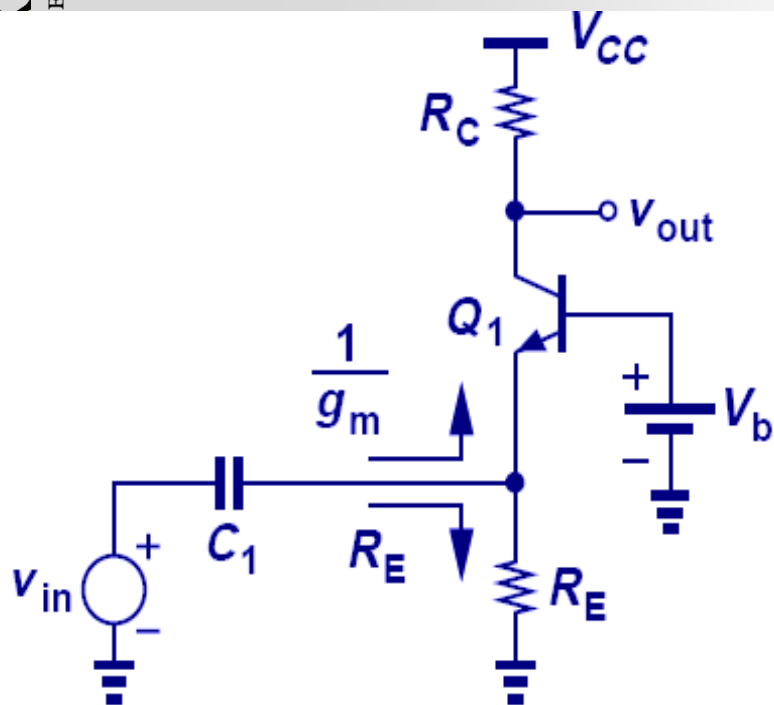


分级计算, $v_{in} \rightarrow X \rightarrow v_{out}$

$$R_{in} = \frac{1}{g_m} \parallel R_E$$

$$\frac{v_{out}}{v_{in}} = \frac{R_E}{R_E + (1 + g_m R_E) R_S} g_m R_C$$




$$\frac{\frac{1}{g_m} \parallel R_E}{\frac{1}{g_m} \parallel R_E + R_S} \cdot g_m R_C$$

R_E 导致输入阻抗的降低

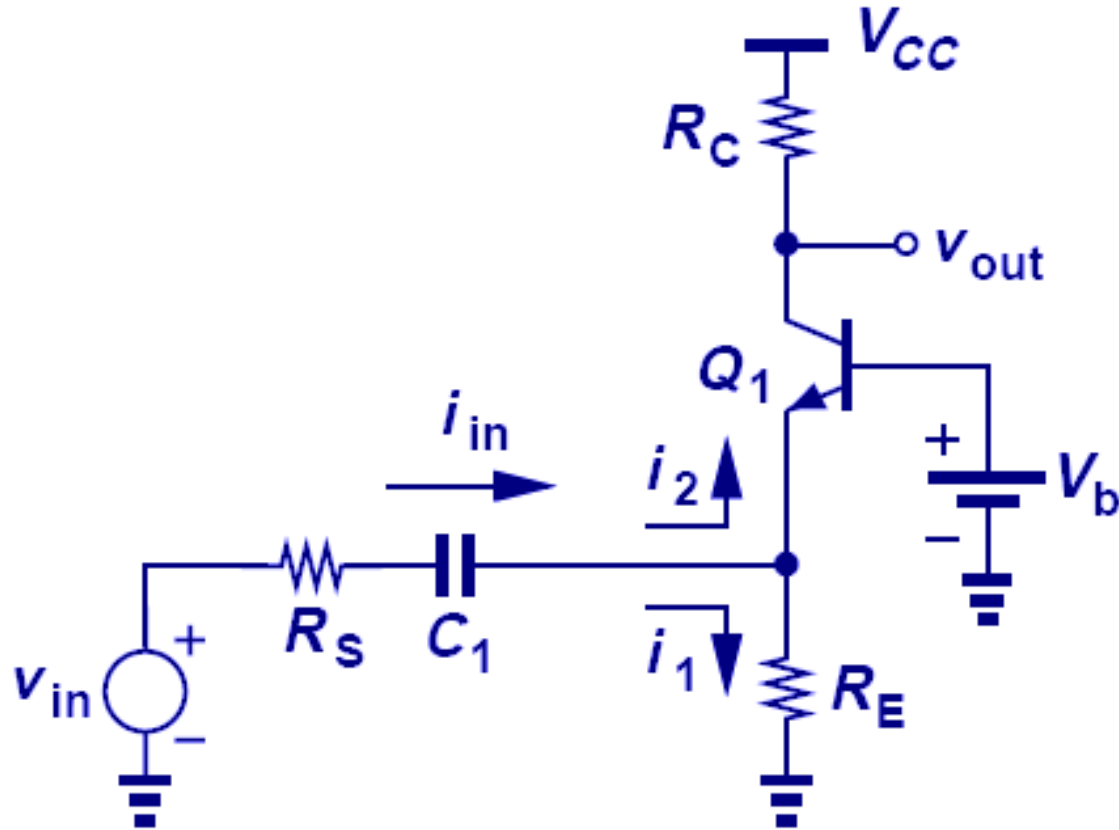


- R_E 分流了部分电流到GND（这部分电流是浪费掉的）

如何获得 V_b

   

- 电阻分压：但降低了增益；
- 为了解决这个问题，可以在B极并联一电容 C_B

举例

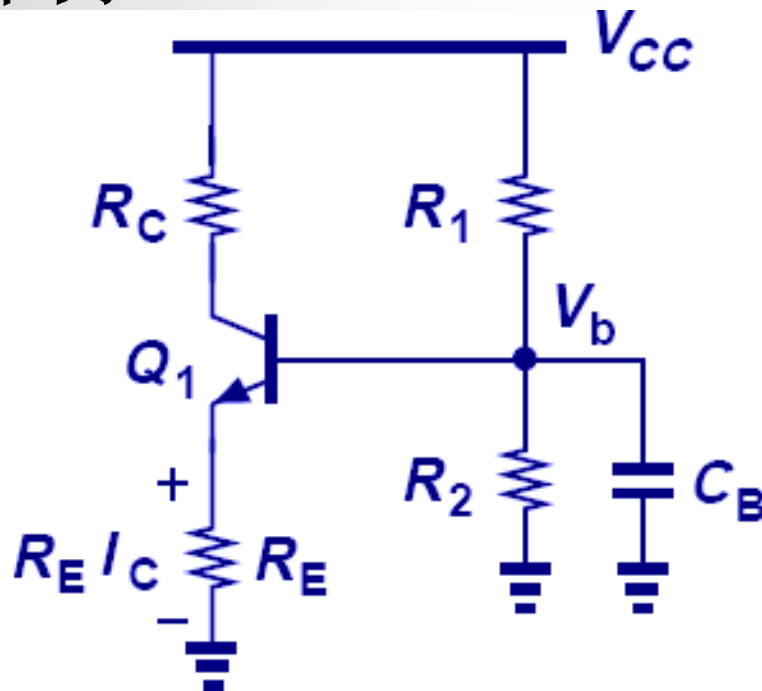

$$A_v \approx \frac{R_C}{R_E + \frac{R_B}{\beta + 1} + \frac{1}{g_m}}$$


- 为了使 R_E 分流较小，需使 $R_E \gg 1/g_m$.
- R_1 、 R_2 分压获得 V_b ，需保证流经 R_1 、 R_2 的电流远大于 I_B ；
- 电容如何选择？其折算到E之后的阻抗需远小于 $1/g_m$.

$$\frac{1}{\beta + 1} \left| \frac{1}{C_B \omega} \right| = \frac{1}{20} \frac{1}{g_m}$$

7.5 Discrete-Circuit Amplifiers


分立电路用BJT比较多
IC用MOSFET比较多

CS

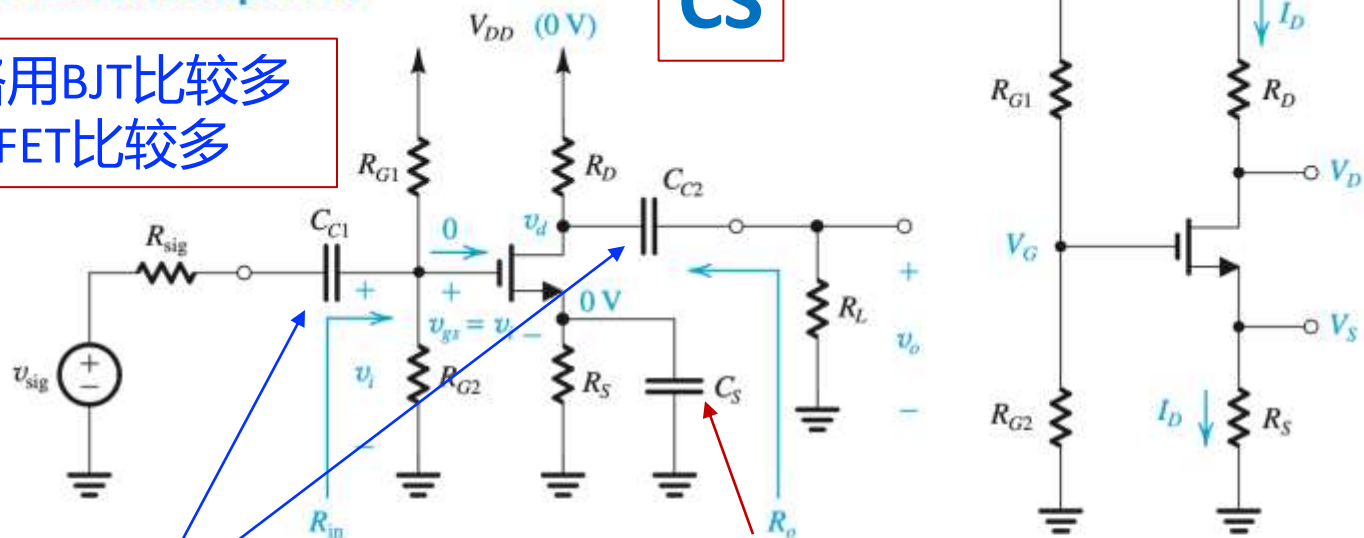

① 隔直电容，隔离直流，通交流小信号

① 旁路电容，直流开路，RS用来稳定直流工作点；交流短路，CS结构

 


$$v_i = v_{sig} \frac{R_{in}}{R_{in} + R_{sig}}$$

$$v_{gs} = v_i$$

$$v_o = -g_m v_{gs} (R_D \parallel R_L \parallel r_o)$$


$$G_v = -\frac{R_{in}}{R_{in} + R_{sig}} g_m (R_D \parallel R_L \parallel r_o)$$

Figure 7.55 (a) A common-source amplifier using the classical biasing arrangement of Fig. 7.48(c). (b) Circuit for determining the bias point. (c) Equivalent circuit and analysis.

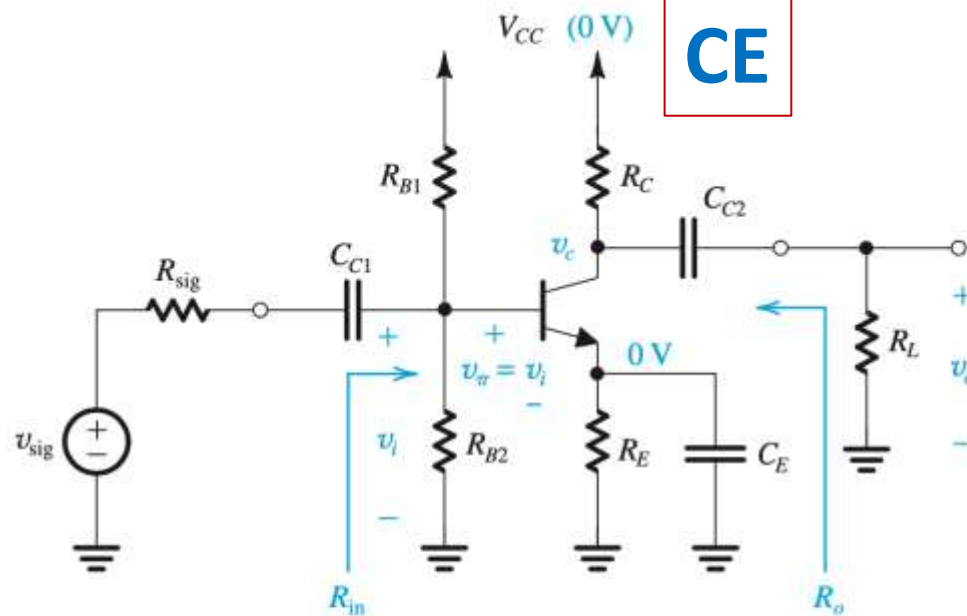

(a)
 
$$G_v = -\frac{R_{in}}{R_{in} + R_{sig}} g_m (R_C \parallel R_L \parallel r_o)$$




(b)

Figure 7.56 (a) A common-emitter amplifier using the classical biasing arrangement of Fig. 7.52(a).


(b) Equivalent circuit and analysis.

射极退化

 

(a)

旁路电容只旁路部分反馈电阻，在小信号分析时，是射极退化结构

 

(b)

$$R_{in} = R_{B1} \parallel R_{B2} \parallel (\beta + 1)(r_e + R_E)$$


$$= R_{B1} \parallel R_{B2} \parallel [r_{\pi} + (\beta + 1)R_E]$$

$$G_v = - \frac{R_{in}}{R_{in} + R_{sig}} \times \alpha \frac{(R_C \parallel R_L)}{r_e + R_E}$$


$$G_v = - \frac{R_{in}}{R_{in} + R_{sig}} \times \alpha \frac{\text{Total resistance in collector}}{\text{Total resistance in emitter}}$$

$$= - \alpha \frac{R_{in}}{R_{in} + R_{sig}} \frac{R_C \parallel R_L}{r_e + R_E}$$

Figure 7.57 (a) A common-emitter amplifier with an unbypassed emitter resistance R_E . (b) The amplifier small-signal model and analysis.

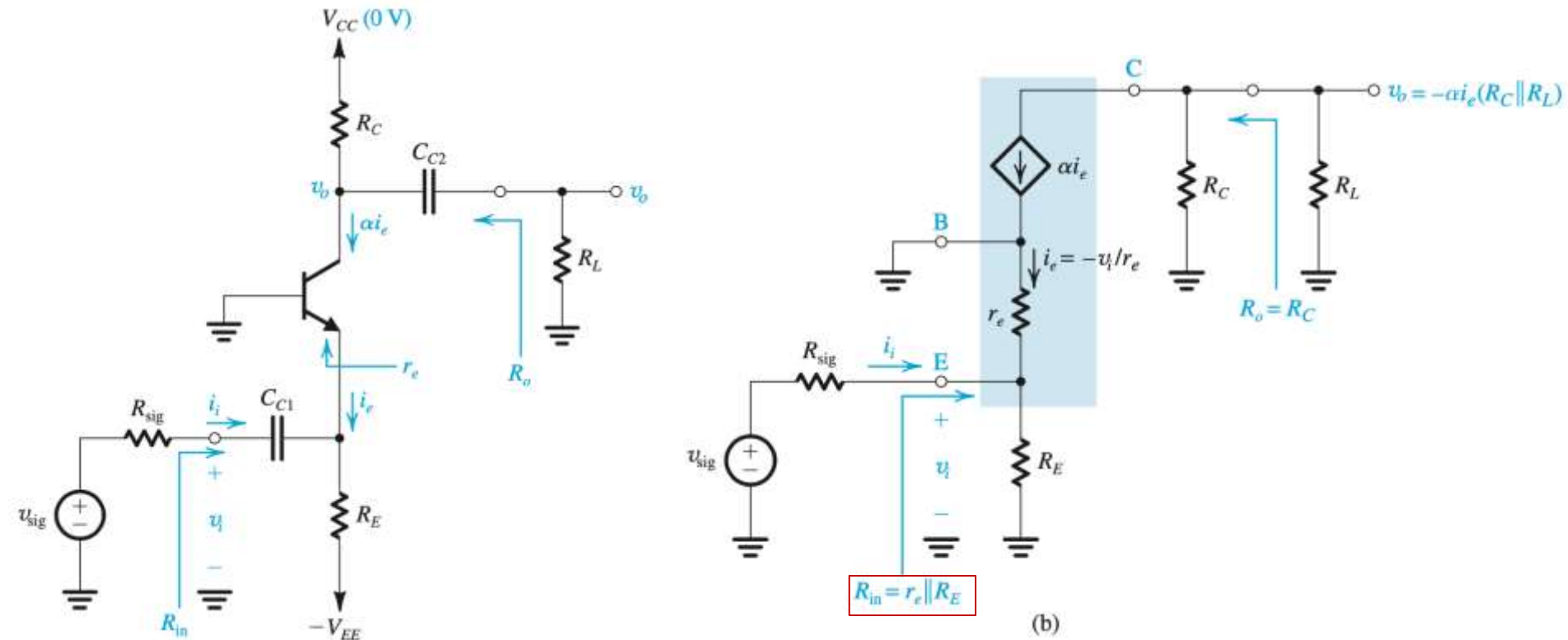
 
$$G_v = \alpha \frac{R_{in}}{R_{in} + R_{sig}} \frac{R_C \parallel R_L}{r_e} = \frac{R_{in}}{R_{in} + R_{sig}} g_m (R_C \parallel R_L)$$




(a)

$$R_{\text{out}} = r_o \parallel R_E \parallel \left[r_e + \frac{R_B \parallel R_{\text{sig}}}{\beta + 1} \right]$$

$$R_{\text{in}} = R_B \parallel R_{ib}$$
 
$$R_{ib} = (\beta + 1)[r_e + (R_E \parallel r_o \parallel R_L)]$$



$$G_v \equiv \frac{v_o}{v_{\text{sig}}} = \frac{R_{\text{in}}}{R_{\text{in}} + R_{\text{sig}}} \frac{(R_E \parallel r_o \parallel R_L)}{r_e + (R_E \parallel r_o \parallel R_L)}$$

频率响应

信号频率较低时，隔直电容和旁路电容不能做理想化处理，会引起增益降低


 


Figure 7.60 Sketch of the magnitude of the gain of a CE (Fig. 7.56) or CS (Fig. 7.55) amplifier versus frequency. The graph delineates the three frequency bands relevant to frequency-response determination.

作业

D7.36 The bias arrangement of Fig. 7.55 is to be used for a common-base amplifier. Design the circuit to establish a dc emitter current of 1 mA and provide the highest possible voltage gain while allowing for a signal swing at the collector of ± 2 V. Use +10-V and -5-V power supplies.

 
Ans. $R_B = 0$; $R_E = 4.3$ k Ω ; $R_C = 8.4$ k Ω



作业


D7.38 Design the bias circuit in Fig. 7.57(b) for the CS amplifier of Fig. 7.57(a). Assume the MOSFET is specified to have $V_t = 1$ V, $k_n = 4$ mA/V², and $V_A = 100$ V. Neglecting the Early effect, design for $I_D = 0.5$ mA, $V_S = 3.5$ V, and $V_D = 6$ V using a power-supply $V_{DD} = 15$ V. Specify the values of R_S and R_D . If a current of 2 μ A is used in the voltage divider, specify the values of R_{G1} and R_{G2} . Give the values of the MOSFET parameters g_m and r_o at the bias point.

 Ans. $R_S = 7$ k Ω ; $R_D = 18$ k Ω ; $R_{G1} = 5$ M Ω ; $R_{G2} = 2.5$ M Ω ; $g_m = 2$ mA/V; $r_o = 200$ k Ω




D7.44 Design the CB amplifier of Fig. 7.60(a) to provide an input resistance R_{in} that matches the source resistance of a cable with a characteristic resistance of $50\ \Omega$. Assume that $R_E \gg r_e$. The available power supplies are $\pm 5\text{ V}$ and $R_L = 8\text{ k}\Omega$. Design for a dc collector voltage $V_C = +1\text{ V}$. Specify the values of R_C and R_E . What is the overall voltage gain? If v_{sig} is a sine wave with a peak amplitude of 10 mV , what is the peak amplitude of the output voltage? Let $\alpha \simeq 1$.

 Ans. $R_C = 8\text{ k}\Omega$; $R_E = 8.6\text{ k}\Omega$; 40 V/V ; 0.4 V



D7.45 Design the emitter follower of Fig. 7.61(a) to operate at a dc emitter current $I_E = 1$ mA. Allow a dc voltage drop across R_B of 1 V. The available power supplies are ± 5 V, $\beta = 100$, $V_{BE} = 0.7$ V, and $V_A = 100$ V. Specify the values required for R_B and R_E . If $R_{sig} = 50$ k Ω and $R_L = 1$ k Ω , find R_{in} , v_i/v_{sig} , v_o/v_i , G_v , and R_{out} . (Note: In the bias design, neglect the Early effect.)

 Ans. $R_B = 100$ k Ω ; $R_E = 3.3$ k Ω ; 44.3 k Ω ; 0.469 V/V; 0.968 V/V; 0.454 V/V; 320 Ω



(a)

