

# 电子电路基础

## 第四讲~过渡过程的经典解法 ~part1

# 课程纲要

- 4.1 一阶电路的响应
  - 4.1.1 一阶电路的零输入和零状态响应
  - 4.1.2 一阶电路的全响应
  - 4.1.3 一阶电路的阶跃响应和冲激响应

# First-Order Circuits

## Chapter 7

7.1 The Source-Free (零输入响应) RC Circuit

7.2 The Source-Free (零输入响应) RL Circuit

7.3 Singularity Function (奇异函数)

7.4 Step Response (阶跃响应) of an RC Circuit

7.5 Step Response (阶跃响应) of an RL Circuit

补充：冲激响应

# 动态电路的概念

- 电感、电容的“电压电流约束关系”与时间  $t$  有关，所以电感、电容又称为**动态元件**，含电感、电容的电路也被称为**动态电路**
- 动态电路的一个**特征**是：当电路结构发生变化时（一般通过“开关”的切换来实现），可能使电路从原来的工作状态，转变到一个新的工作状态，这种转变往往需要一定的时间，这一过程被称为动态电路的**过渡过程**。
- 开关切换的动作也被称为“**换路**”，一般认为换路是在 $t=0$ 时刻进行的，把换路前的最终时刻记为  $t = 0^-$ ，把换路后的最初时刻记为  $t = 0^+$
- 分析动态电路的方法之一：根据KCL、KVL、元件电压电流关系，写出**微分方程**，并求解；这一方法在**时域**中进行，称为**经典解法**

比如电路中只有电容电阻，没有电阻
- ①无**外加激励**电源（**零输入**），仅由动态元件初始储能所产生的响应：**零输入响应**；②动态元件**初始储能**为零（**零状态**），由外加激励电源引起的响应：**零状态响应**；③实际上往往既有输入，也有初始储能：**全响应**

# 常微分方程

· 求出通解后待定系数求解

## · 齐次线性微分方程

$$\frac{d^n y}{dx^n} + A_1 \frac{d^{n-1} y}{dx^{n-1}} + \cdots + A_n y = 0$$

### 1) 求特征方程

$$z^n + A_1 z^{n-1} + \cdots + A_n = 0.$$

获得  $n$  个根  $z_1, \dots, z_n$

若没有重根,  $n$  个独立解  $e^{z_i x}$

若  $z$  是  $m_z$  重根,  $m_z$  个独立解

$$y = x^k e^{zx} \quad k \in \{0, 1, \dots, m_z - 1\}$$

依旧可获得总共  $n$  个独立解

### 2) 写出通解

$n$  个独立解的线性组合就是方程的通解

## · 非齐次线性微分方程

$$y'' + py' + qy = f(x)$$

### 1) 求出对应齐次方程的通解


2) 求出非齐次方程的一个特解  
(电路分析中一般选取  $t = \infty$  稳态时刻的解为特解)

· 无穷大稳态电路好求解

3) 两者相加, 获得非齐次方程的通解
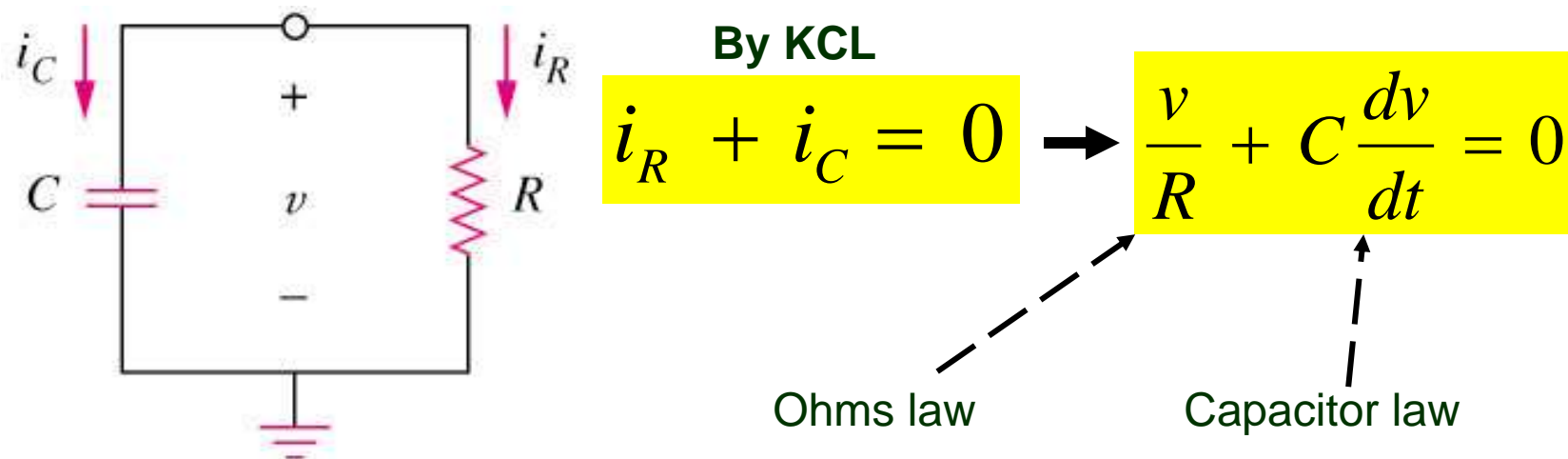
# 7.1 一阶电路的概念

- A **first-order circuit** is characterized by a first-order differential equation.
  - 数学上：一阶电路的方程为**一阶微分方程**
  - 直观上：**化简后**的电路，**仅含一个储能元件（L，或C）**



- Apply Kirchhoff's laws to purely resistive circuit results in algebraic equations.
- Apply the laws to **RC and RL circuits** produces differential equations.  
用电流法和节点法都可以，因为考虑是电容，所以本图片用电流，得微分方程方便解

- 有两种一阶电路： $RC$  &  $RL$
- $0+$ 时刻的电路状态（电容电压 & 电感电流）获得
  - $0-$ 时刻的电路状态
  - 电感电流不能突变；电容电压不能突变
- $0+$ 时刻，**根据有无独立源**，分两种情况：
  - **Source-free circuits**，无独立源。初始时，能量储藏在储能元件  $L$  或  $C$  中，然后逐渐被电阻消耗；**逐渐衰减的过程**（独立源在  $t = 0$  时刻突然撤掉）【即零输入响应】
  - By **independent sources**，有独立源。（独立源在  $t = 0$  时刻突然加入，该情况也称为step-response）**逐渐到达另一个稳态的过程**【全响应】
- 因此，一阶电路有四种组合：
  - ①source-free  $RC$ ；②source-free  $RL$ ；
  - ③step-response of  $RC$ ；④step-response of  $RL$

# The source-free $RC$ circuit


- A **source-free  $RC$  circuit** occurs when its **dc source is suddenly disconnected**. The energy **already stored** in the capacitor is released to the resistors.
- It is a **series combination** of a **resistor** & a **initially charged capacitor**.
- Our **objective** is to determine the circuit **response** (the voltage  **$v(t)$**  across the capacitor)
  - 在  $t = 0+$  初始时刻, 假设  $C$  两端的初始电压为  $V_0$ ;
  - 那么  $C$  的初始储能为  $0.5 CV_0^2$

Applying KCL at the top node of the circuit in Fig. 7.1 yields

$$i_C + i_R = 0 \quad (7.3)$$

By definition,  $i_C = C dv/dt$  and  $i_R = v/R$ . Thus,

$$C \frac{dv}{dt} + \frac{v}{R} = 0 \quad \text{一阶微分方程} \quad (7.4a)$$

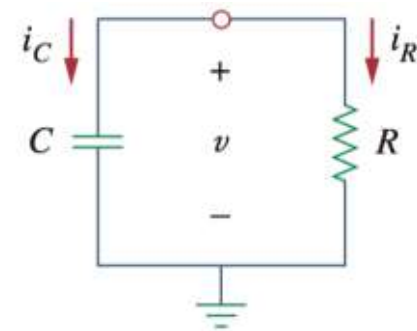

**Figure 7.1**  
A source-free  $RC$  circuit.



- 求解此一阶微分方程，即可得到  $C$  两端电压  $v(t)$ ，问题解决！

$$C \frac{dv}{dt} + \frac{v}{R} = 0 \quad \Longrightarrow \quad \frac{dv}{v} = -\frac{1}{RC} dt$$

Integrating both sides, we get

$$\ln v = -\frac{t}{RC} + \ln A$$

where  $\ln A$  is the integration constant. Thus,

$$\ln \frac{v}{A} = -\frac{t}{RC}$$

Taking powers of  $e$  produces

$$v(t) = Ae^{-t/RC}$$

But from the initial conditions,  $v(0) = A = V_0$ . Hence,

$$v(t) = V_0 e^{-t/RC}$$

- 结论：** source-free  $RC$  电路的电压响应是初始电压值的指数衰减。

抓住关键参数（电容电压、电感电流），列出微分方程，剩下的就是数学问题了


通用方法：

特征方程  $C \cdot s + 1/R = 0$

特征根：  $s_1 = -1/RC$

通解：  $A \cdot e^{(-t/RC)}$

· 通解后待定系数，使用 **0+时刻**（本质是已知）

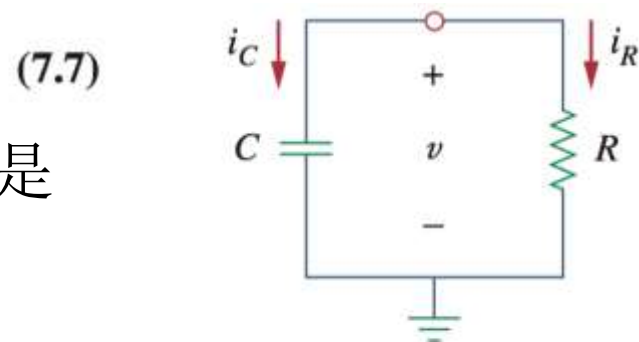


**Figure 7.1**

A source-free  $RC$  circuit.


$$v(t) = V_0 e^{-t/RC}$$

电压响应**仅与**初始储能 $V_0$ 、电路的物理特性  $RC$  **有关**，与外部电压和电流源无关，故也称为电路的 **natural response** (自然响应、零输入响应)

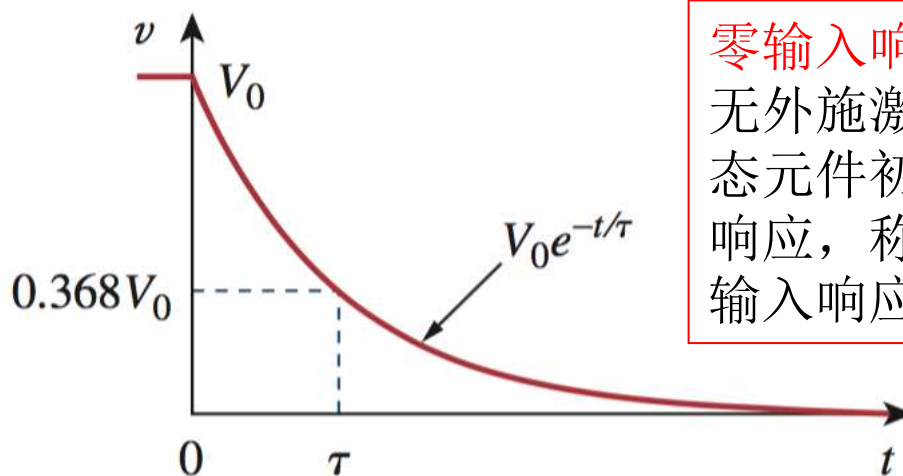The **natural response** of a circuit refers to the behavior (in terms of voltages and currents) of the circuit itself, with no external sources of excitation.



**零输入响应：**动态电路中无外施激励电源，仅由动态元件初始储能所激励的响应，称为动态电路的零输入响应

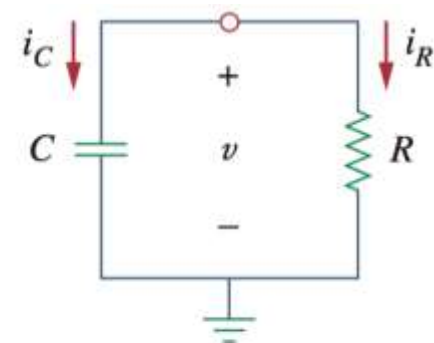


**Figure 7.2**

The voltage response of the  $RC$  circuit.



**Figure 7.1**

A source-free  $RC$  circuit.

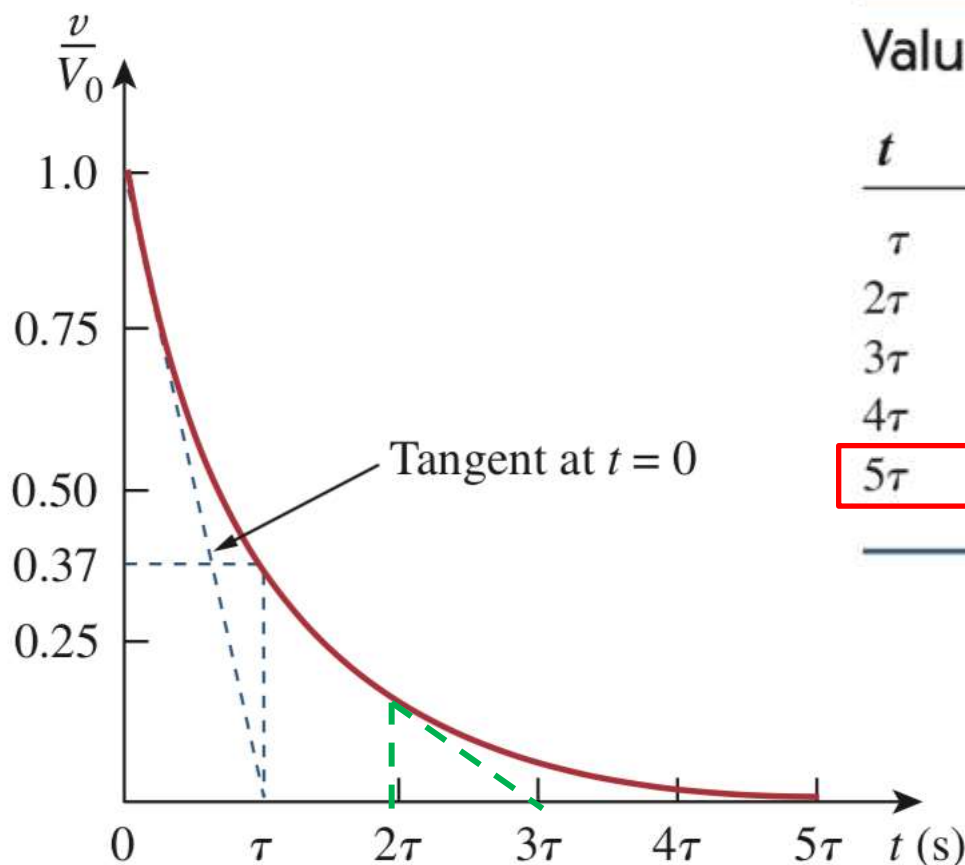

**Figure 7.3**

Graphical determination of the time constant  $\tau$  from the response curve.

如何从实测曲线推出时间常数？

**TABLE 7.1**

Values of  $v(t)/V_0 = e^{-t/\tau}$ .

$t$	$v(t)/V_0$
$\tau$	0.36788
$2\tau$	0.13534
$3\tau$	0.04979
$4\tau$	0.01832
$5\tau$	0.00674

### 自然响应曲线的衰减特性

- 5个时间常数  $\tau$  之后才几乎衰减完 (衰减>99%)。因此，我们说：经过5倍的时间常数，电容被**完全放电（或充电）** → 电路达到最终态或**稳态**
- 在曲线上任意一点作**切线**，在横坐标方向经过  $\tau$  后与  $t$  轴相交



# 7.1 The Source-Free RC Circuit (2)

定义时间常数:

$$\tau = RC$$



$$v(t) = V_0 e^{-t/\tau}$$

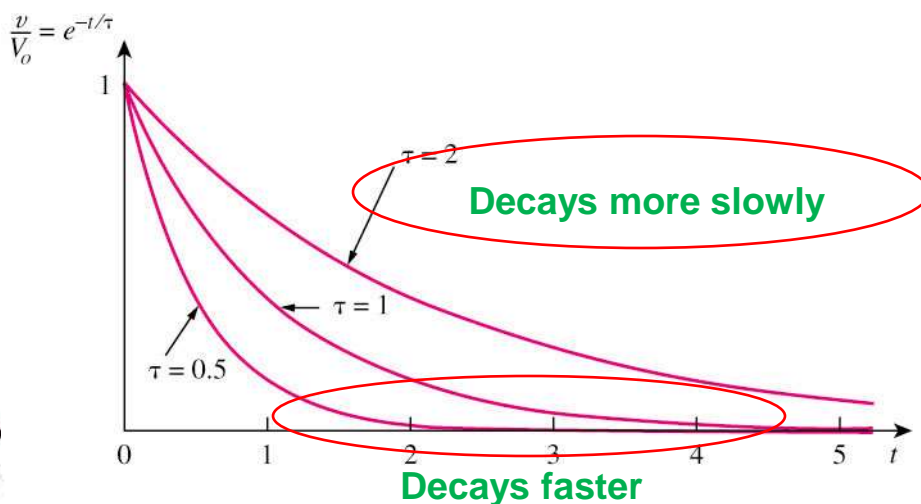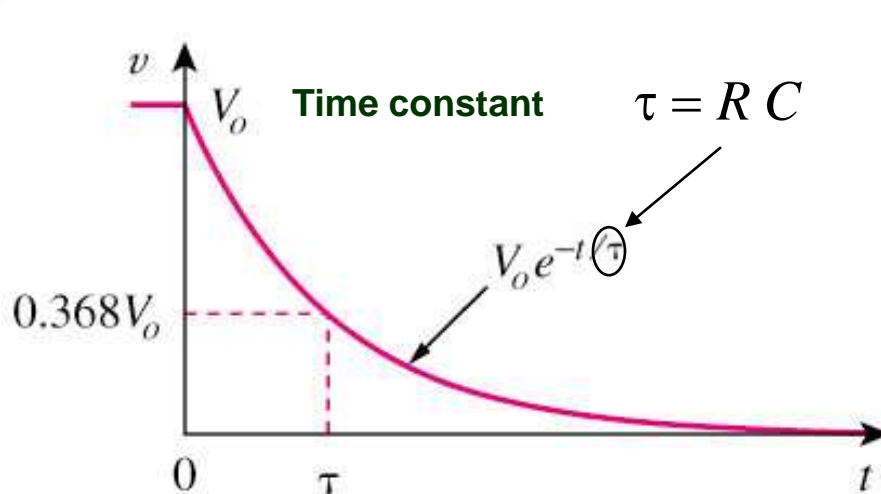

- The **time constant**  $\tau$  of a circuit is the time required for the response to decay by a factor of  $1/e$  or 36.8% of its initial value.
- 时间常数越小, 衰减越快.
- 不管  $\tau$  的具体值是多少, 都是经过5倍的  $\tau$  后衰减完

- 电路的其他量可以从 $v(t)$ 导出

$$i_R(t) = \frac{v(t)}{R} = \frac{V_0}{R} e^{-t/\tau}$$


The power dissipated in the resistor is

$$p(t) = vi_R = \frac{V_0^2}{R} e^{-2t/\tau} \quad (7.11)$$

The energy absorbed by the resistor up to time  $t$  is

$$\begin{aligned} w_R(t) &= \int_0^t p(\lambda) d\lambda = \int_0^t \frac{V_0^2}{R} e^{-2\lambda/\tau} d\lambda \\ &= -\frac{\tau V_0^2}{2R} e^{-2\lambda/\tau} \Big|_0^t = \frac{1}{2} CV_0^2 (1 - e^{-2t/\tau}), \quad \tau = RC \end{aligned} \quad (7.12)$$

Notice that as  $t \rightarrow \infty$ ,  $w_R(\infty) \rightarrow \frac{1}{2} CV_0^2$ , which is the same as  $w_C(0)$ , the energy initially stored in the capacitor. The energy that was initially stored in the capacitor is eventually dissipated in the resistor.

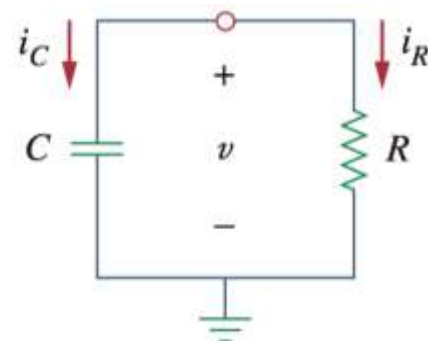

**Figure 7.1**  
A source-free  $RC$  circuit.



# Source-free $RC$ 电路总结

The Key to Working with a Source-Free  $RC$  Circuit Is Finding:

1. The initial voltage  $v(0) = V_0$  across the capacitor.
2. The time constant  $\tau$ .

- 求解source-free  $RC$  电路的方法:

- 第一步: 求出 $0+$ 时刻电容两端的初始电压值  $V_0$ ; (根据 $0$ -时刻电路和电容电压不能突变的特性)
- 第二步: 求出 时间常数  $RC$ ;
  - $R$  为  $C$  两端的等效电阻 (即戴维南电阻);
- 然后可以直接写出  $v(t)$  的表达式:
- 电路中其他的量可由  $v(t)$  导出

$$v(t) = V_0 e^{-t/\tau}$$


复杂电阻网络可以化简和等效

## Example 7.1

In Fig. 7.5, let  $v_C(0) = 15$  V. Find  $v_C$ ,  $v_x$ , and  $i_x$  for  $t > 0$ .

**Solution:**

We first need to make the circuit in Fig. 7.5 conform with the standard RC circuit in Fig. 7.1. We find the equivalent resistance or the Thevenin

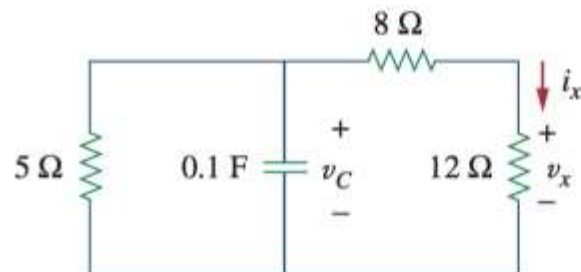**Figure 7.5**

For Example 7.1.

**Figure 7.6**

Equivalent circuit for the circuit in Fig. 7.5.

resistance at the capacitor terminals. Our objective is always to first obtain capacitor voltage  $v_C$ . From this, we can determine  $v_x$  and  $i_x$ .

The 8- $\Omega$  and 12- $\Omega$  resistors in series can be combined to give a 20- $\Omega$  resistor. This 20- $\Omega$  resistor in parallel with the 5- $\Omega$  resistor can be combined so that the equivalent resistance is

$$R_{eq} = \frac{20 \times 5}{20 + 5} = 4 \Omega$$

Hence, the equivalent circuit is as shown in Fig. 7.6, which is analogous to Fig. 7.1. The time constant is

$$\tau = R_{eq}C = 4(0.1) = 0.4 \text{ s}$$

Thus,

$$v = v(0)e^{-t/\tau} = 15e^{-t/0.4} \text{ V}, \quad v_C = v = 15e^{-2.5t} \text{ V}$$


From Fig. 7.5, we can use voltage division to get  $v_x$ ; so

$$v_x = \frac{12}{12 + 8}v = 0.6(15e^{-2.5t}) = 9e^{-2.5t} \text{ V}$$

Finally,

$$i_x = \frac{v_x}{12} = 0.75e^{-2.5t} \text{ A}$$

注意：所有的量都具有相同的时间常数

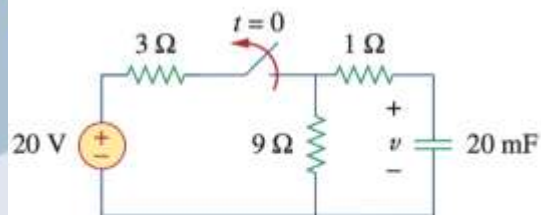

**Figure 7.8**  
For Example 7.2.

The switch in the circuit in Fig. 7.8 has been closed for a long time, and it is opened at  $t = 0$ . Find  $v(t)$  for  $t \geq 0$ . Calculate the initial energy stored in the capacitor.

## Solution:

For  $t < 0$ , the switch is closed; the capacitor is an open circuit to dc, as represented in Fig. 7.9(a). Using voltage division

$$v_C(t) = \frac{9}{9 + 3}(20) = 15 \text{ V}, \quad t < 0$$

①求电容两端的初始电压

电容两端电压不能突变

Since the voltage across a capacitor cannot change instantaneously, the voltage across the capacitor at  $t = 0^-$  is the same at  $t = 0$ , or

$$v_C(0) = V_0 = 15 \text{ V}$$

For  $t > 0$ , the switch is opened, and we have the  $RC$  circuit shown in Fig. 7.9(b). [Notice that the  $RC$  circuit in Fig. 7.9(b) is source free; the independent source in Fig. 7.8 is needed to provide  $V_0$  or the initial energy in the capacitor.] The 1- $\Omega$  and 9- $\Omega$  resistors in series give

$$R_{eq} = 1 + 9 = 10 \Omega$$

The time constant is

$$\tau = R_{eq}C = 10 \times 20 \times 10^{-3} = 0.2 \text{ s}$$

Thus, the voltage across the capacitor for  $t \geq 0$  is


$$v(t) = v_C(0)e^{-t/\tau} = 15e^{-t/0.2} \text{ V}$$

or


$$v(t) = 15e^{-5t} \text{ V}$$

The initial energy stored in the capacitor is
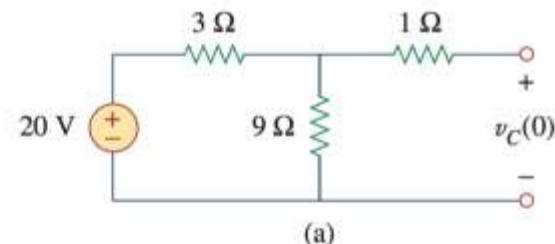
$$w_C(0) = \frac{1}{2}Cv_C^2(0) = \frac{1}{2} \times 20 \times 10^{-3} \times 15^2 = 2.25 \text{ J}$$



(a)

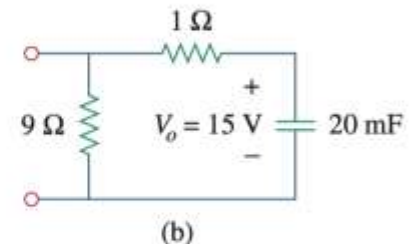

(b)

**Figure 7.9**

For Example 7.2: (a)  $t < 0$ , (b)  $t > 0$ .

②求时间常数



# The source-free $RL$ circuit

- Consider the **series connection** of a **resistor** & a **inductor**.
- Our **goal** is to determine the circuit **response** (the current  $i(t)$  through the inductor)
  - Why choose  $i(t)$ ? 因为**流经电感的电流不能突变**
  - 在  $t = 0$  初始时刻, 假设流经电感的初始电流为  $I_0$ ;
  - 那么  $L$  的初始储能为  $0.5 LI_0^2$


Applying KVL around the loop in Fig. 7.11,

$$v_L + v_R = 0$$

But  $v_L = L di/dt$  and  $v_R = iR$ . Thus,

$$L \frac{di}{dt} + Ri = 0$$

一阶微分方程

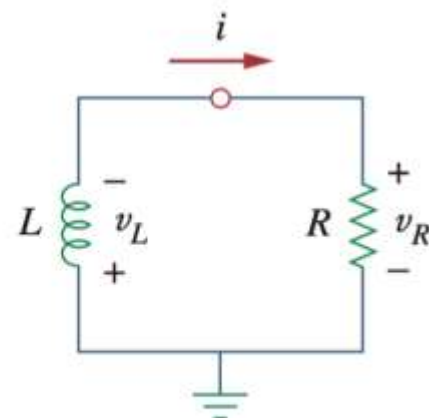

**Figure 7.11**  
A source-free  $RL$  circuit.

- 求解此一阶微分方程，即可得到流经  $L$  的电流  $i(t)$ ，问题解决！

$$L \frac{di}{dt} + Ri = 0 \quad \Longrightarrow \quad \frac{di}{dt} + \frac{R}{L}i = 0$$

Rearranging terms and integrating gives

$$\int_{I_0}^{i(t)} \frac{di}{i} = - \int_0^t \frac{R}{L} dt$$

$$\ln i \Big|_{I_0}^{i(t)} = - \frac{Rt}{L} \Big|_0^t \quad \Rightarrow \quad \ln i(t) - \ln I_0 = - \frac{Rt}{L} + 0$$

or

$$\ln \frac{i(t)}{I_0} = - \frac{Rt}{L}$$

Taking the powers of  $e$ , we have

$$i(t) = I_0 e^{-Rt/L}$$

- 结论：** source-free  $RL$  电路的电流响应是初始电流值的指数衰减。（与  $RC$  类似）

抓住关键参数（电容电压、电感电流），列出微分方程，剩下的就是数学问题了

通用方法：


特征方程  $L \cdot s + R = 0$

特征根：  $s_1 = -R/L$

通解：  $A \cdot e^{(-Rt/L)}$

(7.17) 初始状态求  $A$

(7.18)

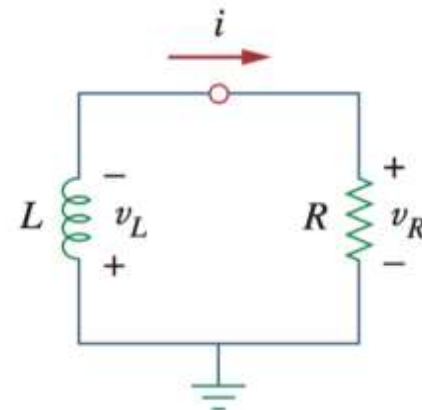

**Figure 7.11**

A source-free  $RL$  circuit.

$$i(t) = I_0 e^{-Rt/L}$$


电流响应仅与初始储能  $I_0$ 、电路的物理特性  $L/R$  有关，与外部电压和电流源无关，故也是电路的 natural response (自然响应)

定义时间常数：

$$\tau = \frac{L}{R}$$




$$i(t) = I_0 e^{-t/\tau}$$

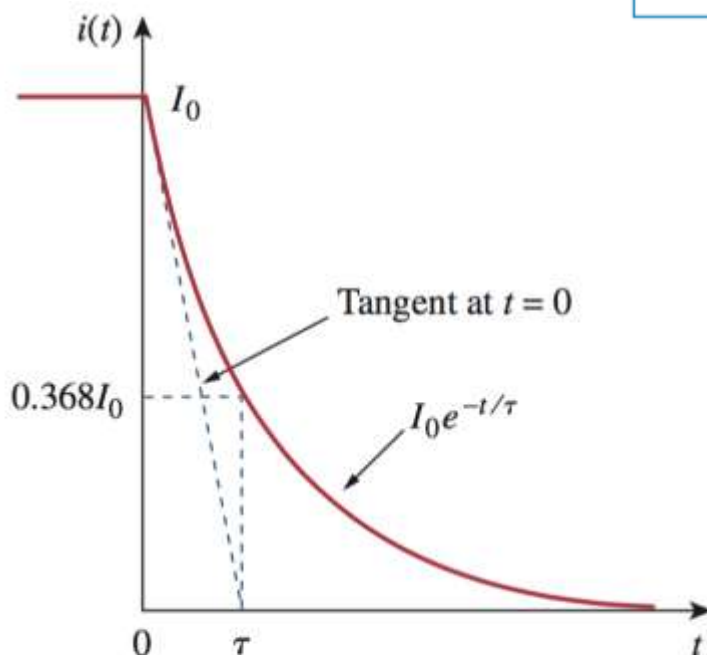

**Figure 7.12**

The current response of the  $RL$  circuit.

\*时间常数的另一物理意义：  
 $i(t)$ 在  $t=0$  时刻的切线与  $t$  轴的交点

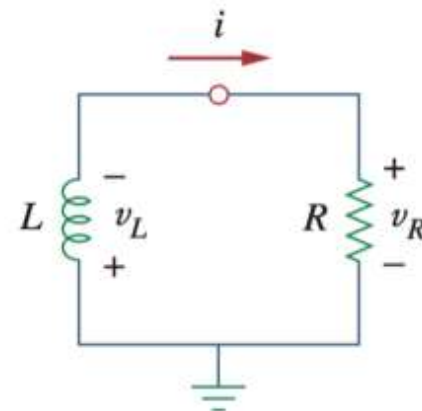

**Figure 7.11**

A source-free  $RL$  circuit.

- 电路的其他量可以从  $i(t)$  导出

$$v_R(t) = iR = I_0 R e^{-t/\tau} \quad (7.21)$$

The power dissipated in the resistor is

$$p = v_R i = I_0^2 R e^{-2t/\tau} \quad (7.22)$$


The energy absorbed by the resistor is

$$w_R(t) = \int_0^t p(\lambda) d\lambda = \int_0^t I_0^2 R e^{-2\lambda/\tau} d\lambda = -\frac{\tau}{2} I_0^2 R e^{-2\lambda/\tau} \bigg|_0^t, \quad \tau = \frac{L}{R}$$

or

$$w_R(t) = \frac{1}{2} L I_0^2 (1 - e^{-2t/\tau}) \quad (7.23)$$

Note that as  $t \rightarrow \infty$ ,  $w_R(\infty) \rightarrow \frac{1}{2} L I_0^2$ , which is the same as  $w_L(0)$ , the initial energy stored in the inductor as in Eq. (7.14). Again, the energy initially stored in the inductor is eventually dissipated in the resistor.

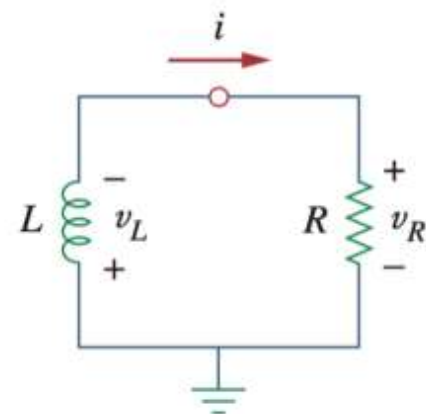

**Figure 7.11**

A source-free  $RL$  circuit.

# Source-free $RL$ 电路总结

The Key to Working with a Source-Free  $RL$  Circuit Is to Find:

1. The initial current  $i(0) = I_0$  through the inductor.
2. The time constant  $\tau$  of the circuit.

## • 求解source-free $RL$ 电路的方法:

- 第一步: 求出 $0+$ 时刻流经电感的初始电流值  $I_0$ ; (根据 $0-$ 时刻电路和电感电流不能突变的特性)
- 第二步: 求出时间常数  $L/R$ ;
  - $R$  为  $L$  两端的等效电阻 (即戴维南电阻);
- 然后可以直接写出  $i(t)$  的表达式:
- 电路中其他的量可由  $i(t)$  导出

$$i(t) = I_0 e^{-t/\tau}$$




# 7.2 The Source-Free $RL$ Circuit
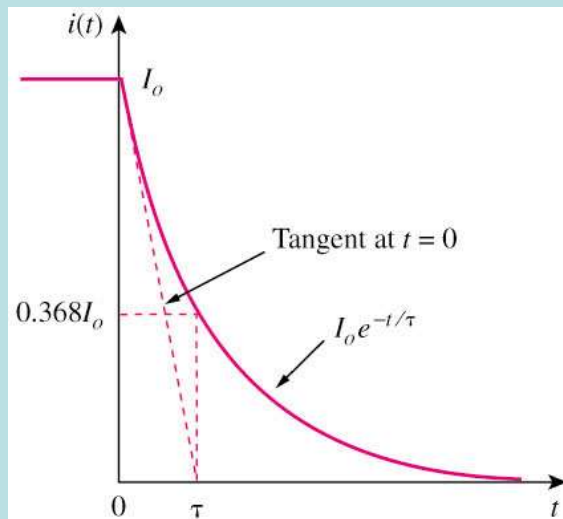
## Comparison between a $RL$ and $RC$ circuit


A  $RL$  source-free circuit

$$i(t) = I_0 e^{-t/\tau} \quad \text{where} \quad \tau = \frac{L}{R}$$




A  $RC$  source-free circuit
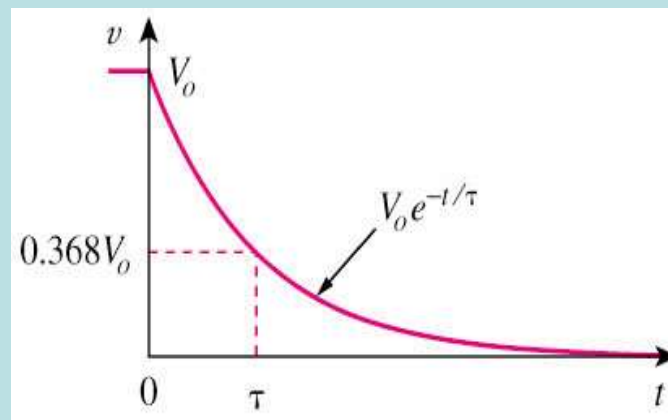
$$v(t) = V_0 e^{-t/\tau} \quad \text{where} \quad \tau = RC$$



Assuming that  $i(0) = 10$  A, calculate  $i(t)$  and  $i_x(t)$  in the circuit of Fig. 7.13.


### Example 7.3

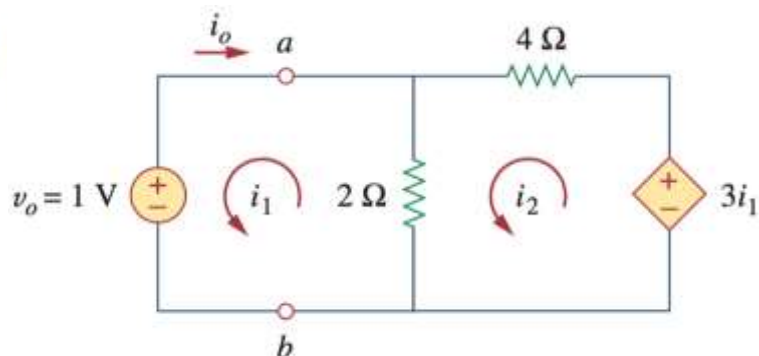

$$2(i_1 - i_2) + 1 = 0$$

$$6i_2 - 2i_1 - 3i_1 = 0$$

$$i_o = -i_1 = 3 \text{ A}$$

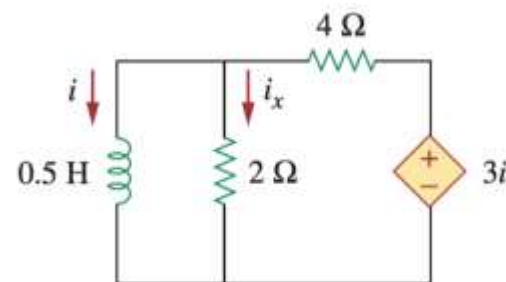

**Figure 7.13**  
For Example 7.3.

Hence,

戴维南等效? ——就是加激励

$$R_{\text{eq}} = R_{\text{Th}} = \frac{v_o}{i_o} = \frac{1}{3} \Omega$$

①求电感两端的等效电阻

The time constant is

$$\tau = \frac{L}{R_{\text{eq}}} = \frac{\frac{1}{2}}{\frac{1}{3}} = \frac{3}{2} \text{ s}$$


②写出时间常数  $L/R$

Thus, the current through the inductor is

$$i(t) = i(0)e^{-t/\tau} = 10e^{-(2/3)t} \text{ A}, \quad t > 0$$

## Example 7.4

The switch in the circuit of Fig. 7.16 has been closed for a long time. At  $t = 0$ , the switch is opened. Calculate  $i(t)$  for  $t > 0$ .

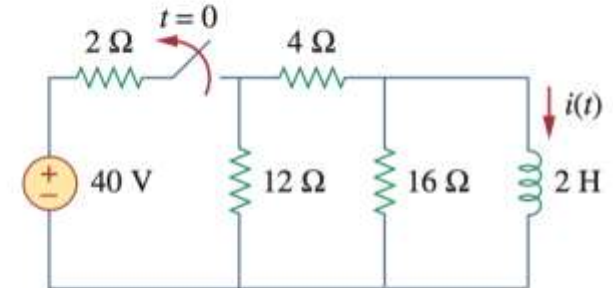**Figure 7.16**

For Example 7.4.



## Example 7.5

In the circuit shown in Fig. 7.19, find  $i_o$ ,  $v_o$ , and  $i$  for all time, assuming that the switch was open for a long time.

For  $t < 0$ , the switch is open. Since the inductor acts like a short circuit to dc, the  $6\text{-}\Omega$  resistor is short-circuited, so that we have the circuit shown in Fig. 7.20(a). Hence,  $i_o = 0$ , and

$$i(t) = \frac{10}{2 + 3} = 2 \text{ A}, \quad t < 0$$

$$v_o(t) = 3i(t) = 6 \text{ V}, \quad t < 0$$

$i$ 与 $i_o$ 的关系由并联得出

Thus,  $i(0) = 2$ .

For  $t > 0$ , the switch is closed, so that the voltage source is short-circuited. We now have a source-free  $RL$  circuit as shown in Fig. 7.20(b). At the inductor terminals,

$$R_{\text{Th}} = 3 \parallel 6 = 2 \text{ }\Omega$$

so that the time constant is

$$\tau = \frac{L}{R_{\text{Th}}} = 1 \text{ s}$$


问电路

Hence,


$$i(t) = i(0)e^{-t/\tau} = 2e^{-t} \text{ A}, \quad t > 0$$

$$v_o(t) = -v_L = -L \frac{di}{dt} = -2(-2e^{-t}) = 4e^{-t} \text{ V}, \quad t > 0$$

$$i_o(t) = \frac{v_L}{6} = -\frac{2}{3}e^{-t} \text{ A}, \quad t > 0$$

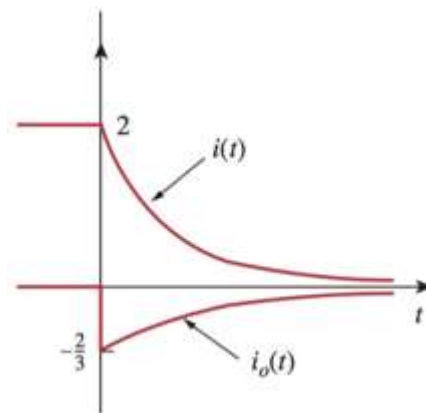

**Figure 7.19**  
For Example 7.5.

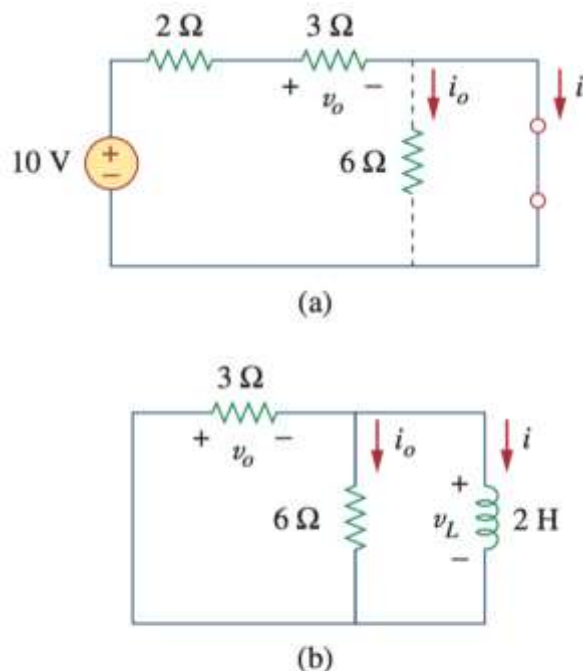

**Figure 7.20**


The circuit in Fig. 7.19 for: (a)  $t < 0$ ,  
(b)  $t > 0$ .

## 7.3 Singularity Functions 奇异函数

**Singularity functions** are functions that either are discontinuous or have discontinuous derivatives. 函数本身不连续，或者其导数不连续


- The **unit step function**  $u(t)$  is 0 for negative values of  $t$  and 1 for positive values of  $t$ . (**undefined at  $t=0$** )
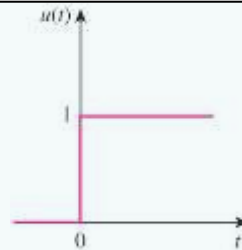
$$u(t) = \begin{cases} 0, & t < 0 \\ 1, & t > 0 \end{cases}$$




单位阶跃函数
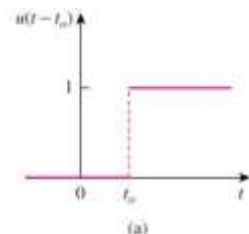
$$u(t - t_o) = \begin{cases} 0, & t < t_o \\ 1, & t > t_o \end{cases}$$



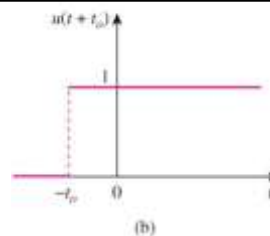
$$u(t + t_o) = \begin{cases} 0, & t < -t_o \\ 1, & t > -t_o \end{cases}$$




# 7.3 Unit-Step Function

Represent an **abrupt change** for:

1. voltage source.

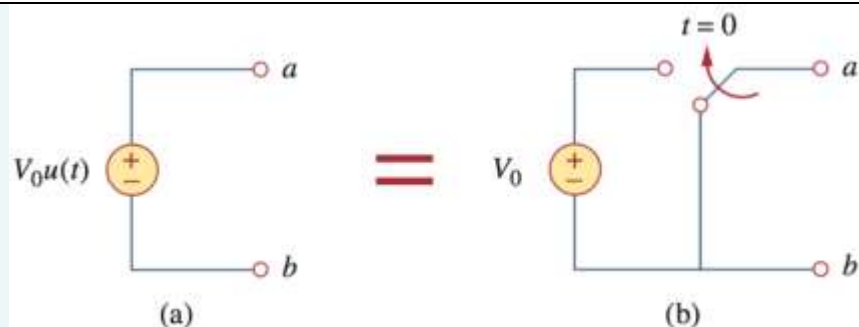


2. for current source:

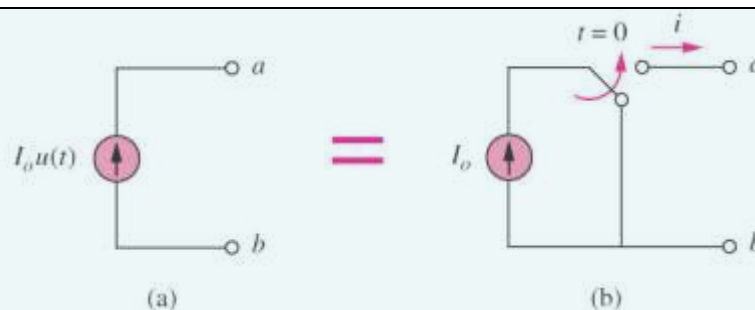

# Unit impulse /delta function

$$\delta(t) = \frac{d}{dt}u(t) = \begin{cases} 0, & t < 0 \\ \text{Undefined}, & t = 0 \\ 0, & t > 0 \end{cases}$$

单位冲激函数  
(delta函数)

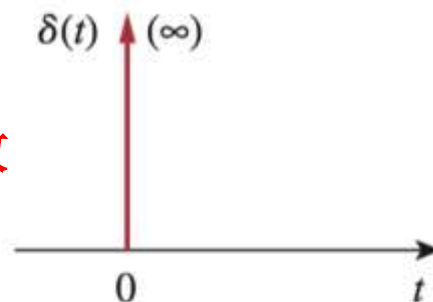

**Figure 7.27**


The unit impulse function.

The **unit impulse function**  $\delta(t)$  is zero everywhere except at  $t = 0$ , where it is undefined.

- 单位冲激函数是单位阶跃函数的导数
- 单位冲激函数在物理上是不能实现的，但在数学上非常有用；
- 单位冲激函数可看成面积为1的时间非常短的脉冲函数；

$$\int_{0^-}^{0^+} \delta(t) dt = 1$$

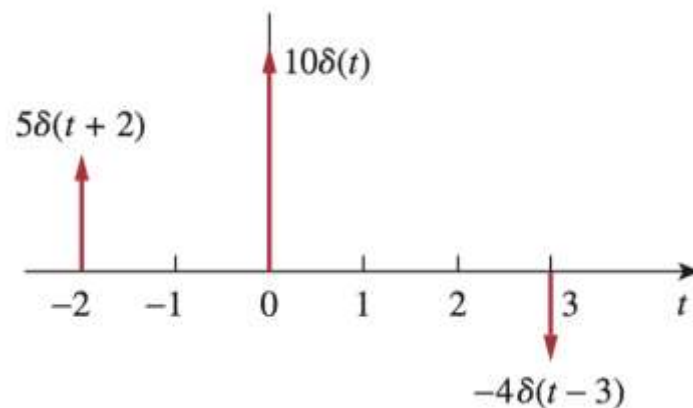- 冲激函数的面积也可以不是1，如右图所示，数字表示面积值，也称为冲激函数的强度 (strength)



- 冲激函数对其他函数的作用：

$$\begin{aligned}\int_a^b f(t)\delta(t-t_0)dt &= \int_a^b f(t_0)\delta(t-t_0)dt \\ &= f(t_0) \int_a^b \delta(t-t_0)dt = f(t_0)\end{aligned}$$



$$\int_a^b f(t)\delta(t-t_0)dt = f(t_0)$$

$$a < t_0 < b$$

若  $t_0=0$ :  $\int_{0^-}^{0^+} f(t)\delta(t)dt = f(0)$

- 冲激函数有把某一函数在某一时刻的值“筛”出来的本领，该性质称为“筛分”性质，也称**取样**性质。

$$f * g = \int_{-\infty}^{\infty} f(\tau)g(t-\tau)d\tau \quad f * \delta = f$$


# Unit ramp function

- 单位斜坡函数是单位阶跃函数的积分

$$r(t) = \int_{-\infty}^t u(\lambda) d\lambda = tu(t)$$

$$r(t) = \begin{cases} 0, & t \leq 0 \\ t, & t \geq 0 \end{cases}$$

单位斜坡函数

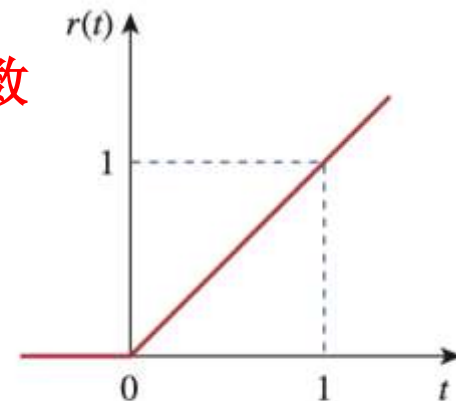

**Figure 7.29**  
The unit ramp function.

The **unit ramp function** is zero for negative values of  $t$  and has a unit slope for positive values of  $t$ .

- 三个奇异函数的关系： 单位斜坡函数  $\rightarrow$  单位阶跃函数  $\rightarrow$  单位冲激函数

$$\delta(t) = \frac{du(t)}{dt}, \quad u(t) = \frac{dr(t)}{dt}$$

或

$$u(t) = \int_{-\infty}^t \delta(\lambda) d\lambda, \quad r(t) = \int_{-\infty}^t u(\lambda) d\lambda$$



Express the voltage pulse in Fig. 7.31 in terms of the unit step. Calculate its derivative and sketch it.


### Solution:

The type of pulse in Fig. 7.31 is called the *gate function*. It may be regarded as a step function that switches on at one value of  $t$  and switches off at another value of  $t$ . The gate function shown in Fig. 7.31 switches on at  $t = 2$  s and switches off at  $t = 5$  s. It consists of the sum of two unit step functions as shown in Fig. 7.32(a). From the figure, it is evident that

$$v(t) = 10u(t - 2) - 10u(t - 5) = 10[u(t - 2) - u(t - 5)]$$


Taking the derivative of this gives
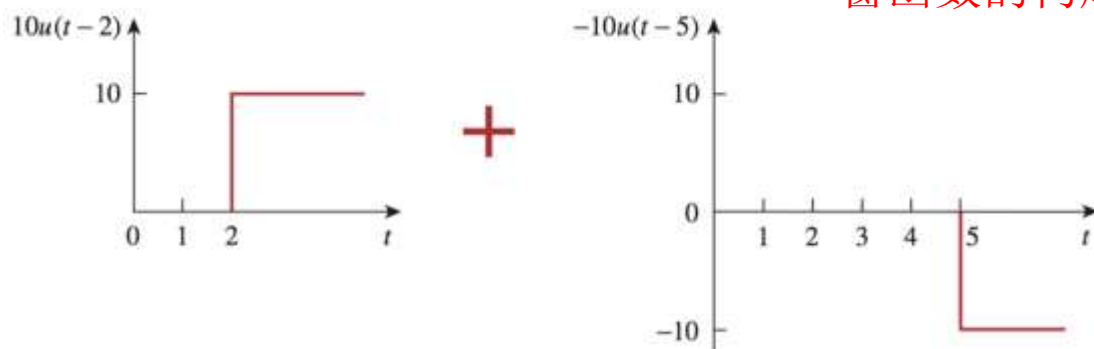
$$\frac{dv}{dt} = 10[\delta(t - 2) - \delta(t - 5)]$$




### Example 7.6

Gate functions are used along with switches to pass or block another signal.

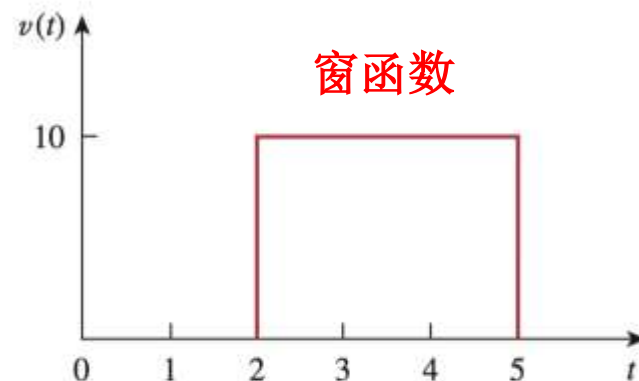


**Figure 7.31**  
For Example 7.6.

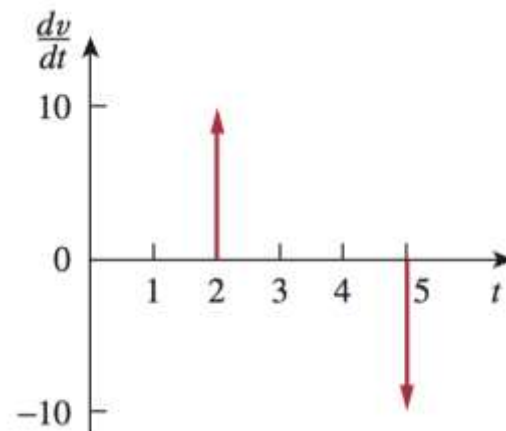


## Example 7.7

Express the *sawtooth* function shown in Fig. 7.35 in terms of singularity functions.

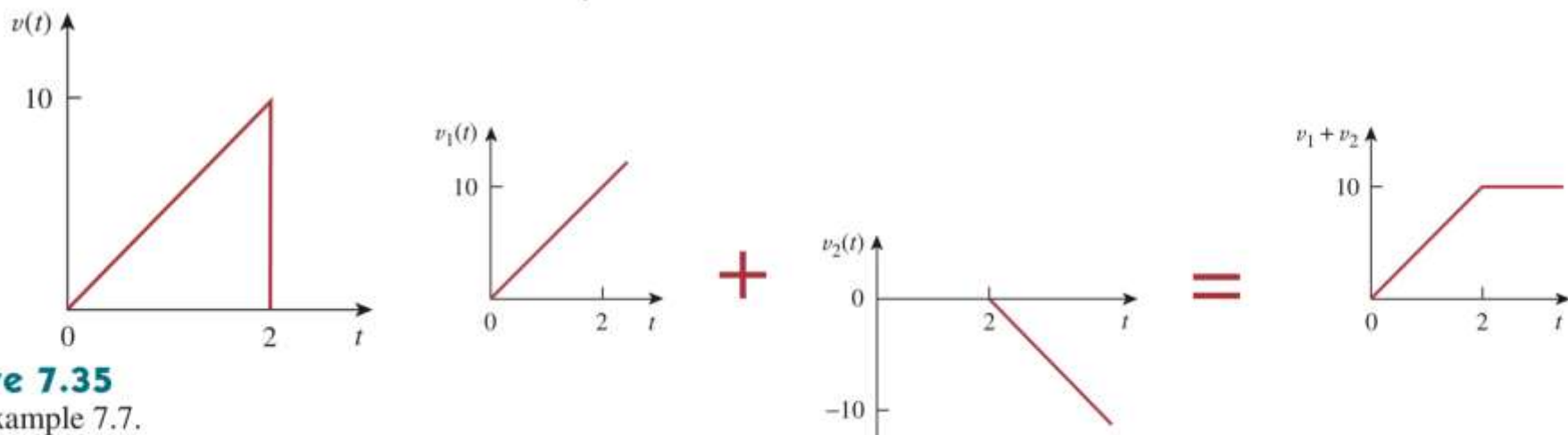

**Figure 7.35**  
For Example 7.7.

锯齿函数

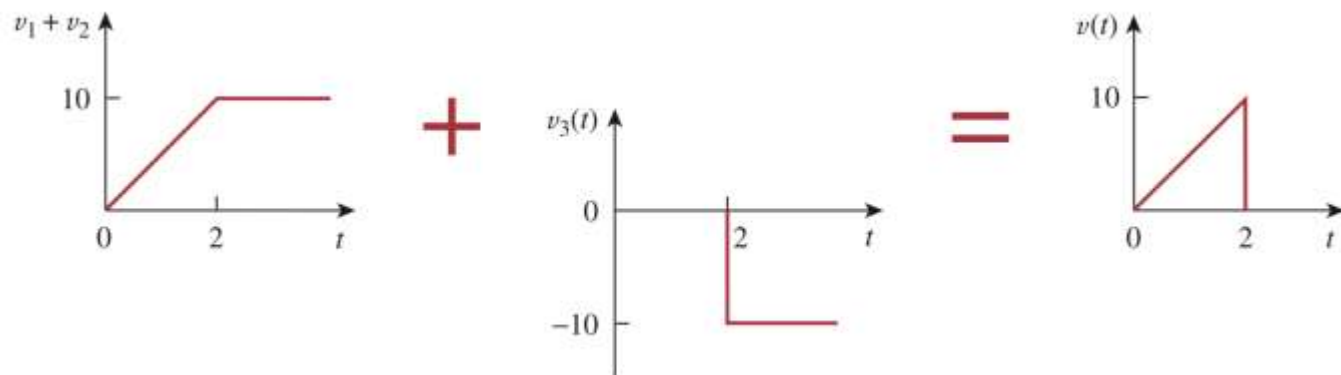

$$v(t) = 5r(t) - 5r(t - 2) - 10u(t - 2)$$



# Step response of an $RC$ Circuit

- $RC$  电路的阶跃响应：若一直流源 (电压源或电流源) 突然加到  $RC$  电路中，则该直流源可以用一个阶跃函数表示，因此，我们把该响应称为阶跃响应 (step response)

The **step response** of a circuit is its behavior when the excitation is the step function, which may be a voltage or a current source.

- 阶跃响应，是电路对突然施加的 dc 电流源或电压源的响应

- 我们的目标：求得  $C$  两端的电压值  $v(t)$ 
  - 假设  $C$  两端的初始电压值为  $V_0$

$$v(0^-) = v(0^+) = V_0$$

- 电源施加后，应用 KCL:

$$C \frac{dv}{dt} + \frac{v - V_s u(t)}{R} = 0 \quad \xrightarrow{t > 0} \quad \frac{dv}{dt} + \frac{v}{RC} = \frac{V_s}{RC}$$

Rearranging terms gives

$$\frac{dv}{dt} = -\frac{v - V_s}{RC}$$

or

$$\frac{dv}{v - V_s} = -\frac{dt}{RC}$$

(7.43)

Integrating both sides and introducing the initial conditions,

$$\begin{aligned} \ln(v - V_s) \Big|_{V_0}^{v(t)} &= -\frac{t}{RC} \Big|_0^t \\ \ln(v(t) - V_s) - \ln(V_0 - V_s) &= -\frac{t}{RC} + 0 \end{aligned}$$

or

$$\ln \frac{v - V_s}{V_0 - V_s} = -\frac{t}{RC}$$

(7.44)

通用方法:


特征方程  $s + 1/RC = 0$

特征根:  $s_1 = -1/RC$


齐次通解:  $A * e^{(-t/RC)}$

特解( $t \rightarrow \infty$ ):  $V_s$

通解:  $V_s + A * e^{(-t/RC)}$

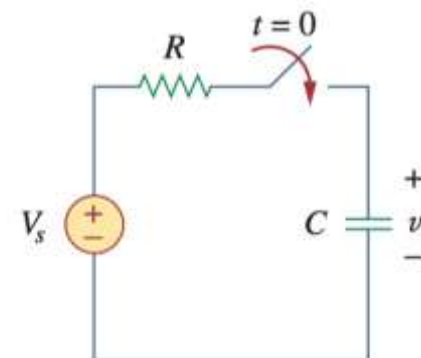

(a)

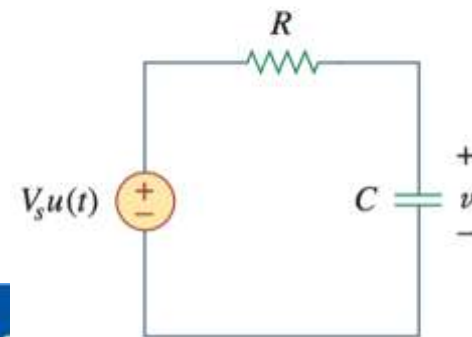

(b)

- 我们的目标：求得  $C$  两端的电压值  $v(t)$

$$\ln \frac{v - V_s}{V_0 - V_s} = -\frac{t}{RC} \quad (7.44)$$

Taking the exponential of both sides

$$\begin{aligned} \frac{v - V_s}{V_0 - V_s} &= e^{-t/\tau}, \quad \tau = RC \\ v - V_s &= (V_0 - V_s)e^{-t/\tau} \end{aligned}$$

or


$$v(t) = V_s + (V_0 - V_s)e^{-t/\tau}, \quad t > 0 \quad (7.45)$$

Thus,


$$v(t) = \begin{cases} V_0, & t < 0 \\ V_s + (V_0 - V_s)e^{-t/\tau}, & t > 0 \end{cases} \quad (7.46)$$
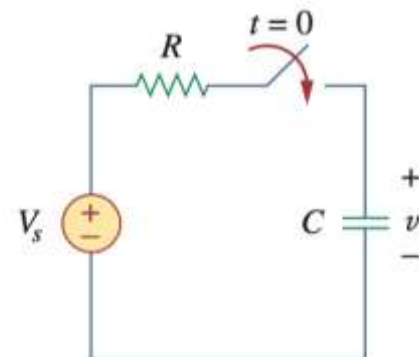
### 观察


- 电容两端电压不能突变； $t = 0$ 时刻为转折点
- 最终趋向于稳态： $v = V_s$
- 初始态与最终态的差额自然衰减，衰减常数为  $\tau$



(a)

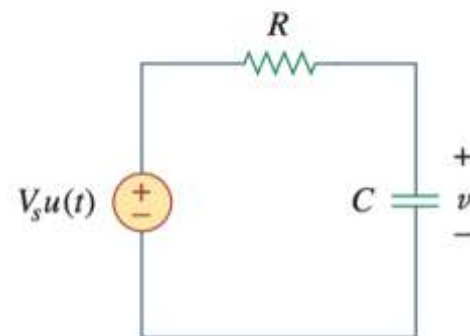

(b)

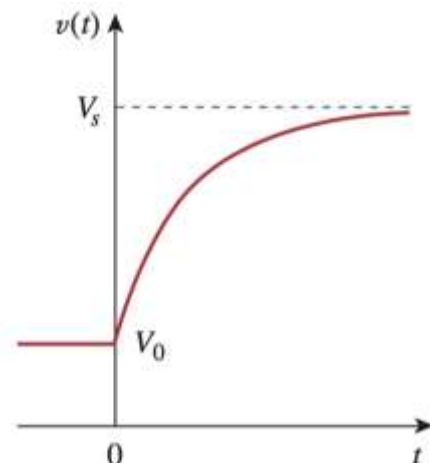

$$v(t) = \begin{cases} V_0, & t < 0 \\ \underline{V_s} + (\underline{V_0} - \underline{V_s})e^{-t/\tau}, & t > 0 \end{cases}$$

## 电路的全响应(观察1)

- 若电容在初始状态是未充电的，则  $V_0 = 0$ ，此时的响应称为**零状态响应**

$$v(t) = \begin{cases} 0, & t < 0 \\ V_s(1 - e^{-t/\tau}), & t > 0 \end{cases} \quad \text{或}$$

$$v(t) = V_s(1 - e^{-t/\tau})u(t)$$

**零状态响应**：电路在零初始状态下（动态元件初始储能值为零），由外施激励引起的响应

- 观察1a（中文教材）**：
- 全响应=零输入响应+零状态响应**

**回顾：零输入响应**：动态电路中无外施激励电源，仅由动态元件初始储能所激励的响应，称为动态电路的零输入响应

$$v(t) = V_0 e^{-t/RC}$$

$$v(t) = \begin{cases} V_0, & t < 0 \\ \underline{V_s} + \underline{(V_0 - V_s)e^{-t/\tau}}, & t > 0 \end{cases}$$

电路的全响应（观察2）

- 观察1b: （英文教材） 零输入响应 就是 自然响应
- 全响应=自然响应（ $V_0$ ）+ 强制响应（外部有强加的 $V_s$ ）

Complete response = natural response + forced response  
stored energy independent source

$$v_n = V_0 e^{-t/\tau} \quad v_f = V_s (1 - e^{-t/\tau})$$

若  $t \rightarrow$  无穷大

$$V_n = 0$$

$$V_f = V_s$$

- 观察2: 对应于 “齐次微分方程的通解” + “ $\infty$ 时的特解”
- 全响应=瞬态响应（临时量）+ 稳态响应（永久量）

Complete response = transient response + steady-state response  
temporary part permanent part

瞬态响应自然衰减

$$v_t = (V_0 - V_s)e^{-t/\tau}$$

$$v_{ss} = V_s$$



# RC 阶跃响应总结

Whichever way we look at it, the complete response in Eq. (7.45) may be written as ①先写最终态（稳态） ②再初始态与最终态（稳态）的差值

$$v(t) = \underline{v(\infty)} + [\underline{v(0)} - \underline{v(\infty)}]e^{-t/\tau}$$

③最后添加自然衰减项

(7.53)

where  $v(0)$  is the initial voltage at  $t = 0^+$  and  $v(\infty)$  is the final or steady-state value. Thus, to find the step response of an  $RC$  circuit requires three things:


1. The initial capacitor voltage  $v(0)$ .
2. The final capacitor voltage  $v(\infty)$ .
3. The time constant  $\tau$ .

1. 三要素法：①  $C$  的初始电压值；②  $C$  的稳态电压值；③时间常数；
2. 若电路是在  $t = t_0$  时刻切换，则

$$v(t) = v(\infty) + [v(t_0) - v(\infty)]e^{-(t-t_0)/\tau}$$

## Example 7.10

The switch in Fig. 7.43 has been in position *A* for a long time. At  $t = 0$ , the switch moves to *B*. Determine  $v(t)$  for  $t > 0$  and calculate its value at  $t = 1$  s and 4 s.

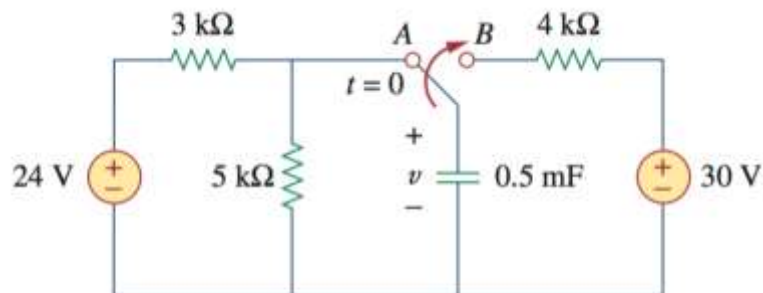

**Figure 7.43**  
For Example 7.10.

$$v(0^-) = \frac{5}{5+3}(24) = 15 \text{ V} \quad \text{①求初始值}$$

Using the fact that the capacitor voltage cannot change instantaneously,

$$v(0) = v(0^-) = v(0^+) = 15 \text{ V}$$

For  $t > 0$ , the switch is in position *B*. The Thevenin resistance connected to the capacitor is  $R_{Th} = 4 \text{ k}\Omega$ , and the time constant is

$$\text{③求时间常数} \quad \tau = R_{Th}C = 4 \times 10^3 \times 0.5 \times 10^{-3} = 2 \text{ s}$$

Since the capacitor acts like an open circuit to dc at steady state,  $v(\infty) = 30 \text{ V}$ . Thus,

②求稳态值

$$\begin{aligned} v(t) &= v(\infty) + [v(0) - v(\infty)]e^{-t/\tau} \\ &= 30 + (15 - 30)e^{-t/2} = (30 - 15e^{-0.5t}) \text{ V} \end{aligned}$$

At  $t = 1$ ,

$$v(1) = 30 - 15e^{-0.5} = 20.9 \text{ V}$$

At  $t = 4$ ,

$$v(4) = 30 - 15e^{-2} = 27.97 \text{ V}$$

### Example 7.11

In Fig. 7.45, the switch has been closed for a long time and is opened at  $t = 0$ . Find  $i$  and  $v$  for all time.

**All Time 节点+电流**

①求初始值

$$v = 10 \text{ V}, \quad i = -\frac{v}{10} = -1 \text{ A}$$

②求稳态值

$$v(\infty) = \frac{20}{20 + 10}(30) = 20 \text{ V}$$

③求时间常数

The Thevenin resistance at the capacitor terminals is


$$R_{Th} = 10 \parallel 20 = \frac{10 \times 20}{30} = \frac{20}{3} \Omega$$

and the time constant is


$$\tau = R_{Th}C = \frac{20}{3} \cdot \frac{1}{4} = \frac{5}{3} \text{ s}$$

$$\begin{aligned} v(t) &= v(\infty) + [v(0) - v(\infty)]e^{-t/\tau} \\ &= 20 + (10 - 20)e^{-(3/5)t} = (20 - 10e^{-0.6t}) \text{ V} \end{aligned}$$


$$\begin{aligned} i &= \frac{v}{20} + C \frac{dv}{dt} \\ &= 1 - 0.5e^{-0.6t} + 0.25(-0.6)(-10)e^{-0.6t} = (1 + e^{-0.6t}) \text{ A} \end{aligned}$$

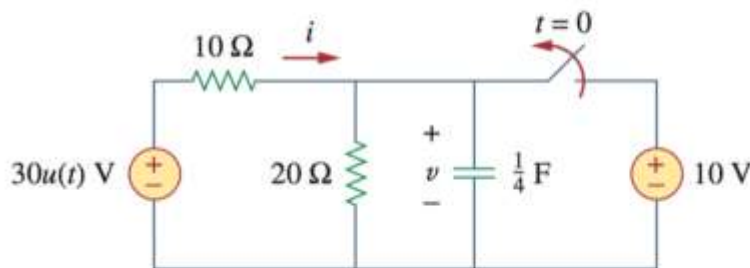

**Figure 7.45**  
For Example 7.11.

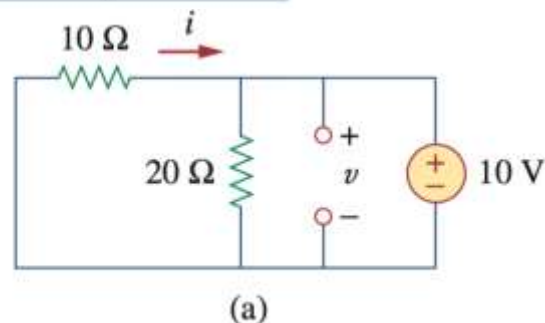

(a)

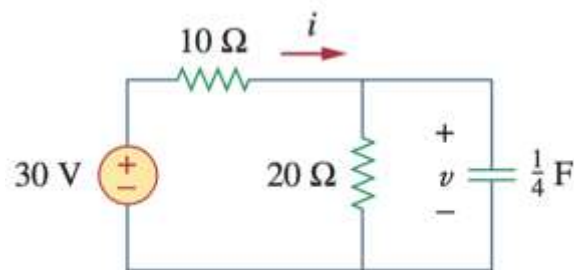

(b)

\*  $t < 0$ 时刻的  $i$   
要单独计算

$$\begin{aligned} v &= \begin{cases} 10 \text{ V}, & t < 0 \\ (20 - 10e^{-0.6t}) \text{ V}, & t \geq 0 \end{cases} \\ i &= \begin{cases} -1 \text{ A}, & t < 0 \\ (1 + e^{-0.6t}) \text{ A}, & t > 0 \end{cases} \end{aligned}$$



# $RL$ 阶跃响应~与 $RC$ 类似

$$i(t) = i(\infty) + [i(0) - i(\infty)]e^{-t/\tau}$$

where  $i(0)$  and  $i(\infty)$  are the initial and final values of  $i$ , respectively. Thus, to find the step response of an  $RL$  circuit requires three things:

1. The initial inductor current  $i(0)$  at  $t = 0$ .
2. The final inductor current  $i(\infty)$ .
3. The time constant  $\tau$ .

1. 三要素法：①  $L$  的初始电流值；②  $L$  的稳态电流值；③时间常数；
2. 若电路是在  $t = t_0$  时刻切换，则

$$i(t) = i(\infty) + [i(t_0) - i(\infty)]e^{-(t-t_0)/\tau}$$

**Example 7.12**

Find  $i(t)$  in the circuit of Fig. 7.51 for  $t > 0$ . Assume that the switch has been closed for a long time.

**Solution:**

When  $t < 0$ , the  $3\text{-}\Omega$  resistor is short-circuited, and the inductor acts like a short circuit. The current through the inductor at  $t = 0^-$  (i.e., just before  $t = 0$ ) is

$$i(0^-) = \frac{10}{2} = 5 \text{ A}$$

**①求初始电流值**

$$i(0) = i(0^+) = i(0^-) = 5 \text{ A}$$

When  $t > 0$ , the switch is open. The  $2\text{-}\Omega$  and  $3\text{-}\Omega$  resistors are in series, so that

**②求稳态电流值**

$$i(\infty) = \frac{10}{2 + 3} = 2 \text{ A}$$

The Thevenin resistance across the inductor terminals is

$$R_{\text{Th}} = 2 + 3 = 5 \text{ }\Omega$$


For the time constant,

**③求时间常数**

$$\tau = \frac{L}{R_{\text{Th}}} = \frac{\frac{1}{3}}{5} = \frac{1}{15} \text{ s}$$

Thus,

$$\begin{aligned} i(t) &= i(\infty) + [i(0) - i(\infty)]e^{-t/\tau} \\ &= 2 + (5 - 2)e^{-15t} = 2 + 3e^{-15t} \text{ A}, \quad t > 0 \end{aligned}$$

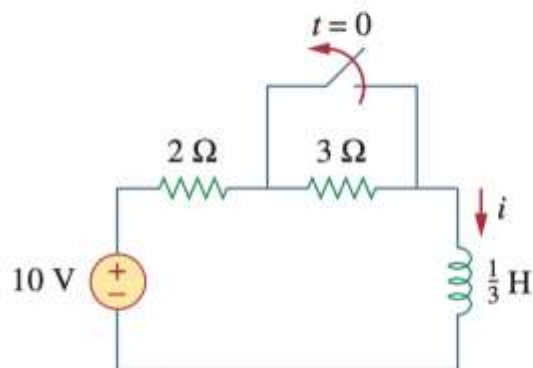**Figure 7.51**

For Example 7.12.

先看开关变化前后  
是否是**source free**

## Example 7.13


At  $t = 0$ , switch 1 in Fig. 7.53 is closed, and switch 2 is closed 4 s later.

Find  $i(t)$  for  $t > 0$ . Calculate  $i$  for  $t = 2$  s and  $t = 5$  s. ①分三个阶段考虑

We need to consider the three time intervals  $t \leq 0$ ,  $0 \leq t \leq 4$ , and  $t \geq 4$  separately. For  $t < 0$ , switches  $S_1$  and  $S_2$  are open so that  $i = 0$ .

Since the inductor current cannot change instantly,
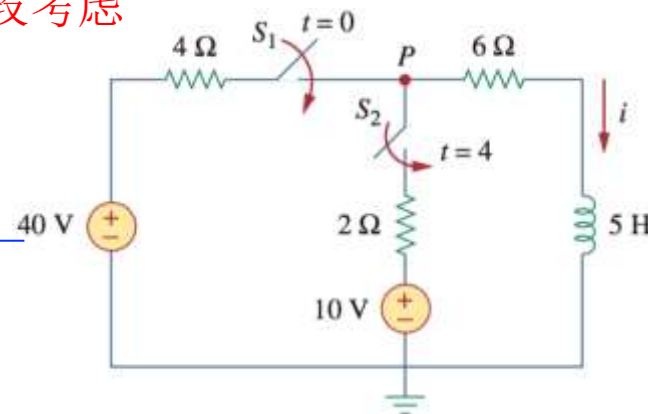
$$i(0^-) = i(0) = i(0^+) = 0 \quad \text{②求初始电流}$$



For  $0 \leq t \leq 4$ ,  $S_1$  is closed so that the  $4\text{-}\Omega$  and  $6\text{-}\Omega$  resistors are in series. (Remember, at this time,  $S_2$  is still open.) Hence, assuming for now that  $S_1$  is closed forever,

$$i(\infty) = \frac{40}{4 + 6} = 4 \text{ A}, \quad R_{\text{Th}} = 4 + 6 = 10 \text{ }\Omega$$

$$\tau = \frac{L}{R_{\text{Th}}} = \frac{5}{10} = \frac{1}{2} \text{ s}$$

③第二阶段的稳态、时间常数

Thus,

$$\begin{aligned} i(t) &= i(\infty) + [i(0) - i(\infty)]e^{-t/\tau} \\ &= 4 + (0 - 4)e^{-2t} = 4(1 - e^{-2t}) \text{ A}, \quad 0 \leq t \leq 4 \end{aligned}$$

$$i(4) = i(4^-) = 4(1 - e^{-8}) \simeq 4 \text{ A}$$

To find  $i(\infty)$ , let  $v$  be the voltage at node  $P$  in Fig. 7.53. Using KCL,

$$\frac{40 - v}{4} + \frac{10 - v}{2} = \frac{v}{6} \Rightarrow v = \frac{180}{11} \text{ V}$$

$$i(\infty) = \frac{v}{6} = \frac{30}{11} = 2.727 \text{ A}$$

$$R_{\text{Th}} = 4 \parallel 2 + 6 = \frac{4 \times 2}{6} + 6 = \frac{22}{3} \text{ }\Omega \quad \tau = \frac{L}{R_{\text{Th}}} = \frac{5}{\frac{22}{3}} = \frac{15}{22} \text{ s}$$

④第三阶段的初始态、稳态、时间常数

$$i(t) = \begin{cases} 0, & t \leq 0 \\ 4(1 - e^{-2t}), & 0 \leq t \leq 4 \\ 2.727 + 1.273e^{-1.4667(t-4)}, & t \geq 4 \end{cases}$$



$$i(t) = i(\infty) + [i(4) - i(\infty)]e^{-(t-4)/\tau}, \quad t \geq 4$$

# 中文教材内容补充

- 单位阶跃响应：电路对于**单位阶跃函数**输入的**零状态响应**
- 单位冲激响应：电路对于**单位冲激函数**激励的**零状态响应**
  - 零状态：储能元件（ $L$ 、 $C$ ）没有初始储能；
  - 把一个单位冲激电流加到初始电压为零的电容  $C$  上，则：


$$u_C = \frac{1}{C} \int_{0_-}^{0_+} \delta_i(t) dt = \frac{1}{C}$$

单位冲击等于初始值

- 相当于在  $t_{0+}$  时刻，电容有了初始电压  $1/C$ ；（注意：此时电容两端的电压有突变： $t_{0-}$ 时刻为0， $t_{0+}$ 时刻为 $1/C$ ）
- $t > 0$ 时，输入为零。因此，单位冲激响应可当作电容两端**初始电压为  $1/C$  的零输入响应**来处理；
- 把一个单位冲激电压加到初始电流为零的电感  $L$  上，则：


$$i_L = \frac{1}{L} \int_{0_-}^{0_+} \delta_u(t) dt = \frac{1}{L}$$

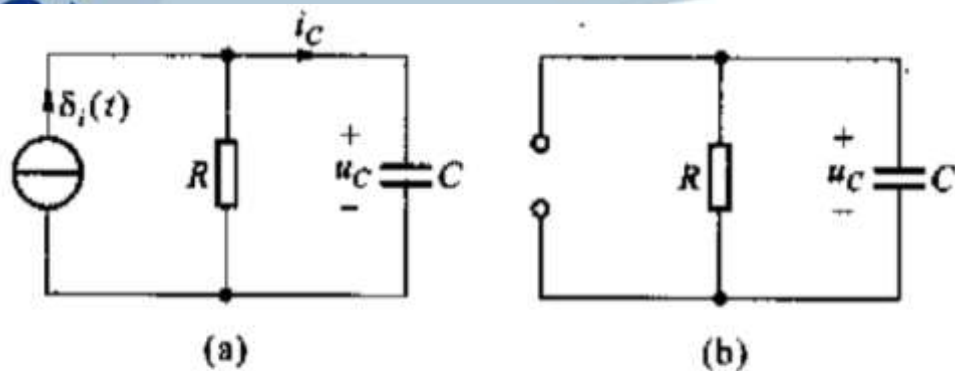- 相当于在  $t_{0+}$ 时刻，电感有了初始电流  $1/L$ ；（注意：此时流经电感的电流有突变： $t_{0-}$ 时刻为0， $t_{0+}$ 时刻为 $1/L$ ）
- $t > 0$ 时，输入为零。因此，单位冲激响应可当作流经电感的**初始电流为  $1/L$  的零输入响应**来处理；



$$u_C = u_C(0_+)e^{-\frac{t}{\tau}} = \frac{1}{C}e^{-\frac{t}{\tau}}$$

图 7-35 RC 电路的冲激响应

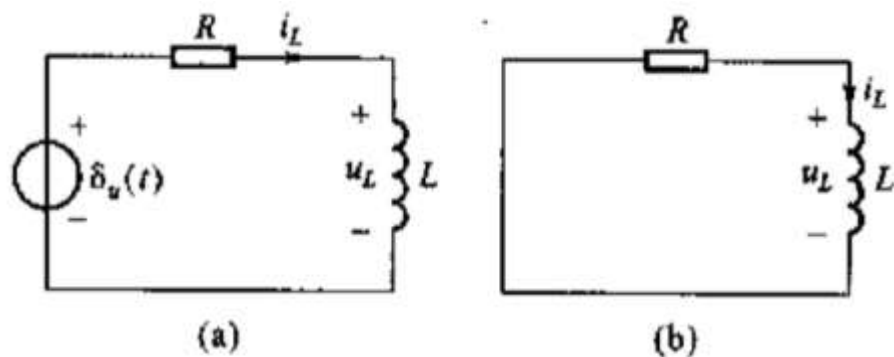


$$i_L = \frac{1}{L}e^{-\frac{t}{\tau}}$$

图 7-36 RL 电路的冲激响应



# 应用——简化的闪光灯电路

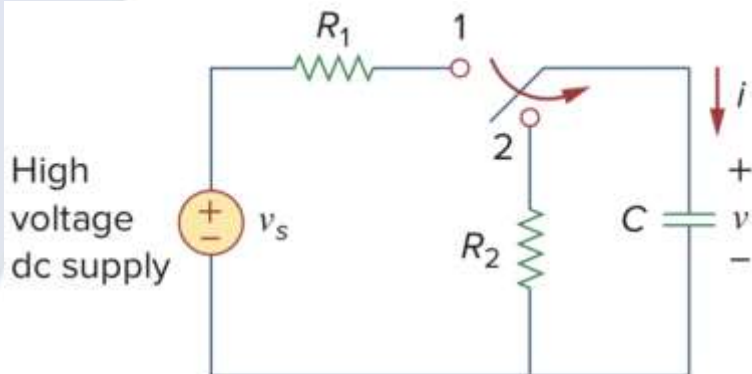


**Figure 7.75**

Circuit for a flash unit providing slow charge in position 1 and fast discharge in position 2.

$$t_{\text{charge}} = 5R_1C$$

$$t_{\text{discharge}} = 5R_2C$$

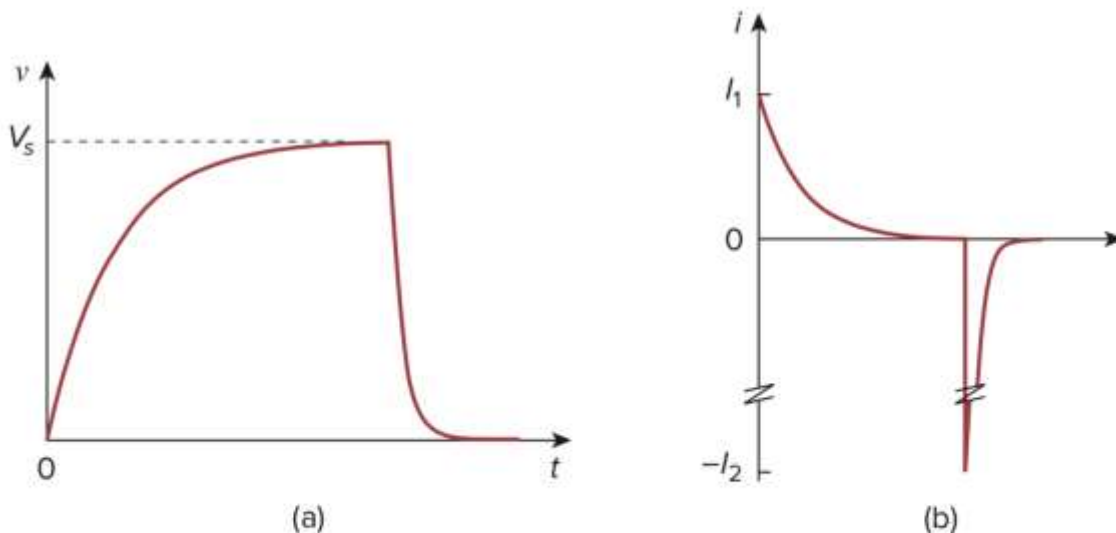

**Figure 7.76**

(a) Capacitor voltage showing slow charge and fast discharge, (b) capacitor current showing low charging current  $I_1 = V_s/R_1$  and high discharge current  $I_2 = V_s/R_2$ .

电容两端电压不能突变  
→ 切换到2时，因 $R_2$ 阻值较小，  
可产生**瞬间大电流**（瞬间闪光）



# 小结

- 动态电路（含有L、C储能元件的电路）的分析
  - 同样基于KCL、KVL，以及“元件的电压电流约束关系”（依次为：电阻、电容、电感）

$$v = iR$$

$$i = C \frac{dv}{dt}$$

$$v = L \frac{di}{dt}$$

- 但现在要求解的是微分方程。需要 1) 确定初始条件；2) 写出通解；
- 初始条件（0+时刻）由0-时刻的电容电压、电感电流确定（利用电容电压不能突变、电感电流不能突变的原则）

# 小结

- 一阶电路的“source-free（零输入）”响应
  - 先确定初始条件：0+时刻，电容两端的电压  $V_0$ ，流过电感的电流  $I_0$
  - 再计算时间常数（R 为C或者L两端的等效电阻）

$$\tau = RC$$

$$\tau = \frac{L}{R}$$

- 再写出电容电压、电感电流的表达式

$$v(t) = V_0 e^{-t/\tau}$$

$$i(t) = I_0 e^{-t/\tau}$$

- 计算电路中其他的量
- 
- 奇异函数：
    - 单位斜坡函数、单位阶跃函数、单位冲激函数，为依次求导关系；
    - 单位阶跃函数可用来表征“开关”的切换

# 小结

- 一阶电路的“全响应”，两种表述：
  - 表述1: **全响应** = **零输入响应**（有储能，无输入） + **零状态响应**（无储能，有输入）
  - 表述2: **全响应** = **稳态响应** + **瞬态响应**
- **表述2的实际求解电路应用【重点】**：
  - 第一步：求初始值；
  - 第二步：求稳态值；
  - 第三步：求时间常数；
  - 然后，可以写出电容电压、电感电流的表达式：

$$v(t) = v(\infty) + [v(0) - v(\infty)]e^{-t/\tau}$$

$$i(t) = i(\infty) + [i(0) - i(\infty)]e^{-t/\tau}$$

# 作业


If the switch in Fig. 7.10 opens at  $t = 0$ , find  $v(t)$  for  $t \geq 0$  and  $w_C(0)$ .

## Practice Problem 7.2

**Answer:**  $8e^{-2t}$  V, 5.333 J.

The Key to Working with a Source-Free  $RC$  Circuit Is Finding:

1. The initial voltage  $v(0) = V_0$  across the capacitor.
2. The time constant  $\tau$ .

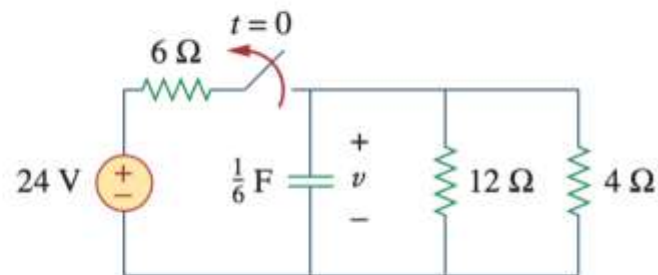


**Figure 7.10**  
For Practice Prob. 7.2.

## Practice Problem 7.3

Find  $i$  and  $v_x$  in the circuit of Fig. 7.15. Let  $i(0) = 7$  A.

**Answer:**  $7e^{-2t}$  A,  $-7e^{-2t}$  V,  $t > 0$ .

含受控源情况下求时间常数

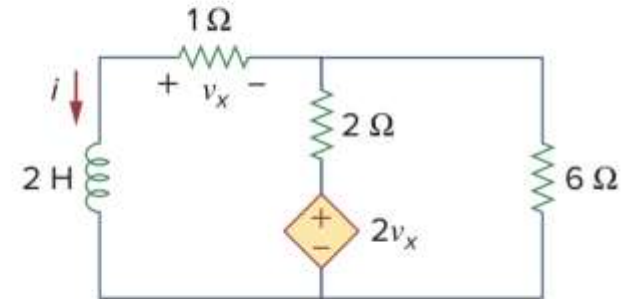


**Figure 7.15**  
For Practice Prob. 7.3.



## Practice Problem 7.10

Find  $v(t)$  for  $t > 0$  in the circuit of Fig. 7.44. Assume the switch has been open for a long time and is closed at  $t = 0$ . Calculate  $v(t)$  at  $t = 0.5$ .

**Answer:**  $(9.375 + 5.625e^{-2t})$  V for all  $t > 0$ , 11.444 V.

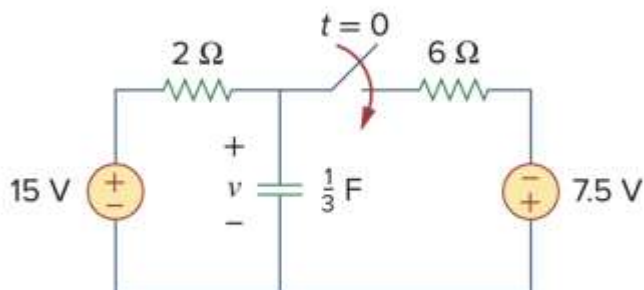


**Figure 7.44**

For Practice Prob. 7.10.

1. The initial capacitor voltage  $v(0)$ .
2. The final capacitor voltage  $v(\infty)$ .
3. The time constant  $\tau$ .

## Practice Problem 7.11

The switch in Fig. 7.47 is closed at  $t = 0$ . Find  $i(t)$  and  $v(t)$  for all time. Note that  $u(-t) = 1$  for  $t < 0$  and 0 for  $t > 0$ . Also,  $u(-t) = 1 - u(t)$ .

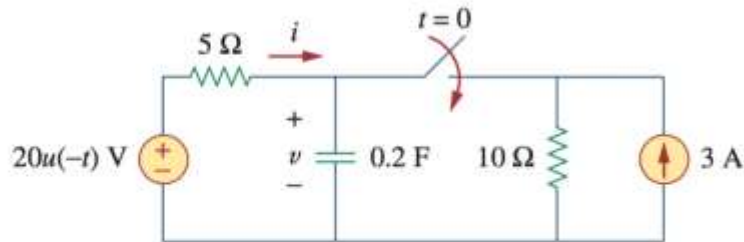

**Figure 7.47**

For Practice Prob. 7.11.

熟悉阶跃函数在电路描述中的应用

**Answer:** 
$$i(t) = \begin{cases} 0, & t < 0 \\ -2(1 + e^{-1.5t}) \text{ A}, & t > 0, \end{cases}$$


$$v = \begin{cases} 20 \text{ V}, & t < 0 \\ 10(1 + e^{-1.5t}) \text{ V}, & t > 0 \end{cases}$$

1. The initial capacitor voltage  $v(0)$ .
2. The final capacitor voltage  $v(\infty)$ .
3. The time constant  $\tau$ .

电流根据可以节点电压相除而得
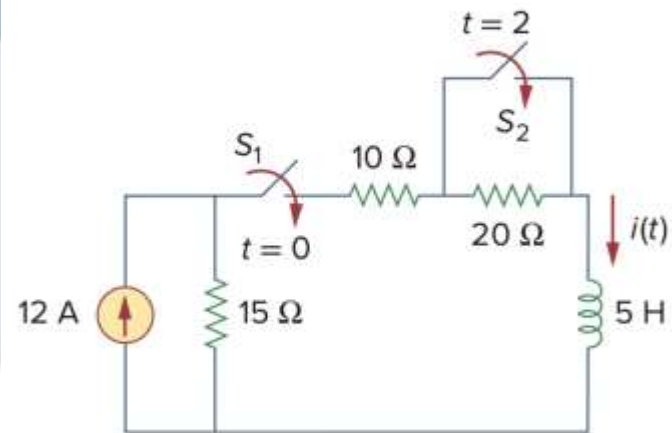
## Practice Problem 7.13

Switch  $S_1$  in Fig. 7.54 is closed at  $t = 0$ , and switch  $S_2$  is closed at  $t = 2$  s. Calculate  $i(t)$  for all  $t$ . Find  $i(1)$  and  $i(3)$ .



**Answer:**

$$i(t) = \begin{cases} 0, & t < 0 \\ 4(1 - e^{-9t}), & 0 < t < 2 \\ 7.2 - 3.2e^{-5(t-2)}, & t > 2 \end{cases}$$

$$i(1) = 4 \text{ A}, i(3) = 7.178 \text{ A}.$$

多开关多阶段分析

**Figure 7.54**

For Practice Prob. 7.13.